

Engin 103

Fall '06

Meeting #16: October 24, 2006

Today we completed CW1 and the Circuit Analysis with LabVIEW II: the equations for wiring in the Block Diagram are shown in the link to this lab in the e-syllabus.

LabVIEW Circuit #2 (related to HW3.8)


Step 1

Make a sketch of the circuit shown using Paint, then copy into LabVIEW Front Panel

Put in 3 numeric controls for V and R1 and R2 (type in label after each insert);

2 numeric indicators, one for I, one for V1

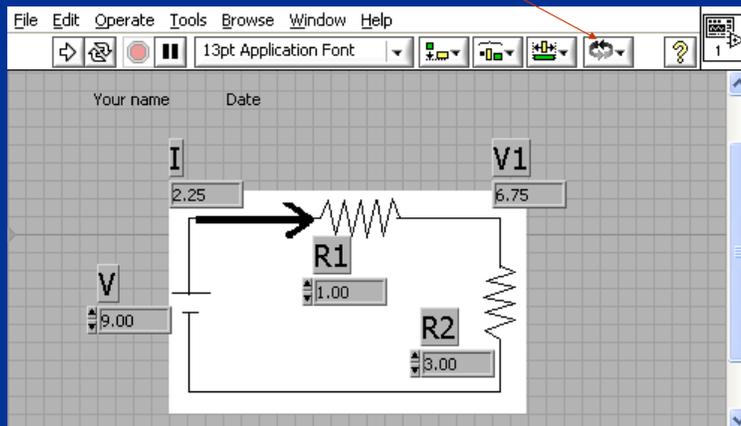
To show icons on top of circuit, select circuit, then "reorder"/"move to back"



1

Step 2:

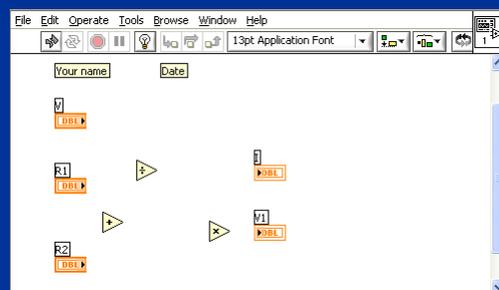
In the Block Diagram arrange the inputs in the left, output in the right, and put in the Needed operations:



5

Step 3:

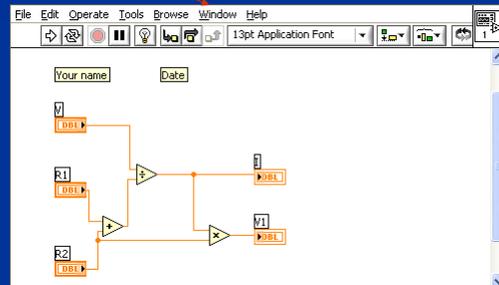
To complete the VI, use the Wiring Tool (in Tools Palette: Window/Show Tools Palette) to connect the icons



6

Step 4:

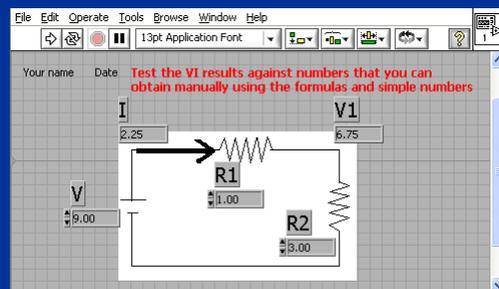Check the VI's results against numbers you can obtain from the formulas and using "easy numbers" such as $V=9V$; $R1=1\text{ Ohm}$; $R2=3\text{ Ohm}$, then $I=V/(R1+R2)=2.25A$ and $V1=I*R2=6.75V$. This may be trivial here, but it is very important to do this check when we work with a larger circuit!



7

Suggested items to write in the Engin 103 logbook:

- 1) What is the engineering field assigned to your team in Project 0? Illustrate the difference between a scientist and an engineer with a specific example comparing an engineer's approach and a related scientist's approach in that field.**
- 2) In Circuit Analysis with LabVIEW II, are "Is" and "V1" numeric controls or numeric indicators, what is the difference on the corresponding icons, what**

happens to the wires if you use a numeric control instead of a correct numeric indicator?