| Engin 103          | Topics:                          |
|--------------------|----------------------------------|
| March 31, 2009     | <u>CW7</u>                       |
|                    | Circuit Analysis with LabVIEW IV |
| back to e-syllabus | Logbook questions                |

## Engineering 103 –UMass Boston CW 7

(In-Class-Work 7)

Circuit Analysis with LabVIEW IV: Follow Instructions in today's class notes, produce a VI that solves a circuit with one battery and six resistors, producing four outputs: total current I, and voltages V2, V4, and V6, now using three <a href="mailto:subVI"><u>subVI</u></a>'s: "parallel", "V\_next", and "I\_after"

In each team, students working together at a computer numbered between 1 and 10 will submit LabVIEW LLB file cw7\_XX\_a.llb, students working at a computer numbered between 11 and 20 will submit LabVIEW LLB file cw7\_XX\_b.llb, to the *files* folder in the server. Replace XX by 01 if team 1, etc. Include your names within the files.

\*Remember that this is an individual work (turn it in, as instructed, with your name and date). Home-works and class-works count 20% toward the course grade. Class-works are done in class.

## back

Circuit Analysis with LabVIEW IV (See also the link with the same name in the e-syllabus)

If you observe the Block Diagram in the Virtual Instrument we built for Circuit Analysis with LabVIEW III, there are three repeating groups of operations as shown in the figure below. For each group we will create a sub-VI that we will call in every time we need to perform that same group of operations. Sub-VI's, subroutines, or super operators are commonly used in programming languages, with the goals of simplifying the codes for reading and debugging.


$$I = \frac{V}{R1 + R2 \| \{R3 + [R4\| (R5 + R6)]\}}$$


$$(1) \quad V2 = V - I \cdot R1$$


$$V4 = V2 - \left(I - \frac{V2}{R2}\right) \cdot R3$$


$$(3)$$

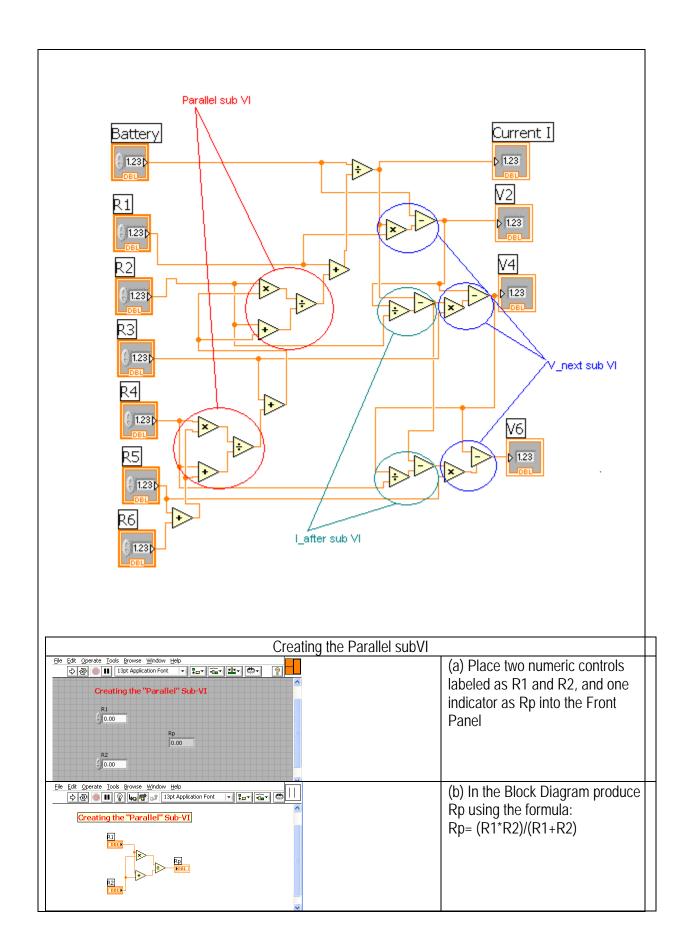
$$V6 = V4 - \left[ \left( I - \frac{V2}{R2} \right) - \frac{V4}{R4} \right] \cdot R5 \tag{4}$$



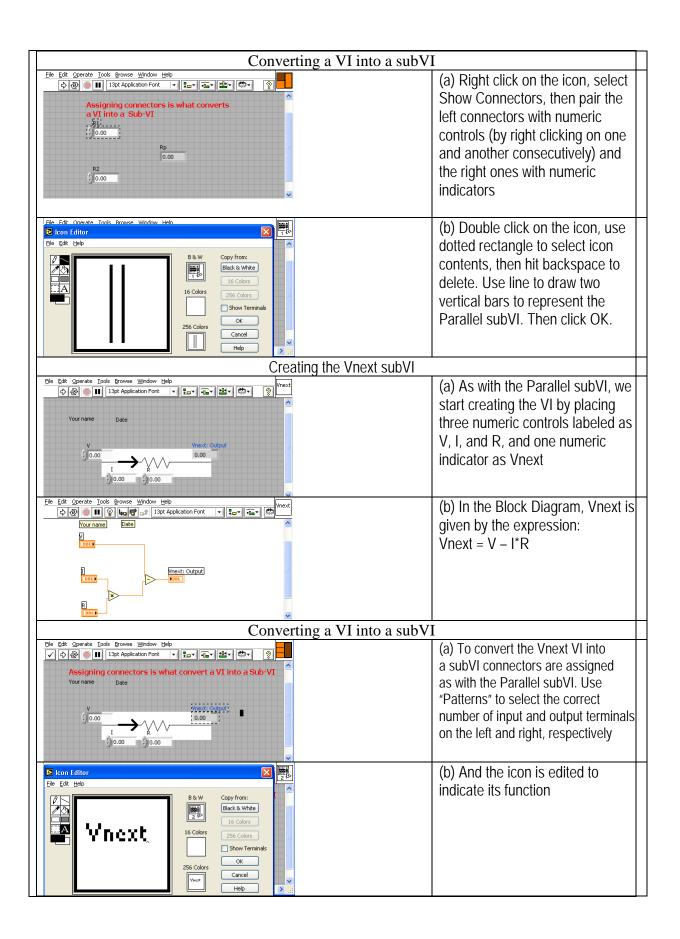

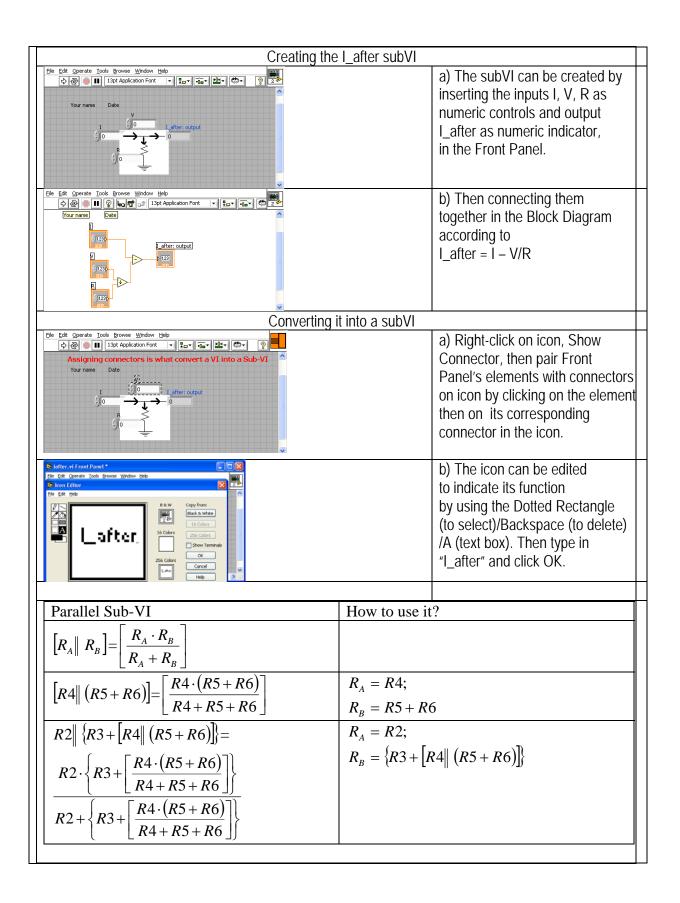

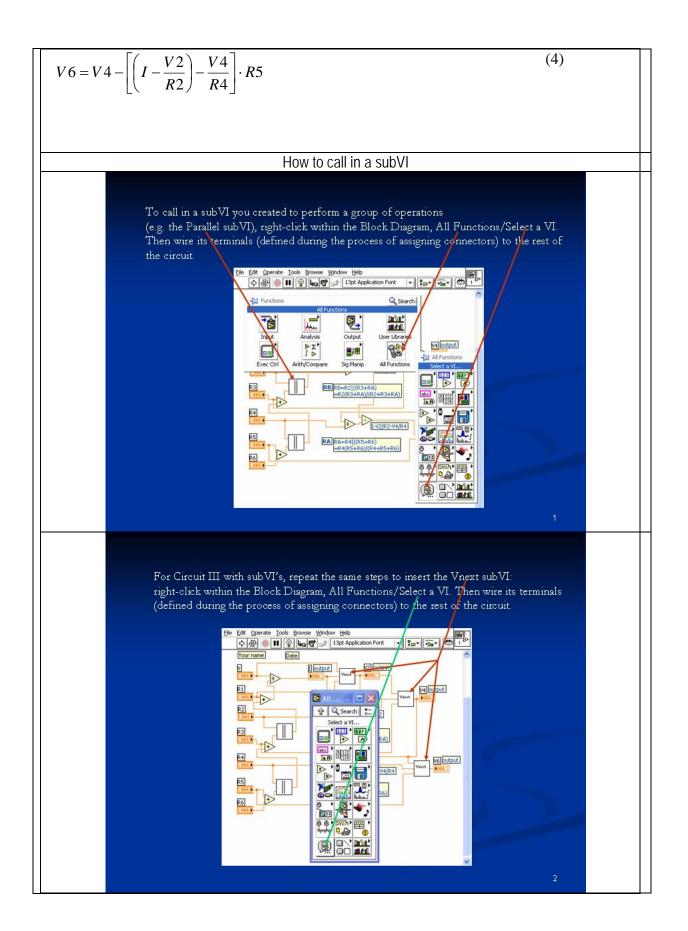

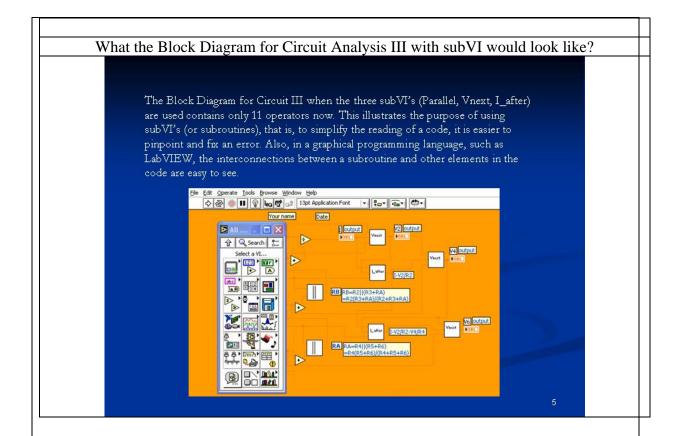

back

back

back

## **LOGBOOK:** example of a logbook page

- -Use a quadrille notebook; number all pages; date all entries
- -Write your notes for all activities, thoughts, problems and solutions, and learning conclusions related to Engin 103. You should write down progress, outcomes, and conclusions on projects and teamwork; conclusions from class work (including LabVIEW) and homework.
- -In addition you should answer in the logbook all questions listed in these notes in blue, as shown below:
- 31) How many sub-VI's did you create in this exercise? What is the difference between creating a VI and creating a sub-VI?
- 32) How do you call in a sub-VI? How do you wire it? What would happen if you did not properly assign connectors when creating the sub-VI?

back