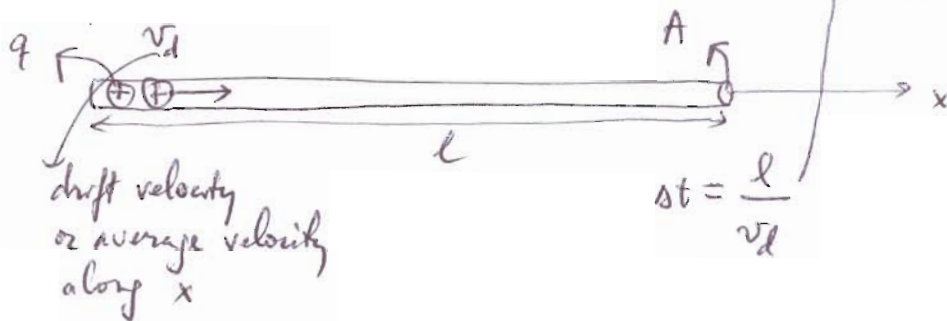


## Ch. 27 Electric Current:

$$I \equiv \frac{\Delta q}{\Delta t} \quad ; \quad I = \frac{dq}{dt} \quad \left( \frac{C}{s} \equiv A \text{ for Amp.} \right)$$

Microscopic expression:  $I = \frac{\Delta q}{\Delta t} = \frac{n A l q}{\frac{l}{v_d}} = n q A v_d$



drift velocity  
or average velocity  
along  $x$

$n = \#$  of charge per unit volume

Copper wire ;  $A = 1 \text{ mm}^2$  ;  $I = 5 \text{ A}$   
each atom of copper contribute  $1.3e$  of charge

$\rightarrow v_d ?$   $v_d = \frac{I}{n q A}$

need  $\rightarrow$  # atoms of copper per unit volume

Mass density:  $\rho = 8920 \text{ kg/m}^3$  : if we divide this by the mass of one atom of copper  $\rightarrow$  we get  $n$

$\rightarrow \text{Cu: } 63.55 \text{ a.u.} = 63.55 \times 1.66 \times 10^{-27} \text{ kg}$

$$n = \frac{8920 \frac{\text{kg}}{\text{m}^3}}{63.55 \times 1.66 \times 10^{-27} \frac{\text{kg}}{\text{atom Cu}}} = 8.5 \times 10^{28} \frac{\text{atoms Cu}}{\text{m}^3}$$

$$\rightarrow v_d = \frac{5 \text{ A}}{8.5 \times 10^{28} \times 1.3 \times 1.6 \times 10^{-19} \times 10^{-6}} \frac{\text{m}}{\text{s}} = 0.283 \frac{\text{mm}}{\text{s}}$$

$$\frac{1}{2} m \overline{v^2} = \frac{3}{2} kT \quad \text{only for gas!}$$

$$v_d = 283 \times 10^{-6} \frac{m}{s} \rightarrow T = 6.1 \times 10^{-12} \text{ oK !}$$

Current density =  $J = \frac{I}{\text{Area}} = \frac{nq A_{\text{area}} v_d}{A_{\text{area}}} = nq v_d \left( \frac{A}{m^2} \right)$



Normal materials:

$$\vec{J} = \sigma \vec{E}$$

"sigma" conductivity

(this agrees with what we said about conductors in equilibrium:  $E=0 \Rightarrow J=0$  or  $I=0$ )

$\rho \equiv \frac{1}{\sigma}$  : resistivity  
"rho"

Conductivity:  $[\sigma] = \frac{[J]}{[E]} = \frac{\frac{A}{m^2}}{\frac{N}{C}} = \frac{A \cdot C}{N \cdot m \cdot m} = \frac{1}{\Omega m}$

Volt  
or V

$$\text{Ohm's law: } I = \frac{V}{R} \text{ or } R = \frac{V}{I} \left( \frac{V}{A} \equiv \Omega \right)$$

resistance

"omega"  
ohm

Resistivity:  $[\rho] = \Omega m$

$$J = \sigma E$$

Microscopic  
Ohm's Law

$$\rightarrow J = \frac{1}{\rho} E = \frac{1}{\rho} \frac{dV}{dx}$$
$$\downarrow$$
$$\frac{I}{\text{Area}} = \frac{1}{\rho} \frac{dV}{dx}$$


$$I = \frac{1}{\rho} \frac{dV}{dx} \text{Area} = \frac{V}{\left(\frac{\rho}{l}\right)} \rightarrow R$$

$$\boxed{I = \frac{V}{R}}$$

- 
- Conductors: high conductivity
  - Semiconductors: become conductors when doped with impurities
  - Superconductors: will have zero resistivity at certain T
- 

Ohm's law:  $I = \frac{V}{R}$

↖ resistance ( $\Omega$ )

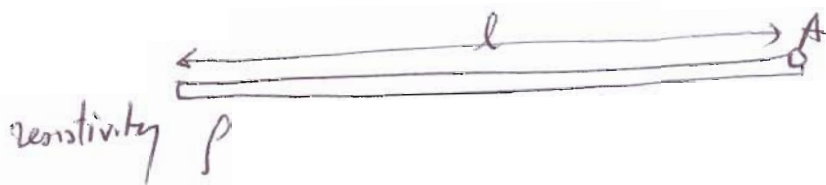


$$\boxed{R = \rho \frac{l}{A}}$$

↙ material-specific


Energy dissipation = lost energy when charged particles are moving thru the wire, in the form of heat loss:

$$P = IV \quad \left\{ \begin{array}{l} = \frac{V}{R} V \\ = I IR = I^2 R \end{array} \right. = \frac{V^2}{R}$$

power  
or heat loss  
per unit time



26.73

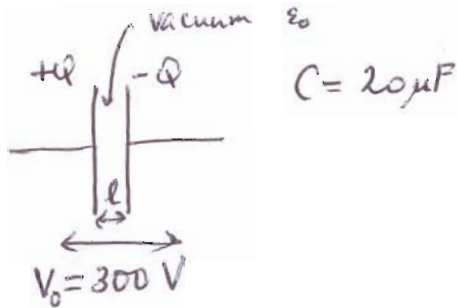


$$U_0 = \frac{1}{2} C_0 V_0^2$$

$$= \frac{1}{2} (20 \times 10^{-6}) 300^2$$

$$= 0.9 \text{ J}$$

Total energy stored =  $U_0$

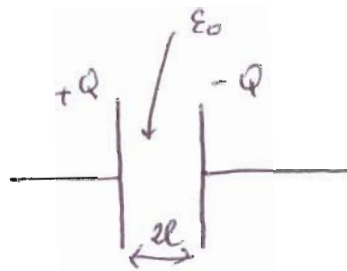

$$U = \frac{1}{2} C V^2 = \frac{1}{2} \frac{C_0}{2} (2V_0)^2 = \frac{1}{2} C_0 V_0^2 \cdot 2 = 2U_0$$

→ same charges since it is disconnected from the charging battery →  $E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$  (same)


$$\rightarrow C = \frac{Q}{V} \rightarrow E \cdot d = E \cdot 2d = 2V_0$$

$$= \frac{Q}{2V_0} = \frac{C_0}{2}$$


Total energy stored is  $2U_0$   
 Where did the extra  $U_0$  come from? → by pulling the plates apart.

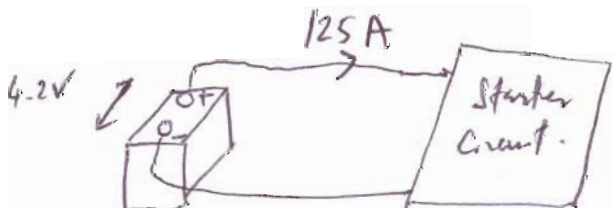27.41

$$\left. \begin{array}{l} V = 4.2 \text{ V} \\ I = 125 \text{ A} \end{array} \right\} R = ? \quad \frac{V}{I} = \frac{4.2 \text{ V}}{125 \text{ A}} = 0.0336 \Omega$$



27.45

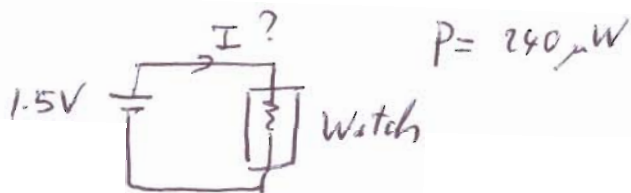

$$P = IV = \begin{cases} = \frac{V^2}{R} & (1) \\ = I^2 R & (2) \end{cases}$$

$$I = \frac{P}{V} = \frac{240 \times 10^{-6}}{1.5} \text{ A} = 160 \times 10^{-6} \text{ A} = 160 \mu A$$

27.58



Potassium (K):  $J = 470 \frac{\text{A}}{\text{m}^2}$

$$v_d = 0.2 \text{ nm/s}$$

Mass density  $\rho_K = 860 \frac{\text{kg}}{\text{m}^3}$

$N_e \equiv$  # of free electrons contributed by each atom of potassium?


$$I = nqAv_d \Rightarrow J = nqvd = n N_e e v_d$$

$$N_e = \frac{J}{n e v_d} = \frac{470 \times 10^3}{1.32 \times 10^{28} \times 1.6 \times 10^{-19} \times 0.2 \times 10^{-3}} = 1.1$$


We need to find  $n$  or # of atom of potassium per unit volume from the mass density for potassium =

$$n = \frac{\rho_K}{M_K} = \frac{860 \frac{\text{kg}}{\text{m}^3}}{39.10 \times 1.66 \times 10^{-27} \text{ kg}} = 1.32 \times 10^{28} \frac{\text{atoms K}}{\text{m}^3}$$

29.67 | GM's EVI (electric vehicle) }  $M = 1500 \text{ kg}$   
 26 12-V batteries in series.

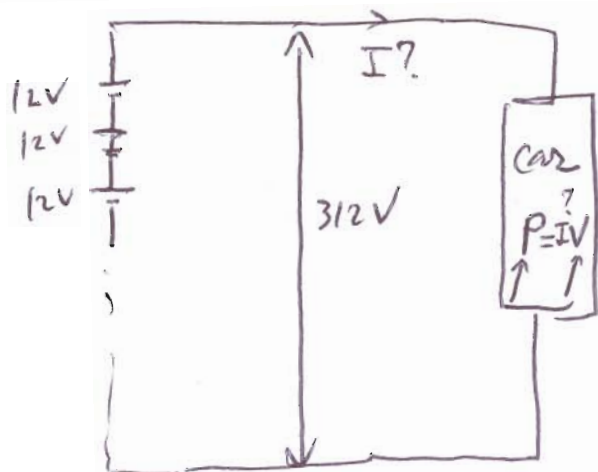

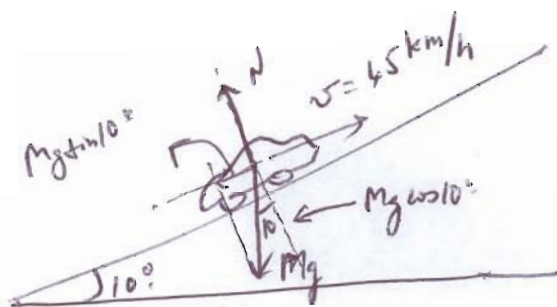85% of E. energy  $\rightarrow$  Mech. energy



No friction, no air resistance.

We need to overcome  $Mg \sin 10^\circ$  to bring car up the ramp at constant speed.

$$P = F \cdot \frac{d}{t} = F \cdot v = Mg \sin 10^\circ \cdot v$$

$$= 1500 \times 9.81 \times \sin 10^\circ \times \frac{45 \text{ km/h} \cdot \frac{1 \text{ h}}{3600 \text{ s}} \cdot \frac{1000 \text{ m}}{1 \text{ km}}}$$

$$= \underline{\underline{46 \text{ kW}}}$$


31940 W  $\rightarrow$  Mechanical power needed.

$$\rightarrow I = \frac{P_{\text{electrical}}}{V} = \frac{\left(\frac{31940}{0.85}\right)}{312} = 120 \text{ A}$$

# Series and parallel combination of resistors

## Parallel

Voltage across each is the same:  $V$

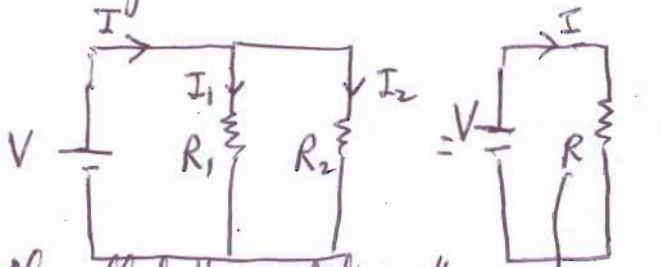

Also called "current division"

$$I = I_1 + I_2$$

(If  $R_1 > R_2$  :  $I_2 > I_1$ )

Ohm's law: relating

$$V_1, I_1, R_1$$

$$I_1 = \frac{V}{R_1}$$

$$V_1, I_2, R_2$$

$$I_2 = \frac{V}{R_2}$$

$$I = \frac{V}{R_1} + \frac{V}{R_2} = V \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= \frac{V}{\left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}}$$


$$\Rightarrow R = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$= \left( \frac{R_2 + R_1}{R_1 R_2} \right)^{-1}$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

## Series

Current thru each is the same  $I'$

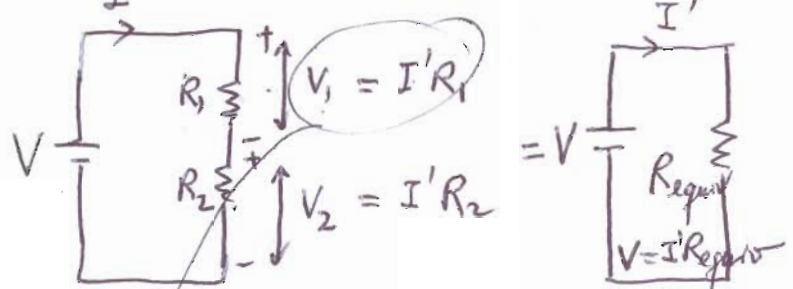

$$V = V_1 + V_2 = I'(R_1 + R_2)$$

$$V = I' R_{equiv}$$

$$R_{equiv} = R_1 + R_2$$

Consequences:  $I' = \frac{V}{R_{equiv}} = \frac{V}{R_1 + R_2}$

$$V_1 = \frac{V}{R_1 + R_2} R_1 = V \frac{R_1}{R_1 + R_2}$$

$$V_2 = V \frac{R_2}{R_1 + R_2}$$

Also called "voltage division"

Power consumption:  $R_1 = R_2 = R$

Parallel

$$R_{equiv} = \frac{R}{2}$$

$$P = I_1 V_1 = \frac{I}{2} V$$

$$= \frac{V}{R/2} \frac{V}{2}$$

$$= \frac{4V^2}{R}$$

Series

$$R_{equiv} = 2R$$

$$P' = I' V_1$$

$$= \frac{I}{2} \frac{V}{2}$$

$$= \frac{V}{2R} \frac{V}{2} = \frac{V^2}{4R}$$






# Ch. 28 Electric Circuits

Linear (relation b/w  $V$  &  $I$ )


2 types { - with resistors only:

- resistors and capacitors

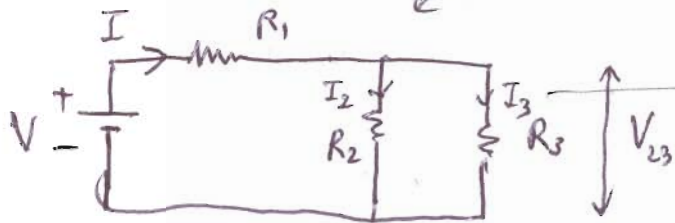
{ 1) reduce to  with series & parallel combinations  
2) can reduce to  using loop or node analysis



Given:  $V, R_1, R_2, R_3$

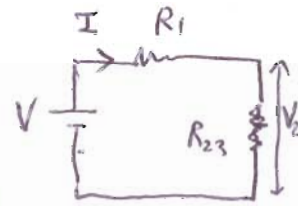

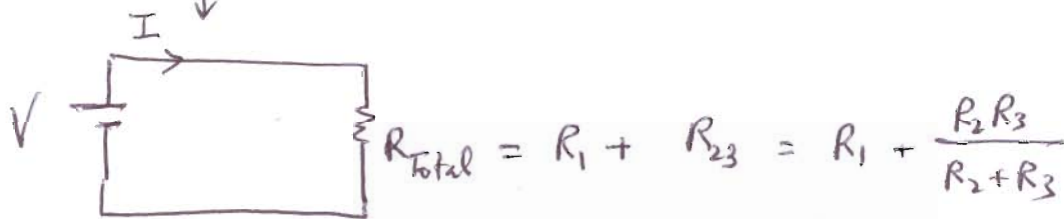
Solve for this circuits = providing  $I, I_2, I_3, V_{23}$



$$\textcircled{1} \quad I = \frac{V}{R_{\text{Total}}} = \frac{V}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} \quad \checkmark$$

$$\textcircled{2} \quad \frac{I_2}{I} = \frac{V_{23}}{V} = \frac{I \frac{R_2 R_3}{R_2 + R_3}}{I} = I \frac{R_3}{R_2 + R_3} \quad \checkmark \quad \left( V_{23} = I \frac{R_2 R_3}{R_2 + R_3} \right)$$
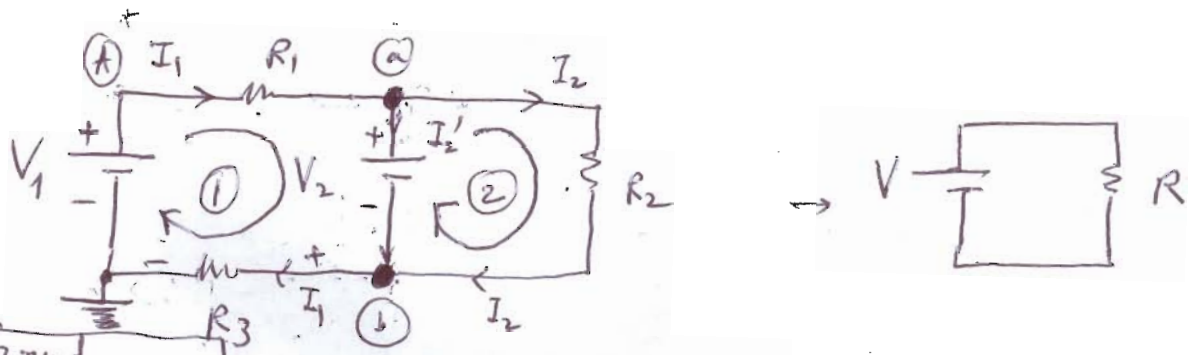
$$\textcircled{4} \quad I_3 = I - I_2 \quad \checkmark$$



Ground  
(ref. point  
for potential)

### Kirchoff's Laws.

#### Loop

Total voltage difference across elements in a closed loop = 0

→ Signs: assume a direction for current thru closed loops

- 1) Current thru a battery from - to + → positive sign
- 2) Current thru battery from + to - → negative sign.
- 3) Negative across any resistor (voltage drop)

#### Loop equations

$$\textcircled{1} +V_1 - I_1 R_1 - V_2 - I_3 R_3 = 0$$

$$\textcircled{2} +V_2 - I_2 R_2 = 0$$

$$I_1 = \frac{V_1 - V_2}{R_1 + R_3}$$

$$I_2 = \frac{V_2}{R_2}$$

#### Nodal

Total current at any node = 0

→ Signs:

- 1) Current into node → positive sign
- 2) Current leaving node → negative sign

$$\textcircled{a} +I_1 - I_2' - I_2 = 0 \quad \leftarrow$$

$$\textcircled{b} I_2' + I_2 - I_1 = 0 \quad (\text{repeated})$$

$$\frac{V_A - V_a}{R_1} - I_2' - \frac{V_a - V_b}{R_2} = 0$$

or

$$\frac{V_1 - (V_2 + I_1 R_3)}{R_1} - I_2' - \frac{V_2}{R_2} = 0$$

$$\rightarrow I_2' = \frac{V_1 - V_2}{R_1} - \frac{V_2}{R_2}$$


Find  $I_1$  &  $I_2$

$$I_1 = \frac{V_1 - (V_2 + I_1 R_3)}{R_1} \rightarrow I_1 R_1 + I_1 R_3 = V_1 - V_2$$

$$I_1 = \frac{V_1 - V_2}{R_1 + R_3}$$

isolated capacitor


26.47

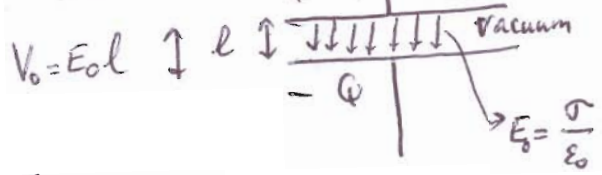

$$V_0 = E_0 l$$

$$C_0 = \frac{Q}{V_0}$$

$$U_0 = \frac{1}{2} C_0 V_0^2$$

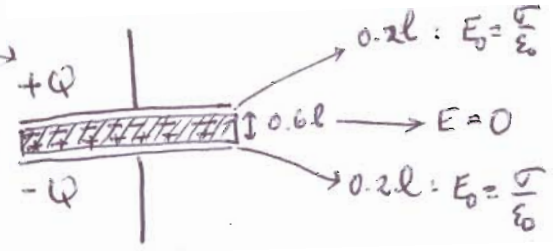

$$V = E_0 \times 0.2l + 0 \times 0.6l + E_0 \times 0.2l$$


$$= E_0 \times 0.4l = 0.4V_0$$

$$C = \frac{Q}{V} = \frac{Q}{0.4V_0} = 2.5 C_0$$

$$U = \frac{1}{2} C V^2 = \frac{1}{2} 2.5 C_0 (0.4V_0)^2$$

$$U = \frac{1}{2} C_0 V_0^2 \frac{2.5 \times 0.4^2}{0.4} = 0.4 U_0$$


26.37

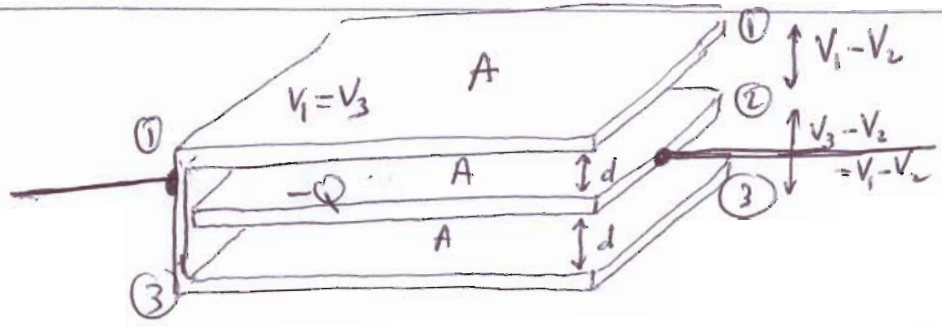

Prove:

$$C = \frac{2\epsilon_0 A}{d}$$

Neglect edge effects:

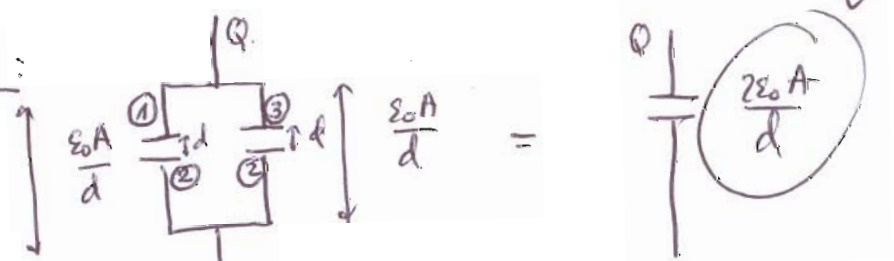

→ Same potential across 1 & 3 as 3 & 2 ✓

→  $Q_1 + Q_3 = Q$   
 $Q_2 = -Q$  } Assume 2 is -Q ✓

27.22



12-gauge copper wire  $\rightarrow$  20A  
 $d = 0.21\text{cm}$

$$a) J = \frac{I}{\text{Area}} = \frac{20\text{A}}{\pi \left(\frac{0.0021}{2}\right)^2} = 5.77 \times 10^6 \frac{\text{A}}{\text{m}^2}$$

$$b) E = \frac{J}{\sigma} = \rho J = 1.68 \times 10^{-8} \times 5.77 \times 10^6 \frac{\text{N}}{\text{C}} = 0.097 \frac{\text{N}}{\text{C}} \text{ or } 0.097 \frac{\text{V}}{\text{m}}$$

(Microscopic Ohm Law:  $J = \sigma E$ )

$\sigma$  or conductivity  $\left(\frac{1}{\Omega\text{m}}\right)$   
 $\downarrow$   
ohm

$\rho$  or resistivity  $\frac{1}{\sigma}$   
 $\left(\Omega\text{m}\right)$   
 $\downarrow$   
ohm

Table 27.1 :

$$\rho_{\text{copper}} = 1.68 \times 10^{-8} \Omega\text{m}$$

$$\left[ V = \frac{\text{N}}{\text{C}}\text{m} \rightarrow \frac{\text{N}}{\text{C}} = \frac{\text{V}}{\text{m}} \right]$$

---