


## Ch 32 Inductance & Magnetic Energy

Capacitance:

$$C = \frac{Q}{V}$$

Mutual Inductance

$$M = \frac{\phi_2}{I_1}$$

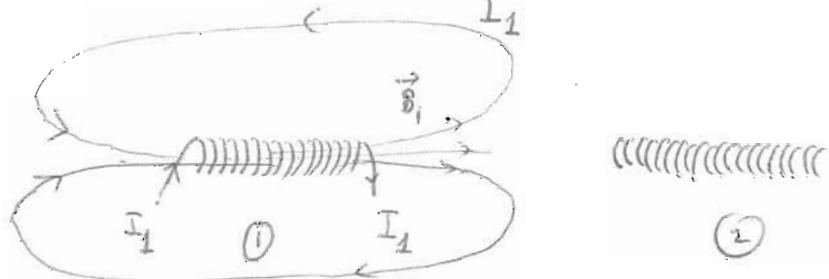

solenoid or electromagnet

similar to  
natural  
[S | N] magnet

$\phi_2$ : magnetic flux through solenoid #2 ("Phi") due to the magnetic field created by solenoid #1  $\rightarrow \vec{B}_1$ .

$\phi_2 = M I_1$  if  $I_1$  is changing with time  
 $\rightarrow \phi_2$  would be changing with time  $\rightarrow$  there will be a  $E_2$  inside solenoid #2 trying to compensate for any change in  $\phi_2$  (Faraday's law)

$$[-E_2 = \frac{d\phi_2}{dt} = M \frac{dI_1}{dt}]$$

it is clear here why  
M is called  
"mutual inductance"

Question:  $-E_1 = M \frac{dI_2}{dt}$ ? Yes! it is the same mutual inductance for a set of 2 solenoids or INDUCTORS

Now:  $\vec{B}_i$  also creates a magnetic flux through its solenoid (#1)  $\rightarrow \phi$  or the self-magnetic flux


$$L = \frac{\phi}{I} \quad ; \quad \text{"self inductance"}$$

$$\Rightarrow -\varepsilon = L \frac{dI}{dt}$$


$\downarrow$   
self-induced voltage      self current

Units:  $L$  or  $M$  :  $\frac{[\varepsilon]}{[I]} = \frac{V_s}{A} = H$  for Henry  
(SI system)

RC circuit:

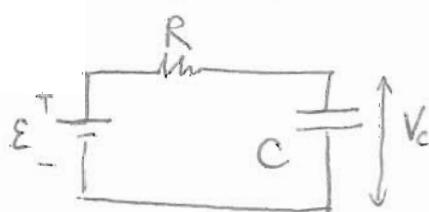


RL circuit:

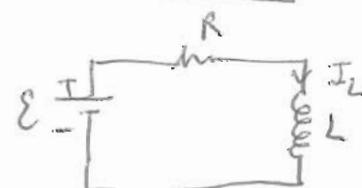

(Helix for inductors)  
or coils

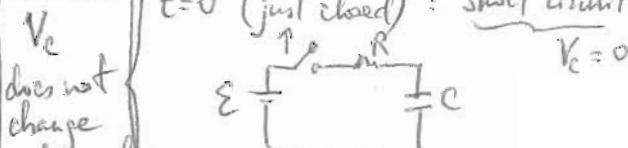$t=0$  (just closed): short circuit across  $C$   
 $V_c = 0$



$t=\infty$  (long after): open circuit across  $C$   
 $V_c = \infty$

$$I_C = \frac{\varepsilon}{R} e^{-\frac{t}{RC}}$$


(current decreases exponentially from  $\frac{\varepsilon}{R}$  to zero value)

$t=0$ : open circuit across  $L$   
 $I_L = 0$   
 $V_L = \varepsilon$

$t=\infty \rightarrow$  short circuit across  $L$   
 $V_L = 0$

$$V_L = \varepsilon e^{-\frac{t}{(L/R)}}$$

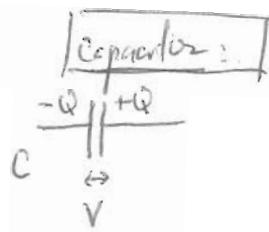(voltage decreases exponentially from  $\varepsilon$  to zero value)




$$U = \frac{1}{2} CV^2 \quad (\text{J})$$

$$\left[ u = \frac{U}{AL} = \frac{1}{2} \epsilon_0 E^2 \right] \quad \left( \frac{\text{J}}{\text{m}^3} \right)$$

volume

**inductor**

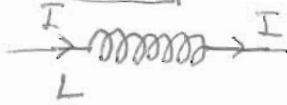

$$\mathcal{E} = -L \frac{dI}{dt}$$

$$\begin{aligned} U_L &= \int_0^t P_L dt = \int_0^t I \mathcal{E} dt = L \int_0^t I \frac{dI}{dt} dt \\ &= \frac{1}{2} L [I^2]_0^t = \boxed{\frac{1}{2} L I^2} \end{aligned}$$

$$\boxed{u_L = \frac{U_L}{Vol} = \frac{\frac{1}{2} L I^2}{AL} = \frac{1}{2} \frac{\mu_0 N^2}{A l^2} I^2 = \frac{1}{2} \frac{\mu_0 N^2 A^2}{l^2} B^2}$$




N turns

$$B = \frac{\mu_0 N I}{l} \rightarrow L = \frac{\phi}{I} = \frac{BAN}{I}$$

$$= \frac{\mu_0 N I}{l} A N$$


$$L = \frac{\mu_0 N^2 A}{l}$$

$$( C = \frac{A \epsilon_0}{d} )$$

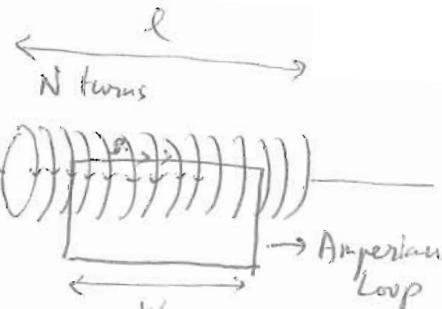

$$B_{ext} = \mu_0 \frac{NI}{l} \rightarrow B = \frac{\mu_0 NI}{l}$$

32.3i

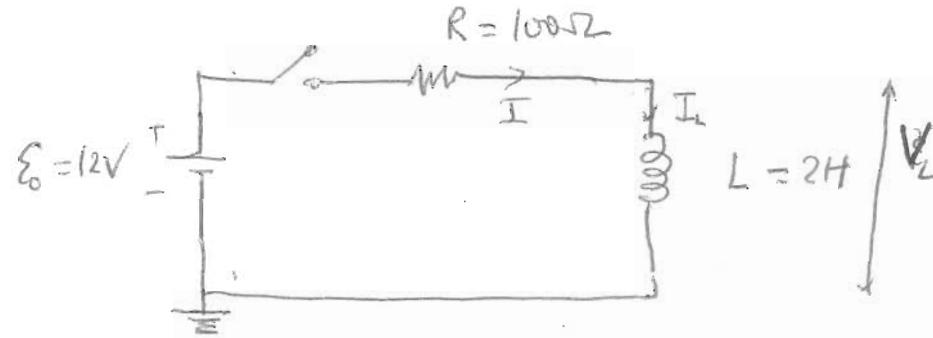

$t = 20\text{ms}$  after switch is closed:

$$\text{a) Circuit current : } I_L = I = \frac{E_0 - V_L}{R} = \frac{E_0 - (E_0 e^{-\frac{t}{L}})}{R}$$

$$= \frac{12 \left(1 - e^{-\frac{2 \times 10^{-2}}{0.02}}\right)}{100} = 75.9\text{mA}$$

$$\text{b) } V_L(t=20\text{ms}) = E_0 e^{-\frac{t}{L}} = 12 e^{-\frac{2 \times 10^{-2}}{0.02}} = 4.41\text{V}$$


$$\text{c) } V_R(t=20\text{ms}) = 12 - 4.41 = 7.59\text{V}$$

$$\text{d) } \frac{dI}{dt}(t=20\text{ms}) = \frac{dI_L}{dt}(t=20\text{ms}) = \frac{V_L(t=20\text{ms})}{L} = \frac{4.41}{2} = 2.2\text{A}$$

$$\left( \mathcal{E}_L = -L \frac{dI_L}{dt} \right)$$

$$\text{e) } P_R = IV_R = 75.9 \times 10^{-3} \times 7.59 = 0.576\text{W}$$

32-36


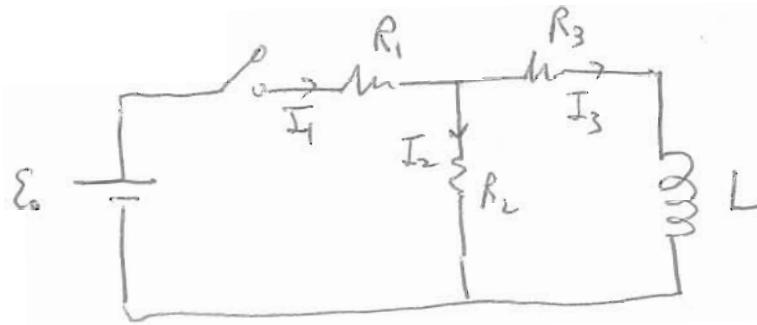


$$E_0 = 12V$$

$$R_1 = 4\Omega; R_2 = 8\Omega;$$


$$R_3 = 2\Omega; L = 2H$$

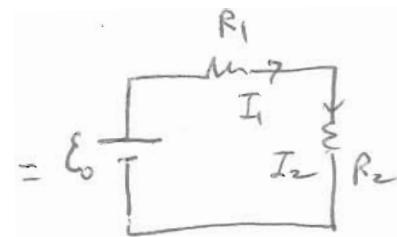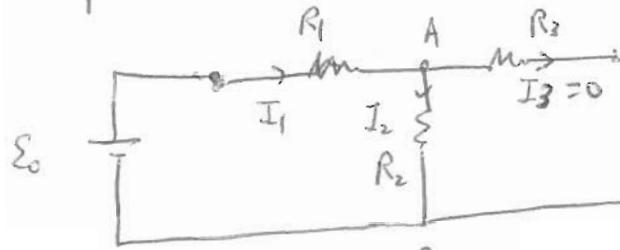$I_2$ ? a)  $t=0$  (right after switch is closed)  
open circuit across inductor for  $L$



$$I_2 = I_1 = \frac{12V}{4\Omega + 8\Omega} = 1A$$

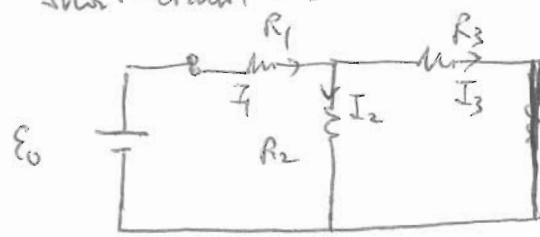b)  $t=\infty$  (long after switch is closed)  
short-circuit across  $L$



$$I_1 = I_2 + I_3$$

$$I_1 = \frac{E_0}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} = \frac{12}{4 + \frac{16}{10}} = \frac{12}{5.6} A = 2.14 A$$

Can get  $I_2$  or  $I_3$  from  $I_1$  by "current division":


$$I_2 = I_1 \frac{R_3}{R_2 + R_3} = 2.14 A \frac{2}{8+2} = 0.429 A$$

$$I_3 = I_1 \frac{R_2}{R_2 + R_3} = 2.14 A \frac{8}{8+2} = 1.71 A$$

Note:  
 $0.429 A$   
 $+ 1.71 A = 2.14 A$

c) Now switch is again opened :  $I_2$ ?

32.66

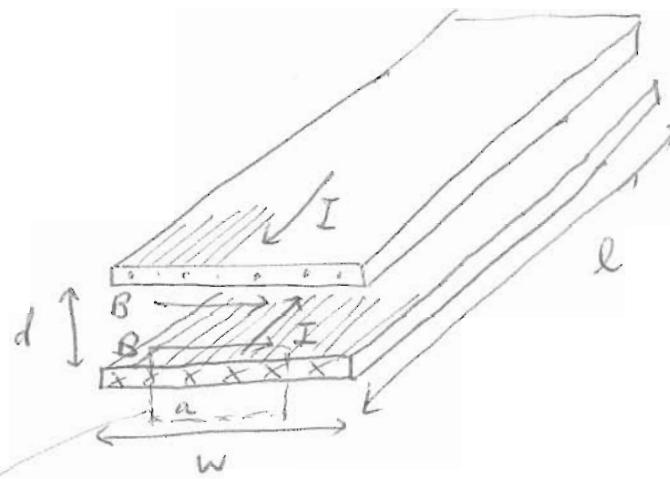

Vol b/w bars = dwl

a) B b/w bars using Ampere's law:

$$\text{Amperian loop } \not\rightarrow \rightarrow B \cdot l = \mu_0 I_{\text{enclosed}}$$

due to geometry of B: rectangle:

$$B \cdot l = \mu_0 \frac{I}{w} d$$

(assume field  
outside bars  
is zero)

$$\rightarrow B = \frac{\mu_0 I}{w}$$

$$b) \frac{U}{l} = \frac{n \times \text{Vol}}{l} = \frac{n \times dwl}{l} = \frac{B^2}{2\mu_0} dw = \frac{\mu_0 I^2}{2\mu_0 w^2} dw$$

$$\frac{U}{l} = \frac{\mu_0 I^2 d}{2w}$$

$$c) \text{ Compare this with } \frac{U}{l} = \frac{1}{2} L I^2 \quad \left. \right\} \boxed{\frac{L}{d} = \frac{\mu_0 d}{w}}$$

These structures ~ parallel plate capacitors

## Ch. 34 Maxwell's Equations & EM waves

- Gauss Law :  $\oint \vec{E} \cdot d\vec{A} = \frac{\text{charge}}{\epsilon_0}$   
 - ( )  $\oint \vec{B} \cdot d\vec{A} = 0$  (there are no magnetic monopoles discovered yet)

- Ampere's Law :  $\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{enclosed}} = \mu_0 \int \vec{J} \cdot d\vec{A} +$   
 - Faraday's Law :  $\oint \vec{E} \cdot d\vec{l} = - \int \frac{\partial \vec{B}}{\partial t} \cdot d\vec{A}$ 

 current  
 Maxwell's  
 contribution


$\left. \begin{array}{l} \text{change of magnetic} \\ \text{flux w.r.t. time} \\ \text{due to } \vec{B} \end{array} \right\}$

$$\mu_0 \epsilon_0 \frac{d\phi_E}{dt} = \mu_0 \epsilon_0 \frac{d}{dt} \int \vec{E} \cdot d\vec{A}$$

"displacement  
current"  
(unit: A)

This term gives complete symmetry for  $\vec{E}$  &  $\vec{B}$  in the sense: from Ampere's law: a time-varying  $\vec{E}$  is the source of a  $\vec{B}$ ; from Faraday's law: a time-varying  $\vec{B}$  is the source of a  $\vec{E}$ .  $\rightarrow$  EM waves

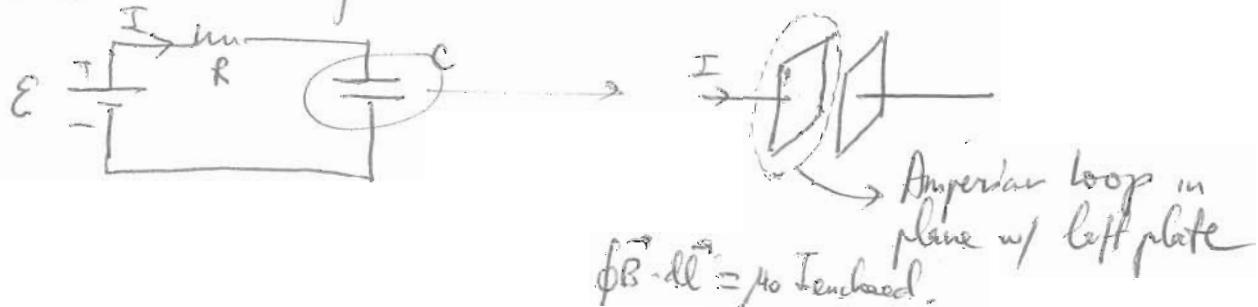A situation that requires this additional term is:



Since  $I$  stops at center of this Amperian loop w/o moving the loop  $\rightarrow I_{\text{enclosed}} = 0$

$\rightarrow \oint \vec{B} \cdot d\vec{l} = 0$  but there is a measurable magnetic field, when a AC power source is applied.

$\rightarrow$  Maxwell addition of  $\epsilon_0 \frac{d}{dt} \int \vec{E} \cdot d\vec{A}$  "the displacement current".

EM waves (electromagnetic waves) in vacuum:  $\left. \begin{array}{l} \text{no materials:} \\ \text{no charges, no} \\ \text{currents,} \\ \text{yes } \vec{E} \& \vec{B}! \end{array} \right\}$

Gauss' law:

$$\left. \begin{array}{l} \oint \vec{E} \cdot d\vec{A} = 0 \\ \oint \vec{B} \cdot d\vec{A} = 0 \end{array} \right\} \text{provide no info.}$$

Ampere's law:


$$\oint \vec{B} \cdot d\vec{l} = \mu_0 \epsilon_0 \frac{d\Phi_E}{dt} = \mu_0 \epsilon_0 \int \frac{\partial \vec{E}}{\partial t} \cdot d\vec{A}$$

Faraday's law:

$$\left. \begin{array}{l} \oint \vec{E} \cdot d\vec{l} = - \int \frac{\partial \vec{B}}{\partial t} \cdot d\vec{A} \end{array} \right\} \begin{array}{l} \leftarrow \text{complete symmetry} \\ \text{b/w } \vec{E} \& \vec{B} \text{ in} \\ \text{vacuum!} \end{array}$$

↳  $\vec{E}$  &  $\vec{B}$  creates themselves:  $E \xrightarrow[\substack{\text{time} \\ \text{varying}}]{} B \xrightarrow[\substack{\text{time} \\ \text{varying}}]{} E \xrightarrow[\substack{\text{time} \\ \text{varying}}]{} \dots = \text{EM waves}$
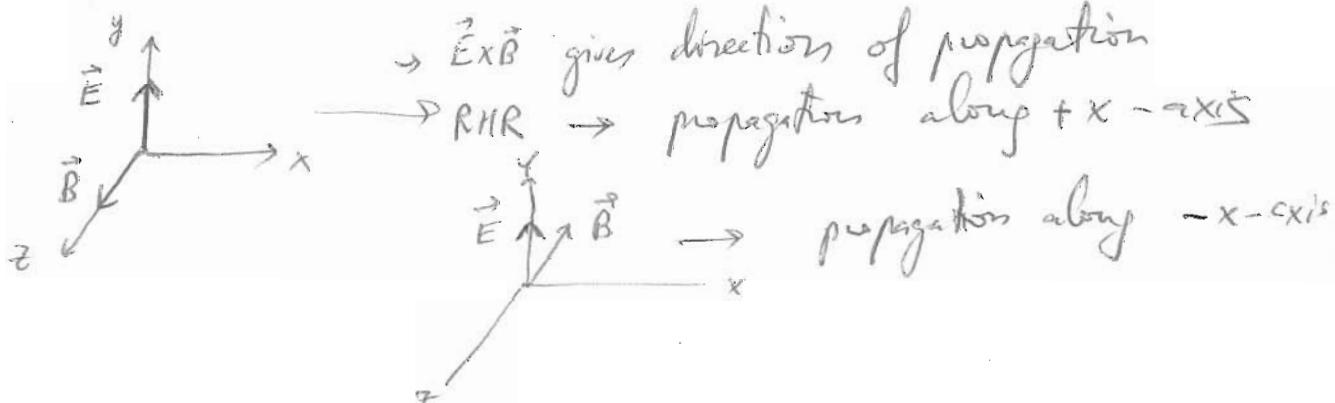
$$\left. \begin{array}{l} \vec{E} = E_p \sin(kx - wt) \hat{j} \\ \vec{B} = B_p \sin(kx - wt) \hat{k} \end{array} \right\} \text{they are perpendicular!}$$



along direction of propagation (either  $x, y$  or  $z$ )



10

$$\vec{E} = E_0 \sin(kx - \omega t) \hat{j}$$

position time  
wave number =  $\frac{2\pi}{\lambda}$   
wavelength.

magnitude or amplitude of  $E$

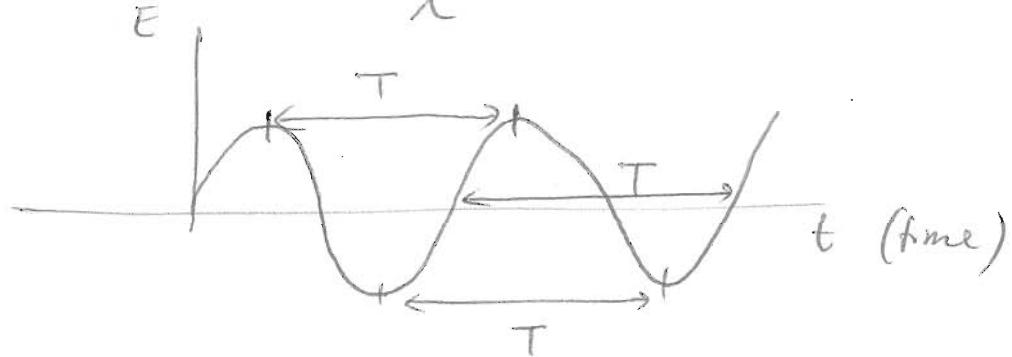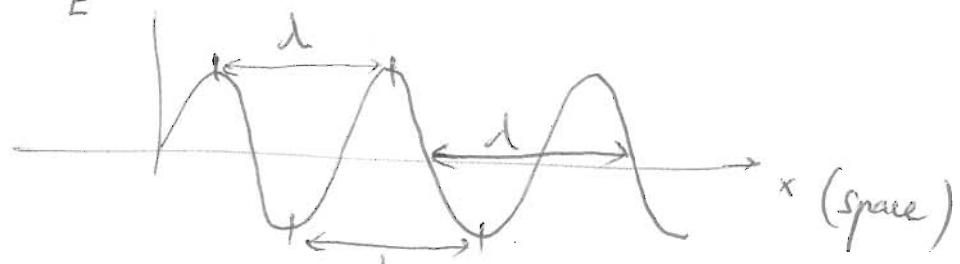angular frequency:  $\omega f$   
 $= \frac{2\pi}{T}$   
period



$$\vec{E} = E_0 \sin(kz - \omega t) \hat{k}$$

(direction of propagation was given by  $\vec{E} \times \vec{B}$  which is perpendicular to both  $\vec{E}$  and  $\vec{B}$ )  
if propagation is along  $z \rightarrow \vec{E}$  cannot point along  $z$  as well.