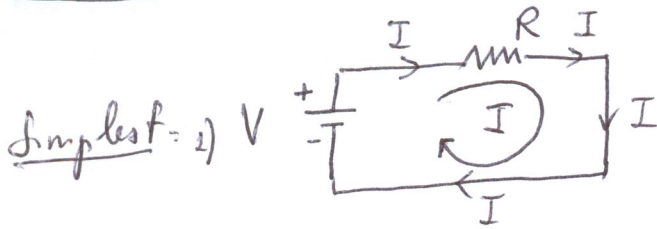


Ch 25 Electrical Circuits:

Circuits: batteries & resistors

(later will add capacitor, inductor)




$$I = \frac{V}{R} \text{ (Ohm's Law)}$$

linear circuits follow Ohm's Law

2) One battery & two resistors:

Parallel connection
(Current division)

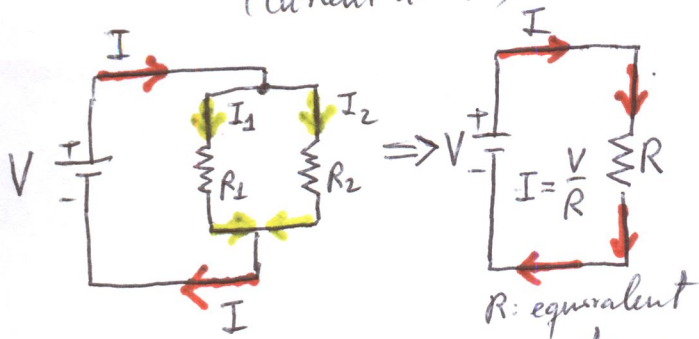

1) $I = I_1 + I_2$ Current division for R_1 & R_2

If we replace R_1 & R_2 by R , battery can't tell the difference as it draws the same current I out of the battery

2) Same voltage V is applied to R_1 & R_2

$$I = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$I = \frac{V}{R}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$R = \frac{R_1 R_2}{R_1 + R_2}$$

Current Division:

$$I_1 = \frac{V}{R_1} = \frac{I}{\left(\frac{1}{R_1} + \frac{1}{R_2} \right) R_1} = I \frac{1}{\frac{R_1 + R_2}{R_1 R_2}} = I \cdot \frac{R_2}{R_1 + R_2}$$

$$I_2 = \frac{V}{R_2} = \frac{I}{\left(\frac{1}{R_1} + \frac{1}{R_2} \right) R_2} = I \frac{1}{\frac{R_1 + R_2}{R_1 R_2}} = I \cdot \frac{R_1}{R_1 + R_2}$$

Series Connection
(Voltage division)

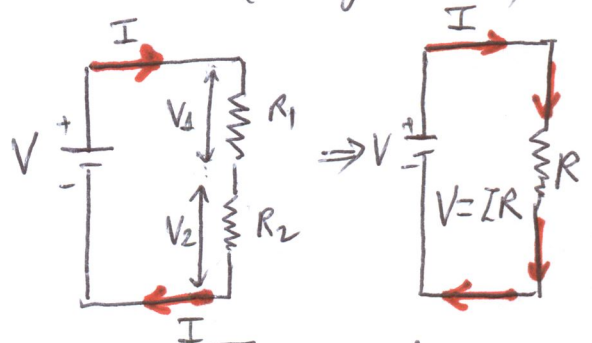

1) $V = V_1 + V_2$ Voltage division
 $V = IR$

2) Same current I goes through R_1 & R_2

$$V = IR_1 + IR_2 = I(R_1 + R_2) \Rightarrow R = R_1 + R_2$$

$$V = IR$$

Voltage Division:


$$V_1 = I \cdot R_1 = \frac{V}{R_1 + R_2} \cdot R_1 = V \cdot \frac{R_1}{R_1 + R_2}$$

$$V_2 = I \cdot R_2 = \frac{V}{R_1 + R_2} \cdot R_2 = V \cdot \frac{R_2}{R_1 + R_2}$$

Power Consumption $R_1 = R_2 = R$

$P = I \cdot V = \frac{V^2}{R} = I^2 R$
 $I = \frac{V}{R}$ or $V = IR$

Parallel

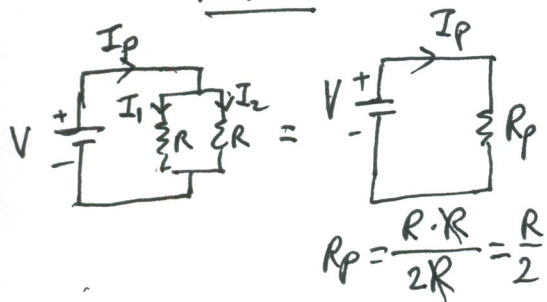


Power consumption can be calculated on either the original or the equivalent circuit:

$P_p = I_p \cdot V = \frac{V}{\frac{R}{2}} \cdot V = 2 \frac{V^2}{R}$

$I_1 = I_p \frac{R}{2R} = \frac{I_p}{2} = I_2$

Since $I_p = \frac{2V}{R} \rightarrow \begin{cases} I_1 = \frac{V}{R} \\ I_2 = \frac{V}{R} \end{cases}$

Series

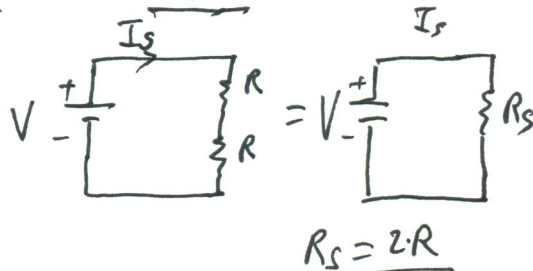


$P_s = I_s \cdot V = \frac{V}{2R} \cdot V = \frac{V^2}{2R}$



$I_s = \frac{V}{2R}$ (current through each R)
 (half compared to parallel connection)

$(P_s = \frac{P_p}{4})$ since $P = I^2 \cdot R$


light bulbs as resistors \rightarrow they are brighter in parallel connections!

Analysis of Circuits with Resistors Only

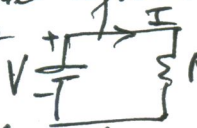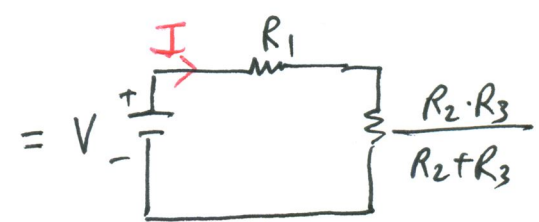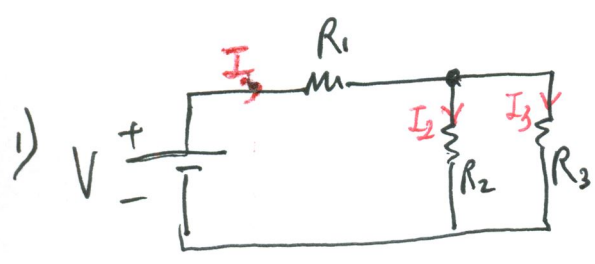- 1) Can use parallel/series equivalent to reduce to simplest  $I = \frac{V}{R}$
 Then find currents through each resistor.
- 2) Can't use parallel/series, there are more than one battery. Must use Loop or Node Analysis



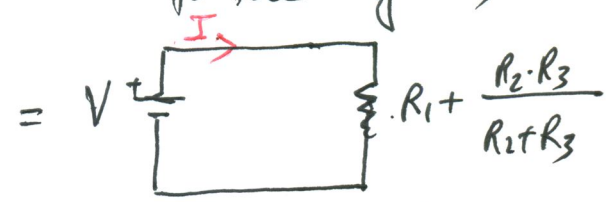same V, same I
(this circuit is equivalent to the original)



same V, same I
(this is also equivalent to the original circuit)

$$I = \frac{V}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3}}$$

Now we can find currents through individual resistors:


a) Current through R_1 is I

b) Current through R_2 & R_3 2 different ways:

(i) Use current division:

$$\begin{cases} I_2 = I \cdot \frac{R_3}{R_2 + R_3} = \frac{V}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3}} \cdot \frac{R_3}{R_2 + R_3} \\ I_3 = I \cdot \frac{R_2}{R_2 + R_3} \end{cases}$$


(ii) Use voltage division:

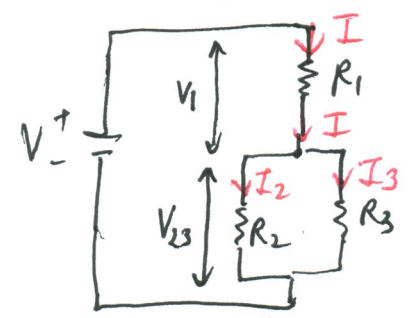

$$\begin{cases} I_2 = \frac{V_{23}}{R_2} = \frac{V \cdot \frac{R_2 \cdot R_3}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3}}}{R_2} \\ I_3 = \frac{V_{23}}{R_3} = \end{cases}$$

$V = V_1 + V_{23}$
& Ohm's Law

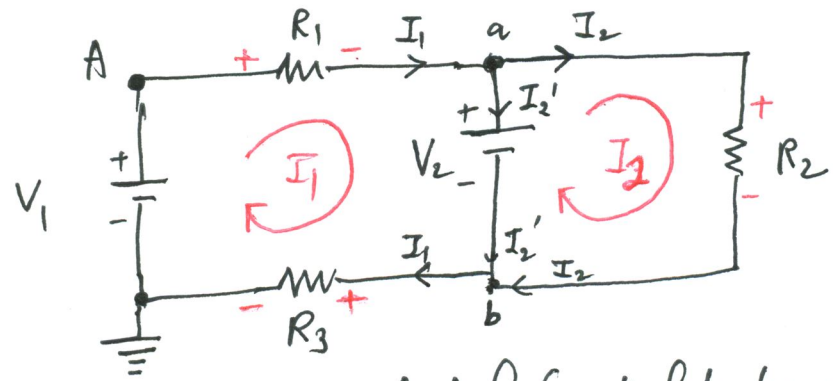2) Reduction to $V \frac{+I}{-I} R$ using only parallel & series equivalent is not possible \rightarrow use Loop or Node Analysis or Kirchoff's Laws



Ground or zero potential (critical to know for Loop/Node analysis)

- Note:
- 1) R_1 & R_2 are not in series as not same current going through both
 - 2) R_2 & R_3 are not in parallel as not same voltage across each of them

Loop Analysis

Kirchoff's Law: total voltage difference across elements in a closed loop (in the circuit) is 0
($\sum V_i = 0$)

Signs: first assume a direction for the current in each closed loop

- 1) If this current goes through battery from - to + \rightarrow battery voltage is positive. Negative if the opposite happens.
- 2) Voltage difference across any resistor is always negative.

Node Analysis

Kirchoff's Law: total current at any node in circuit is 0
($\sum I_i = 0$)

Signs:

- 1) Any current going into node is positive
- 2) Any current leaving node is negative

Loop Analysis

→ By visual inspection there are 2 loops

→ Assume CW currents in each loop I_1 & I_2

$$\text{Loop 1: } +V_1 - I_1 \cdot R_1 - V_2 - I_1 \cdot R_3 = 0$$

$$\left\{ \begin{array}{l} (V = \frac{V}{R} \text{ or } V = I \cdot R) \\ \text{Ohm's Law} \end{array} \right.$$

$$\text{Loop 2: } +V_2 - I_2 \cdot R_2 = 0$$

→ Find currents I_1 & I_2

$$I_1 = \frac{V_1 - V_2}{R_1 + R_3}$$

$$I_2 = \frac{V_2}{R_2}$$

$$I_1 - I_2 = I_2'$$

Node Analysis

(70)

→ Visual inspection: 2 nodes a, b

$$\text{Node a: } I_1 - I_2 - I_2' = 0$$

$$\text{Node b: } -I_1 + I_2 + I_2' = 0 \text{ (same equation)}$$

→ Only one independent node!

→ Write currents in terms of data (V_1, V_2, R_1, R_2, R_3) based on the location of the ground in circuit

$$\left. \begin{array}{l} V_A = V_1 \\ V_a = V_2 \oplus I_1 \cdot R_3 \end{array} \right\} I_1 = \frac{V_A - V_a}{R_1}$$


$$\rightarrow I_1 = \frac{V_1 - (V_2 + I_1 \cdot R_3)}{R_1}$$

$$I_1 \cdot R_1 = V_1 - V_2 - I_1 \cdot R_3$$

$$I_1 (R_1 + R_3) = V_1 - V_2$$
$$\boxed{I_1 = \frac{V_1 - V_2}{R_1 + R_3}}$$

also $\boxed{I_2 = \frac{V_2}{R_2}}$ (Ohm's law)
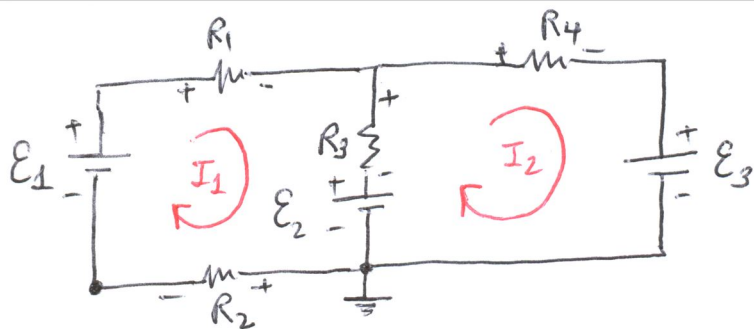
$$\text{Node a: } \frac{V_1 - V_2}{R_1 + R_3} - \frac{V_2}{R_2} = I_2'$$



$$E_1 = 6V$$

$$E_2 = 1.5V$$

$$E_3 = 4.5V$$

$$R_1 = 270\Omega; R_2 = 150\Omega$$

$$R_3 = 560\Omega; R_4 = 820\Omega$$

(71)

→ Find current through R_3 with direction (up or down)

Loop Analysis:

Visual inspection: 2 loops, assume CW currents I_1 & I_2

$$\text{Loop 1: } +E_1 - I_1 R_1 - \underbrace{(I_1 - I_2) R_3}_{\text{net current thru } R_3} - E_2 - I_1 R_2 = 0 \quad (1)$$

$$\text{Loop 2: } +E_2 - \underbrace{(I_2 - I_1) R_3} - I_2 R_4 - E_3 = 0 \quad (2)$$

Algebraic manipulations to solve for currents I_1 & I_2

$$(1) + (2) \rightarrow E_1 - E_3 - I_1 (R_1 + R_2) - I_2 R_4 = 0$$

$$\text{Solve for } I_1 \rightarrow I_1 = \frac{E_1 - E_3 - I_2 R_4}{R_1 + R_2} \quad (3)$$

$$\text{Eq(2): } E_2 - E_3 - I_2 (R_3 + R_4) + I_1 R_3 = 0$$

$$E_2 - E_3 - I_2 (R_3 + R_4) + \frac{E_1 - E_3}{R_1 + R_2} R_3 - I_2 \frac{R_3 R_4}{R_1 + R_2} = 0$$

$$E_2 - E_3 + \frac{E_1 - E_3}{R_1 + R_2} R_3 = I_2 \left(R_3 + R_4 + \frac{R_3 R_4}{R_1 + R_2} \right)$$


$$I_2 = \frac{E_2 - E_3 + \frac{E_1 - E_3}{R_1 + R_2} R_3}{R_3 + R_4 + \frac{R_3 R_4}{R_1 + R_2}}$$

$$I_2 = \frac{-3 + \frac{1.5}{420} \cdot 560}{1380 + \frac{560 \cdot 820}{420}}$$

$$\text{Eq(3): } I_1 = \frac{1.5 - (-0.4 \cdot 10^{-3}) 820}{420} = -0.4 \cdot 10^{-3} A = -0.4 \text{ mA}$$

$$\text{Current through } R_3 \text{ is } I_1 - I_2 = 4.76 - (-0.4) = 4.76 \text{ mA downward (+)}$$

Node Analysis:

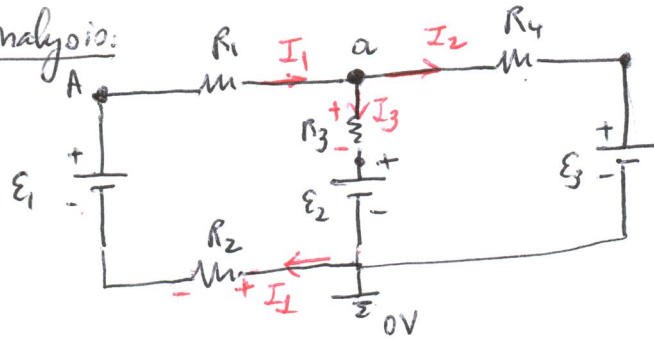

Same circuit
Current through R3?

- Visual inspection =
- (i) one independent node : a
 - (ii) assign directions for I_1, I_2, I_3 on circuit.
 - (iii) locate ground in circuit.

Node a: $I_1 - I_2 - I_3 = 0$

Now write these currents in terms of \mathcal{E} 's & R 's (data)

a) $I_1 = \frac{V_A - V_a}{R_1} = \frac{(\mathcal{E}_1 - I_1 R_2) - (I_3 R_3 + \mathcal{E}_2)}{R_1} = \frac{V_a}{\mathcal{E}_1 - I_1 R_2 - V_a}$
 Ohm's Law $I_1 R_1 = \mathcal{E}_1 - I_1 R_2 - V_a \rightarrow \boxed{I_1 = \frac{\mathcal{E}_1 - V_a}{R_1 + R_2}}$

b) $\boxed{I_2 = \frac{V_a - \mathcal{E}_3}{R_4}}$ (Ohm's Law through R_4)


c) $\boxed{I_3 = \frac{V_a - \mathcal{E}_2}{R_3}} \Rightarrow V_a = I_3 R_3 + \mathcal{E}_2$

$\frac{\mathcal{E}_1 - V_a}{R_1 + R_2} - \frac{V_a - \mathcal{E}_3}{R_4} - \frac{V_a - \mathcal{E}_2}{R_3} = 0$

$\frac{6 - V_a}{420} - \frac{V_a - 4.5}{820} - \frac{V_a - 1.5}{560} = 0 \Rightarrow V_a = 4.17 \text{ V}$

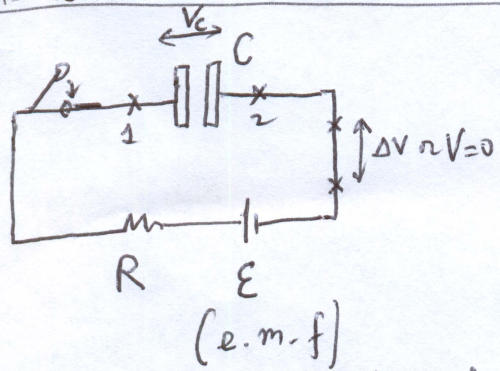c) $I_3 = \frac{4.17 - 1.5}{560} = 4.76 \text{ mA}$ (positive downward)


Circuits with both resistors & capacitors:




What happens if an uncharged capacitor of capacitance C is connected to rest of this circuit?

(e.m.f)
(electro motive force)

Starts connection to circuit

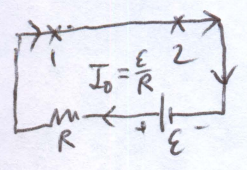

t	Q	V_C (potential across plates)	Capacitor behaves like	I
0	0	0	a wire "short circuit"	$\frac{E}{R} = I_0$ (max)
$t > 0$	Charges are moved by the current in the circuit. (harder to move next charge as it has to go against the new electric field)	$\neq 0$	current gets smaller! $I < I_0$	Loop equation: (w current I): $E - I'R - V_C = 0$ $I'R = E - V_C$ $I = \frac{E - V_C}{R}$ $= \frac{E}{R} - \frac{V_C}{R} < I_0$
$t \rightarrow \infty$	Capacitor is fully charge Max charge ↓ Max E ↓ max V_C	max $V_C = E$	open circuit	$I = 0$

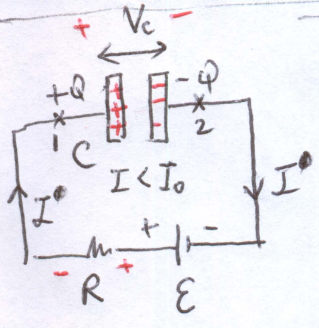

$$\frac{d}{dt}(E - IR - V_C) = 0$$

$$V_C = \frac{Q}{C} \rightarrow \frac{dV_C}{dt} = \frac{I}{C}$$



$$\frac{dE}{dt} = 0$$

$$\rightarrow -R \frac{dI}{dt} - \frac{I}{C} = 0$$


$$\frac{dI}{dt} = -\frac{I}{RC} \rightarrow \frac{dI}{I} = -\frac{dt}{RC}$$

$$\rightarrow \ln I = -\frac{t}{RC} + \text{constant}$$

$$I(t) = I_0 e^{-\frac{t}{RC}}$$

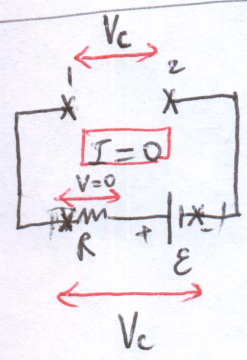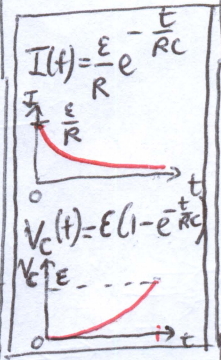

25.60]


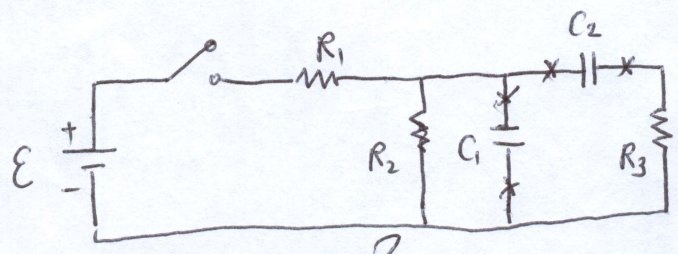


$R_1 = R_2 = R$
 Capacitors initially uncharged

Current in R_2 @ $t=0$ & @ $t \rightarrow \infty$?

Statements:

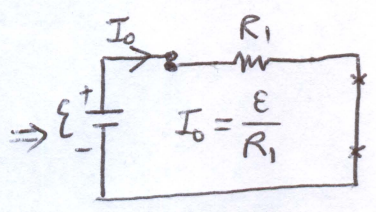
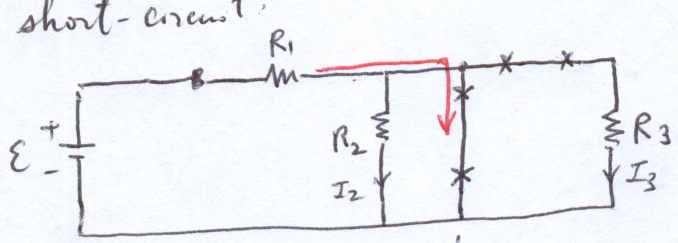
- 1) @ $t=0$ (just after switch is closed)
 $Q=0 \rightarrow V_c=0 \rightarrow$ capacitors behave like a piece of wire or short-circuit.



↓ wire: all current coming in from R_1 will go down this wire (path of least resistance)


Current in R_2 @ $t=0$ is 0 $I_2 = 0 = I_3$

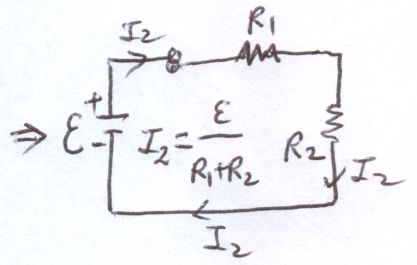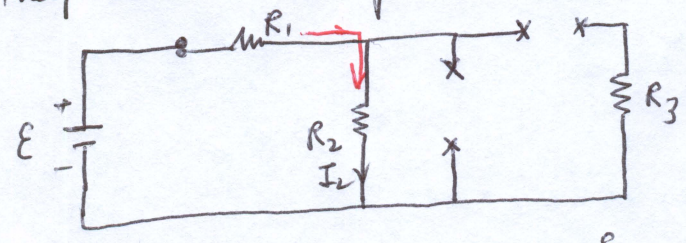- 2) @ $t \rightarrow \infty$: sufficiently long after, ^{both} the capacitors get fully charged? They don't allow any further current $I=0$
 \rightarrow they behave like open circuit:





Current in R_2 @ $t \rightarrow \infty$ is $I_2 = \frac{\epsilon}{R_1 + R_2}$

25.75

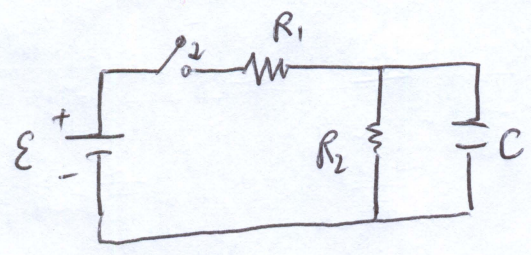

Write loop & Node equation & find time constant

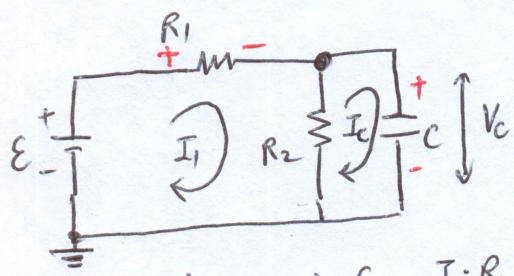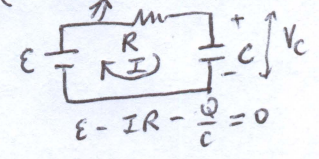(tan)
 Time constant τ time for current across capacitor to decay by a factor of e ($I(t) = I_0 e^{-\frac{t}{RC}} \rightarrow \tau = R \cdot C$)




Loop equation:

- $\epsilon - I_1 \cdot R_1 - (I_1 - I_2) \cdot R_2 = 0$
- $-(I_2 - I_1) \cdot R_2 - V_c = 0$ ($V_c = \frac{Q}{C}$)

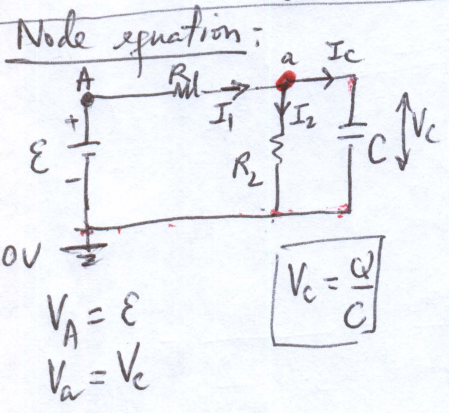(b) in (a) $+\frac{Q}{C} = I_1 \cdot R_2 = I_2 \cdot R_2$
 $= (\epsilon - \frac{Q}{C}) \frac{R_2}{R_1} - I_2 \cdot R_2$
 $\frac{d}{dt} \left[\frac{Q}{C} \left(1 + \frac{R_2}{R_1} \right) \right] = \epsilon \frac{R_2}{R_1} - I_2 \cdot R_2$
 $I_2 \left(\frac{1 + \frac{R_2}{R_1}}{C} \right) = - \frac{dI_2}{dt} \cdot \frac{R_2}{R_2 C} \Rightarrow \frac{dI_2}{I_2} = - \frac{R_1 + R_2}{R_1 R_2 C} dt = - \frac{dI_2}{I_2} \Rightarrow$

$-V_c = (I_2 - I_1) \cdot R_2$
 $-\frac{Q}{C} = -(I_1 - I_2) \cdot R_2$ (a)
 $I_1 = \frac{\epsilon - \frac{Q}{C}}{R_1}$ (b)



$I_1 - I_2 - I_3 = 0 \rightarrow$
 $I_1 = \frac{V_A - V_a}{R_1} = \frac{\epsilon - V_c}{R_1}$
 $I_2 = \frac{V_c}{R_2}$
 $I_3 = \frac{dQ}{dt}$

$\frac{\epsilon - V_c}{R_1} - \frac{V_c}{R_2} - \frac{dQ}{dt} = 0$

$\frac{\epsilon}{R_1} - V_c \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - I_3 = 0$

$\frac{d}{dt} \left[\frac{\epsilon}{R_1} - \frac{Q}{C} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - I_3 = 0 \right]$

$-\frac{1}{C} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \frac{dQ}{dt} - \frac{dI_3}{dt} = 0$

$\frac{dI_3}{dt} = - \frac{1}{C} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) I_3 \rightarrow \frac{dI_3}{I_3} = - \frac{dt}{C \left(\frac{1}{R_1} + \frac{1}{R_2} \right)} \rightarrow I_3(t) = I_0 e^{-\frac{t}{C \left(\frac{1}{R_1} + \frac{1}{R_2} \right)}} \rightarrow \tau$
 $\tau = \frac{C}{\left(\frac{1}{R_1} + \frac{1}{R_2} \right)} = \frac{C R_1 R_2}{R_1 + R_2}$

Cont. from Node Equation for 25.75:


$$-\frac{dt}{\left(\frac{R_1 R_2}{R_1 + R_2}\right) \cdot C} = \frac{dI_c}{I_c} \rightarrow \ln I_c = -\frac{t}{\frac{R_1 R_2}{R_1 + R_2} \cdot C}$$

$$I_c(t) = I_0 e^{-\frac{t}{\frac{R_1 R_2}{R_1 + R_2} \cdot C}}$$


$$\tau = \frac{R_1 R_2}{R_1 + R_2} \cdot C = \frac{C}{\left(\frac{R_1 + R_2}{R_1 R_2}\right)} = \frac{C}{\left(\frac{1}{R_2} + \frac{1}{R_1}\right)}$$

Ch 26 Magnetic Field

Electric field

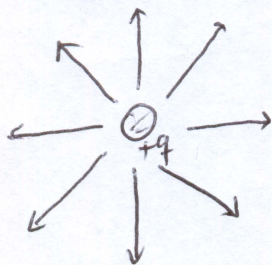

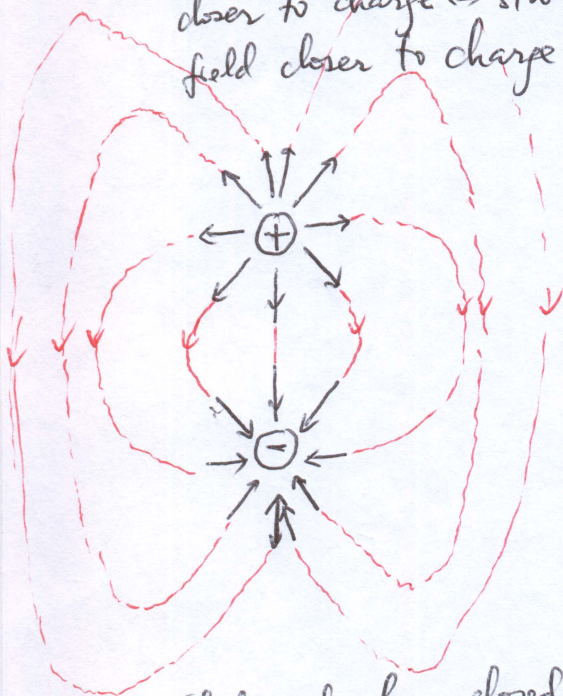→ Field lines = higher density closer to charge ↔ stronger field closer to charge




→ Electric dipoles: closed field lines

→ Effect: in printing, \vec{E} pushed the charged ink droplet off its original trajectory

Magnetic field

No magnetic monopole has been found.

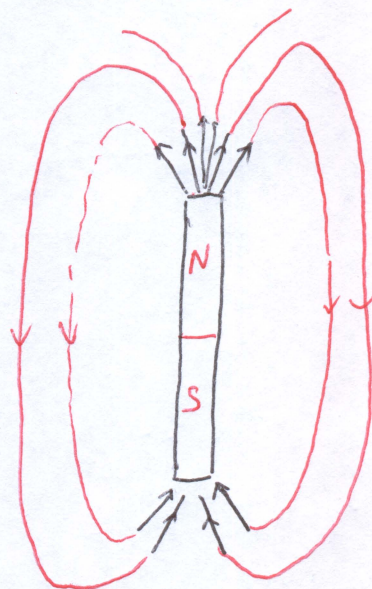

→ Magnets: always with 2 poles → Magnetic field lines are always closed

Effect: keep charged and moving particles in circular trajectories

$$\vec{F} = q \vec{v} \times \vec{B}$$

(Lorentz force by a magnetic field \vec{B} on a moving particle of charge q & velocity \vec{v})

(78)

$$\vec{F} = q\vec{v} \times \vec{B} \rightarrow F = qvB\sin\theta \quad (\theta \text{ angle b/w } \vec{v} \text{ \& } \vec{B})$$

↓
cross product → use RHR to find direction for \vec{F}
which is perpendicular to both \vec{v} & \vec{B}

A particle won't feel the magnetic force if:

- a) If it is neutral!
- b) If it is charged but static ($\vec{v} = 0$)
- c) If it is charged and moving along direction of the magnetic field (aurora borealis)

$$\vec{F} = q\vec{v} \times \vec{B} \rightarrow F = qvB\sin\theta \quad (\theta \text{ angle b/w } \vec{v} \text{ \& } \vec{B})$$

Cross product \rightarrow use RHR to find direction for \vec{F} which is perpendicular to both \vec{v} & \vec{B}

A particle won't feel the magnetic force if:



- a) If it is neutral!
- b) If it is charged but static ($\vec{v}=0$)
- c) If it is charged and moving along direction of the magnetic field (aurora borealis)

Region of magnetic field, uniform (not varying from point to point), pointing out of the page \odot

Dots are equally spaced in both directions

$$\vec{B} = B\hat{k}$$

\uparrow
unit vector in direction z

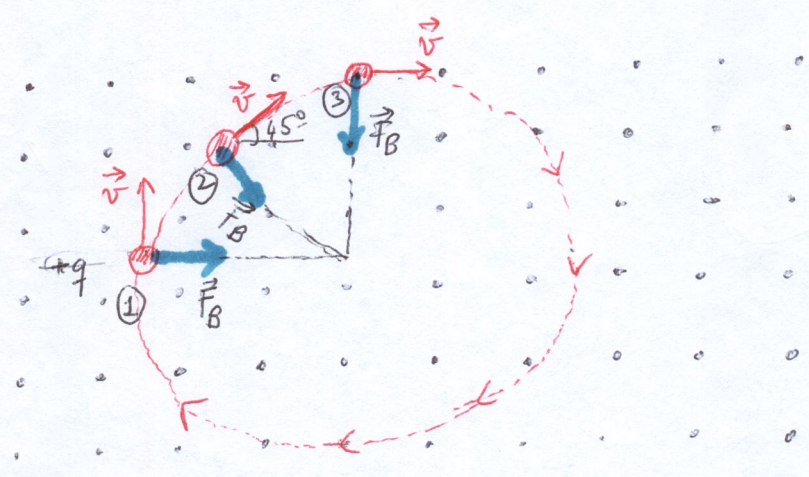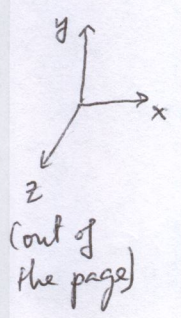

$$\textcircled{a} \textcircled{1} \quad \vec{v} = v\hat{j} \rightarrow \vec{F} = qvB\hat{i}$$

RHR: right hand fingers along 1st vector in the cross product, as we ~~to~~ close them toward the 2nd vector of the cross product, thumb points in the direction of the cross product

As long as the particle moves only in the XY plane, \vec{v} will always be perpendicular to the magnetic field \vec{B} , $\sin\theta = 1 \rightarrow F = qvB$

② $\vec{v} = v \left(\frac{\hat{i} + \hat{j}}{\sqrt{2}} \right) \rightarrow \vec{F} = qvB \left(\frac{\hat{i} - \hat{j}}{\sqrt{2}} \right)$
 1st quadrant 4th quadrant

③ $\vec{v} = v\hat{i} \rightarrow \vec{F} = qvB(-\hat{j})$

Conclusions:

a) Effect of \vec{B} was to confine the ^{moving} charged particle to go along a circular trajectory. In this case $\left\{ \begin{array}{l} \text{CW as charge is +} \\ \text{CCW if charge is -} \end{array} \right.$
 $(\vec{B} = B\hat{k})$ out of page
 $\downarrow r?$

b) Even in the presence of \vec{B} particle is subject to 2nd Newton's Law: $\vec{F}_{\text{net}} = m \cdot \vec{a}$

(i) Our charge follows a UCM (Uniform Circular Motion) = since \vec{F}_B is always perpendicular to \vec{v} , it only changes its direction but not its magnitude $\rightarrow v$ (speed) stays the same throughout the circular orbit.

(ii) The acceleration then is not tangential but radial (toward center of curvature) to changes the direction of velocity $\vec{v} \rightarrow a = \frac{v^2}{r}$

$q\cancel{v}/B = m \cdot \frac{v\cancel{v}}{r} \rightarrow \boxed{r = \frac{mv}{qB}}$
 $\left. \begin{array}{l} \rightarrow \text{larger } v \rightarrow \text{larger orbit} \\ \rightarrow \text{larger } B \rightarrow \text{smaller orbit.} \end{array} \right\}$

one application = particle physics detectors; plasma fusion




\rightarrow Orbital period: T: how long per orbit:

$\boxed{T = \frac{2\pi r}{v} = \frac{2\pi \frac{mv}{qB}}{v} = \frac{2\pi m}{qB}}$

Cyclotron (accelerate charged particles to high speed by running them through circular orbits multiple times)

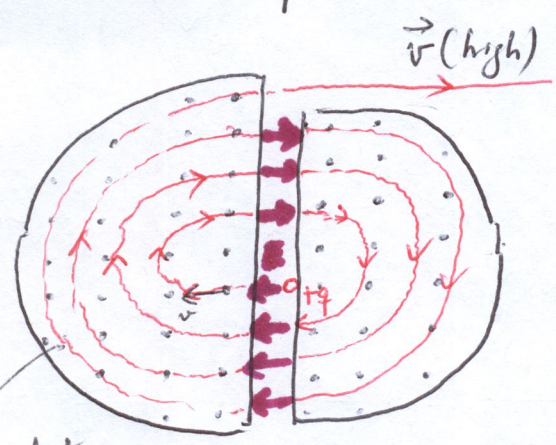- We can also accelerate charged particles to high speed using an electric field & a very long tunnel
- But cyclotron uses \vec{B} & \vec{E} can do the job in a smaller area like a hospital lab.



largest orbit
highest speed
Use radius of
Cyclotron R

- Two dees with a gap b/w them, where an alternating electric field is applied: left, right, left, etc.
- A uniform \vec{B} fill the dees pointing out of page

$$3) KE_{max} = \frac{1}{2} m v_{max}^2$$

$$r = \frac{mv}{qB} \rightarrow R = \frac{m v_{max}}{qB}$$

$$\rightarrow v_{max} = \frac{qBR}{m}$$


$$\rightarrow KE_{max} = \frac{1}{2} m \left(\frac{qBR}{m} \right)^2 = \frac{(qBR)^2}{2m}$$

Note: for $v \ll c = 3 \cdot 10^8 \frac{m}{s}$: Newtonian mechanics applies
 but if $v \rightarrow c$: we need relativistic corrections:
 → synchrotron

Velocity Selector:

We can pick among those ions with different velocities, particular ones with a selected velocity by running them through a region filled with both \vec{E} & \vec{B} .

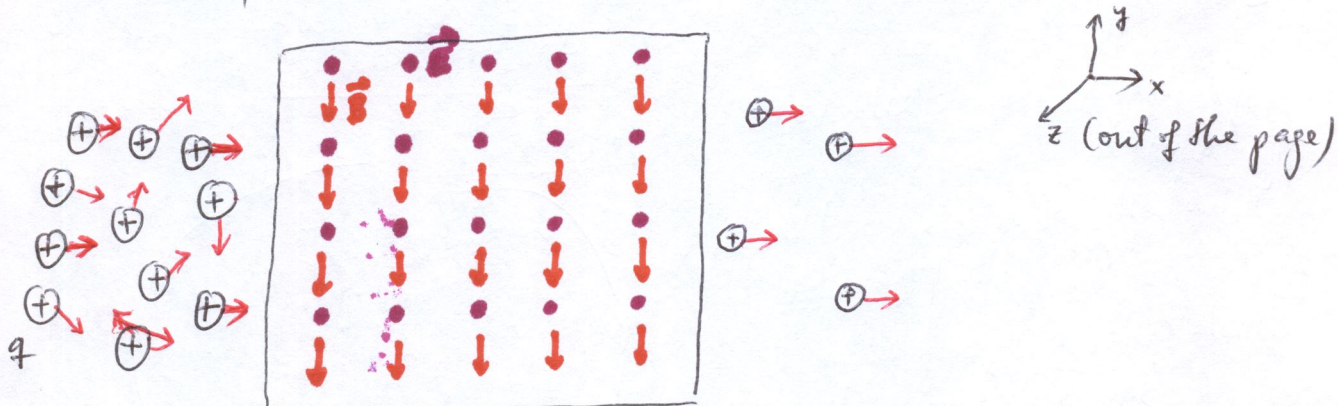For example, to pick among ions with velocities in random direction, those with velocities in the x-direction:



$$\vec{E} = E \hat{k} \quad \& \quad \vec{B} = B (-\hat{j})$$

For those ions with $\vec{v} = v \hat{i}$

$$\begin{cases} \vec{F}_E = q\vec{E} = qE \hat{k} \\ \vec{F}_B = qvB (-\hat{i} \times \hat{j}) = -qvB \hat{k} \end{cases}$$

$$\vec{F}_{net} = \vec{F}_E + \vec{F}_B = (qE - qvB) \hat{k} \quad \text{could be zero}$$

If $\vec{F}_{net} = 0 \rightarrow$ ions go through unaffected:

$$E - vB = 0 \quad \Rightarrow \quad \boxed{v = \frac{E}{B}}$$

Those ions with $\vec{v} = \frac{E}{B} \hat{i}$ they are "selected".

Calculation of the Magnetic Field (Sources of the Magnetic field):

Electric Field


Source → Charge

$$d\vec{E} = \frac{k dq}{r^2} \hat{r}$$

→ Coulomb's Law or Inverse-square law (field $\sim \frac{1}{r^2}$)

\hat{r} : radial unit vector

→ \vec{E} due to a line of charge

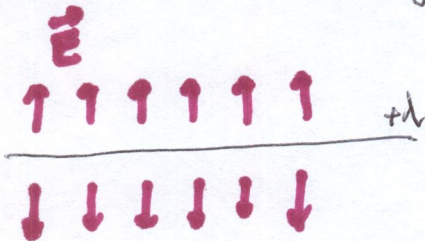

$$E = \frac{2k\lambda}{r}$$

r : separation from line of charge

Magnetic Field

Source → Moving charge or current

$$d\vec{B} = \frac{\mu_0}{4\pi} \frac{I d\vec{l} \times \hat{r}}{r^2}$$


→ Biot-Savart Law Inverse-square law

$$\mu_0 = 4\pi \times 10^{-7} \frac{N}{A^2}$$

permeability in vacuum


→ $d\vec{l} \times \hat{r}$: magnetic field due to a line of current wraps around the current:

→ \vec{B} due to a line of current.

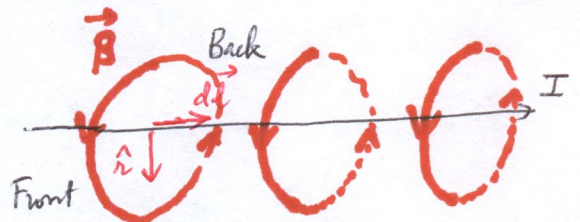

\vec{B} is related to its source I by RHR: if your RH thumb points along the current I [source], \vec{B} wraps around I like the RH fingers

Magnetic Field due to a Loop of Current:

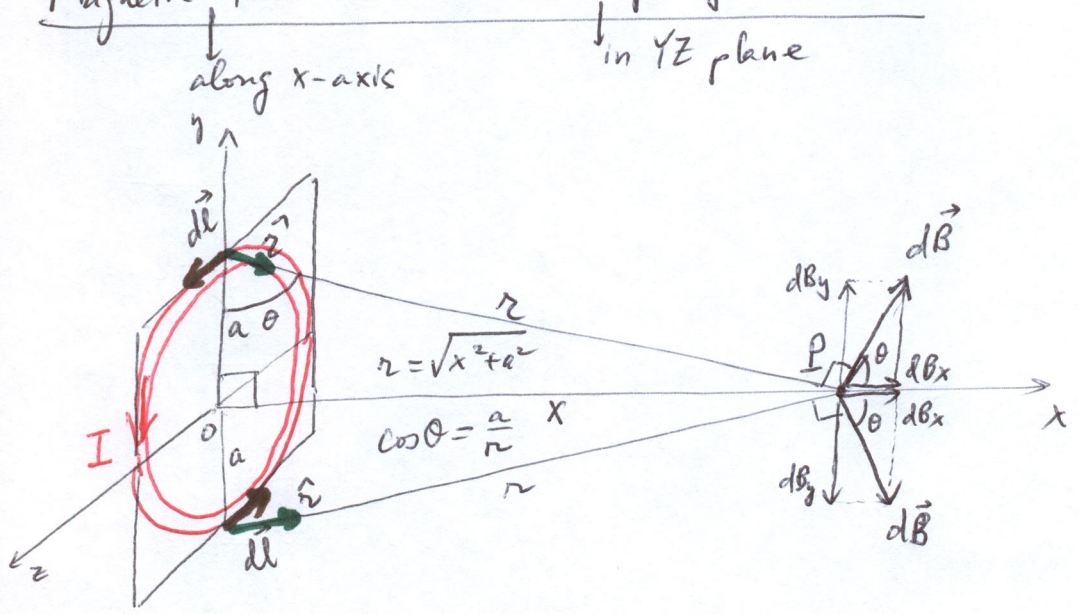

$d\vec{B}$: field @ P by an element of current $I d\vec{l}$, direction given by $d\vec{l} \times \hat{r}$

dB_y 's cancel each other
 dB_x 's are adding
 $dB_x = dB \cos \theta = \frac{dB \cdot a}{r}$

→ Magnetic field $d\vec{B}$ due to top + bottom elements of currents is

$$d\vec{B} = 2 dB_x \hat{i} = \frac{2 dB a}{r} \hat{i} \stackrel{\text{Biot-Savart}}{=} 2 \frac{\mu_0 I dl}{4\pi r^2} \frac{a}{r} \hat{i}$$

$$|d\vec{l} \times \hat{r}| = dl \quad \Rightarrow \quad = \frac{2\mu_0 I a}{4\pi r^3} dl \hat{i}$$

→ Total \vec{B} due to whole ring: $\vec{B} = \int_{\text{half ring}} d\vec{B} = \frac{2\mu_0 I a}{4\pi r^3} \hat{i} \int_{\text{Half Ring}} dl$

$\frac{\pi a}{\pi a}$

$$\boxed{\vec{B} = \frac{\mu_0 I a^2}{2 r^3} \hat{i} = \frac{\mu_0 I a^2}{2 (x^2 + a^2)^{3/2}} \hat{i}}$$



Observation: $x \gg a$ (very far from ring)

$$x^2 + a^2 \sim x^2 \rightarrow \frac{1}{(x^2 + a^2)^{3/2}} \rightarrow \frac{1}{x^3}$$

$$B \sim \frac{\mu_0 I a^2}{2 x^3} \quad (\text{inverse-cube law})$$

Recall: $E_{\text{dipole}} \sim \frac{1}{x^3}$ (far away from dipole)

26.44

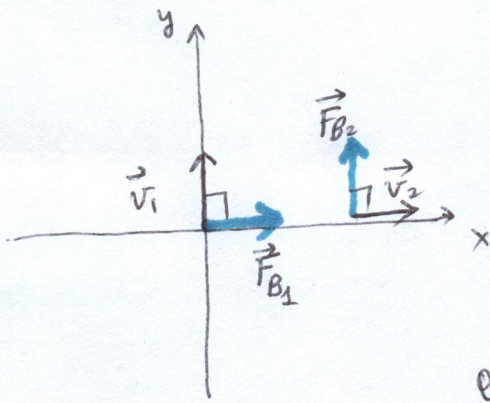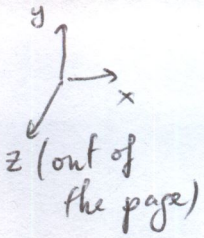

Data

- $\vec{v}_1 = 3.6 \times 10^4 \frac{m}{s} \hat{j}$
- $\vec{F}_{B1} = 7.4 \times 10^{-16} N \hat{i}$
- $\vec{v}_2 = v_2 \hat{i}$ $v_2 ?$
- $\vec{F}_{B2} = 2.8 \cdot 10^{-16} N \hat{j}$
- \vec{B} is uniform: $\vec{B} ?$


Magnetic force on a moving charge q and velocity \vec{v} :

$$\vec{F}_B = q \vec{v} \times \vec{B} = qvB \hat{k}$$

cross-product \rightarrow RHR for direction:
 magnitude is $qvB \sin \theta$

Discussion: 1) \vec{v}_1 & \vec{F}_{B1} are consistent with a negative charge only. $\vec{B} = B \hat{k}$

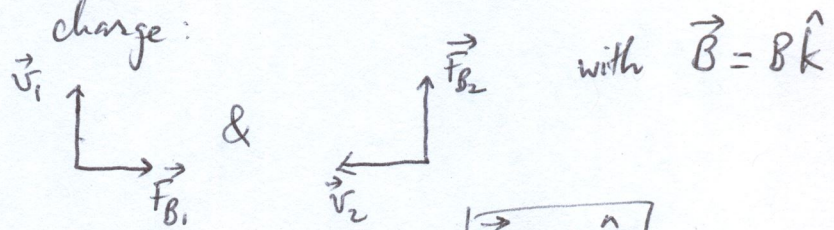2) Since we have two protons, which carry + charge:



Conclusions:

$\vec{v} = v_2 (-\hat{i})$ & $\vec{B} = B \hat{k}$
 angle θ is 90° since $\vec{B} \perp \vec{v}$


proton #1: $7.4 \cdot 10^{-16} = 1.6 \cdot 10^{-19} \cdot 3.6 \cdot 10^4 \cdot B$
 $B = \frac{7.4 \cdot 10^{-16}}{1.6 \cdot 10^{-19} \cdot 3.6 \cdot 10^4} = \frac{7.4 \cdot 10^{-1}}{1.6 \cdot 3.6} T$
 (Tesla)

proton #2: $2.8 \cdot 10^{-16} = 1.6 \cdot 10^{-19} v_2 \cdot 0.128$
 $v_2 = \frac{2.8 \cdot 10^{-16}}{1.6 \cdot 10^{-19} \cdot 0.128} = \frac{2.8 \cdot 10^3}{1.6 \cdot 0.128} \frac{m}{s}$
 $= 13.7 \cdot 10^3 \frac{m}{s}$

26.48

Cyclotron $\left\{ \begin{array}{l} d = 0.9 \text{ m} \\ B = 2 \text{ T} \\ \text{deuterium} = p + n \end{array} \right. \left\{ \begin{array}{l} q = +e \\ m = 2 \cdot 1.67 \cdot 10^{-27} \text{ kg} \end{array} \right.$

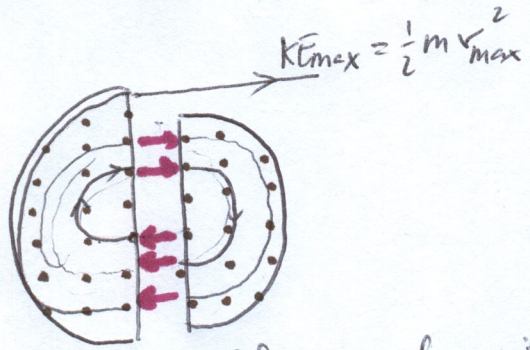a) what is the alternating frequency for the \vec{E} in the gap



\vec{E} cycle should coincide with deuterium cycle: $T = \frac{2\pi m}{qB}$

$$f = \frac{1}{T} = \frac{qB}{2\pi m} = \frac{1.6 \cdot 10^{-19} \cdot 2}{2\pi \cdot 2 \cdot 1.67 \cdot 10^{-27}} = 1.53 \cdot 10^7 \text{ Hz}$$

$\left\{ \begin{array}{l} T: \# \text{ of seconds per cycle} \\ f: \# \text{ of cycles per second} \end{array} \right.$

b) $KE_{max} = \frac{1}{2} m v_{max}^2$

$$\frac{(qBR)^2}{2m} = \frac{(1.6 \cdot 10^{-19} \cdot 2 \cdot 0.45)^2}{2 \cdot 2 \cdot 1.67 \cdot 10^{-27}} \text{ J}$$

$$= 3.1 \cdot 10^{-12} \text{ J}$$

$$r = \frac{mv}{qB} \rightarrow R = \frac{m v_{max}}{qB}$$

↑
Cyclotron radius

c) $V = 1500 \text{ V}$ $V = \frac{U}{q}$ (potential was potential energy per unit charge)


$$(E \cdot d = \frac{F \cdot d}{q})$$

Each crossing, deuterium will receive eV

crossings is $\frac{KE_{max}}{eV} = \frac{3.1 \cdot 10^{-12}}{1.6 \cdot 10^{-19} \cdot 1500} = 12934$

orbits is 6467 (2 crossings per orbit)


26.63

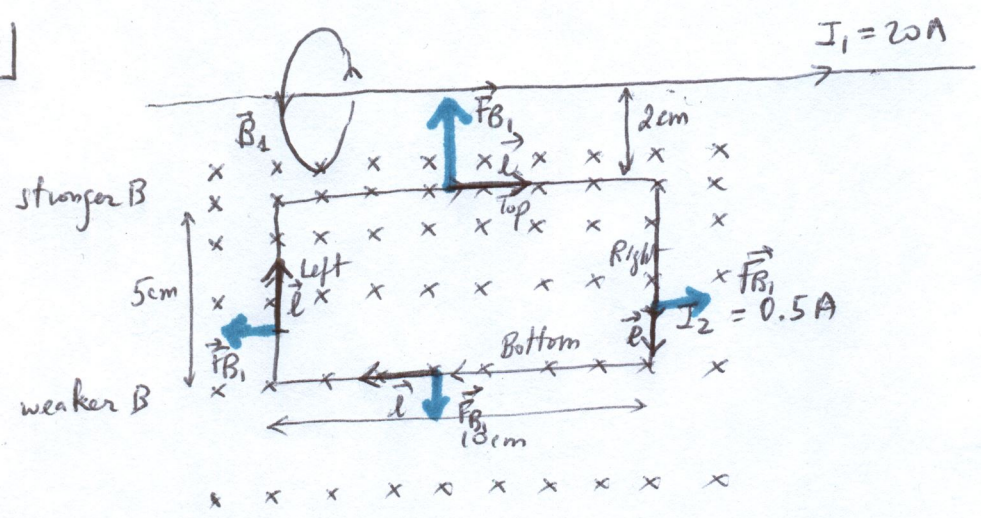

line of current
 ↓
 \vec{B}_1 wraps around,
 direction by RHR:
 in region below I_1
 it goes into the
 page x
 $\vec{B}_1 = \frac{\mu_0 I_1}{2\pi r} \hat{\theta}$

loop is form by 4 straight wires carrying I_2 , each in principle will feel the effect of \vec{B}_1 as given by:
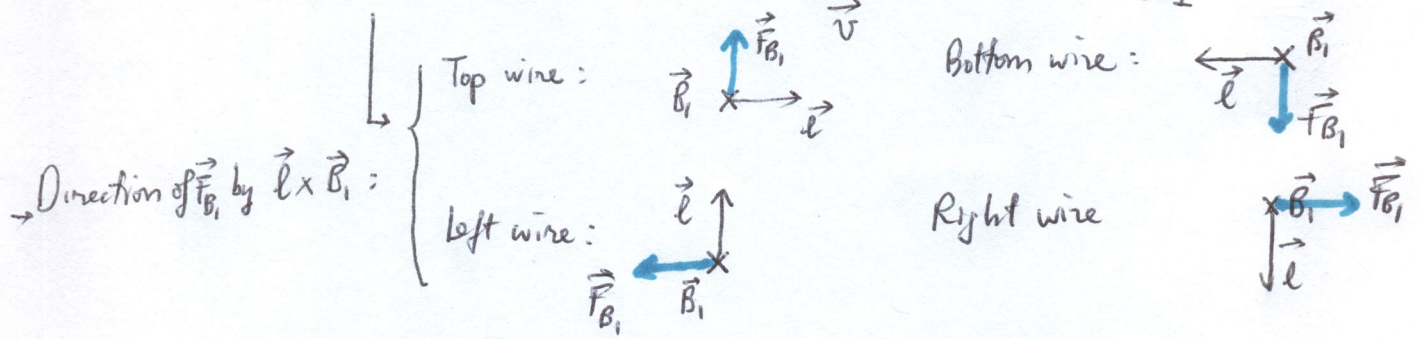
$$\vec{F}_{B_1} = q_2 \vec{v} \times \vec{B}_1 = I_2 \frac{d\vec{l}}{dt} \times \vec{B}_1 = I_2 \underbrace{d\vec{l} \times \vec{B}_1}_{\ell B_1 \sin 90^\circ \text{ \& direction by RHR}}$$



→ Magnitudes: $F_{B_1, \text{Top}} > F_{B_1, \text{Bottom}}$; $F_{B_1, \text{left}} = F_{B_1, \text{right}}$

$$\begin{aligned} \vec{F}_{B_1, \text{net}} &= F_{B_1, \text{Top}} \hat{j} - F_{B_1, \text{Bottom}} \hat{j} = \left(I_2 \ell \frac{\mu_0 I_1}{2\pi \cdot 0.02} - I_2 \ell \frac{\mu_0 I_1}{2\pi \cdot 0.07} \right) \hat{j} \\ &= \frac{\mu_0 I_1 I_2}{2\pi} \left(\frac{1}{0.02} - \frac{1}{0.07} \right) \hat{j} = \frac{2}{4\pi} \cdot 10^{-7} \cdot 0.1 \cdot 20 \cdot 0.5 \left(\frac{1}{0.02} - \frac{1}{0.07} \right) \hat{j} \\ &= 7.14 \cdot 10^{-6} \text{ N } \hat{j} \quad (\text{toward long straight line of current}) \end{aligned}$$

Calculation of Fields

Electric

→ Vector addition using Coulomb's Law

→ Gauss' Law

$$\oint \vec{E} \cdot d\vec{A} = \frac{q_{\text{enclosed}}}{\epsilon_0}$$

over a closed Gaussian surface

Electric flux Φ

→ Electric potential V
(Scalar → arithmetic addition)

$$\vec{E} = -\vec{\nabla} V$$

$$\vec{\nabla} = \frac{\partial}{\partial x} \hat{i} + \frac{\partial}{\partial y} \hat{j} + \frac{\partial}{\partial z} \hat{k}$$

Magnetic

- Vector addition using Biot-Savart law

→ Ampere's Law

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{enclosed}}$$

over a closed Amperian loop

→ Vector potential \vec{A}

$$\vec{B} = \vec{\nabla} \times \vec{A}$$

Rotational of \vec{A}
Curl of \vec{A}

Ampere's Law : $\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{enclosed}}$

Amperian loop


1) Determine the Amperian loop: so \vec{B} would be constant along that loop so it can be factored out.

$$\vec{B} \cdot \oint d\vec{l}$$

simple on simple loop { circumference
perimeter

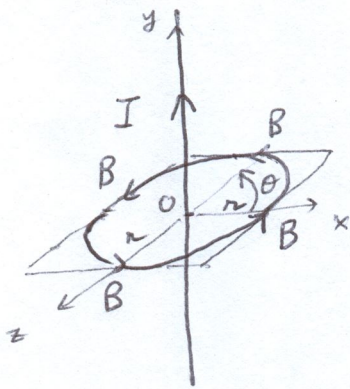2) Find current enclosed by that loop: I_{enclosed}

Magnetic field \vec{B} due to a long line of current I :



1) Amperian loop is a circle of radius r centered @ current

θ is angle from x -axis on xz plane

$\rightarrow \hat{\theta}$ goes around loop $\rightarrow \vec{B} = B(r) \hat{\theta}$


$$\oint_{\text{Along Amperian loop}} \vec{B} \cdot d\vec{l} = B(r) \cdot \underbrace{\oint dl}_{\text{Circumference } 2\pi r}$$

2) Current enclosed by this loop is I

\rightarrow Ampere's Law:

$$B \cdot 2\pi r = \mu_0 I \rightarrow B = \frac{\mu_0 I}{2\pi r}$$

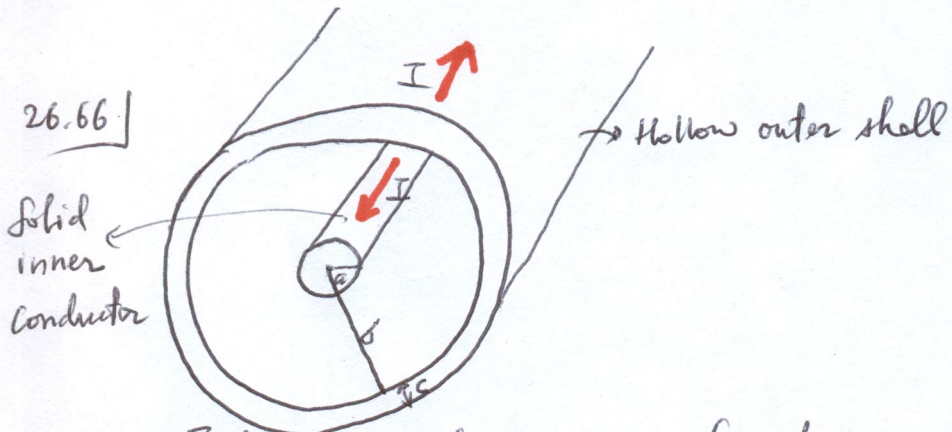
$$\boxed{\vec{B} = \frac{\mu_0 I}{2\pi r} \hat{\theta}}$$



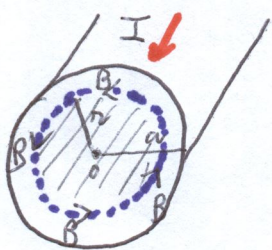a) Find $B(r)$ when $r < a$ (inside inner conductor):

Ampere's Law:


$$B \cdot 2\pi r = \mu_0 I \frac{r^2}{a^2} \rightarrow \boxed{B(r) = \frac{\mu_0 I}{2\pi a^2} r}$$



I goes through solid inner conductor cross sectional area πa^2

$$I_{\text{enclosed}} = \frac{\pi r^2}{\pi a^2} I$$

b) Find $B(r)$ when $a < r < b$

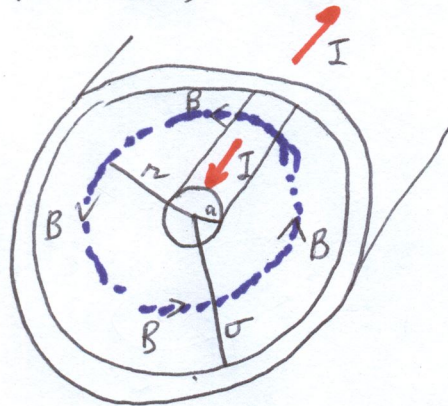

Ampere's law:

$$B \cdot 2\pi r = \mu_0 I$$


circumference
of Amperian
loop

$$B(r) = \frac{\mu_0 I}{2\pi r}$$

Field due to a long wire
of current.

In this region $a < r < b$
outer shell has no effect.

c) Find $B(r)$ when $r > (b+c)$

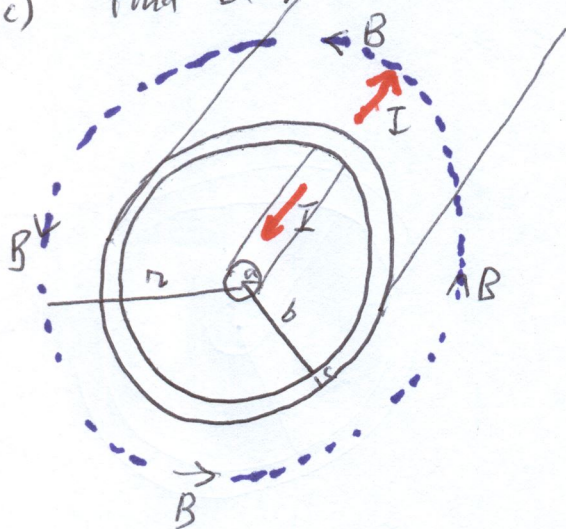

Ampere's law:


$$B \cdot 2\pi r = \mu_0 \cdot \frac{I - I}{0}$$

$$B(r) = 0$$

↓

Coaxial cable shields
outside environment from
the magnetic field due to
the inner conductor

26-74

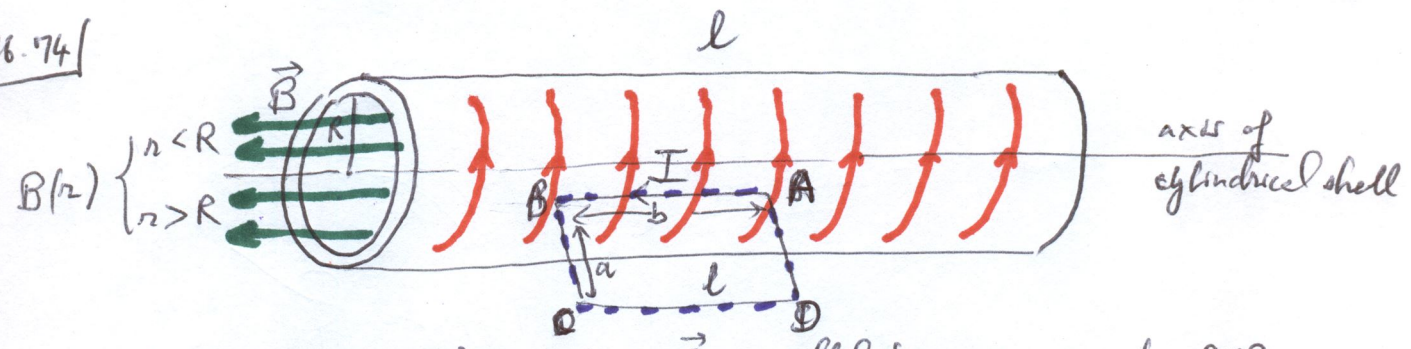

Magnetic field: ring of current $\rightarrow \vec{B}$ parallel to axis given by RHR

1) $B(r)$ $r < R$:
Ampere's Law

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{\text{enclosed}}$$

Ampere's loop: $ABCD$: $\int_{AB} \vec{B} \cdot d\vec{l} + \int_{BC} \vec{B} \cdot d\vec{l} + \int_{DA} \vec{B} \cdot d\vec{l} + \int_{CD} \vec{B} \cdot d\vec{l}$

$\cos 90^\circ = 0$ $\cos 90^\circ$

$= B \cdot b$

Current enclosed: $I_{\text{enclosed}} = I \frac{b}{R}$ \rightarrow $B \cdot b = \mu_0 I \frac{b}{R}$

$B = \frac{\mu_0 I}{R}$

2) $B(r) = 0$ $r > R$:

26-26