

Problem 10.6

Sketch a phasor representation of a balanced three-phase system containing both phase voltages and line voltages if $\mathbf{V}_{ab} = 208\angle 45^\circ$ V rms. Label all phasors and assume an *abc*-phase sequence.

Suggested Solution

$$\mathbf{V}_{ab} = 208\angle 45^\circ \text{ V rms}$$


$$\mathbf{V}_{an} = \frac{|\mathbf{V}_{ab}|}{\sqrt{3}} \angle (\theta_{\mathbf{V}_{ab}} - 30^\circ) = 120\angle 15^\circ \text{ V rms}$$

$$\mathbf{V}_{bc} = 208\angle -75^\circ \text{ V rms}$$

$$\mathbf{V}_{bn} = 120\angle -105^\circ \text{ V rms}$$

$$\mathbf{V}_{ca} = 208\angle 165^\circ \text{ V rms}$$

$$\mathbf{V}_{cn} = 120\angle 135^\circ \text{ V rms}$$

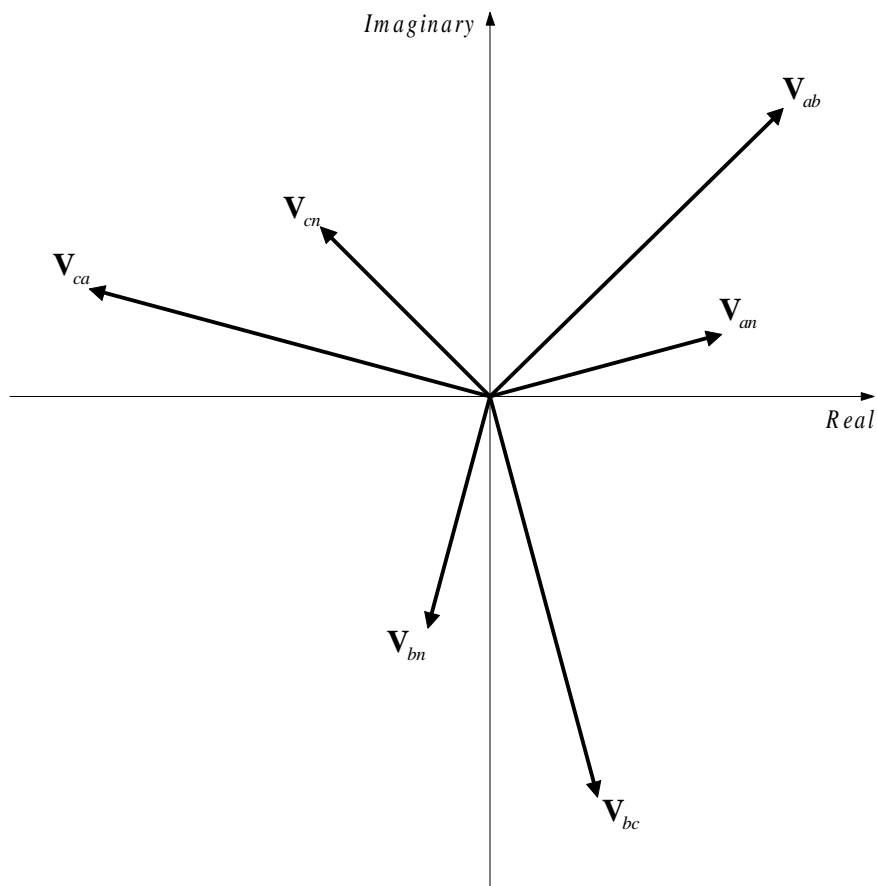

Problem 10.14

In a balanced three-phase wye-wye system, the source is an *abc*-sequence set of voltages. $\mathbf{Z}_{line} = 1 + j1.8 \, \Omega$, $\mathbf{Z}_{load} = 14 + j12 \, \Omega$, and the load voltage on the *a* phase is $\mathbf{V}_{AN} = 398.1 \angle 17.99^\circ \text{ V rms}$. Find the line voltage \mathbf{V}_{ab} .

Suggested Solution

$$\mathbf{I}_a = \frac{\mathbf{V}_{AN}}{\mathbf{Z}_{load}} = \frac{398.1 \angle 17.99^\circ}{14 + j12} = 21.59 \angle -22.61^\circ \text{ A rms}$$

$$\mathbf{V}_{an} = \mathbf{I}_a (\mathbf{Z}_{line} + \mathbf{Z}_{load}) = (21.59 \angle -22.61^\circ)(15 + j13.8) = 440 \angle 20^\circ \text{ V rms}$$

$$\Rightarrow \mathbf{V}_{ab} = 440\sqrt{3} \angle 50^\circ = 762.1 \angle 50^\circ \text{ V rms}$$

Problem 10.25

In a balanced three-phase delta-wye system the source had an *abc*-phase sequence. The line and load impedances are $0.6 + j0.3 \, \Omega$ and $12 + j7 \, \Omega$, respectively. If the line current $\mathbf{I}_{aA} = 9.6 \angle -20^\circ \text{ A rms}$, determine the phase voltages of the source.

Suggested Solution

$$\mathbf{V}_{an} = (9.6 \angle -20^\circ)(12.6 + j7.3) = 139.78 \angle 10.09^\circ \text{ V rms}$$

$$\mathbf{V}_{ab} = 139.78\sqrt{3} \angle (10.09^\circ + 30^\circ) = 242.11 \angle 40.09^\circ \text{ V rms}$$


$$\mathbf{V}_{bc} = 242.11 \angle (40.09^\circ - 120^\circ) = 242.11 \angle -79.91^\circ \text{ V rms}$$

$$\mathbf{V}_{ca} = 242.11 \angle (40.09^\circ + 120^\circ) = 242.11 \angle 160.09^\circ \text{ V rms}$$

Problem 10.36

In a balanced three-phase system, the *abc*-phase-sequence source is wye connected and $\mathbf{V}_{an} = 120 \angle 20^\circ \text{ V rms}$. The load consists of two balanced wyes with phase impedances of $8 + j6 \, \Omega$ and $12 + j8 \, \Omega$. If the line impedance is zero, find the line currents and the phase currents in each load.

Suggested Solution

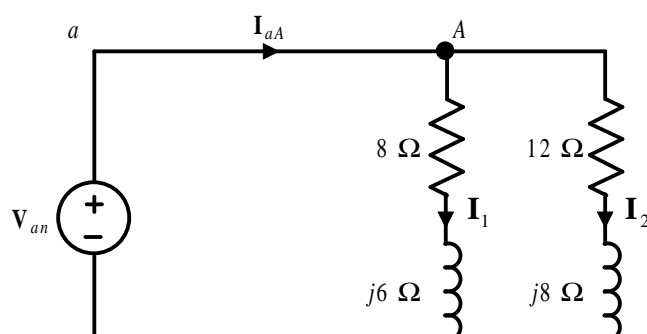

$$\mathbf{I}_1 = \frac{120\angle 20^\circ}{8 + j6} = 12\angle -16.87^\circ \text{ A rms}$$

$$\mathbf{I}_2 = \frac{120\angle 20^\circ}{12 + j8} = 8.32\angle -13.69^\circ \text{ A rms}$$

$$\mathbf{I}_{aA} = \mathbf{I}_1 + \mathbf{I}_2 = 20.3\angle -15.57^\circ \text{ A rms}$$

The other currents are shifted by -120° and -240°