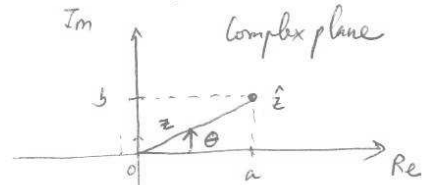


Circuit Analysis II (Linear)

Complex numbers : ① $\hat{z} = a + jb$ $\begin{cases} \text{Re}[\hat{z}] = a \\ \text{Im}[\hat{z}] = b \end{cases}$

$$j = \sqrt{-1}$$

↓
rectangular coordinates



② $\hat{z} = z e^{j\theta}$
↓
polar coordinates

z : magnitude of $\hat{z}$
or phase
 θ : angle, w.r.t. to
Re axis

(Here $\hat{z}$ is located
in the first quadrant)

① $\rightarrow$ ② : $z = \sqrt{a^2 + b^2}$
 $\theta = \tan^{-1}\left(\frac{b}{a}\right)$

② $\rightarrow$ ① : $a = z \cos \theta$
 $b = z \sin \theta$ $\Rightarrow$ ① $\hat{z} = z \cos \theta + j z \sin \theta$

② $\rightarrow$ $e^{j\theta} = \cos \theta + j \sin \theta$
de Moivre Formula

Consequence : $1 e^{j\frac{\pi}{2}} = j$ $\because$ phase of j is 90° ($\frac{\pi}{2}$ radians)

Vectors space : $(1, 0)$ $(0, 1)$
Real axis Imaginary axis $\downarrow j$

Polar coordinates for $\begin{cases} \hat{z}_1 = -3 + j4 \\ \hat{z}_2 = 3 - j4 \end{cases} \rightarrow \begin{cases} z_1 = 5 \\ \theta_1 = -53.13^\circ \end{cases} \rightarrow \begin{cases} \hat{z}_1 = 5 e^{-j53.13^\circ} \text{ (sec. quadrant)} \\ \hat{z}_2 = 5 e^{-j53.15^\circ} \text{ (fourth quadrant)} \end{cases}$

Sinusoids

$$x(t) = A \cos(\omega t + \theta)$$

$\downarrow$ amplitude $\downarrow$ angular frequency = ω rad/s $\rightarrow$ phase

$$= \operatorname{Re} [A e^{j(\omega t + \theta)}]$$

Sinusoid can be associated with a vector in the complex plane

$$\cos(\omega t + \theta_1) = \cos \omega t$$

$$\cos(\omega t + \theta_2) = \cos\left[\omega\left(t + \frac{\theta_2}{\omega}\right)\right]$$


$$\uparrow \text{time shift} = \frac{\theta}{\omega} =$$

$$\frac{\theta_2}{\omega} = \frac{\pi}{\omega}$$

$$x(t) = \operatorname{Re} [e^{j\omega t} A e^{j\theta}]$$

Phasor

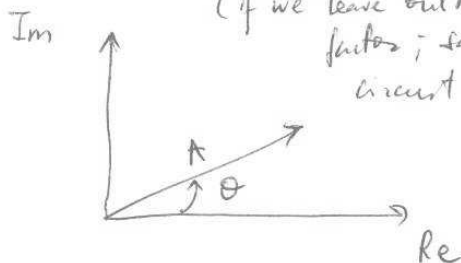Sinusoid can also be associated with this vector in complex plane (if we leave out time-dependence factor; same w thru-out circuit)



- Phase change b/w two sinusoids using phasors =

$$v_1(t) = 6 \sin(100t + 60^\circ)$$


$$v_2(t) = -6 \cos(100t + 30^\circ)$$

Trig. identities:

$$\cos \alpha = \sin \left(\alpha + \frac{\pi}{2} \right)$$

$$\cos \omega t = \sin(\omega t + 90^\circ)$$


$$v_2(t) = -6 \sin(100t + 120^\circ)$$

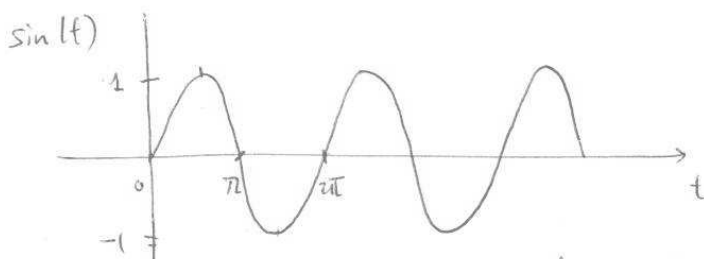

if shifted π to the left = change of sign.

$$v_2(t) = 6 \sin(100t + 300^\circ)$$

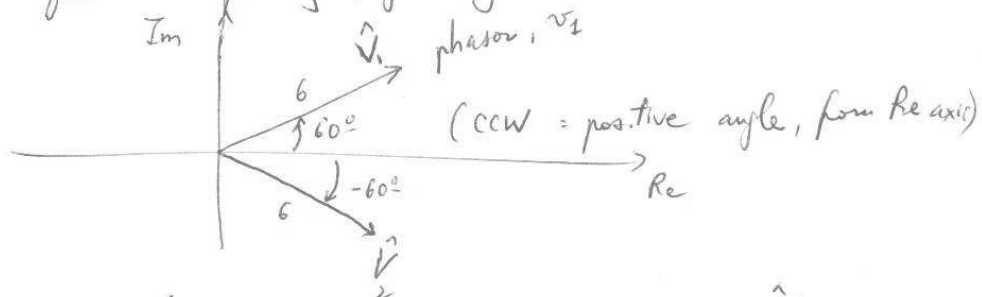Let's see their relative phase by drawing the phasor diagram (ignoring frequency and time)




Then v_1 or $\hat{V}_1$ is 120° ahead of v_2 or $\hat{V}_2$
 $\downarrow$ $\downarrow$
 signal phase signal phase

④

Phasors & AC Circuit Analysis (Linear Circuits)

R

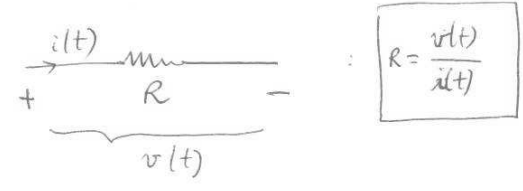

AC circuit : $i(t) = I \cos(\omega t + \theta_I)$
 b/c of Ohm's law : $v(t) = V \cos(\omega t + \theta_V)$ ↑ same (linear circuit)

$i(t) = \text{Re} \left[\underbrace{I e^{j\theta_I}}_{\text{phasor } \hat{I}} e^{j\omega t} \right] \quad (\text{can represent } i(t) \text{ by } \hat{I} = I e^{j\theta_I})$
 $v(t) = \text{Re} \left[\underbrace{V e^{j\theta_V}}_{\text{phasor } \hat{V}} e^{j\omega t} \right] \quad (\text{can represent } v(t) \text{ by } \hat{V} = V e^{j\theta_V})$

$$R = \frac{\hat{V}(t)}{i(t)} = \frac{\text{Re}[\hat{V} e^{j\omega t}]}{\text{Re}[\hat{I} e^{j\omega t}]} = \frac{\text{Re}[\hat{V}]}{\text{Re}[\hat{I}]} = \text{Re} \left[\frac{\hat{V}}{\hat{I}} \right] = \text{Re} \left[\frac{V}{I} e^{j(\theta_V - \theta_I)} \right]$$

$\Rightarrow \theta_V - \theta_I = 0 \quad \text{or} \quad \text{voltage \& current are in phase at R}$
 or $\theta_V = \theta_I$

With this result I can write : $R = \frac{\hat{V}}{\hat{I}} = \hat{Z}_R$


(impedance at a resistance is R)

$\begin{array}{c} i(t) \\ \rightarrow \\ + \text{---} R \text{---} - \\ v(t) \end{array}$

$R = \frac{v(t)}{i(t)} \quad ; \quad \text{also} \quad \begin{array}{c} \hat{I} \\ \rightarrow \\ + \text{---} R \text{---} - \\ \hat{V} \end{array} \quad R = \frac{\hat{V}}{\hat{I}}$

"Ohm's law also applies to phasors" !!

(5)

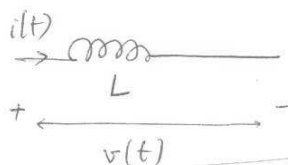
At L :

$$v(t) = L \frac{di}{dt}$$

AC: i & v


$$\begin{aligned} \text{Re}[\hat{V} e^{j\omega t}] &= L \frac{d}{dt} \text{Re}[\hat{I} e^{j\omega t}] = L \text{Re}\left[\frac{d}{dt}(\hat{I} e^{j\omega t})\right] \\ &= \text{Re}[\hat{I} j\omega e^{j\omega t}] \end{aligned}$$

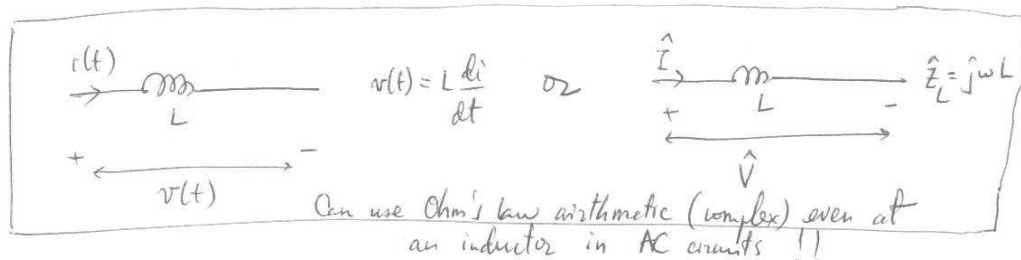$\rightarrow \hat{V} = Lj\omega \hat{I}$: Now, with this result, I can define a impedance at the inductor as $\hat{Z}_L = \frac{\hat{V}}{\hat{I}} = j\omega L$




6

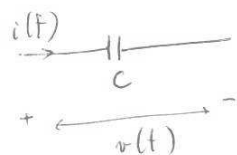at C: Derive $\hat{Z}_C$ (extra credit = 0.5 one HW set)




$$i(t) = C \frac{dv}{dt}$$

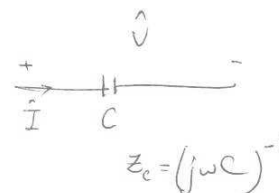
$$\rightarrow Z_C = \frac{1}{j\omega C} = \frac{\hat{V}}{\hat{I}}$$



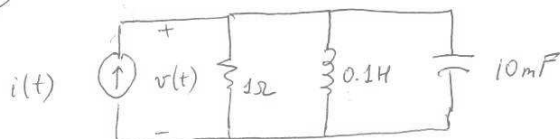7.21 $i(t) = 20 \cos(377t + 120^\circ) \text{ A}$ $\rightarrow$ find $v(t)$ via frequency domain analysis.



$\downarrow$ F.D.

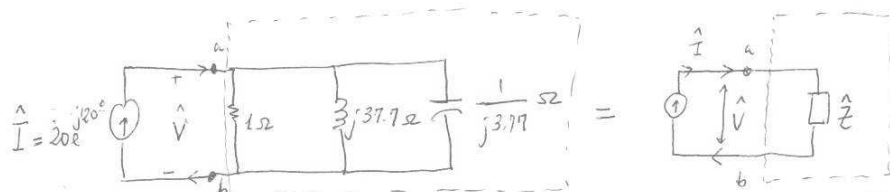

$$\hat{V} = 20 e^{j120^\circ} \cdot \hat{Z} = 20 e^{j120^\circ} \left(1 \parallel \frac{10}{j37.7 + j\frac{1}{3.77}} \right) = 20 e^{j120^\circ} \left(1 \parallel \frac{10}{j37.43} \right)$$

$$\begin{aligned} j &= \sqrt{-1} \\ j^2 &= -1 \\ -j &= e^{-j90^\circ} \\ &= 20 e^{j120^\circ} \frac{0.26 e^{-j90^\circ}}{\sqrt{1^2 + 0.26^2} e^{-j44.96^\circ}} = \frac{20 \cdot 0.26}{1.033} e^{j(120^\circ - 90^\circ + 44.96^\circ)} \\ &= 5.03 e^{j44.96^\circ} \text{ V} \approx 5 e^{j45^\circ} \text{ V} \end{aligned}$$

$$\rightarrow v(t) = 5 \cos(377t + 45^\circ) \text{ V}$$

(8)

$$\rightarrow \begin{cases} V = RI_1 + \omega L I_2 \\ 0 = RI_2 - \omega L I_1 \end{cases} \rightarrow \text{solve for } I_1 \text{ \& } I_2$$

$$I_1 = \frac{R}{(\omega L)^2 + R^2} V ; \quad I_2 = \frac{\omega L}{(\omega L)^2 + R^2} V$$

since we defined I_1 & I_2 as $\begin{cases} I_1 = I \cos \theta \\ I_2 = -I \sin \theta \end{cases}$

$$\rightarrow \frac{I_2}{I_1} = -\tan \theta \rightarrow \theta = -\tan^{-1} \frac{I_2}{I_1} = -\tan^{-1} \frac{\omega L}{R}$$


$$\begin{aligned} I^2 = I_1^2 + I_2^2 &\rightarrow I = \sqrt{\frac{R^2}{[(\omega L)^2 + R^2]^2} V^2 + \frac{(\omega L)^2}{[(\omega L)^2 + R^2]^2} V^2} \\ &= \frac{V}{(\omega L)^2 + R^2} \sqrt{R^2 + (\omega L)^2} = \frac{V}{\sqrt{(\omega L)^2 + R^2}} \end{aligned}$$

$$\Rightarrow i(t) = I \cos(\omega t + \theta)$$

$$i(t) = \frac{V}{\sqrt{(\omega L)^2 + R^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

9

Phasors:

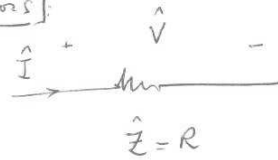



Ohm's law: $\hat{Z} = \frac{\hat{V}}{\hat{I}} = \frac{V}{I} e^{j(\theta_V - \theta_I)}$

(Complex numbers: $\hat{z}_1 = z_1 e^{j\theta_1}$; $\hat{z}_2 = z_2 e^{j\theta_2} \rightarrow \frac{\hat{z}_1}{\hat{z}_2} = \frac{z_1 e^{j\theta_1}}{z_2 e^{j\theta_2}} = \frac{z_1}{z_2} e^{j(\theta_1 - \theta_2)}$)

$R = \frac{V}{I} e^{j(\frac{\theta_V - \theta_I}{0})}$
(zero phase)

→ "Voltage & current at a resistor are in phase."


Phasor diagram:

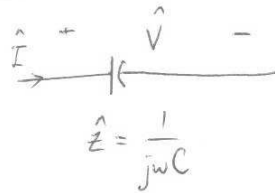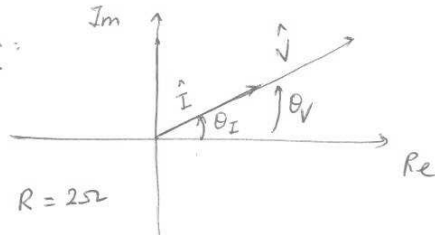

Ohm's law: $\hat{Z}_C = \frac{1}{j\omega C} = \frac{V}{I} e^{j(\theta_V - \theta_I)}$


→ $\theta_V - \theta_I = -90^\circ$

Phasor diagram:

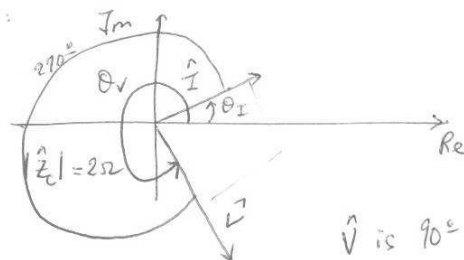


$\hat{V}$ is 90° behind $\hat{I}$
across a capacitor.

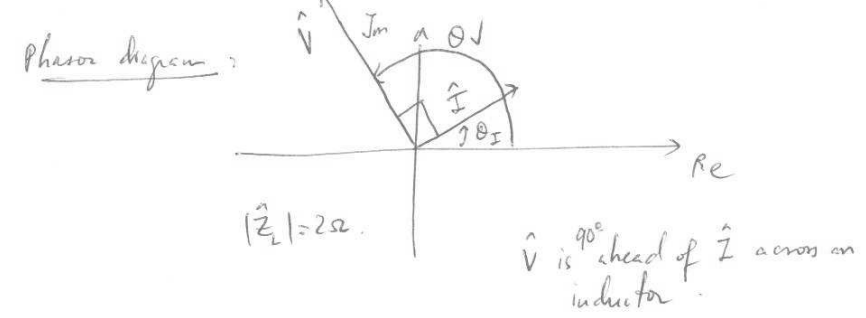$\hat{I} \rightarrow \text{---} \hat{V}$
 $\hat{Z}_L = j\omega L$
 Ohm's law: $\hat{Z}_L = j\omega L = \frac{V}{I} e^{j(\theta_V - \theta_I)}$
 $\theta_V - \theta_I = 90^\circ$



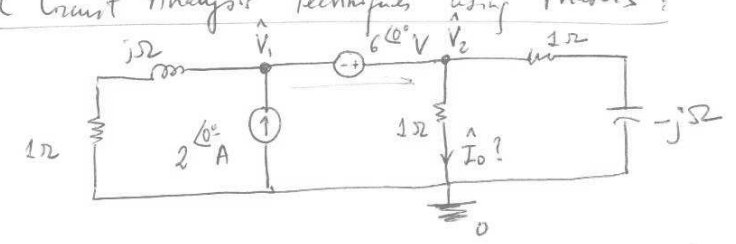AC Circuit Analysis Techniques using Phasors:



1) Nodal Analysis: KCL assign a voltage at each node

At node 1: KCL =


$$+2 - \frac{\hat{V}_1}{1+j} - \left(\frac{\hat{V}_2}{4} + \frac{\hat{V}_2}{1-j} \right) = 0$$

This current is leaving node 1

$\hat{V}_2 = \hat{V}_1 + 6$

Since we need to compute $\hat{I}_0 \rightarrow$ we need $\hat{V}_2 \rightarrow$ let's eliminate $\hat{V}_1$

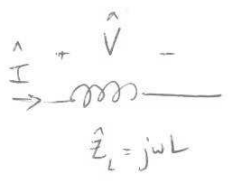
$\hat{V}_1 \rightarrow$ KCL: $2 - \frac{\hat{V}_2 - 6}{1+j} - \hat{V}_2 - \frac{\hat{V}_2}{1-j} = 0$



Ohm's law: $\hat{Z}_L = j\omega L = \frac{V}{I} e^{j(\theta_V - \theta_I)}$


$\theta_V - \theta_I = 90^\circ$

Phasor diagram:

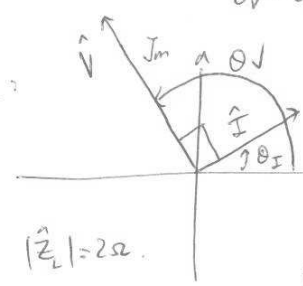

$\hat{V}$ is 90° ahead of $\hat{I}$ across an inductor.

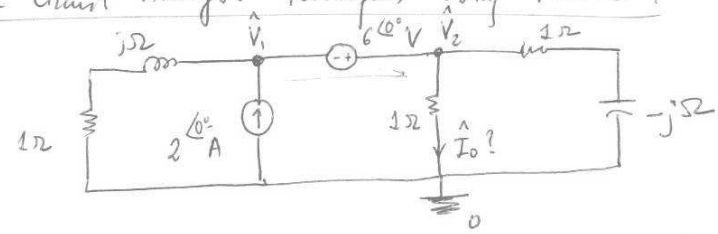AC Circuit Analysis Techniques using Phasors:



1) Nodal Analysis: KCL assign a voltage at each node

At node 1: KCL =

$$+2 - \frac{\hat{V}_1}{1+j} - \left(\frac{\hat{V}_2}{4} + \frac{\hat{V}_2}{1-j} \right) = 0$$

This current is leaving node 1

$\hat{V}_2 = \hat{V}_1 + 6$

Since we need to compute $I_0 \rightarrow$ we need $\hat{V}_2 \rightarrow$ let's eliminate

$\hat{V}_1 \rightarrow$ KCL: $2 - \frac{\hat{V}_2 - 6}{1+j} - \hat{V}_2 - \frac{\hat{V}_2}{1-j} = 0$