

$$\hat{V}_L ? \hat{I}_0$$

(11)

$$2 + \frac{6}{1+j} = \hat{V}_L \left(\frac{1}{1+j} + 1 + \frac{1}{1-j} \right) = \hat{V}_L \frac{1-j+2+1+j}{2} = 2\hat{V}_L$$

$$\rightarrow \hat{V}_L = 1 + \frac{3}{1+j} = \frac{4+j}{1+j} = \frac{(4+j)(1-j)}{(1+j)(1-j)} = \frac{5-3j}{2} = \frac{\sqrt{34}}{2} e^{-j \tan^{-1} \frac{3}{5}}$$

$$= 2.92 e^{-j 30.96^\circ} \text{ V}$$


$$\rightarrow \hat{I}_0 = \frac{\hat{V}_L}{1} = 2.92 e^{-j 30.96^\circ} \text{ A}$$

Complex conjugate of $1+j$ is $1-j$. Product of any complex number with its conjugate gives its magnitude squared.

$$\text{If } f = 60 \text{ Hz} \Rightarrow \omega = 377 \text{ s}^{-1} \Rightarrow i_0(t) = 2.92 \cos(377t - 30.96^\circ) \text{ A}$$

Polar forms allow quick conversion between frequency & time-domain expressions.

2) Loop Analysis:

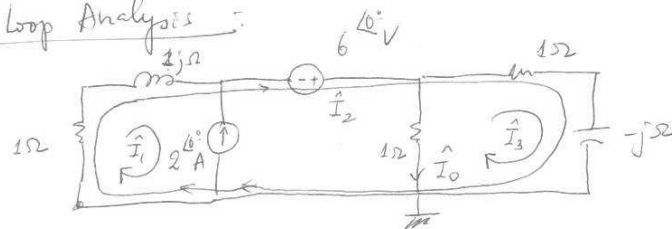

KVL: voltages (with signs) around a closed loop add up to zero

3 loops $\rightarrow$ 3 KVL's $\rightarrow$ choose a direction for current in each loop

$$\hookrightarrow \text{loop \#1 (left)} \quad \text{a) use current: } \hat{I}_1 = -2 \text{ A}$$

$$\text{loop \#2 (outer, global)} \quad \text{b) } 1(\hat{I}_1 + \hat{I}_2) + 1j(\hat{I}_1 + \hat{I}_2) - 6 + (1-j)(\hat{I}_2 + \hat{I}_3)$$



$$\text{loop \#3 (right)} \quad \text{c) } (1-j)(\hat{I}_2 + \hat{I}_3) + \hat{I}_3 = 0$$

We need $\hat{I}_0 = -\hat{I}_3 \rightarrow$ eliminate $\hat{I}_3$ from eqns b) & c)

$$\begin{aligned}
 & b) (\hat{I}_2 - 2)(1+j) - 6 + \underbrace{(\hat{I}_2 + \hat{I}_3)(1-j)}_{-\hat{I}_3 \text{ from c)} } = 0 \\
 & c) \quad \hat{I}_2(1-j) + \hat{I}_3(2-j) = 0 \rightarrow \hat{I}_2 = \hat{I}_3 \frac{j-2}{1-j} \\
 & \rightarrow \hat{I}_2(1+j) - 8 - 2j - \hat{I}_3 = 0 \\
 & \quad \hat{I}_3 \underbrace{\frac{(1+j)(j-2)}{1-j}}_{\frac{-3-j}{1-j}} - 8 - 2j - \hat{I}_3 = 0 \\
 & \Rightarrow \hat{I}_2 = \frac{8+2j}{\frac{-3-j}{1-j} - 1} = \frac{(8+2j)(1-j)}{(-3-j) - 1+j} = \frac{10-6j}{-4} \\
 & \quad \hat{I}_2 = \frac{-5+3j}{2} \text{ A} \quad \text{or} \quad \boxed{\hat{I}_0 = \frac{5-3j}{2} \text{ A}}
 \end{aligned}$$

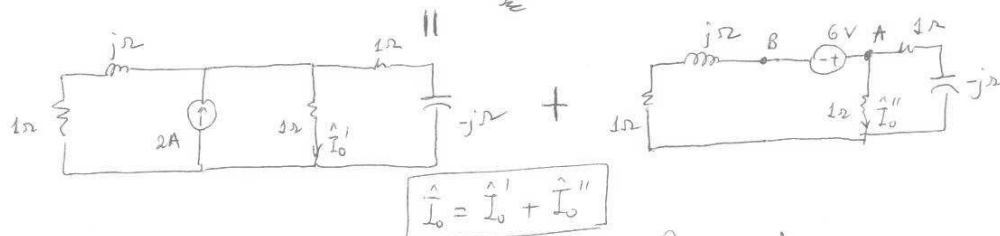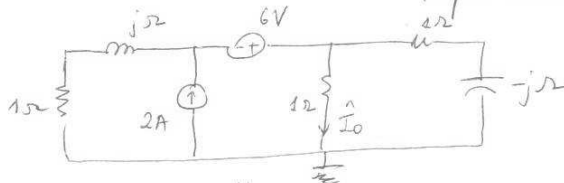
3) Superposition Method using Phasors:

→ adding circuits with single sources $\left\{ \begin{array}{l} \text{short-circuiting voltage source} \\ \text{or} \\ \text{open-circuiting current source} \end{array} \right.$




Instead of one complex circuit we solve two single-source circuits

a) We find $\hat{I}_0'$:

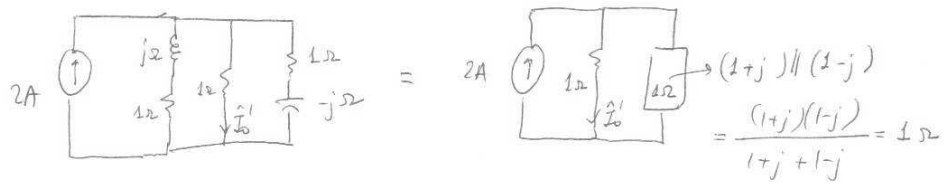

$$\hat{I}_0' = 1A \text{ ("current division")}$$

b) We find $\hat{I}_0''$: redrawing:

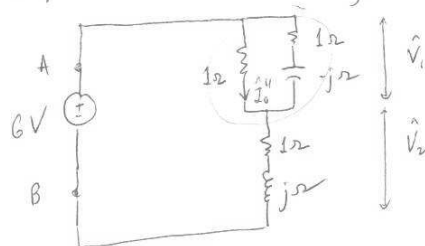

Find $\hat{V}_1$ using "Voltage Division"

$$\rightarrow \hat{I}_0'' = \frac{\hat{V}_1}{1\Omega}$$

$$\hat{V}_1 = \frac{6V \cdot \frac{1(1-j)}{1+1-j}}{\frac{1-j}{2-j} + 1+j}$$

$$= 6V \frac{(1-j)}{(1-j) + (1+j)(2-j)}$$

$$= 6V \frac{1-j}{1-j+3+j} = \frac{6(1-j)}{4} \checkmark$$

$$\hat{I}_0'' = \frac{3}{2}(1-j)A$$


$$\Rightarrow \hat{I}_0 = \hat{I}_0' + \hat{I}_0'' = 1 + \frac{3}{2}(1-j) = \frac{5-3j}{2} A$$

4) Source Exchange using Phasors





$$\hat{I} = \frac{\hat{V}}{\hat{Z}}$$

$$\hat{V} = \hat{I} \hat{Z}$$

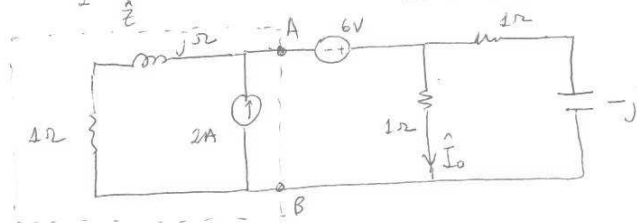

For example:

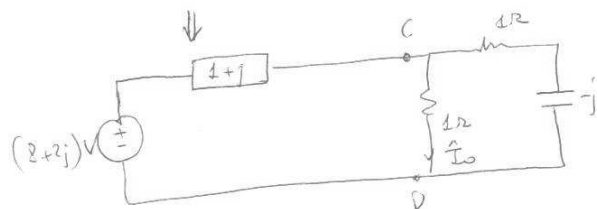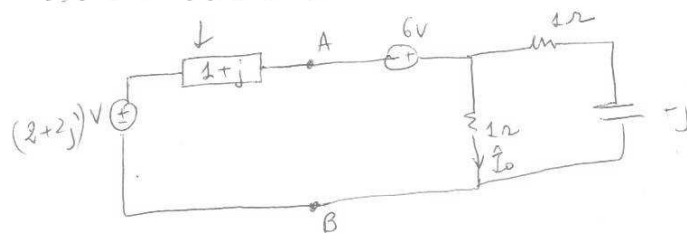change a current source into a voltage source.




$$\hat{Z}_L = j\omega L$$

$$\hat{Z}_C = \frac{1}{j\omega C}$$


$$\hat{V}_{CD} = (8+2j) \frac{\frac{1-j}{2-j}}{\frac{1-j}{2-j} + 1+j} = (8+2j) \frac{1-j}{1-j + (1+j)(2-j)} = \frac{10-6j}{3+j+1-j}$$

$$= \frac{10-6j}{4} \rightarrow \hat{I}_0 = \frac{\hat{V}_{CD}}{1\Omega} = \frac{5-3j}{2} \text{ A}$$

5) Thevenin Equivalence using Phasors

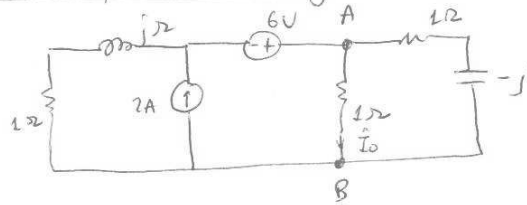


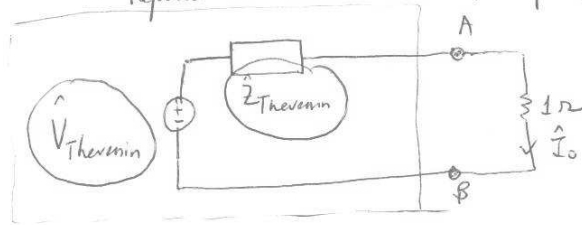
Replace the whole circuit (except for branch AB) by:




$$\hat{V}_T = \hat{V}_{OC} \text{ (across AB) open-circuit}$$

$$\hat{Z}_T = \hat{Z}_{NS} \text{ (across AB) no sources}$$

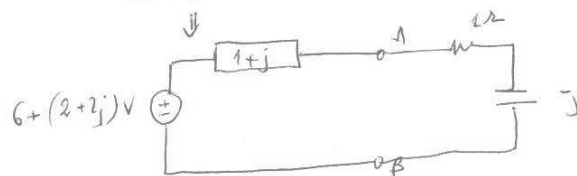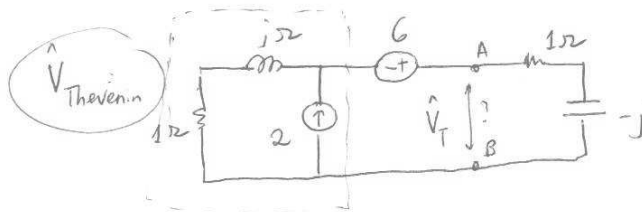
(Current source: open
Voltage source: short circuit)



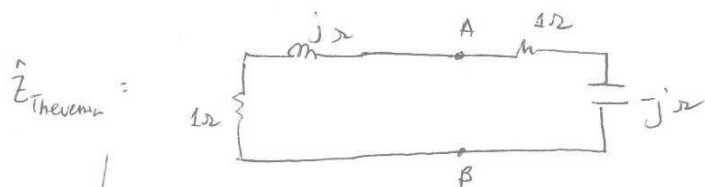
$$\hat{V}_T = \hat{V}_{AB} = (8 + 2j) \frac{1 - j}{1 - j + 1 + j} = \frac{(8 + 2j)(1 - j)}{2} = 5 - 3j \text{ V}$$


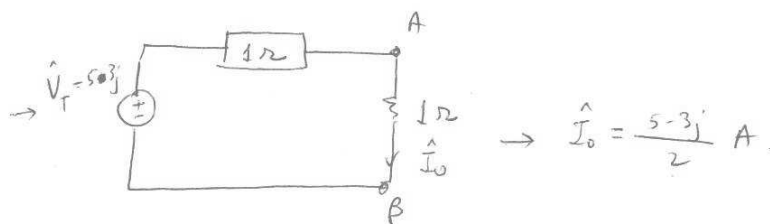
$$\hat{Z}_{AB} = (1+j) \parallel (1-j) = \frac{(1+j)(1-j)}{(1+j)+1-j} = 1 \Omega$$




6) Norton Equivalence using Phasors:

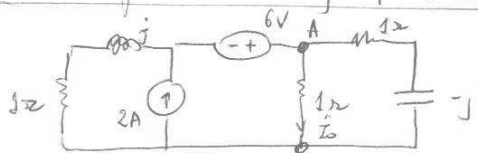


$\hat{I}_{Norton} = \hat{I}_{SC}$ (across AB)
Short-circuit.

$\hat{Z}_T = 1 \Omega$ as before.


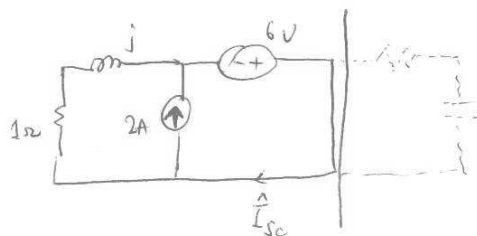


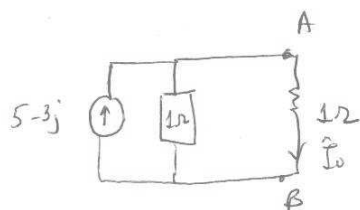$\hat{I}_{S.C} = \frac{8+2j}{1+j} = \frac{(8+2j)(1-j)}{2} = \frac{10-6j}{2} = 5-3j$ A



$$\hat{I}_0 = \frac{5-3j}{2} \text{ A} = 2.91 e^{-j31^\circ} \text{ A}$$

7.70 using PSpice:

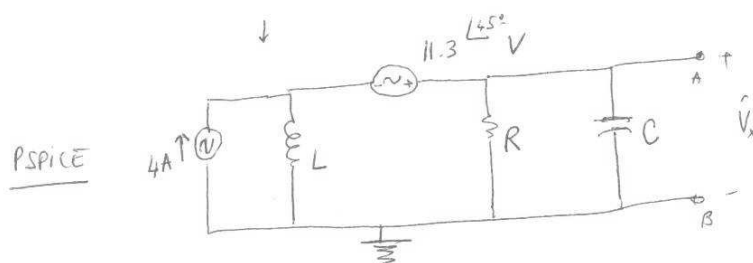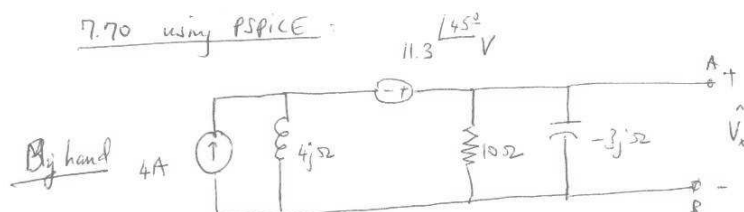

$$\hat{Z}_L = j\omega L = j4 \rightarrow L = \frac{4}{\omega} = \frac{4}{377} = 10.6 \text{ mH}$$

$$\hat{Z}_C = \frac{1}{j\omega C} = -j3 \rightarrow C = \frac{1}{3\omega} = \frac{1}{3 \times 377} = 884 \text{ } \mu\text{F}$$

$$f = 60 \text{ Hz} \rightarrow \omega = 377 \text{ s}^{-1}$$



EXC = HW set

What is the result using Norton's equivalent? By comparing with PSpice, what is the right order of signs for current source &

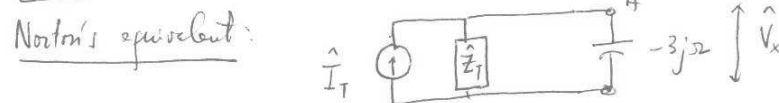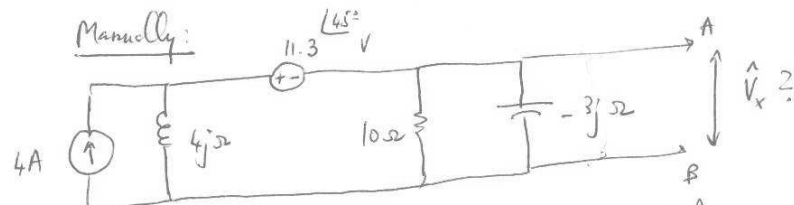
7.70

Pspice


$$\begin{cases} \oplus \text{ IAC} & \hat{V}_x = 48.58 \angle 121.8^\circ \downarrow \\ \ominus \text{ IAC} & \hat{V}_x = 21.7 \angle 5^\circ \uparrow \end{cases}$$



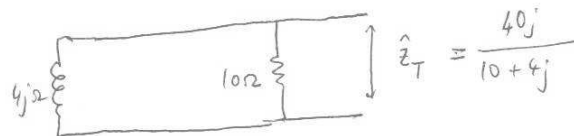$\hat{Z}_T$ (D.C. capacitor; O.C. 4A $\uparrow$; S.C. 11.3V $\angle 45^\circ$)



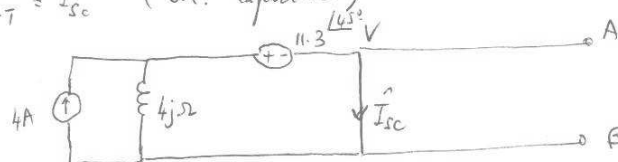$\hat{I}_T = \hat{I}_{sc}$ (S.C. capacitor)




Source exchange:

$$\begin{aligned} \hat{I}_{sc} &= \frac{16j - 11.3(\cos 45^\circ + j \sin 45^\circ)}{4j} \\ &= \frac{-7.44 + 8.01j}{4j} = \frac{11.3}{4} \angle 135^\circ \\ \hat{I}_{sc} &= 2.825 \angle 45^\circ \text{ A} \end{aligned}$$

PSICE: IAC; VAC; GND; C; L; R; VPRINT1
 $\uparrow = \oplus$
 AC = γ
 MAG = γ
 Phase = γ
 Analysis Setup: AC Sweep
 { one fpt: 1pt: 60 to 60
 sweep: decade; 100 pts; f_{min} to f_{max}
 Simulate.
 Results { one frequency: "examine output" file
 sweep: "add trace"; M()
 $\uparrow$
 $V(V_o)$

Mutual Inductance & Energy Analysis

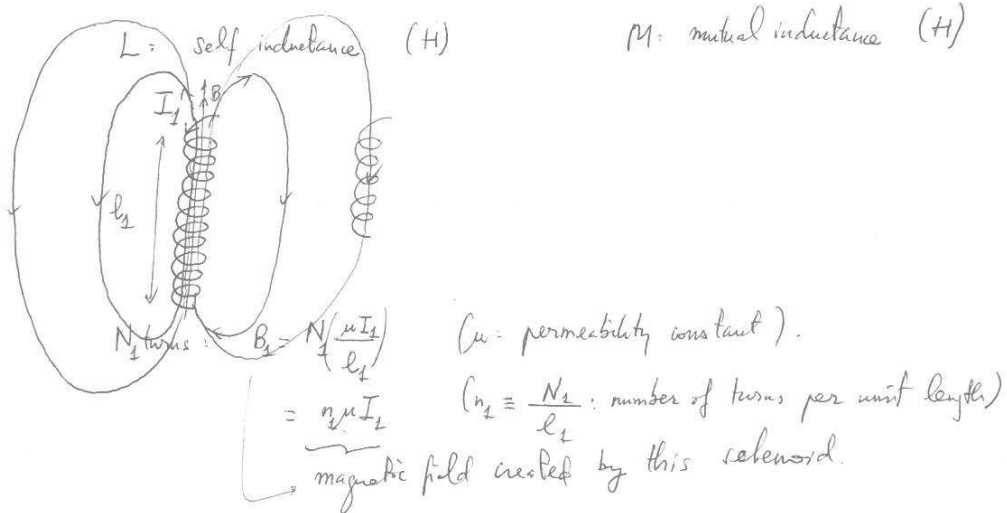

This B may go thru some other loop in the same region
 $\rightarrow$ creating a flux: $\Phi = B \cdot S$ If S is constant (as in our case), and B is constant $\rightarrow$ nothing interesting. (DC)

If B changes with time $\rightarrow \frac{d\Phi}{dt} = -V_{\text{induced in second solenoid}} =$
 (Faraday's Law). Same with second solenoid: it would induce a voltage in the first solenoid as well $\rightarrow$ solenoids interact mutually in AC circuits! To account for this we need another term =

DC circuits: $V_1 = L_1 \frac{dI_1}{dt}$ $\frac{d\Phi}{dt} = \frac{dB}{dt} S = \underbrace{n_2 \mu S}_{L_2} \frac{dI_1}{dt}$

AC circuits: $V_1 = L_1 \frac{dI_1}{dt} + \underbrace{M \frac{dI_2}{dt}}_{M = \frac{N_1 N_2 \mu S_1}{l_2}}$