
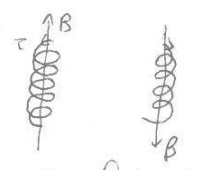


$$\left. \begin{aligned} M_{n1 \text{ by } 2} &= \frac{N_1 N_2 \mu S_1}{l_2} \\ M_{n2 \text{ by } 1} &= \frac{N_1 N_2 \mu S_2}{l_1} \end{aligned} \right\} \text{Same } M \quad \left(\frac{S_1}{l_2} = \frac{S_2}{l_1} \right)$$

$\Rightarrow S_1 l_1 = S_2 l_2$
(same volume in both solenoid!)

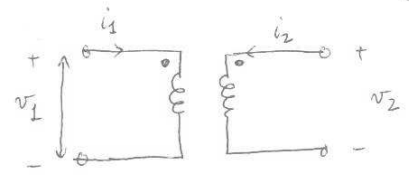Rest of chapter: use correct sign for mutual inductance term.
↓
assisted by the "dot convention"



this internal (to solenoid) info is coded by "dot convention"

↓
correct equation (signs)


$$\begin{aligned} v_1 &= L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 &= L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \end{aligned}$$

T.D. equations

$$v_1 \rightarrow \hat{V}_1 e^{j\omega t}; \quad i_1 \rightarrow \hat{I}_1 e^{j\omega t}$$

$$\begin{aligned} \hat{V}_1 &= j\omega L_1 \hat{I}_1 + M j\omega \hat{I}_2 \\ \hat{V}_2 &= j\omega L_2 \hat{I}_2 + j\omega M \hat{I}_1 \end{aligned}$$

F.D. equations

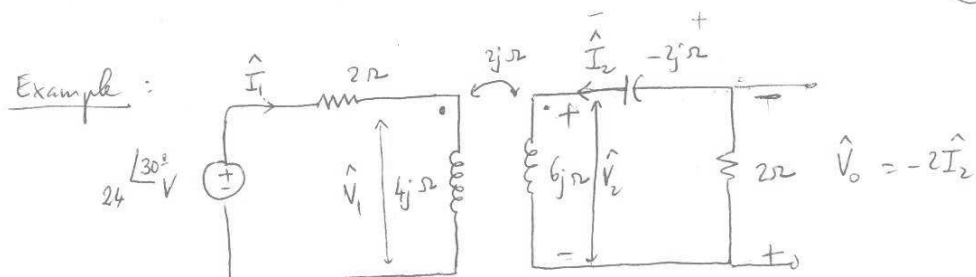

Left loop: $24 \angle 30^\circ = j4 \hat{I}_1 + j2 \hat{I}_2 + 2 \hat{I}_1 = \hat{I}_1 (2 + j4) + j2 \hat{I}_2$

Right loop: $\textcircled{V_o} = j6 \hat{I}_2 + j2 \hat{I}_1 + \textcircled{V_o} - j2 \hat{I}_2 = \hat{I}_2 (2 + j4) + j2 \hat{I}_1 + 2 \hat{I}_2$


$\hat{I}_1 = -\hat{I}_2 \frac{(2 + j4)}{2j} = -\hat{I}_2 (-j + 2)$

$24 \angle 30^\circ = -\hat{I}_2 \underbrace{(2 - j)(2 + j)}_{8 + 6j} + \hat{I}_2 2j = \hat{I}_2 (j^2 - 8 - 6j) = \hat{I}_2 (-8 - 6j)$

$\hat{I}_2 = \frac{6 \angle 70^\circ}{-2 - j} = \frac{6 \angle 70^\circ}{\sqrt{5} \angle 110.7^\circ} = \frac{6 \angle 30^\circ}{\sqrt{5} \angle 206.56^\circ} = 2.68 \angle -176.56^\circ \text{ A}$

$\hat{V}_o = \textcircled{-2} \times 2.68 \angle -176.56^\circ = 5.36 \angle 3.43^\circ \checkmark$

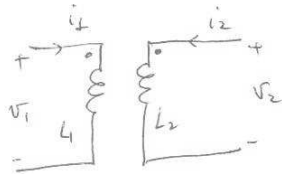Energy of two magnetically coupled inductors:



$$\mathcal{E} = \int \underbrace{P(t) dt}_{\text{power (energy per unit time)}}$$

Total time interval: $0 \rightarrow t_1 \rightarrow t_2$


$\underbrace{\hspace{10em}}_{\text{current building up in } L_1}$
 $\underbrace{\hspace{10em}}_{\text{current building up in } L_2}$

- | | |
|--|--|
| <p>1) i_1 increases from 0 to I_1</p> <p>2) $i_2 = 0$</p> | <p>1) $i_1 = \text{constant} = I_1$</p> <p>2) i_2 increases from 0 to I_2</p> |
|--|--|

$$\mathcal{E}_{0 \rightarrow t_2} = \int_0^{t_1} P(t) dt + \int_{t_1}^{t_2} P(t) dt$$

$$\begin{aligned}
 P(t) &= v_1(t) i_1(t) + v_2(t) i_2(t) = \left(L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \right) i_1 + \left(L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \right) i_2 \\
 &= \int_0^{t_1} \left(L_1 \frac{di_1}{dt} i_1 + M \frac{di_1}{dt} \underbrace{i_2}_0 \right) dt + \int_{t_1}^{t_2} \left(M \frac{di_2}{dt} \underbrace{i_1}_{I_1} + L_2 \frac{di_2}{dt} i_2 \right) dt \\
 &= L_1 \int_0^{t_1} i_1 di_1 + M I_1 \int_{t_1}^{t_2} di_2 + L_2 \int_{t_1}^{t_2} i_2 di_2 \\
 &= L_1 \left(\frac{i_1^2}{2} \right)_0^{t_1} + M I_1 [i_2]_{t_1}^{t_2} + L_2 \left(\frac{i_2^2}{2} \right)_{t_1}^{t_2} \\
 &= \frac{L_1 I_1^2}{2} + \underbrace{M I_1 I_2}_{\text{mutual energy}} + \frac{L_2 I_2^2}{2}
 \end{aligned}$$

Ideal Transformer : (change a voltage)

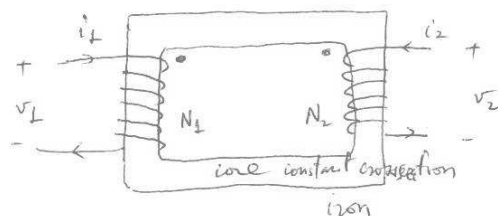

The two solenoids can have different diameters but iron core then then has same cross-section
 $\rightarrow$ same magnetic flux

$$\Phi_1 = B_1 S_1$$

$$\Phi_2 = B_2 S_2$$

$$v_1 = N_1 \frac{d\Phi_1}{dt}$$

$$v_2 = N_2 \frac{d\Phi_2}{dt}$$

Since $\Phi_1 = \Phi_2$

$$\Rightarrow \boxed{\frac{v_1}{N_1} = \frac{v_2}{N_2}} \quad \text{or} \quad \boxed{\frac{v_1}{v_2} = \frac{N_1}{N_2}}$$

Ampere's law : $\oint_{\text{loop}} \vec{H} \cdot d\vec{l} = i_{\text{enclosed by the loop}} = N_1 i_1 + N_2 i_2$

$$\vec{B} = \mu \vec{H}$$

iron core : $\mu = \infty$, for finite values for $\vec{B} \Rightarrow \vec{H}$ needs to be 0 $\rightarrow$

$$N_1 i_1 = -N_2 i_2 \rightarrow \boxed{\frac{i_1}{i_2} = -\frac{N_2}{N_1}}$$

Power Analysis


Instantaneous Power: $p(t) = i(t) v(t)$

AC circuit: $i(t) = I_m \cos(\omega t + \theta_i)$; $v(t) = V_m \cos(\omega t + \theta_v)$

$$p(t) = I_m V_m \frac{1}{2} \left[\cos(2\omega t + \theta_i + \theta_v) + \cos(\theta_i - \theta_v) \right]$$

trig id: $\cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha + \beta) + \cos(\alpha - \beta)]$
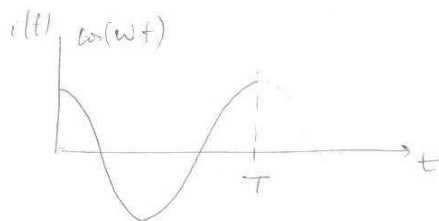
$$p(t) = \underbrace{\frac{1}{2} I_m V_m \cos(\theta_v - \theta_i)}_{\text{D.C.}} + \underbrace{\frac{1}{2} I_m V_m \cos(2\omega t + \theta_v + \theta_i)}_{\text{A.C.}}$$




$$\overline{i} = \overline{v} = 0 \quad \text{but} \quad \overline{p} \neq 0$$

(need to pay utility bill)

Average power: $P = \frac{1}{T} \int_{t_0}^{t_0+T} p(t) dt$

↓
period
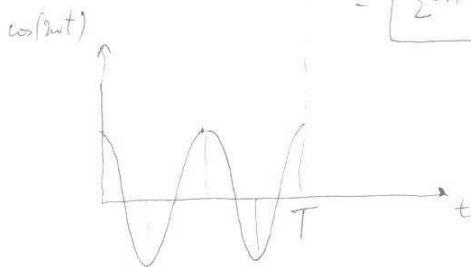
$$= \boxed{\frac{1}{2} I_m V_m \cos(\theta_v - \theta_i)} + \frac{1}{2} I_m V_m \underbrace{\frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt}_{\substack{\text{area under} \\ \text{curve} \\ = 0}}$$



$$\hat{Z} = R + jX \quad \begin{cases} R: \text{resistive} \\ X: \text{reactive} \end{cases}$$

26

$$p(t) = \frac{1}{2} I_m V_m + \frac{1}{2} I_m V_m \cos(2\omega t + 2\theta_v)$$


at pure-resistive (impedance is real #) $\rightarrow$
voltage & current are in phase $\theta_v = \theta_i$

$$p(t) = 0 + \frac{1}{2} I_m V_m \cos(2\omega t + \theta_i + \theta_v)$$

at pure-reactive (impedance is imaginary #)
voltage & current are $\pm 90^\circ$ out of phase $= \theta_v - \theta_i = \pm 90^\circ$

Maximum power I can get out of a circuit:

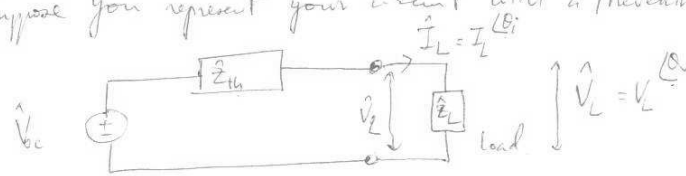Suppose you represent your circuit with a Thevenin's equivalence



Need to find $\hat{Z}_{Lmax}$ that will draw the most power from this circuit. Average power at load is

$$P_L = \frac{1}{2} \hat{V}_L \hat{I}_L \cos(\theta_v - \theta_i) \quad \leftarrow (1)(2)$$

$$\hat{I}_L = \frac{\hat{V}_{oc}}{\hat{Z}_{th} + \hat{Z}_L} = \frac{\hat{V}_{oc}}{R_{th} + R_L + j(X_{th} + X_L)} \quad \Rightarrow \quad \hat{I}_L = \frac{V_{oc}}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}} \quad (1)$$

$$\hat{V}_L = \hat{V}_{oc} \frac{\hat{Z}_L}{\hat{Z}_{th} + \hat{Z}_L} \quad \rightarrow \quad \hat{V}_L = \frac{V_{oc} \sqrt{R_L^2 + X_L^2}}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}} \quad (2)$$

voltage div.

$$\cos(\theta_v - \theta_i) = \frac{\hat{V}_L}{\hat{I}_L} \frac{1}{\hat{Z}_L} \quad \Rightarrow \quad \hat{Z}_L = \frac{\hat{V}_L}{\hat{I}_L} = \frac{V_L}{I_L} \frac{1}{\cos(\theta_v - \theta_i)} = R_L + jX_L = \sqrt{R_L^2 + X_L^2} \angle \tan^{-1} \frac{X_L}{R_L}$$

$\theta_v - \theta_i = \tan^{-1} \frac{X_L}{R_L}$

$$\cos(\theta_v - \theta_i) = \frac{R_L}{\sqrt{R_L^2 + X_L^2}} \quad (3)$$

(27)

$$\text{Then } P_L = \frac{1}{2} \frac{V_{oc} \sqrt{R_L^2 + X_L^2}}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}} \cdot \frac{V_{oc}}{\sqrt{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}} \cdot \frac{R_L}{\sqrt{R_L^2 + X_L^2}}$$

$$= \frac{1}{2} \frac{V_{oc}^2 R_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2} \quad \text{Average Power at load.}$$

Max P_L : in 2 steps. $\left\{ \begin{array}{l} 1) \quad X_L = \omega L \quad X_C = \frac{-1}{\omega C} \Rightarrow X's \text{ (reactances)} \\ \text{can have } + \text{ or } - \text{ signs} \end{array} \right.$

while $R's$ can only be +

$\rightarrow P_L$ is higher when $X_L = X_{th}$ (1)

2) Maximize : $\frac{1}{2} \frac{V_{oc}^2 R_L}{(R_{th} + R_L)^2}$ with respect to R_L
 $f(R_L)$

$$\frac{\partial f}{\partial R_L} = 0 = \frac{V_{oc}^2}{2(R_{th} + R_L)^2} - \frac{2}{2} \frac{V_{oc}^2 R_L}{(R_{th} + R_L)^3} =$$

$$\rightarrow 0 = \frac{V_{oc}^2}{2} - \frac{V_{oc}^2 R_L}{R_{th} + R_L}$$

$$\rightarrow \frac{R_L}{R_{th} + R_L} = \frac{1}{2} \rightarrow 2R_L = R_{th} + R_L$$

$$\boxed{R_L = R_{th}} \quad (2)$$


① & ② $\Rightarrow \hat{Z}_L = \hat{Z}_{th}^*$ (*) to draw max power out of the circuit.

* Complex conjugate: $\hat{Z} = a + jb : \hat{Z}^* = a - jb$ (change sign of imaginary term).

$$\rightarrow \left[P_{L_{max}} = \frac{1}{2} \frac{V_{oc}^2 R_{th}}{4 R_{th}^2} = \frac{V_{oc}^2}{8 R_{th}} \right] \quad \text{max power I can draw from a given circuit.}$$

8.29


28

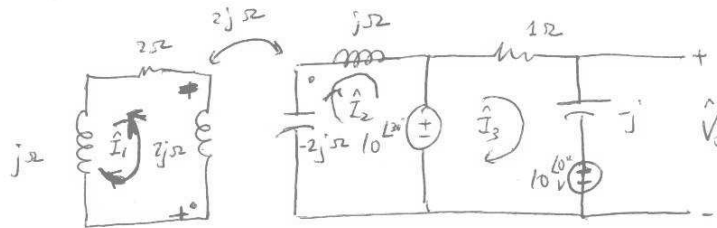

Loop analysis: 3 loops:

$$\hat{I}_1: \text{ccw}; \hat{I}_2: \text{cw}; \hat{I}_3: \text{cw}$$

for + for Mutual Inductance Term

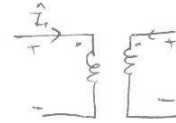

$$1) \quad j\hat{I}_1 + j\hat{I}_2 + 2\hat{I}_1 + \hat{I}_1' = 0 = \hat{I}_1(2+j) + j\hat{I}_2 \quad \checkmark$$

$$2) \quad 10 \angle 30^\circ - 2j\hat{I}_2 + j\hat{I}_2 + j\hat{I}_1 = 0 \Rightarrow 10 \angle 30^\circ = j\hat{I}_2 - j\hat{I}_1 \quad \checkmark$$

$$3) \quad -10 \angle 30^\circ + \hat{I}_3(1-j) + 10 = 0 \quad \checkmark$$

$$\hat{I}_3 = \frac{10 \angle 30^\circ - 10}{1-j} = \frac{10(\cos 30^\circ - 1) + j10 \sin 30^\circ}{\sqrt{2} \angle -45^\circ}$$

$$= \frac{-1.34 + j5}{\sqrt{2} \angle -45^\circ} = \frac{5.17 \angle 105^\circ}{\sqrt{2} \angle -45^\circ}$$

$$= 3.67 \angle 150^\circ \text{ A}$$

$$\hat{V}_o = -j\hat{I}_3 + 10 = 3.67 \angle 60^\circ + 10 = (3.67 \cos 60^\circ + 10) + j3.67 \sin 60^\circ$$

$$= 11.835 + j3.18 = 12.25 \angle 15.8^\circ \text{ V}$$