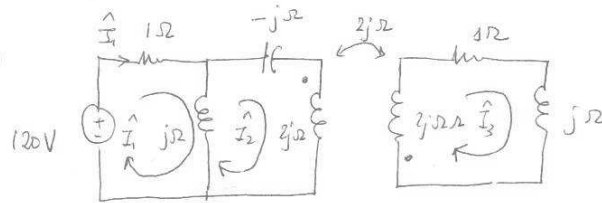


8.36



Impedance seen by voltage source: $\hat{Z} = \frac{120}{\hat{I}_1}$

Find $\hat{I}_1$: loop analysis.

$$1) \quad 120 - \hat{I}_1 - (\hat{I}_1 - \hat{I}_2)j = 0 \quad \rightarrow \quad 120 - \hat{I}_1(1+j) + \hat{I}_2j = 0$$

$$2) \quad (\hat{I}_2 - \hat{I}_1)j - j\hat{I}_2 + 2j\hat{I}_2 + 2j\hat{I}_3 = 0 \rightarrow -j\hat{I}_1 + 2j\hat{I}_2 + 2j\hat{I}_3 = 0$$

$$3) \quad \hat{I}_3 2j + 2j\hat{I}_2 + \hat{I}_3(1+j) = 0 \rightarrow 2j\hat{I}_2 + \hat{I}_3(1+3j) = 0$$

Need $\hat{I}_1 \rightarrow$ eliminate $\hat{I}_2$ & $\hat{I}_3$: $3) - 2) \rightarrow j\hat{I}_1 + \hat{I}_3(1+j) = 0$
 $\rightarrow \hat{I}_3 = -\frac{j}{1+j}\hat{I}_1$

Back in 3) $2j\hat{I}_2 - \frac{j(1+3j)}{1+j}\hat{I}_1 = 0$

$$\hat{I}_2 = \frac{j(1+3j)}{(1+j)2j}\hat{I}_1$$

Back in 1) $120 - \hat{I}_1(1+j) + \frac{j(1+3j)}{2(1+j)}\hat{I}_1 = 0$

$$\frac{\hat{I}_1}{1+j} = \frac{120}{1+j - \frac{-3+j}{2(1+j)}}$$

$$\Rightarrow \hat{Z}_{\text{source}} = \frac{120}{\hat{I}_1} = 1+j + \frac{3-j}{2(1+j)} = \frac{4 + 3-j}{2(1+j)} = \frac{3}{2}\Omega$$

Complex Power: $\hat{S} \equiv \hat{V}_{RMS} \hat{I}_{RMS}^*$

$\downarrow$ $\downarrow$ $\downarrow$
 complex complex complex
 # # #

$$= V_{RMS} e^{j\theta_V} \cdot I_{RMS} e^{-j\theta_I} = V_{RMS} I_{RMS} e^{j(\theta_V - \theta_I)}$$

this sign comes from I^*
 can be related to average power P

Av. Power: $\dot{P} = \frac{1}{2} I_m V_m \cos(\theta_V - \theta_I) = \text{Re}(\hat{S}) \checkmark$



$\uparrow$ $\uparrow$ $\uparrow$
 I_m V_m $\cos(\theta_V - \theta_I)$

RMS: Root Mean Square

$$I_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = I_m \sqrt{\frac{1}{T} \int_0^T \omega^2 (t + \theta_i) dt} = I_m \sqrt{\frac{1}{T} \int_0^T \omega^2 t^2 dt} = \frac{I_m}{\sqrt{2}}$$


$i(t) = I_m \cos(\omega t + \theta_i)$
 can choose start point so $\theta_i = 0$

$\frac{1}{T} \int_0^T \omega^2 t^2 dt$
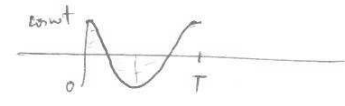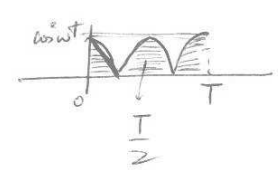
$$I_{RMS} V_{RMS} = \frac{I_m}{\sqrt{2}} \frac{V_m}{\sqrt{2}} = \frac{I_m V_m}{2}$$

Application of Complex Power:

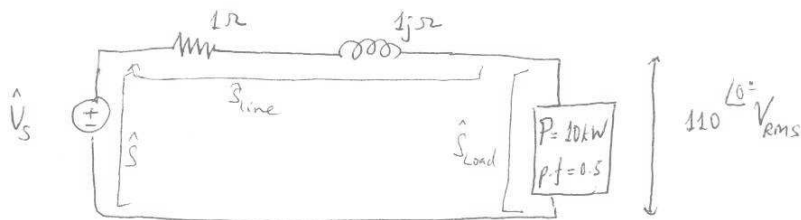

→ What is the p.f. at the source?

$$\text{p.f.} = \text{power factor} \equiv \cos(\theta_v - \theta_i)$$

$$P = \frac{1}{2} I_m V_m \cos(\theta_v - \theta_i) = I_{\text{RMS}} V_{\text{RMS}} \cos(\theta_v - \theta_i) = I_{\text{RMS}} V_{\text{RMS}} \cdot \text{p.f.}$$

(When p.f. = 1 → similar expression to DC Power)

Pure resistive element: full power consumption: p.f. = 1

Pure reactive element: no power consumption: p.f. = 0

1) Find complex power at the load $\hat{S}_L = I_{\text{RMS}} V_{\text{RMS}} e^{j(\theta_v - \theta_i)}$

$$\theta_v - \theta_i = \cos^{-1}(0.5) = 60^\circ; \quad P = \text{Re}(\hat{S}_L) = I_{\text{RMS}} V_{\text{RMS}} \cdot \text{p.f.}$$

$$I_{\text{RMS}} V_{\text{RMS}} = \frac{P}{\text{p.f.}} = 20000 \text{ V-A}$$

$$\rightarrow \hat{S}_L = 20000 e^{j60^\circ} \text{ V-A}$$

2) Find complex power at the line (upper branch)

$$\hat{S}_{\text{Line}} = \hat{V}_{\text{RMS}} \hat{I}_{\text{RMS}}^* = (\hat{I}_{\text{RMS}} \hat{Z}_{\text{Line}}) \hat{I}_{\text{RMS}}^* = I_{\text{RMS}}^2 \hat{Z}_{\text{Line}} = I_{\text{RMS}}^2 (1+j)$$

$$I_{\text{RMS}} = \frac{20000}{110} \approx 181.82 \text{ A} \quad \left(\hat{I}_{\text{RMS}} = \left(\frac{\hat{S}_L}{\hat{V}_L} \right)^* = \frac{20000 \angle -60^\circ}{110} = 181.82 \angle -60^\circ \text{ A} \right)$$

$$\hat{S}_{\text{Line}} = 181.82^2 (1+j)$$

3) Find complex power at the source → p.f. at source.

$$\hat{S} = \hat{S}_{\text{Line}} + \hat{S}_L = (20000 \angle 60^\circ + 181.82^2) + j(20000 \sin 60^\circ + 181.82^2)$$

$$\hat{S} = 43058.5 + j 50379 \quad \text{V-A}$$

$$= 66227.8 \angle 49.5^\circ \quad \text{V-A}$$

$$\rightarrow \text{p.f.}_{\text{source}} = \cos(49.5^\circ) = 0.65$$

→ What is $\hat{V}_s$?

$$\hat{V}_s = \frac{\hat{S}}{\hat{I}_s^*} = \frac{66227.8 \angle 49.5^\circ}{181.82 \angle 60^\circ} = 364.5 \angle -10.5^\circ \quad V_{\text{RMS}}$$

→ What is $\hat{V}_{\text{line}}$?

$$\hat{V}_{\text{line}} = \frac{\hat{S}_{\text{line}}}{\hat{I}_{\text{line}}^*} = \frac{181.82^2 \sqrt{2} \angle 45^\circ}{181.82 \angle 60^\circ} = 257 \angle -15^\circ \quad V_{\text{RMS}}$$

If we are correct: $\hat{V}_{\text{line}} + \hat{V}_L = \hat{V}_s$


$$(257 \cos(15) + 110) + j(257 \sin(-15^\circ)) = 358.39 - j66.55$$

$$= 364.5 \angle -10.5^\circ \quad V_{\text{RMS}} \rightarrow \text{Yes! Same as } \hat{V}_s$$

Single-Phase Three-wire Circuit:

Dryer or Stove (there are gas options for these)

35

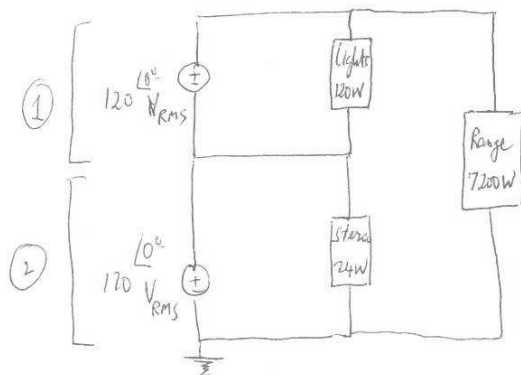

How much is utility bill a month
(\$0.08 / kWh)
energy.

1) Total energy consumed per day =
integrating power over time:
Lights: on for 15 hours
Range: on for 4 hours
Stereo: on for 8 hours

$$E_1 = \int P_1 dt = \int V_1 I_1 dt = 120V [I_{lights} \times 15\text{hrs} + I_{range} \times 4\text{hrs}]$$

p.f. at these appliances are 1 (pure resistive)

$$P = I_{RMS} V_{RMS} \cdot 1 \rightarrow I_{RMS} = \frac{P}{V_{RMS}} = \begin{cases} \frac{120}{120} = 1A \text{ at lights.} \\ \frac{7200}{240} = 30A \text{ at range.} \end{cases}$$

$$E_1 = 120V [1A \times 15\text{hrs} + 30A \times 4\text{hrs}] = 16.2 \text{ kWh}$$


$$E_2 = \int P_2 dt = \int V_2 I_2 dt = 120 V_{RMS} \left[\underset{\substack{\downarrow \\ 0.2A}}{I_{stereo}} \times 8\text{hrs} + \underset{\substack{\downarrow \\ 30A}}{I_{range}} \times 4\text{hrs} \right]$$

$$= 14.592 \text{ kWh}$$

$$\text{Total energy consumed a day} = (16.2 + 14.592) \text{ kWh} = 30.8 \text{ kWh a day}$$

$$\text{One month } 30.8 \times 30 \text{ kWh} = 924 \text{ kWh} \cdot \frac{\$0.08}{\text{kWh}} = \$73.9 / \text{month}$$

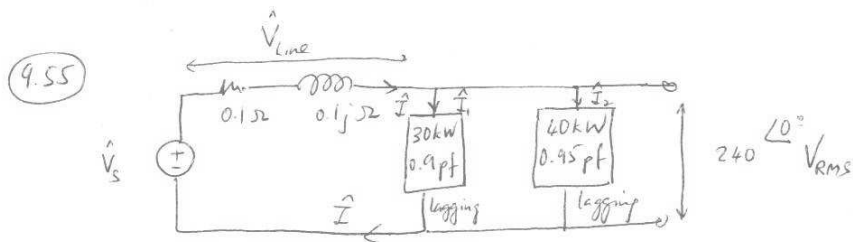Exam 2 Apr 6, 06 / HW 4 & HW 5 are due / HW 6 due next week / HW 7 following week.



Find $\hat{V}_s$ $\hat{V}_s = \hat{V}_{line} + 240 = \hat{V} (0.1 + 0.1j) + 240$

$$\hat{I} = \hat{I}_1 + \hat{I}_2; \quad \hat{S} = \hat{V} \hat{I}^*$$

$$= \left(\frac{\hat{S}_1}{240} \right)^* + \left(\frac{\hat{S}_2}{240} \right)^* = \left(\frac{\hat{S}_1 + \hat{S}_2}{240} \right)^*$$

$$\hat{S}_L = I_{RMS} V_{RMS} e^{j(\theta_v - \theta_i)} \rightarrow P_L = I_{RMS} V_{RMS} \cos(\theta_v - \theta_i)$$

$$\rightarrow \hat{S}_1 = \frac{P_L}{\text{pf}_1} \frac{1/\cos^{-1} \text{pf}_1}{\cos^{-1} \text{pf}_1} = \frac{30000}{0.9} \frac{1/25.8^\circ}{25.8^\circ} = 33333$$

$$\rightarrow \hat{S}_2 = \frac{40000}{0.95} \frac{1/\cos^{-1} 0.95}{\cos^{-1} 0.95} = 42105 \frac{1/18.2^\circ}{18.2^\circ}$$



$$\hat{I} = \frac{1}{240} \left[(33333 \cos 25.8^\circ + 42105 \cos 18.2^\circ) + j (33333 \sin 25.8^\circ + 42105 \sin 18.2^\circ) \right]$$

$$= \frac{1}{240} \left[7 \times 10^4 + j 2.77 \times 10^4 \right]^* \text{ A}$$

$$\hat{V}_s = \frac{10^3}{240} \left(\frac{7 - j 2.77}{(7 + 2.77 + j 4.23)} (1 + j) \right) + 240 = 280.71 + 17.63j$$

$$= 284.86 \angle 3.59^\circ \checkmark$$

Three-Phase Quantities

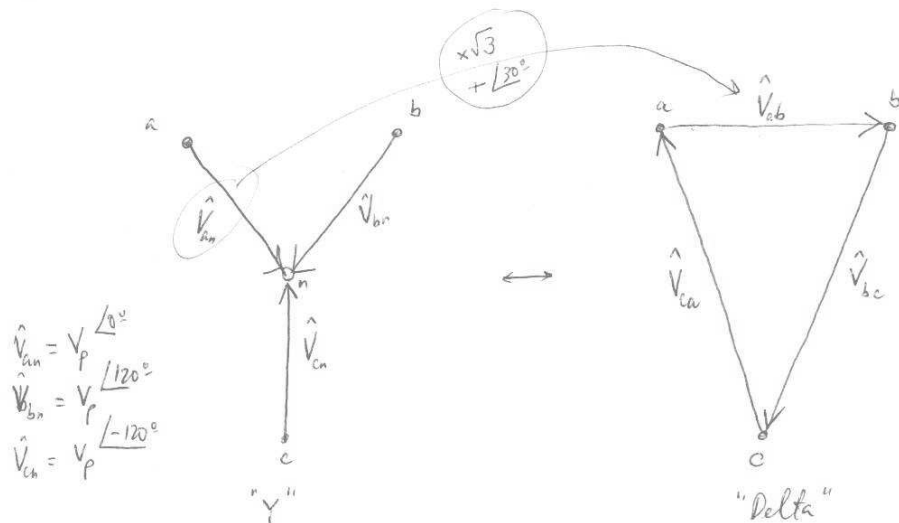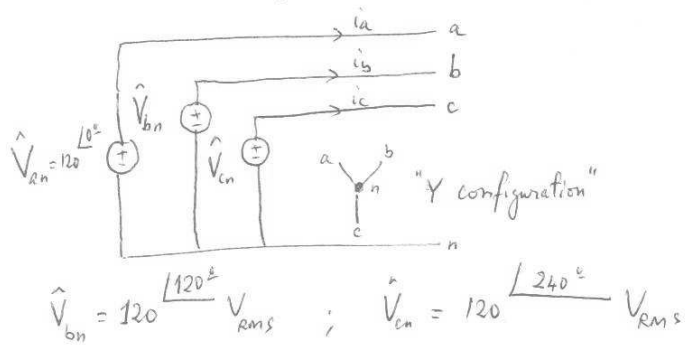

$$\hat{V}_{ab} \equiv \hat{V}_{an} - \hat{V}_{bn} = V_p - V_p \cos 120^\circ - j V_p \sin 120^\circ = V_p (1 - \cos 120^\circ) - j V_p \sin 120^\circ$$

$$= V_p \sqrt{3} \angle 30^\circ$$


(In vector notation: $\hat{V}_{na} + \hat{V}_{ab} = \hat{V}_{nb}$)

$$\Rightarrow \hat{V}_{ab} = \hat{V}_{nb} - \hat{V}_{na} = \hat{V}_{bn} - \hat{V}_{an}$$

$$\begin{aligned}\hat{V}_{bc} &= \hat{V}_{bn} - \hat{V}_{cn} = V_p \overbrace{(\cos 120^\circ - \cos 120^\circ)}^0 + V_p (\sin 120^\circ + \sin 120^\circ)j \\ &= V_p \sqrt{3} \angle 90^\circ\end{aligned}\quad (38)$$

$$\begin{aligned}\hat{V}_{ca} &= \hat{V}_{cn} - \hat{V}_{an} = V_p (\cos 120^\circ - 1) + j V_p \sin 120^\circ \\ &= V_p \sqrt{3} \angle 120^\circ\end{aligned}$$

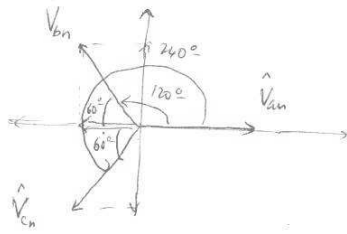Why these phases : $0^\circ, 120^\circ, 240^\circ$



$$\cos 60^\circ = \frac{1}{2} \Rightarrow \hat{V}_{an} + \hat{V}_{bn} + \hat{V}_{cn} = 0$$

Instantaneous power supplied by these 3 sources :

$$p(t) = p_{an}(t) + p_{bn}(t) + p_{cn}(t) = v_{an}(t)i_a(t) + v_{bn}(t)i_b(t) + v_{cn}(t)i_c(t)$$


AC circuits:

$$\begin{cases} v_{an} = V_m \cos(\omega t) & i_a = I_m \cos(\omega t + \theta) \\ v_{bn} = V_m \cos(\omega t + 120^\circ) & i_b = I_m \cos(\omega t + \theta + 120^\circ) \\ v_{cn} = V_m \cos(\omega t + 240^\circ) & i_c = I_m \cos(\omega t + \theta + 240^\circ) \end{cases}$$

$$p(t) = I_m V_m \left[\cos \omega t \cos(\omega t + \theta) + \cos(\omega t + 120^\circ) \cos(\omega t + \theta + 120^\circ) + \cos(\omega t + 240^\circ) \cos(\omega t + \theta + 240^\circ) \right]$$

$$\cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha - \beta) + \cos(\alpha + \beta)]$$
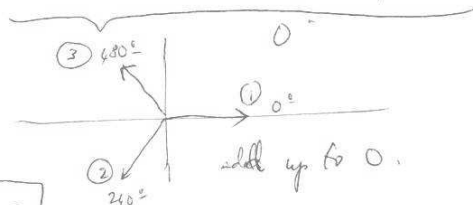
$$= \frac{I_m V_m}{2} \left[3 \cos \theta + \underbrace{\cos(2\omega t + \theta)}_{\textcircled{1} 0^\circ} + \underbrace{\cos(2\omega t + \theta + 240^\circ)}_{\textcircled{2} 240^\circ} + \underbrace{\cos(2\omega t + \theta + 480^\circ)}_{\textcircled{3} 480^\circ} \right]$$




→ $\text{constant } p(t) = \frac{3}{2} I_m V_m \cos \theta$ → 3 sources of same amplitude and phase changed by 120°


Voltages $\hat{V}_{an}, \hat{V}_{bn}, \hat{V}_{cn}$ have phases in CCW order ($0^\circ, 120^\circ, 240^\circ$)
 Powers P_a, P_b, P_c " " in CW order ($0^\circ, 240^\circ, 480^\circ = 120^\circ$)

→ If $\hat{V}_{an}, \hat{V}_{bn}, \hat{V}_{cn}$ also have phase in CW order ($0^\circ, 240^\circ, 120^\circ$)
 → still $p(t) = \frac{3}{2} I_m V_m \cos \theta$ constant. (we only need phase separated by $120^\circ \rightarrow \frac{360^\circ}{3}$)

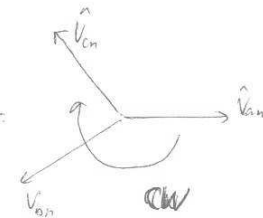
This order is called an abc-sequence.
 Since sum is 0. balanced abc-sequence



Last time:

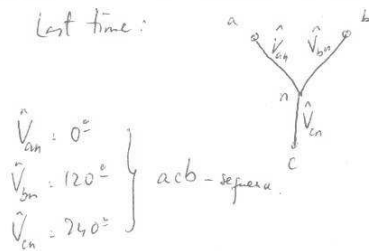

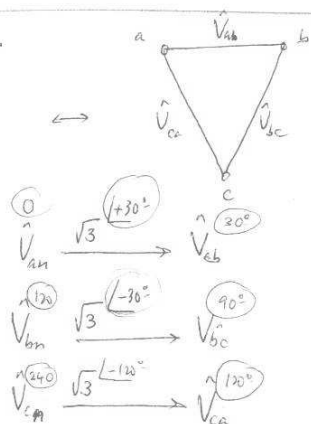$\hat{V}_{an} = 0^\circ$
 $\hat{V}_{bn} = 120^\circ$
 $\hat{V}_{cn} = 240^\circ$ } acb-sequence.



Different transformation for $\hat{V}_{an}, \hat{V}_{bn}, \hat{V}_{cn}$

Now:


$\hat{V}_{an} = 0^\circ$
 $\hat{V}_{bn} = -120^\circ \approx 240^\circ$
 $\hat{V}_{cn} = 120^\circ$ } abc sequence.

$$\begin{aligned} \hat{V}_{ab} &= \hat{V}_{an} - \hat{V}_{bn} = V_p - V_p \cos 120^\circ + j V_p \sin 120^\circ \\ &= V_p \left(\frac{2}{2} + j \frac{\sqrt{3}}{2} \right) = V_p \sqrt{3} \left(\frac{\sqrt{3}}{2} + j \frac{1}{2} \right) \end{aligned}$$

$\sqrt{30^\circ}$

$$\begin{aligned}\hat{V}_{bc} &= \hat{V}_{bn} - \hat{V}_{cn} = V_p \left(-\frac{1}{2} - \frac{\sqrt{3}}{2}j \right) - V_p \left(-\frac{1}{2} + \frac{\sqrt{3}}{2}j \right) \\ &= -V_p \sqrt{3}j = V_p \sqrt{3} \angle -90^\circ\end{aligned}$$

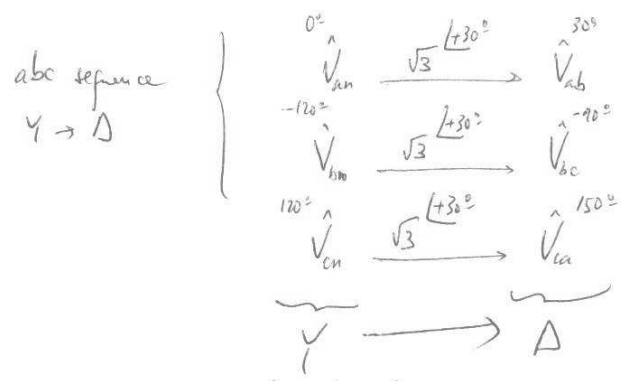
$$\begin{aligned}\hat{V}_{ca} &= \hat{V}_{cn} - \hat{V}_{an} = V_p \left(-\frac{1}{2} + \frac{\sqrt{3}}{2}j \right) - V_p \\ &= V_p \left(-\frac{3}{2} + \frac{\sqrt{3}}{2}j \right) = V_p \sqrt{3} \left(-\frac{\sqrt{3}}{2} + \frac{1}{2}j \right) \\ &\quad \underline{\angle 150^\circ}\end{aligned}$$




→ Conclusion: same transformation $Y \rightarrow \Delta$ for $\hat{V}_{an}, \hat{V}_{bn}, \hat{V}_{cn}$ with phases in abc sequence!

→ For $\Delta \rightarrow Y$ (balanced abc sequence) $\frac{1}{\sqrt{3}} \angle -30^\circ$

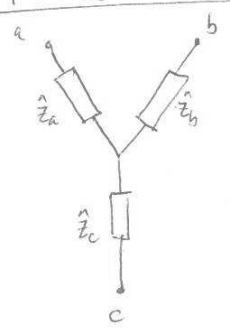$Y \rightarrow \Delta$ load transformation



$\leftrightarrow$

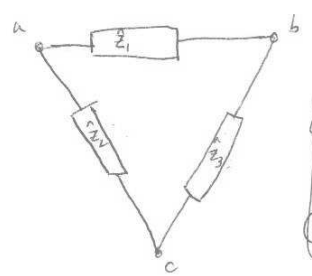

$$\begin{cases} \textcircled{1} \hat{Z}_a + \hat{Z}_b = \hat{Z}_1 \parallel (\hat{Z}_2 + \hat{Z}_3) \\ \textcircled{2} \hat{Z}_a + \hat{Z}_c = \hat{Z}_2 \parallel (\hat{Z}_1 + \hat{Z}_3) \\ \textcircled{3} \hat{Z}_b + \hat{Z}_c = \hat{Z}_3 \parallel (\hat{Z}_1 + \hat{Z}_2) \end{cases}$$

correct!

$$\boxed{\Upsilon \rightarrow \Delta}$$

(42)

$$\hat{z}_1 = \frac{\hat{z}_a \hat{z}_b + \hat{z}_b \hat{z}_c + \hat{z}_a \hat{z}_c}{\hat{z}_c} = \frac{\hat{z}_a \hat{z}_b}{\hat{z}_c} + \hat{z}_b + \hat{z}_a = \frac{\hat{z}_a \hat{z}_b}{\hat{z}_c} \left(\frac{1}{\hat{z}_c} + \frac{1}{\hat{z}_c} + \frac{1}{\hat{z}_c} \right)$$

$$\hat{z}_2 = \frac{\text{same}}{\hat{z}_b} = \frac{\hat{z}_a \hat{z}_c}{\hat{z}_b} + \hat{z}_a + \hat{z}_c = \hat{z}_a \hat{z}_c \left(\frac{1}{\hat{z}_b} + \frac{1}{\hat{z}_c} + \frac{1}{\hat{z}_a} \right)$$

$$\hat{z}_3 = \frac{\text{same}}{\hat{z}_a} = \frac{\hat{z}_b \hat{z}_c}{\hat{z}_a} + \hat{z}_b + \hat{z}_c = \hat{z}_b \hat{z}_c \left(\frac{1}{\hat{z}_a} + \frac{1}{\hat{z}_c} + \frac{1}{\hat{z}_b} \right)$$

$$\hat{z}_1 + \hat{z}_2 = (\hat{z}_a \hat{z}_b + \hat{z}_b \hat{z}_c + \hat{z}_a \hat{z}_c) \left(\frac{1}{\hat{z}_c} + \frac{1}{\hat{z}_b} \right)$$

$$\begin{aligned} \hat{z}_3 \parallel (\hat{z}_1 + \hat{z}_2) &= \frac{(\hat{z}_a \hat{z}_b + \hat{z}_b \hat{z}_c + \hat{z}_a \hat{z}_c) \left(\frac{1}{\hat{z}_c} + \frac{1}{\hat{z}_b} \right)}{(\hat{z}_a \hat{z}_b + \hat{z}_b \hat{z}_c + \hat{z}_a \hat{z}_c) \left(\frac{1}{\hat{z}_a} + \frac{1}{\hat{z}_c} + \frac{1}{\hat{z}_b} \right)} \\ &= \frac{(\hat{z}_a \hat{z}_b + \hat{z}_b \hat{z}_c + \hat{z}_a \hat{z}_c) \frac{\hat{z}_b + \hat{z}_c}{\hat{z}_a \hat{z}_b \hat{z}_c}}{(\hat{z}_c \hat{z}_b + \hat{z}_a \hat{z}_b + \hat{z}_a \hat{z}_c) \frac{1}{\hat{z}_a \hat{z}_b \hat{z}_c}} = \hat{z}_b + \hat{z}_c \end{aligned}$$

$$\boxed{\Delta \rightarrow \Upsilon}$$

$$\textcircled{1} + \textcircled{2} : \hat{z}_a + \hat{z}_b + \hat{z}_c = \hat{z}_1 \parallel (\hat{z}_2 + \hat{z}_3) + \hat{z}_2 \parallel (\hat{z}_1 + \hat{z}_3)$$

$$\hat{z}_a = \frac{1}{2} \left\{ \hat{z}_1 \parallel (\hat{z}_2 + \hat{z}_3) + \hat{z}_2 \parallel (\hat{z}_1 + \hat{z}_3) - \hat{z}_3 \parallel (\hat{z}_1 + \hat{z}_2) \right\}$$

$$\hat{z}_b =$$

$$\hat{z}_c =$$