


(43)

Variable Frequency Network Performance :

$$\hat{Z}_R = R$$

$$\hat{Z}_L = j\omega L$$

$$\hat{Z}_C = \frac{1}{j\omega C}$$

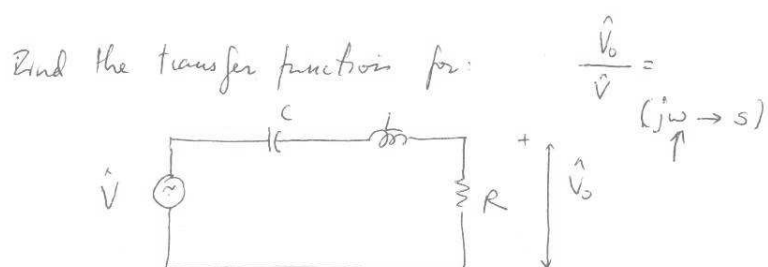

Say it has a poles of what order? (pole = zero of denominator)

By voltage division:
$$\frac{\hat{V}_o}{\hat{V}} = \frac{R}{\frac{1}{j\omega C} + j\omega L + R} \xrightarrow{j\omega \rightarrow s} \frac{R}{\frac{1}{sC} + sL + R}$$

$$= \frac{RCs}{1 + s^2LC + sRC} = \frac{\frac{R}{L}s}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

Zeros of denominator: $s^2 + s\frac{R}{L} + \frac{1}{LC} = 0 \rightarrow s = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$

$$S = -\frac{R}{2L} \pm \frac{1}{2} \sqrt{\frac{R^2C - 4L}{L^2C}} = -\frac{R}{2L} \pm \frac{1}{2L} \sqrt{\frac{R^2C - 4L}{C}}$$

• If $R^2C - 4L = 0$ or $\frac{R^2C}{L} = 4 \Rightarrow S_{\pm} = -\frac{R}{2L}$

Then $S^2 + S\frac{R}{L} + \frac{1}{LC} = \left(S + \frac{R}{2L}\right)^2 \rightarrow$ Transfer function
has a pole of 2nd order.

• If $R^2C - 4L > 0 \Rightarrow S_{\pm}$

$$S^2 + S\frac{R}{L} + \frac{1}{LC} = \left(S + \frac{R}{2L} - \frac{1}{2L} \sqrt{\frac{R^2C - 4L}{C}}\right) \left(S + \frac{R}{2L} + \frac{1}{2L} \sqrt{\frac{R^2C - 4L}{C}}\right)$$

$\rightarrow$ Transfer function has two poles of
1st order

• If $R^2C - 4L < 0 \Rightarrow S_{\pm} = -\frac{R}{2L} \pm j \frac{1}{2L} \sqrt{\frac{4L - R^2C}{C}}$

$$S^2 + S\frac{R}{L} + \frac{1}{LC} = \left(S + \frac{R}{2L} - j \frac{1}{2L} \sqrt{\frac{4L - R^2C}{C}}\right) \left(S + \frac{R}{2L} + j \frac{1}{2L} \sqrt{\frac{4L - R^2C}{C}}\right)$$

$\rightarrow$ Transfer function has a pair of complex
conjugate poles.

We will learn about frequency variation in connection with the
type of poles of the transfer function.

Bode plots

Transfer function: $\hat{H}(j\omega)$ or $\hat{H}(s)$ (e.g. $\hat{H}(j\omega) = \frac{\hat{V}_o(j\omega)}{\hat{V}_i(j\omega)}$)

→ Bode plots: $\left\{ \begin{array}{l} \text{Magnitude: } 20 \log_{10} |\hat{H}(j\omega)| \text{ versus } \log_{10} \omega \\ \text{Phase: } \angle \hat{H}(j\omega) \text{ versus } \log_{10} \omega \end{array} \right.$

We now learn how to make Bode plots from a transfer function.
(two way connection). Let's start with a standard form of $\hat{H}$:
(which is in general a ratio of polynomials for linear circuits containing R, L, C)

$$\hat{H}(j\omega) = \frac{k_0(j\omega)^{\pm N} (1+j\omega\tau_1) [1 + 2\zeta_3 j\omega\tau_3 + (j\omega\tau_3)^2] \dots}{(1+j\omega\tau_a) [1 + 2\zeta_b j\omega\tau_b + (j\omega\tau_b)^2] \dots}$$

(τ_1 "tau sub one")

(ζ_3 "xi sub three")

From our example: $\hat{H} = \frac{\hat{V}_o}{\hat{V}_i} = \frac{RCj\omega}{1 + (j\omega)^2 LC + j\omega RC}$

$\left\{ \begin{array}{l} k_0 = RC; N=1; \\ \tau_1, \tau_3, \zeta_3: \text{none} \\ \tau_a: \text{none} \\ \tau_b^2 = LC \rightarrow \tau_b = \sqrt{LC} \\ 2\zeta_b \tau_b = RC \\ \rightarrow \zeta_b = \frac{RC}{2\tau_b} = \frac{RC}{2\sqrt{LC}} \\ = \frac{R}{2} \sqrt{\frac{C}{L}} \end{array} \right.$

Review: 1) $\frac{\hat{z}_1 \hat{z}_2}{\hat{z}_3} \rightarrow \left| \frac{\hat{z}_1 \hat{z}_2}{\hat{z}_3} \right| = \sqrt{\frac{\hat{z}_1 \hat{z}_2 \hat{z}_1^* \hat{z}_2^*}{\hat{z}_3 \hat{z}_3^*}}$



2) $\log_{10} \frac{|\hat{z}_1| |\hat{z}_2|}{|\hat{z}_3|} = \log_{10} |\hat{z}_1| + \log_{10} |\hat{z}_2| - \log_{10} |\hat{z}_3|$

$= \sqrt{\frac{(\hat{z}_1 \hat{z}_1^*) (\hat{z}_2 \hat{z}_2^*)}{\hat{z}_3 \hat{z}_3^*}} = \frac{|\hat{z}_1| |\hat{z}_2|}{|\hat{z}_3|}$

Magnitude Bode Plot

$$20 \log_{10} |\hat{H}| = \overset{1)}{20 \log_{10} |K_0|} \pm \overset{2)}{20N \log_{10} \omega} + \overset{3)}{20 \log_{10} |1 + j\omega\tau_1|} + \overset{4)}{20 \log_{10} |1 + 2\zeta_2 j\omega\tau_2 + (j\omega\tau_2)^2|} \\ - \overset{5)}{20 \log_{10} |1 + j\omega\tau_3|} - \overset{6)}{20 \log_{10} |1 + 2\zeta_3 j\omega\tau_3 + (j\omega\tau_3)^2|} - \dots$$

Let's see how to plot different terms :

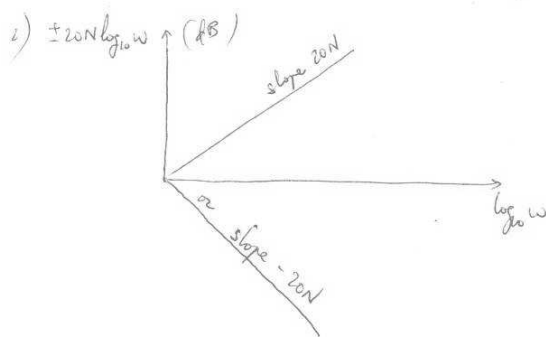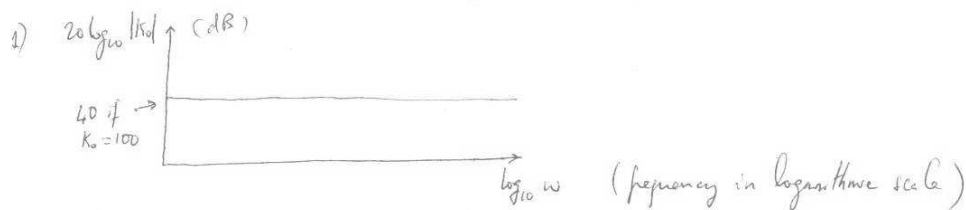

3) Asymptotic analysis : $20 \log_{10} |1 + j\omega\tau_1|$

$\omega \rightarrow 0$ (low freq): sufficiently low such that $j\omega\tau_1 \ll 1$

$$20 \log_{10} |1 + j\omega\tau_1| \approx 0$$

$\omega \rightarrow \infty$ (high freq): sufficiently high such that $j\omega\tau_1 \gg 1$

$$20 \log_{10} |1 + j\omega\tau_1| \approx 20 \log_{10} \omega\tau_1 = 20 \log_{10} \omega + 20 \log_{10} \tau_1$$


$$|j\omega\tau_1| = \omega\tau_1$$

$\omega_c \tau_1 \approx 1$ or $\omega_c = \frac{1}{\tau_1} \rightarrow 20 \log_{10} |1 + j| = 20 \log_{10} \sqrt{2} = 3 \text{ dB}$


critical frequency

$$20 \log_{10} |1 + j\omega \tau_L| = \begin{cases} \omega \rightarrow 0 & 0 \\ \omega = \frac{1}{\tau_L} = \omega_c & 3 \text{ dB} \\ \omega \rightarrow \infty & 20 \log_{10} \omega + 20 \log_{10} \tau_L \end{cases}$$

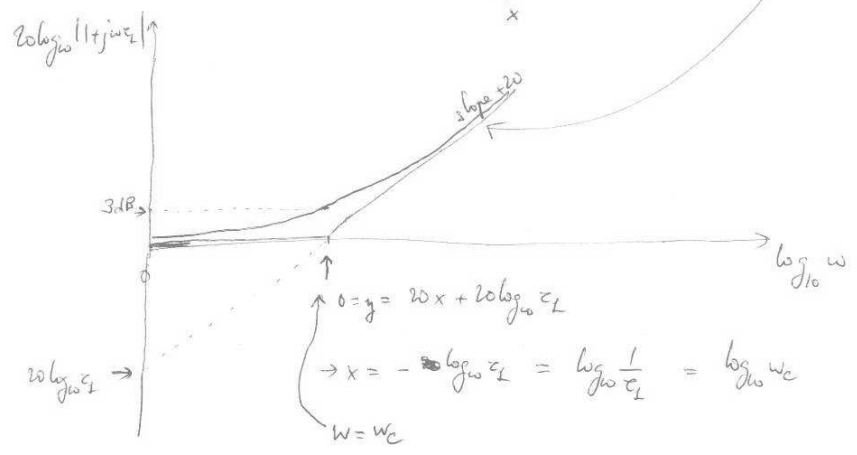or $y = 20x + 20 \log_{10} \tau_L$
negative when $\tau_L < 1$



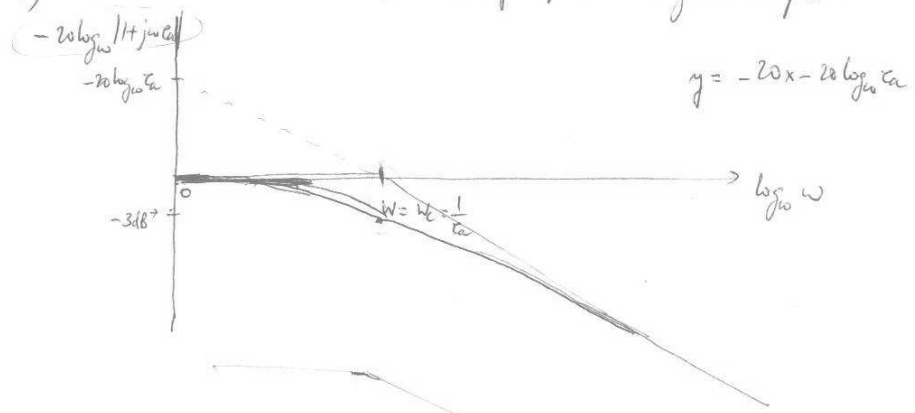5) This term is similar to 3) except for the negative slope.



(11.13)
7th ed.

$$\hat{H}(j\omega) = \frac{100 j\omega}{(1+j\omega)(10+j\omega)(50+j\omega)}$$



Magnitude Bode Plot?




To apply previous results $\rightarrow$ we put all factors in standard format

$$\hat{H}(j\omega) = \frac{\frac{100}{500} j\omega}{(1+j\omega)(1+j\frac{\omega}{10})(1+j\frac{\omega}{50})}$$

$$\rightarrow 20 \log_{10} |\hat{H}| = \overset{(A)}{20 \log_{10} 0.2} + \overset{(B)}{20 \log_{10} \omega} - \overset{(C)}{20 \log_{10} |1+j\omega|} - \overset{(D)}{20 \log_{10} |1+j\frac{\omega}{10}|} - \overset{(E)}{20 \log_{10} |1+j\frac{\omega}{50}|}$$
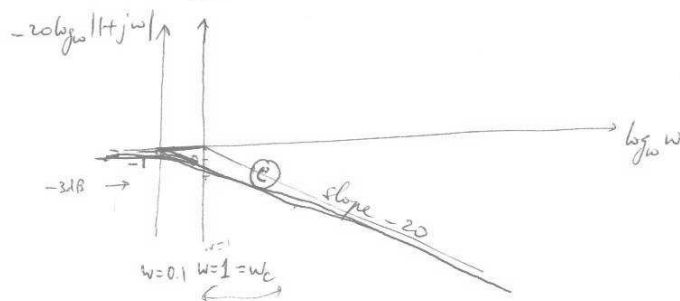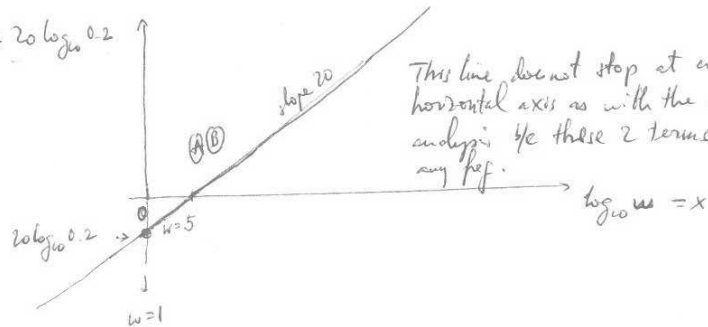
$$y = \underbrace{20 \log_{10} \omega}_x + 20 \log_{10} 0.2$$



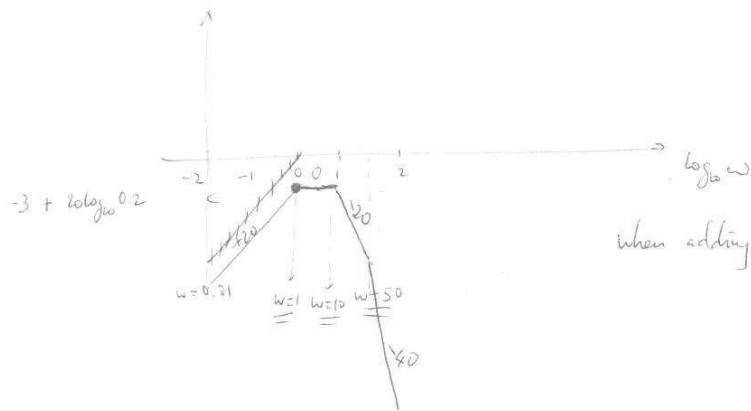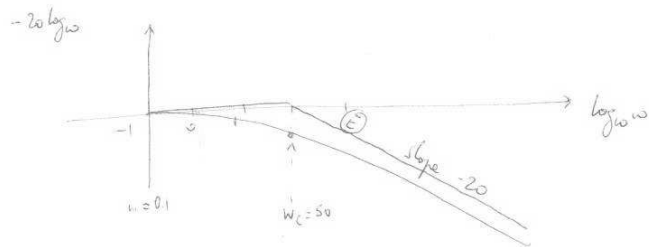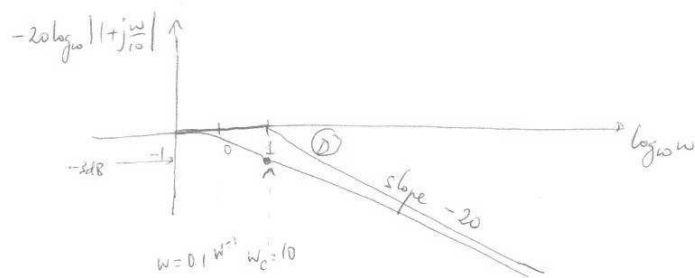

when adding: do by pieces of frequency intervals

In summary: we are plotting the magnitude Bode plot for

$$\hat{H}(j\omega) = \frac{0.2 j\omega}{(1+j\omega)(1+j\frac{\omega}{10})(1+j\frac{\omega}{50})}$$


The numerator gives a line up at slope +20 at all ω (there is no asymptotic analysis on this term). The critical ω 's are 1, 10, 50.

→ Before $\omega_c = 1$: only contribution from the +20 slope line that ends at $20 \log_{10} 0.2 = -3 \text{ dB}$.

→ At $\omega_c = 1$ term $(1+j\omega)$ provides a -20 slope line (from asymptotic analysis of large ω), this combines with the +20 slope line to give a horizontal piece. No contribution from $(1+j\frac{\omega}{10})$ or $(1+j\frac{\omega}{50})$ because they are 0 to the left of their critical points (from asymptotic analysis of small ω). This continues until $\omega_c = 10$.

→ At $\omega_c = 10$ $(1+j\frac{\omega}{10})$ turns down as a -20 slope line while $(j\omega)$ & $(1+j\omega)$ continue their same behavior as before. This gives total behavior of a -20 slope line until $\omega_c = 50$. Since we are b/w 10 & 50, i.e. to the left of the $(1+j\frac{\omega}{50})$'s critical point, it has zero contribution.

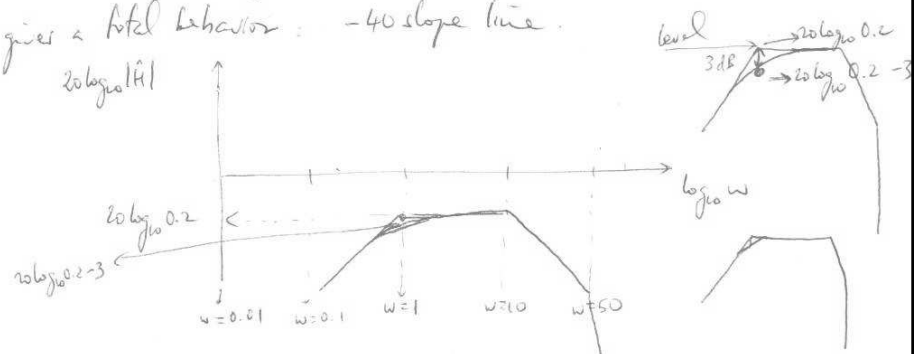→ At $\omega_c = 50$ $(1+j\frac{\omega}{50})$ kicks in with a -20 slope line that gives a total behavior: -40 slope line.



Bode Plot with quadratic poles and zeros:

$$\underbrace{\overset{\text{zero}}{+20 \log_{10} |1 + 2\zeta_b j\omega\tau_b + (j\omega\tau_b)^2|}}_{4)} \underbrace{\overset{\text{pole}}{-20 \log_{10} |1 + 2\zeta_b (j\omega\tau_b) + (j\omega\tau_b)^2|}}_{6)} \quad \text{asymptotic analysis}$$

1) small ω : $\omega\tau_b \ll 1 \rightarrow$
 $-20 \log_{10} | \quad | \approx -20 \log_{10} |1| = 0$

2) large ω : $\omega\tau_b \gg 1 \rightarrow$
 $-20 \log_{10} | \quad | \approx -20 \log_{10} |(j\omega\tau_b)^2|$
 $= -20 \log_{10} \omega^2 - 20 \log_{10} \tau_b^2$
 $= \underbrace{-40 \log_{10} \omega}_{\uparrow} - 40 \log_{10} \tau_b$

3) $\omega\tau_b \approx 1$ or $\omega = \omega_c$

$$-20 \log_{10} | \quad | \approx -20 \log_{10} (2\zeta_b)$$

ζ_b	$-20 \log_{10} 2(\zeta_b)$
0.2	7.96
0.4	1.94
0.5	0 (no rounding at corner)
0.6	-1.58
0.8	-4.1

Corner is now controlled by ζ_b , not a constant of -3dB any more.