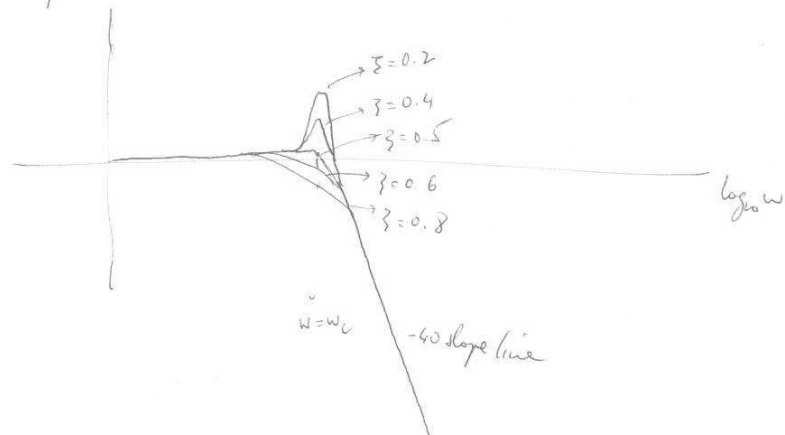


quadratic pole




Extra credit: 50 HW's points

$$\begin{aligned} \text{Draw } 20 \log_{10} |H| \text{ for } H(j\omega) &= \frac{25j\omega}{(j\omega + 0.5)(j\omega)^2 + 4j\omega + 100} \\ &= \frac{0.5j\omega}{\underbrace{(1 + j\frac{\omega}{0.5})}_{\omega_c = 0.5} \underbrace{(1 + 4j\frac{\omega}{100} + (j\frac{\omega}{10})^2)_{\omega_c = 10}} \end{aligned}$$

$$\omega_c = 0.5, 10$$

$$2\zeta_b = \frac{4}{10} \rightarrow \zeta_b = 0.2 \quad (\text{big bump})$$

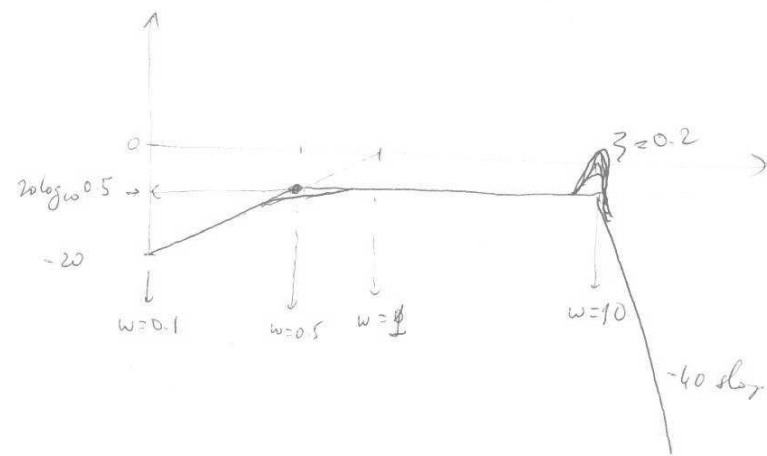- Before 0.5: a line up +20 slope by $(j\omega) \rightarrow 20 \log_{10} 0.5$
- B/w 0.5 & 10: $(1 + j\frac{\omega}{0.5})$ kinks in with -20 slope line.
→ total flat.
- After $\omega = 10$: quadratic kinks in with -40 slope.



Phase Bode plot: $\hat{H}(j\omega) = \frac{0.5j\omega}{(1 + j\frac{\omega}{0.5})(1 + \frac{4}{10}j\frac{\omega}{10} + (j\frac{\omega}{10})^2)}$




$$\angle \hat{H}(j\omega) = \text{Phase}(0.5j\omega) - \underbrace{\text{Phase}(1 + j\frac{\omega}{0.5})}_{\text{asymptotic analysis}} - \underbrace{\text{Phase}(1 + \frac{4}{10}j\frac{\omega}{10} + (j\frac{\omega}{10})^2)}_{\text{asymptotic analysis}}$$

$$= 90^\circ$$

$\left\{ \begin{array}{l} \text{large } \omega \rightarrow 90^\circ \\ \text{small } \omega \rightarrow 0^\circ \\ \text{critical } \omega_c = 0.5 \rightarrow 45^\circ \end{array} \right.$


$\left\{ \begin{array}{l} \text{large } \omega: 180^\circ \\ \text{small } \omega: 0^\circ \\ \omega_c = 10 \rightarrow \text{Phase}(0.4j) = \end{array} \right.$

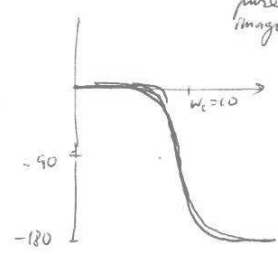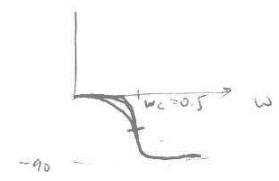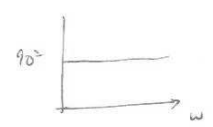$\underbrace{\text{pure imaginary}}_{\text{imaginary}}$




Combining them together: by pieces of ω

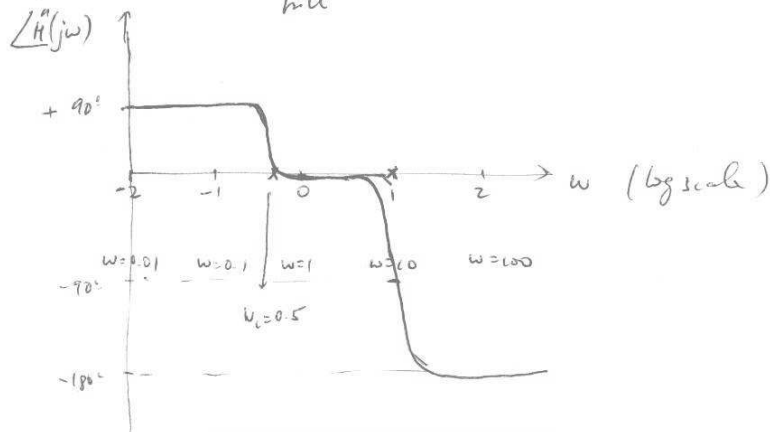- Before $\omega_c = 0.5$: just from numerator : 90°
- B/w $\omega_c = 0.5$ & $\omega_c = 10$: now also from 1st order pole : total phase going down from 90° to 0°
- After $\omega_c = 10$: quad. pole contributes another 180° down till



Resonant Frequency : ω such that $\hat{Z}$ is pure resistive
 or $\theta = 0$ or $p.f. = \cos \theta = 1$

E.g:

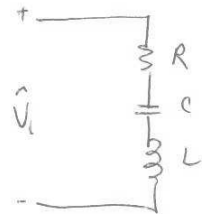

$$\hat{Z}(j\omega) = R + j\omega L + \frac{1}{j\omega C}$$

$$= R + j\left(\omega L - \frac{1}{\omega C}\right)$$


$$\omega_0 L = \frac{1}{\omega_0 C} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

"Quality factor" : $Q = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$

Filter Networks :

- Passive filters : using R, L, C (no gain for a reasonable bandwidth)
 ↓
 just select a range of frequency
- Active filters : Op-Amps (gain higher than 1)
 ↓
 select and enhance a range of frequency


Passive - Low pass :

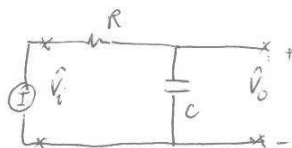

input →  → just low frequency components


$$\hat{H} = \frac{\hat{V}_o}{\hat{V}_i} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$


$$\omega_c = \frac{1}{RC}$$

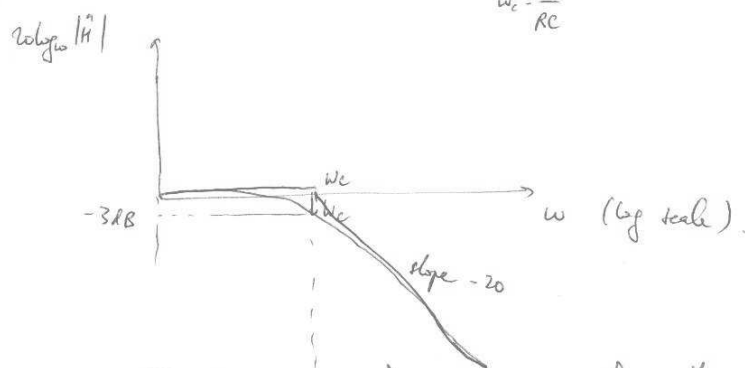




This RC arrangement passes components with $\omega < \omega_c$, and blocks components with $\omega > \omega_c$, i.e. it is a low-pass filter.

$$\angle \frac{1}{1 + j\omega RC}$$

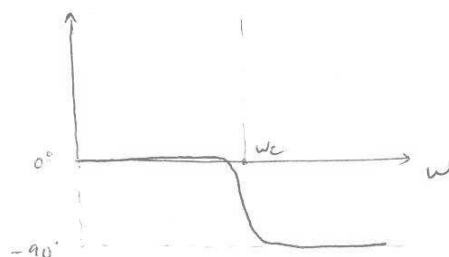

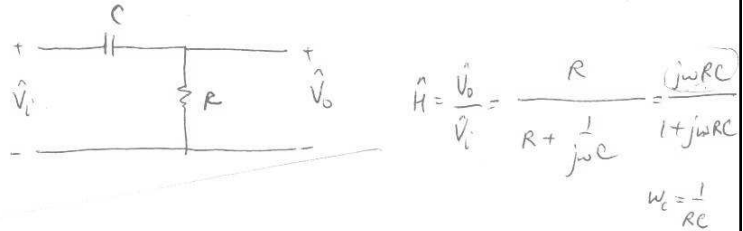

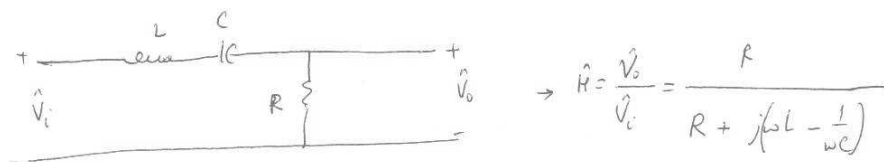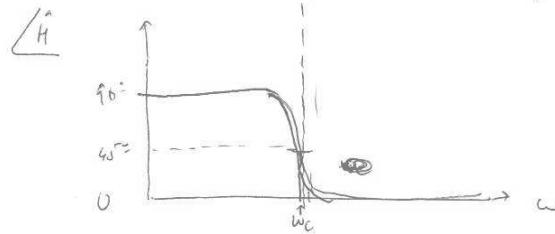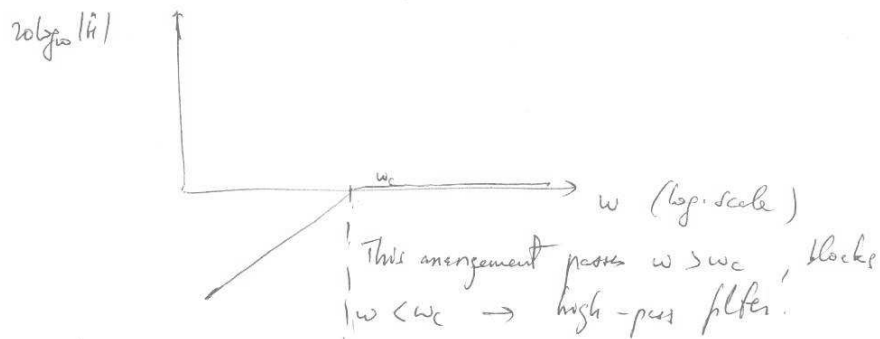- Before $\omega_c = \frac{1}{RC}$: line goes up with slope +20 (from numerator)
 → At $\omega_c = \frac{1}{RC}$: pole contributes a line of slope -20 → total of flat behavior as req.



can reduce to standard form and make Bode plot to determine filter behaviour or use $H = \frac{RC\omega}{RC\omega + j(LC\omega^2 - 1)}$

(57)

$$\hat{H} = \frac{RC\omega}{RC\omega + j(LC\omega^2 - 1)} \left\{ \begin{array}{l} \text{Magnitude: } \frac{RC\omega}{\sqrt{(RC\omega)^2 + (LC\omega^2 - 1)^2}} \\ \text{Phase: } -\tan^{-1}\left(\frac{LC\omega^2 - 1}{RC\omega}\right) \end{array} \right. \quad \left\{ \begin{array}{l} \text{Small } \omega \text{ or } \omega \ll \frac{1}{\sqrt{LC}} \end{array} \right.$$

Small ω or $\omega \ll \frac{1}{\sqrt{LC}} \rightarrow \omega^2 \ll \frac{1}{LC} \rightarrow LC\omega^2 \ll 1 \rightarrow \text{Magn: } \frac{RC\omega}{\sqrt{(RC\omega)^2 + 1}}$

Large ω or $\omega \gg \frac{1}{\sqrt{LC}} \rightarrow \omega^2 \gg \frac{1}{LC} \rightarrow LC\omega^2 \gg 1 \rightarrow \sim RC\omega \rightarrow 0$


$\hookrightarrow \text{Magn: } \frac{RC\omega}{\sqrt{(LC\omega^2)^2}}$

$= \frac{RC\omega}{LC\omega^2} = \frac{R}{L\omega} \rightarrow 0$

$\omega_c = \frac{1}{\sqrt{LC}} \rightarrow \text{Magn } \frac{RC\omega}{\sqrt{(RC\omega)^2}} = 1$

(Resonant
freq)

$|\hat{H}|$


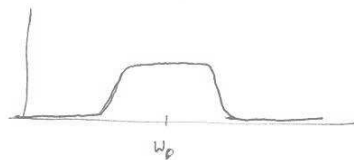


Band-pass filter
(L, C, R)

→ Question (5 exam points) : can we make a band-pass filter with only RC elements? Give concrete values for R's and C's for this to happen.

Active filters: Op-Amp.

Inverting

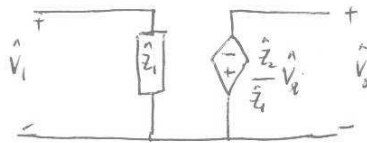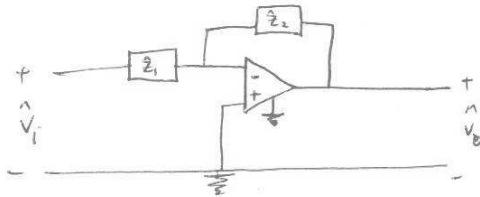

Non-inverting

