


Circuit Analysis II

Sy' 07

AC Steady-state Analysis

Alternate current: Sine wave: $x(t) = A \sin(\omega t + \theta)$

amplitude angular frequency phase

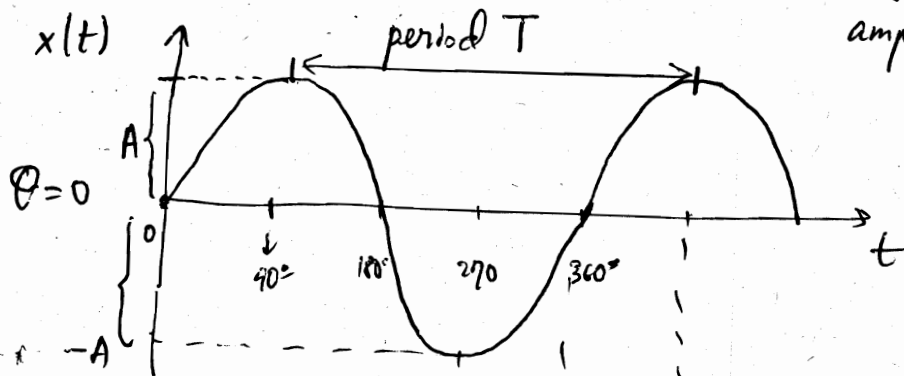


T : how many seconds per cycle; f : frequency: how many cycles per second $\rightarrow f = \frac{1}{T}$

ω : angular frequency = $2\pi f$ (omega)

Standard AC: $f = 60 \text{ Hz}$ $\rightarrow \omega = 377 \text{ s}^{-1}$


θ : phase (in radian) (theta)

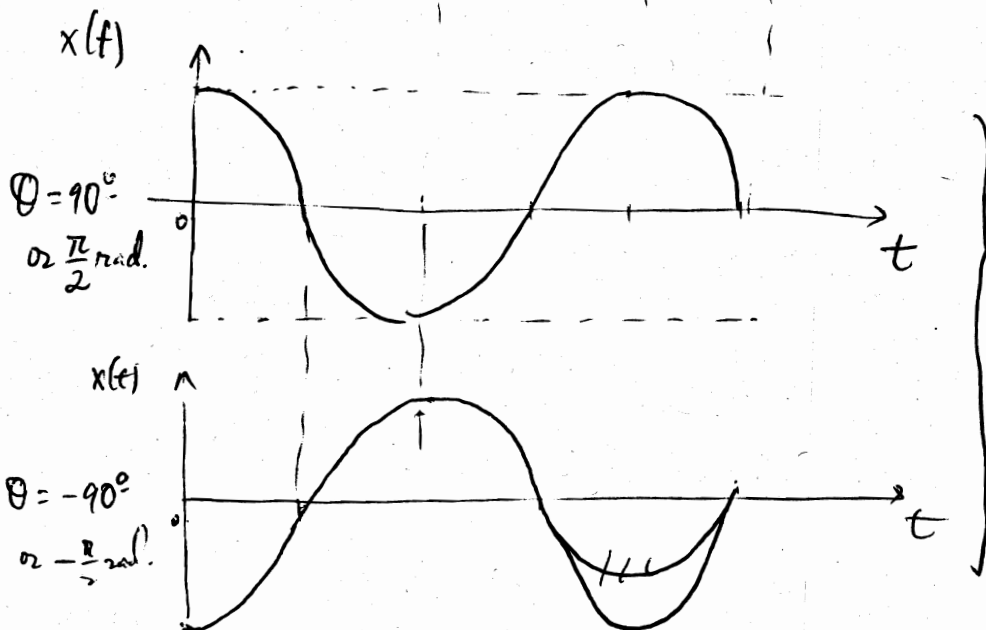

a $\theta = 180^\circ$ or $\pi \text{ rad}$ is a minus sign.

→ Sinusoids : A, ω, θ

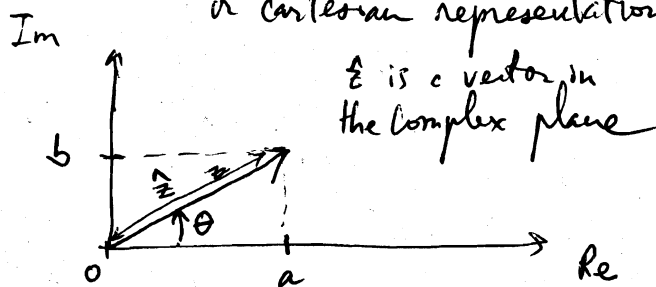→ Complex numbers : $\hat{z} = a + jb$ $\begin{cases} a = \text{Re}(\hat{z}) : \text{real part} \\ b = \text{Im}(\hat{z}) : \text{imaginary part} \end{cases}$
 ↳ rectangular
 or cartesian representation.



$\hat{z} = z \angle \theta$: polar representation

Rectangular
 $\hat{z} = (a, b)$

→ polar
 $\hat{z} = (z, \theta)$

$$\begin{cases} z = \sqrt{a^2 + b^2} \\ \theta = \tan^{-1}\left(\frac{b}{a}\right) \end{cases} \quad \text{Pythagoras Theorem}$$

$$\begin{cases} a = z \cos \theta \\ b = z \sin \theta \end{cases}$$

So why complex numbers?

Linear circuits : (R, L, C) : ω is same for all elements!

→ A, θ → represented by $\hat{z} = (z, \theta)$

Sinusoids & complex numbers:

$$A \sin(\omega t + \theta) = \textcircled{A} \text{Im} [e^{j(\omega t + \theta)}] = \text{Im} [A e^{j(\omega t + \theta)}]$$

$$\boxed{e^{j\alpha} = \cos \alpha + j \sin \alpha} \quad \text{or} \quad \text{Im} [e^{j\alpha}] = \sin \alpha ; \text{Re} [e^{j\alpha}] = \cos \alpha$$

polar form

$$r = 1 \angle \alpha$$

rectangular form

$$1 \cos \alpha + j 1 \sin \alpha$$

$$\boxed{e^{(v+s)} = e^v \cdot e^s}$$

$$\rightarrow \text{Im} [A e^{j\theta} \cdot e^{j\omega t}]$$

ω is same in linear circuits


Phasors

We use phasors to represent sinusoids, phasors are

clearly complex numbers: $A e^{j\theta}$ is the polar form of a complex number of magnitude A & phase θ ; is a vector in a complex plane

Let's compare 2 sinusoids
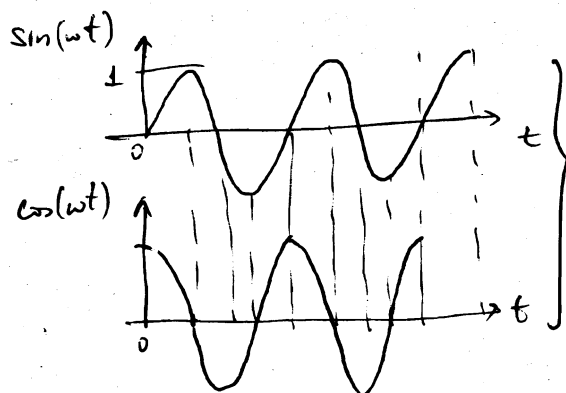
$$\begin{cases} v_1(t) = 12 \sin(100t + 60^\circ) \\ v_2(t) = -6 \cos(100t + 30^\circ) \\ \quad = -6 \sin(100t + 120^\circ) \\ \quad = 6 \sin(100t - 60^\circ) = 6 \sin(100t + 300^\circ) \end{cases}$$




$$\cos(\omega t) = \sin(\omega t + 90^\circ) = \sin(\omega t + 300^\circ)$$


$$v_1(t) = 12 \sin(\underbrace{100t}_\omega + 60^\circ)$$

$$\begin{aligned} v_2(t) &= 6 \sin(100t + 300^\circ) \\ &= 6 \sin(\underbrace{100t}_\omega - 60^\circ) \end{aligned}$$

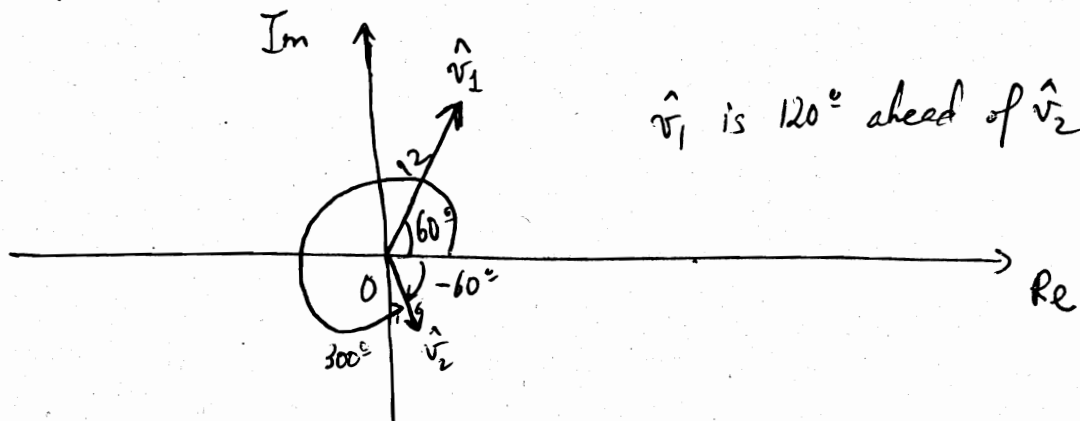Represent as phasors = vectors in a complex plane:



Connection to circuits:

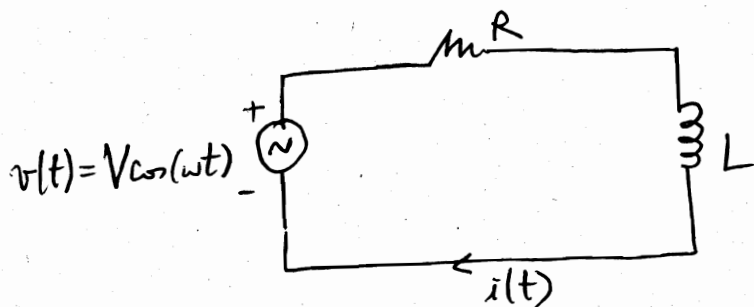

Let's solve for $i(t)$ in the ~~time~~ time-domain or not using phasors

* Loop analysis: $V \cos \omega t = Ri + L \frac{di}{dt}$ (1)

→ Assume: $i(t) = \underset{?}{I} \cos(\omega t + \underset{?}{\theta})$
 same b/c linear circuit

$$\begin{aligned} i(t) &= I [\cos \omega t \cos \theta - \sin \omega t \sin \theta] \\ &\equiv I_1 \cos \omega t + I_2 \sin \omega t \quad \begin{cases} I_1 \equiv I \cos \theta \\ I_2 \equiv -I \sin \theta \end{cases} \end{aligned}$$

(5)

Now substitute into the loop equation:

$$V \cos \omega t = R \underbrace{[I_1 \cos \omega t + I_2 \sin \omega t]}_{i(t)} + L\omega [-I_1 \sin \omega t + I_2 \cos \omega t]$$

$$V \cos \omega t = \underbrace{(RI_1 + L\omega I_2)}_V \cos \omega t + \underbrace{(RI_2 - L\omega I_1)}_0 \sin \omega t$$

(remember $\sin(\omega t)$ & $\cos(\omega t)$ are out of phase by 90° , which means they are perpendicular in phasors complex plane).

$$\rightarrow \begin{cases} RI_1 + L\omega I_2 = V \\ I_2 = \frac{L\omega}{R} I_1 \end{cases} \rightarrow \begin{cases} I_1 = \frac{R}{(L\omega)^2 + R^2} V \\ I_2 = \frac{L\omega}{(L\omega)^2 + R^2} V \end{cases}$$

$$\rightarrow i(t) = I_1 \cos \omega t + I_2 \sin \omega t = I \cos(\omega t + \theta) \begin{cases} I_1^2 + I_2^2 = I^2 \\ \frac{I_2}{I_1} = -\tan \theta \\ \rightarrow \theta = -\tan^{-1} \frac{I_2}{I_1} \end{cases}$$

$$= \sqrt{I_1^2 + I_2^2} \cos\left(\omega t - \tan^{-1} \frac{I_2}{I_1}\right)$$

$$1) \sqrt{I_1^2 + I_2^2} = \sqrt{\frac{R^2}{[(L\omega)^2 + R^2]^2} V^2 + \frac{L^2 \omega^2}{[(L\omega)^2 + R^2]^2} V^2} = V \sqrt{\frac{R^2 + L^2 \omega^2}{[(L\omega)^2 + R^2]^2}}$$

$$= \frac{V}{\sqrt{(L\omega)^2 + R^2}}$$


$$2) -\tan^{-1} \frac{I_2}{I_1} = -\tan^{-1} \left(\frac{L\omega}{R} \right)$$

$$\rightarrow i(t) = \frac{V}{\sqrt{(L\omega)^2 + R^2}} \cos\left(\omega t - \tan^{-1} \left(\frac{L\omega}{R} \right)\right)$$

Solution for the AC current in the RL circuit.

⑥

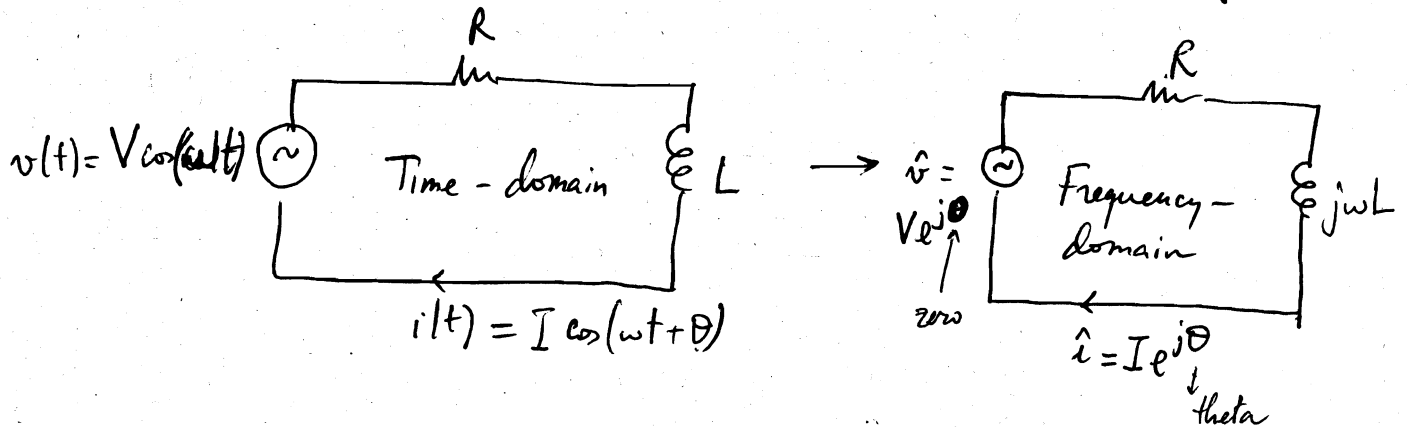Now let's solve the same circuit using phasors $(A e^{j\theta})$
or $(A \angle \theta)$



→ Phasor representation: same variable name, add a hat

$$v(t) = V \cos \omega t \longrightarrow \hat{v} = V e^{j0}$$

→ Impedance = $\hat{Z}$

Resistance in D.C: $R = \frac{V}{I}$ (Ohm's Law)

Impedance in A.C: $\hat{Z} = \frac{\hat{v}}{\hat{i}}$ (Ohm's Law for phasors)

At L : $v_L = L \frac{di}{dt}$

$A \cos(\omega t + \theta) = \text{Re} [A e^{j(\omega t + \theta)}] = \text{Re} [A e^{j\theta} e^{j\omega t}]$

↑ Simusoid

↑ product of complex exponentials (Take real part at the end).

$v_L = L \frac{di}{dt}$

$\hat{v}_L e^{j\omega t} = L \frac{d}{dt} (\hat{i} e^{j\omega t}) = L \hat{i} \frac{d}{dt} (e^{j\omega t}) = L j\omega \hat{i} e^{j\omega t}$

$$\Rightarrow \hat{v}_L e^{j\omega t} = j\omega L \hat{i} e^{j\omega t}$$

$$\frac{\hat{v}_L}{\hat{i}} = j\omega L \quad : \text{ Ohm's law for phasors at the inductor.}$$




$\hat{Z}_L$: impedance at the inductor.

At R:

$$v_R = R i_R \rightarrow \hat{v}_R e^{j\omega t} = R \hat{i}_R e^{j\omega t}$$


$$\hat{Z}_R = \frac{\hat{v}_R}{\hat{i}_R} = R$$

In summary:

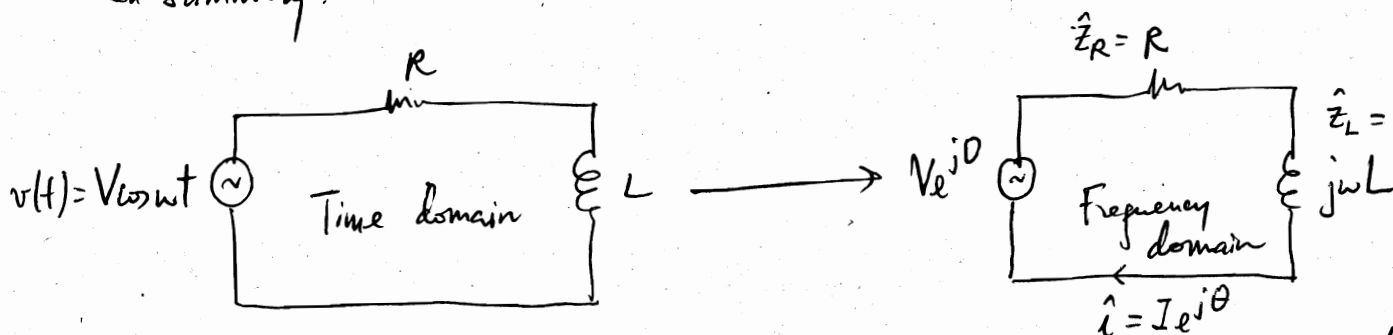

Ohm's law works for phasors:
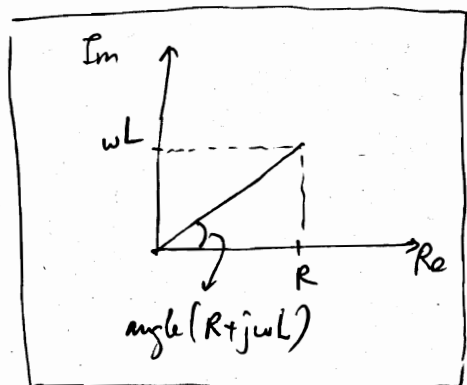
$$\hat{i} = \frac{V e^{j0}}{\hat{Z}_R + \hat{Z}_L} = \frac{V}{R + j\omega L} = \text{Magnitude of } \frac{V}{R + j\omega L} \angle \text{Angle of } \frac{V}{R + j\omega L}$$



$$\hat{i} = \frac{|V|}{|R + j\omega L|} e^{j[\text{Angle}(V) - \text{Angle}(R + j\omega L)]}$$

$$\hat{i} = \frac{V}{\sqrt{R^2 + (\omega L)^2}} e^{j[0 - \tan^{-1} \frac{\omega L}{R}]}$$

$$(i(t) = \text{Re}[\hat{i} e^{j\omega t}])$$

$$i(t) = ?$$

$$i(t) = \text{Re} \left[\frac{V}{\sqrt{R^2 + (\omega L)^2}} e^{-j \tan^{-1} \frac{\omega L}{R}} e^{j\omega t} \right] = \text{Re} \left[\frac{V}{\sqrt{R^2 + (\omega L)^2}} e^{j(\omega t - \tan^{-1} \frac{\omega L}{R})} \right]$$


8

$$i(t) = \frac{V}{\sqrt{R^2 + (\omega L)^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

2

1

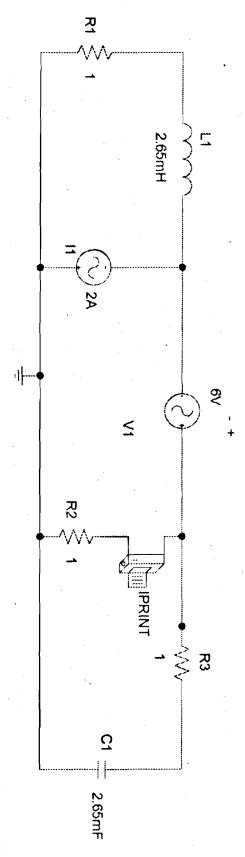We will find current through R2 for $f=60\text{Hz}$ using PSpice



2

1

Pspice01.out

□
 **** 02/06/07 13:45:58 ***** Evaluation Pspice (Nov 1999) *****

* C:\Temp\232s07\Pspice01.sch

**** CIRCUIT DESCRIPTION

* Schematics Version 9.1 - web Update 1
 * Tue Feb 06 13:45:58 2007

** Analysis setup **
 .ac LIN 1 60 60
 .OP

* From [PSPIICE NETLIST] section of pspiceev.ini:
 .lib "nom.lib"

.INC "Pspice01.net"

**** INCLUDING Pspice01.net ****
 * Schematics Netlist *

L_L1 \$N_0001 \$N_0002 2.65mH
 R_R3 \$N_0004 \$N_0003 1
 C_C1 0 \$N_0003 2.65mF
 R_R1 0 \$N_0001 1
 R_R2 0 \$N_0005 1
 I_I1 0 \$N_0002 DC 0A AC 2A
 V_V1 \$N_0004 \$N_0002 DC 0V AC 6V
 V_PRINT1 \$N_0004 \$N_0005 0V

.PRINT AC
 + IM(V_PRINT1)
 + IP(V_PRINT1)

**** RESUMING Pspice01.cir ****
 .INC "Pspice01.als"

**** INCLUDING Pspice01.als ****
 * Schematics Aliases *

.ALIASES
 L_L1 L1(1=\$N_0001 2=\$N_0002)
 R_R3 R3(1=\$N_0004 2=\$N_0003)
 C_C1 C1(1=0 2=\$N_0003)
 R_R1 R1(1=0 2=\$N_0001)
 R_R2 R2(1=0 2=\$N_0005)
 I_I1 I1(+=0 -= \$N_0002)
 V_V1 V1(+= \$N_0004 -= \$N_0002)

V_PRINT1 Pspice01.out
PRINT1(1=\$N_0004 2=\$N_0005)

.ENDALIASES

**** RESUMING Pspice01.cir ****
.probe

.END

02/06/07 13:45:58 ***** Evaluation Pspice (Nov 1999) *****

* C:\Temp\232s07\Pspice01.sch

**** SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(\$N_0001)	0.0000			(\$N_0002)	0.0000		
(\$N_0003)	0.0000			(\$N_0004)	0.0000		
(\$N_0005)	0.0000						

VOLTAGE SOURCE CURRENTS
NAME CURRENT

V_V1 0.000E+00
V_PRINT1 0.000E+00

TOTAL POWER DISSIPATION 0.00E+00 WATTS

02/06/07 13:45:58 ***** Evaluation Pspice (Nov 1999) *****

* C:\Temp\232s07\Pspice01.sch

**** OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG C

02/06/07 13:45:58 ***** Evaluation Pspice (Nov 1999) *****

* C:\Temp\232s07\Pspice01.sch

**** AC ANALYSIS TEMPERATURE = 27.000 DEG C

Pspice01.out

FREQ IM(V_PRINT1) IP(V_PRINT1)




6.000E+01 2.917E+00 -3.095E+01

JOB CONCLUDED

TOTAL JOB TIME .02

□


HW#1:

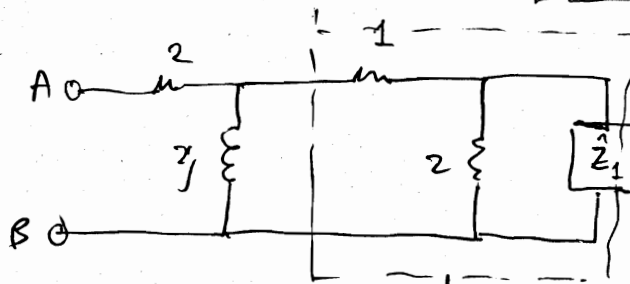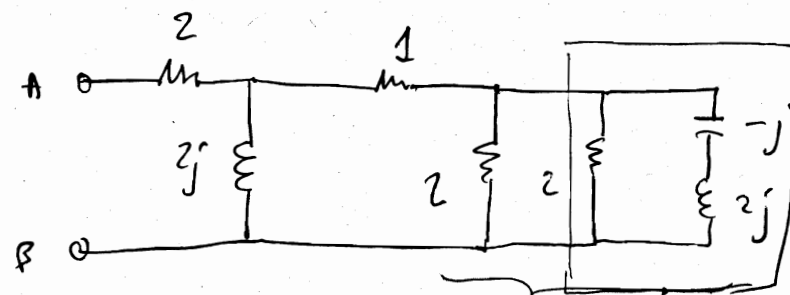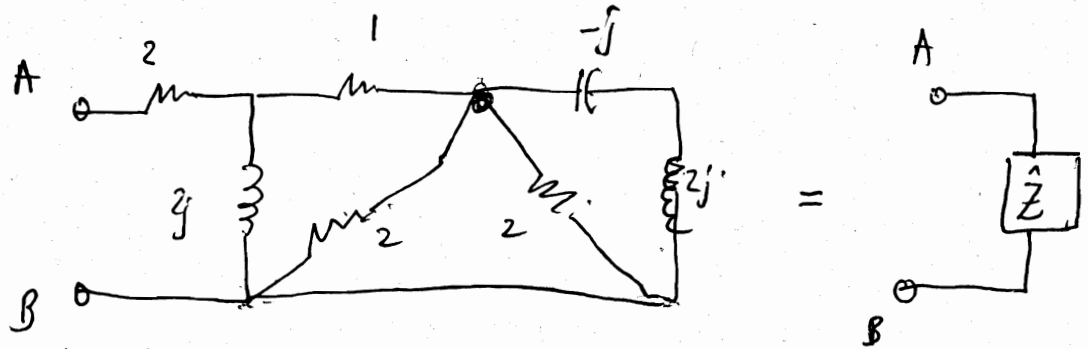

$$\hat{Z}_1 = 2 \parallel j = \frac{2j}{2+j}$$

$$(R_1 \parallel R_2 \Rightarrow \frac{1}{R_{||}} = \frac{1}{R_1} + \frac{1}{R_2})$$

$$R_{||} = \frac{R_1 R_2}{R_1 + R_2}$$

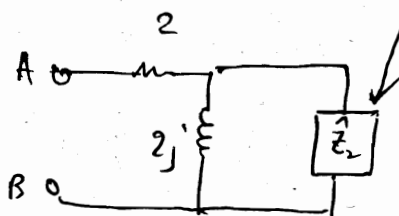

Now implement this using impedances

$$\hat{Z}_2 = 1 + \left(2 \parallel \frac{2j}{2+j} \right) = 1 + \frac{4j/(2+j)}{2 + \frac{2j}{2+j}}$$

$$= 1 + \frac{4j}{2(2+j) + 2j}$$

$$= 1 + \frac{4j}{4 + 4j} = 1 + \frac{j}{1+j}$$

$$\rightarrow \hat{z}_2 = \frac{1+j+j}{1+j} = \frac{1+2j}{1+j}$$

A ○ ————

 |

 | $\hat{z}$

 |

B ○ ————

$$\rightarrow \hat{z} = 2 + \left(2j \parallel \frac{1+2j}{1+j} \right) = 2 + \frac{\frac{2j-4}{1+j}}{2j + \frac{1+2j}{1+j}}$$

$$\boxed{j^2 = -1} \quad \boxed{\frac{1}{j} = -j}$$

$$= 2 + \frac{2j-4}{2j-1+1+2j} = 2 + \frac{2j-4}{4j-1}$$

$$= \frac{-2+8j+2j-4}{4j-1} = \frac{-6+10j}{4j-1}$$


$$= \frac{-6+10j}{-1+4j} = \frac{\sqrt{36+100}}{\sqrt{1+16}} \angle \left(\tan^{-1}\left(\frac{10}{-6}\right) + 180^\circ \right)$$

$$= \frac{11.66}{4.12} \angle \left(-59.9^\circ + 180^\circ \right) = 2.829 \angle -59.9^\circ + 75.96^\circ$$

$$= 2.83 \angle 16.96^\circ$$


$$\boxed{\hat{z} = 2.83 \angle 16.96^\circ}$$
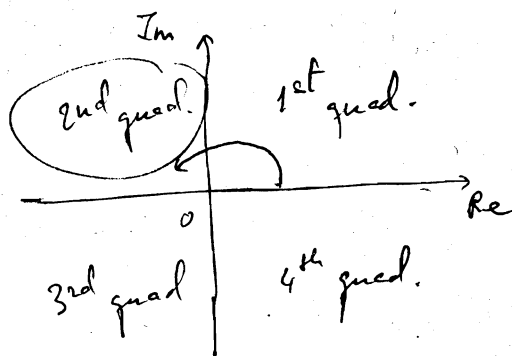
$$\frac{\hat{z}'}{\hat{z}''} = \frac{z' e^{j\theta'}}{z'' e^{j\theta''}} = \frac{z'}{z''} e^{j(\theta' - \theta'')} \quad \text{Minus!}$$




angle: measured from
Re axis, going counterclockwise
If going clockwise $\rightarrow$ negative
angle.


Back to circuit analysis using phasors:

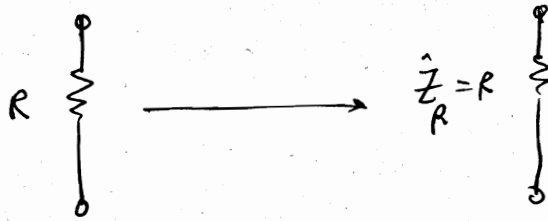

(using Ohm's law
with phasors)

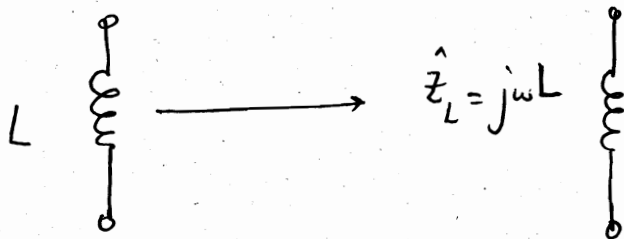

"

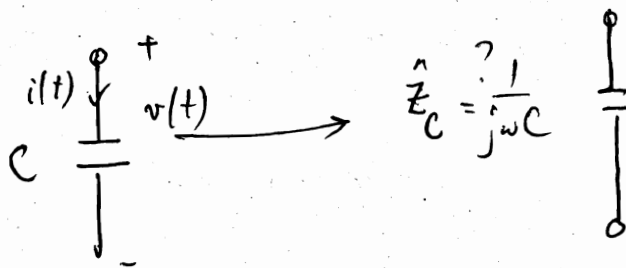

$$i(t) = C \frac{dv}{dt}$$

→ phasors:


$$\hat{I} e^{j\omega t} = C \frac{d(\hat{V} e^{j\omega t})}{dt}$$

$\hat{V} j\omega e^{j\omega t}$

$$\hat{I} = C \hat{V} j\omega$$

$$\hat{Z}_C = \frac{\hat{V}}{\hat{I}} = \frac{1}{j\omega C}$$

AC Circuit Analysis Techniques:

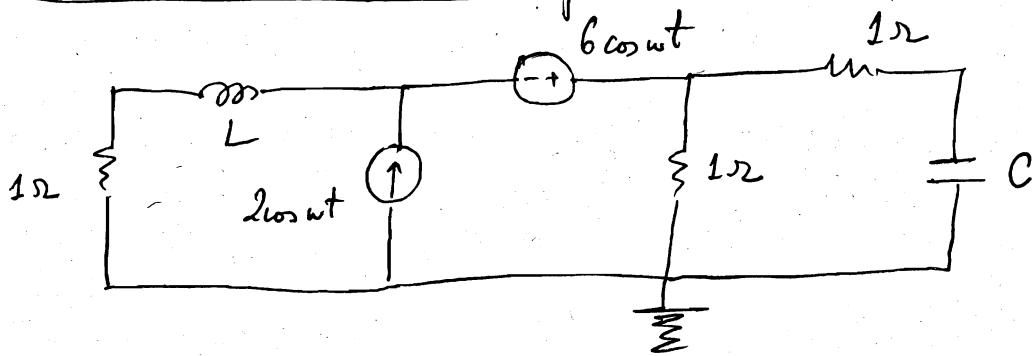

$$L = 2.65 \text{ mH}$$

$$C = 2.65 \text{ nF}$$

$$\omega = 2\pi f; \quad f = 60 \text{ Hz}$$

Redraw same circuit in frequency-domain using phasors.

