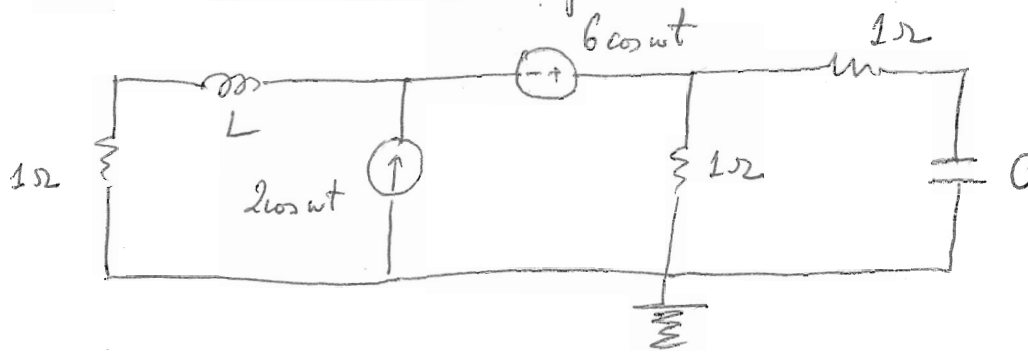


AC Circuit Analysis Techniques:




$$L = 2.65 \text{ mH}$$

$$C = 2.65 \text{ mF}$$

$$\omega = 2\pi f; \quad f = 60 \text{ Hz}$$

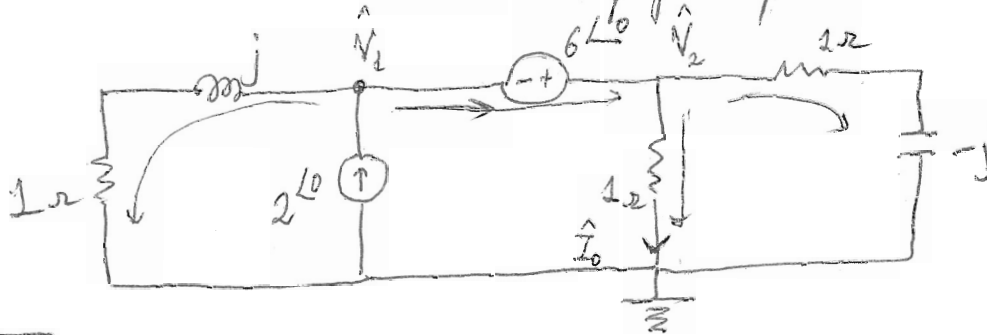Redraw same circuit in frequency-domain using phasors.



Notes #1

Nodal Analysis:

How many nodes? 2 with phasor voltages $\hat{V}_1$ & $\hat{V}_2$

$$1) \text{ Kirchhoff's law for current at node \#1: } \sum_i \hat{I}_i = 0 \quad \left\{ \begin{array}{l} \text{current into node} = + \\ \text{current leaving node} = - \end{array} \right.$$

$$+2 - \frac{\hat{V}_1}{1+j} - \left[\frac{\hat{V}_2}{1} + \frac{\hat{V}_2}{1-j} \right] = 0$$

$$2) \quad \hat{V}_2 = \hat{V}_1 + 6$$

Now this is a system of 2 equations with 2 unknowns. We want to solve for I_0 : eliminate $\hat{V}_1 \rightarrow 2 - \frac{\hat{V}_2 - 6}{1+j} - \frac{\hat{V}_2}{1} - \frac{\hat{V}_2}{1-j} = 0$

$$2 + \frac{6}{1+j} = \hat{V}_2 \left(\frac{1}{1+j} + 1 + \frac{1}{1-j} \right) = \hat{V}_2 \frac{1-j + (1+j)(1-j) + (1+j)}{(1+j)(1-j)}$$

$$(a+jb)(a-jb) = a^2 + b^2 - abj + abj = a^2 + b^2 = |a+jb|^2$$

$$(1+j)(1-j) = (\sqrt{2})^2 = 2$$

$$\rightarrow 2 + \frac{6}{1+j} = \hat{V}_2 \frac{2+2}{2} = 2\hat{V}_2$$


$$\hat{V}_2 = 1 + \frac{3}{1+j} = \frac{1+j+3}{1+j} = \frac{4+j}{1+j}$$

$$\hat{I}_0 = \frac{\hat{V}_2}{1\Omega} = \frac{4+j}{1+j} \text{ A} = \frac{\sqrt{17} e^{j \tan^{-1}(\frac{1}{4})}}{\sqrt{2} e^{j 45^\circ}} = \underline{2.91} e^{j(-31^\circ)}$$

$$\rightarrow i_0(t) = 2.91 \cos(377t - 31^\circ) \text{ A}$$

(assume a standard AC power source at 60 Hz)

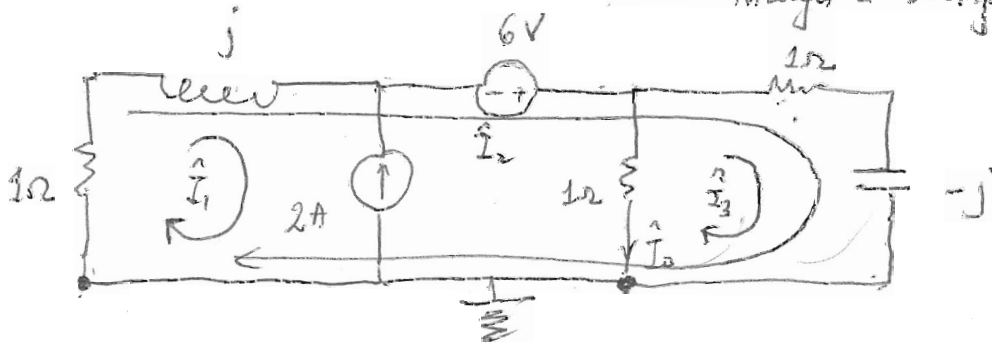Loop Analysis: $\sum_i \hat{V}_i = 0$ $\left\{ \begin{array}{l} \hat{V} \text{ negative across an impedance} \\ \hat{V} \text{ positive if going - to + through a voltage source} \end{array} \right.$



1) $\hat{I}_1 = -2 \text{ A}$ (since we choose our 3 loops as above)

2) $-(1+j)(\hat{I}_1 + \hat{I}_2) + 6 - (1-j)(\hat{I}_2 + \hat{I}_3) = 0$

3) $-1 \cdot \hat{I}_3 - (1-j)(\hat{I}_2 + \hat{I}_3) = 0$

Since $\hat{I}_0 = -\hat{I}_3$, I need to eliminate $\hat{I}_2$

3) $(-2+j)\hat{I}_3 = +(1-j)\hat{I}_2 \rightarrow \boxed{\hat{I}_2 = -\hat{I}_3 \frac{(2-j)}{1-j}}$

plug this back to 2)

$$-(1+j)(-2 + \hat{I}_2) + 6 - (1-j)\hat{I}_2 - (1-j)\hat{I}_3 = 0$$

$$\hat{I}_2(-1-j-1+j) + 2(1+j) + 6 - (1-j)\hat{I}_3 = 0$$

$$-2\hat{I}_2 - (1-j)\hat{I}_3 + 8 + 2j = 0$$

$$\left[\frac{2(2-j)}{1-j} - (1-j) \right] \hat{I}_3 + 8 + 2j = 0$$

$$\frac{4-j-1+j+1}{1-j}$$

$$\rightarrow \hat{I}_3 = - \frac{(8+2j)(1-j)}{4} = - \frac{10-6j}{4}$$




$$\hat{I}_0 = -\hat{I}_3 = \frac{10-6j}{4} = \frac{5-3j}{2} = \frac{\sqrt{34}}{2} e^{j \tan^{-1}(\frac{3}{5})}$$

4th quadrant!

$= 2.91 e^{j(-31^\circ)} \text{ A}$

$$i_0(t) = 2.91 \cos(377t - 31^\circ) \text{ A}$$

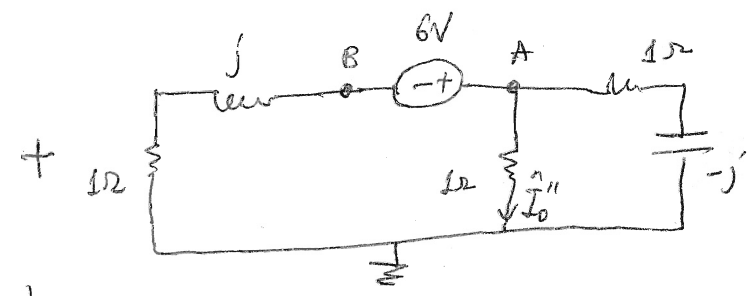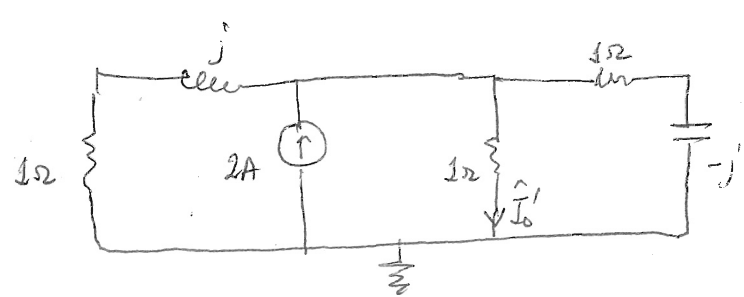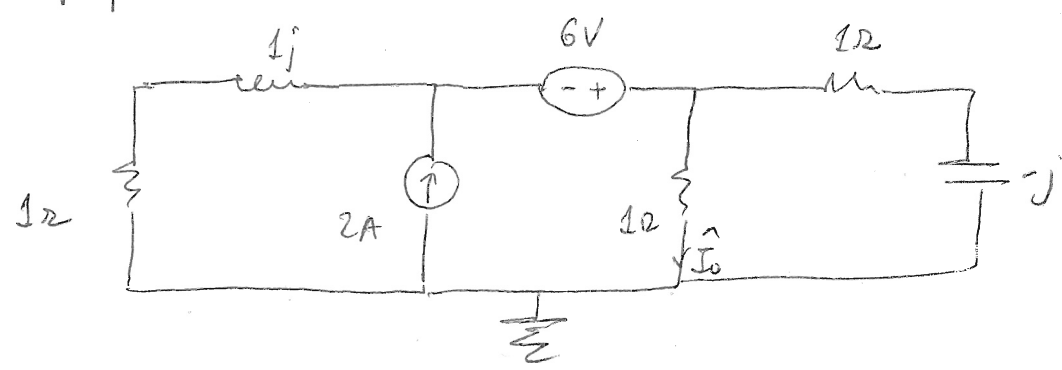
Superposition: (combining results from single sources)



Superposition $\hat{I}_0' + \hat{I}_0'' = \hat{I}_0$

↓
short-circuited voltage source

↘
open-circuited the current source

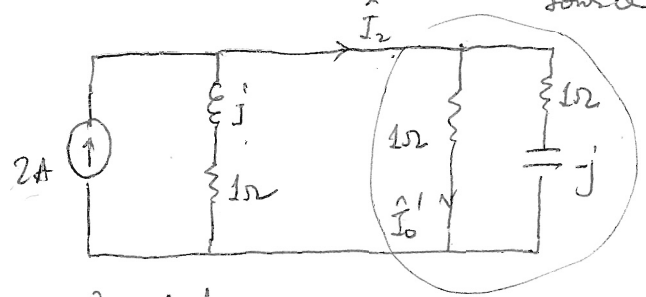


Current division:

$$\hat{I}_2 = 2A \frac{1+j}{1+j + \frac{(1-j) \cdot 1}{2-j}}$$

2nd current division:

$$\hat{I}_0' = \frac{1-j}{2-j} \cdot 2A \frac{1+j}{1+j + \frac{1-j}{2-j}}$$
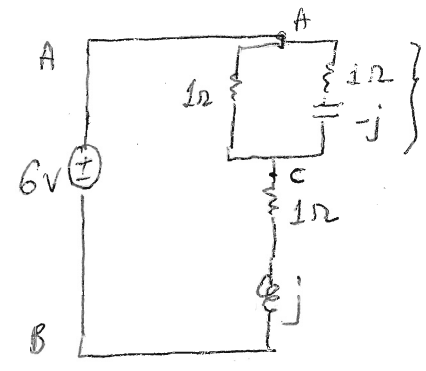
$$= \frac{4A}{(2-j)(1+j) + 1-j} = \frac{4A}{3+j+1-j} = 1A$$



Voltage div.

$$\begin{aligned} \hat{V}_{Ac} &= 6V \frac{(1-j) \cdot 1}{2-j} \bigg/ \left(\frac{1-j}{2-j} + 1+j \right) \\ &= \frac{(1-j) 6V}{(2-j)/(1+j) + (1-j)} \\ &= \frac{6}{4} (1-j) \end{aligned}$$

$$\hat{I}_0'' = \frac{\hat{V}_{Ac}}{1\Omega} = \frac{3}{2} (1-j) A$$


$$\begin{aligned} \hat{I}_0 &= \hat{I}_0' + \hat{I}_0'' = 1A + \frac{3}{2} (1-j) A \\ &= \frac{5-3j}{2} A = 2.91 \angle -31^\circ A \end{aligned}$$

$$i(t) = 2.91 \cos(200\pi t - 31^\circ) A$$

Frantzley Paul

Quiz #1 (5 min)

20

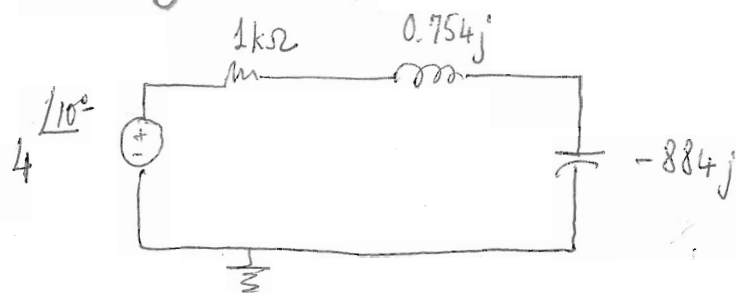

$$f = 60 \text{ Hz.}$$

Write this circuit back into time domain (for later implementation into PSpice)

~~7.38~~ ~~$\hat{N}_s = 5.9 \angle -23^\circ$~~
~~7.21~~ ~~$V(t) = 5.2 \cos(377t + 44.99^\circ) \text{ V}$~~

$$V \cos \omega t = R i + L \frac{di}{dt} + C \frac{dv}{dt}$$

$$4 \angle 10^\circ = 4 \cos(377t + 100^\circ)$$

$$R = 1 \text{ k}\Omega$$

$$Z = j\omega L = 0.754j = j377 \times L$$


$$L = 0.002 \text{ H} = 2 \text{ mH}$$

$$C = \frac{1}{j\omega C} = -884j$$


$$\frac{1}{377 C} = 884j$$

$$C = 3. \mu\text{F}$$


7.38

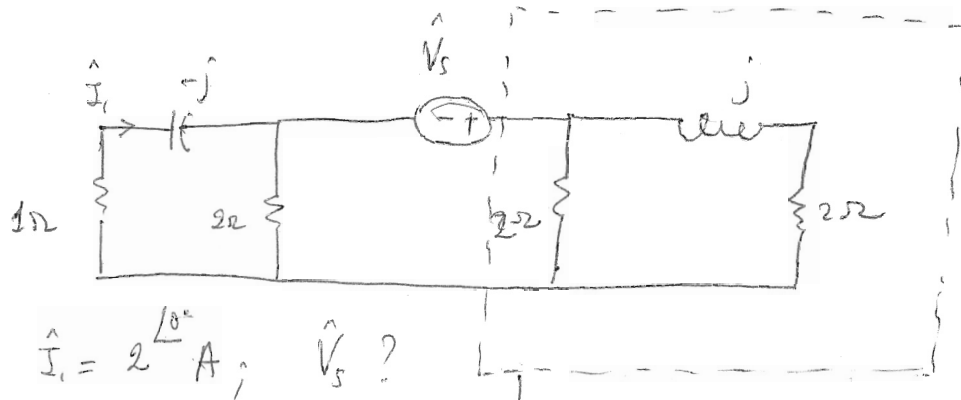
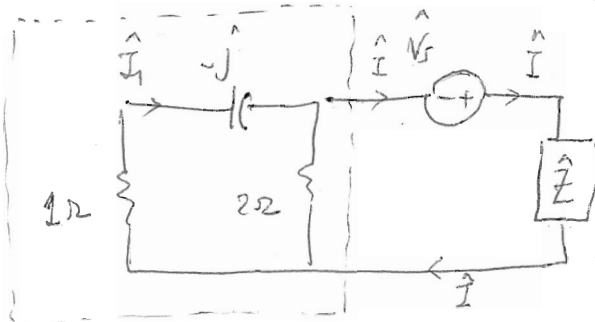
$$\hat{Z} = 2 \parallel (2+j) = \frac{2(2+j)}{4+j}$$


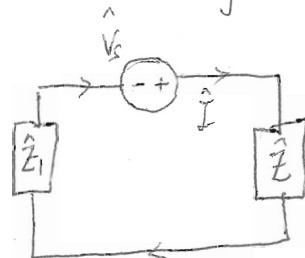
$$\hat{Z}_1 = 2 \parallel (1-j) = \frac{2(1-j)}{3-j}$$



$$\hat{V}_s = \hat{I} (\hat{Z} + \hat{Z}_1)$$

Current div. $\hat{I}_1 = \hat{I} \frac{2}{3-j} \rightarrow \hat{I} = \frac{\hat{I}_1 (3-j)}{2}$


$$\rightarrow \hat{V}_s = \hat{I}_1 \frac{3-j}{2} \left(\frac{2(2+j)}{4+j} + \frac{2(1-j)}{3-j} \right)$$

$$= \cancel{(3-j)} \frac{2(2+j)(3-j) + 2(4+j)(1-j)}{(4+j)\cancel{(3-j)}}$$


$$= 2 \frac{(7+j) + (5-3j)}{4+j} = 2 \frac{12-2j}{4+j} = 4 \frac{6-j}{4+j}$$

$$= 4 \frac{\sqrt{37}}{\sqrt{17}} e^{j(-\tan^{-1} \frac{1}{6} - \tan^{-1} \frac{1}{4})} = 5.9 \angle -23.5^\circ \text{ V}$$

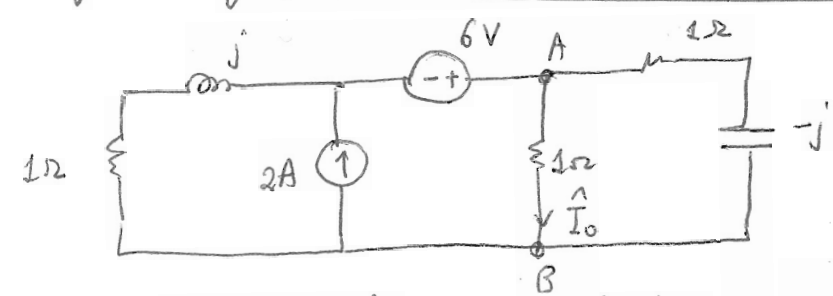AC Analysis using phasors: Thevenin Equivalent:



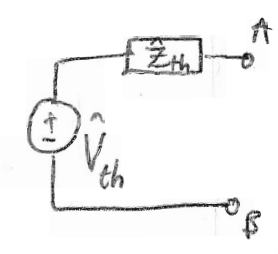Thevenin equivalent: replacing a circuit b/w A & B by




→ We will replace the circuit (without $\begin{matrix} A \\ | \\ 1\Omega \\ | \\ B \end{matrix}$) by a Thevenin equivalent

$$\hat{V}_{th} \equiv \hat{V}_{o.c. \text{ b/w } A \& B}$$


open circuit

$$\hat{Z}_{th} \equiv \hat{Z}_{\text{No sources \& across A\&B}}$$

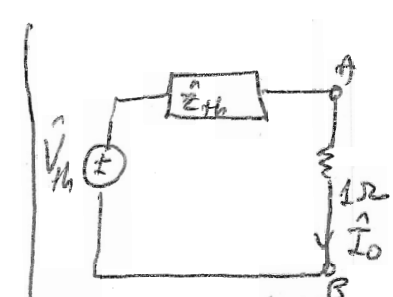
$\rightarrow$ voltage source : short-circuit
 $\rightarrow$ current source : open-circuit



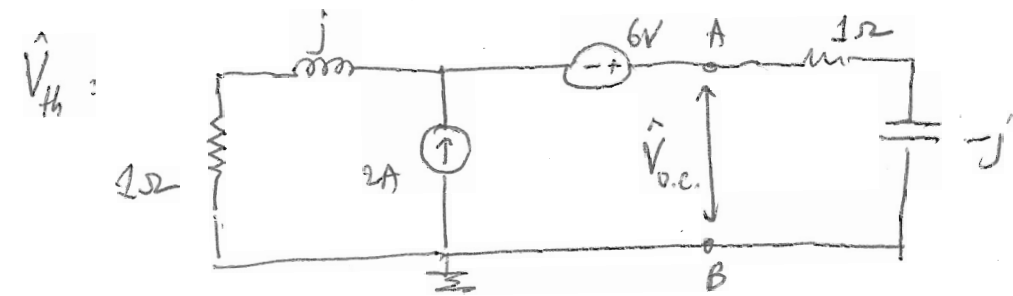
$$\hat{I}_o = \frac{\hat{V}_{th}}{\hat{Z}_{th} + 1}$$



source exchange:

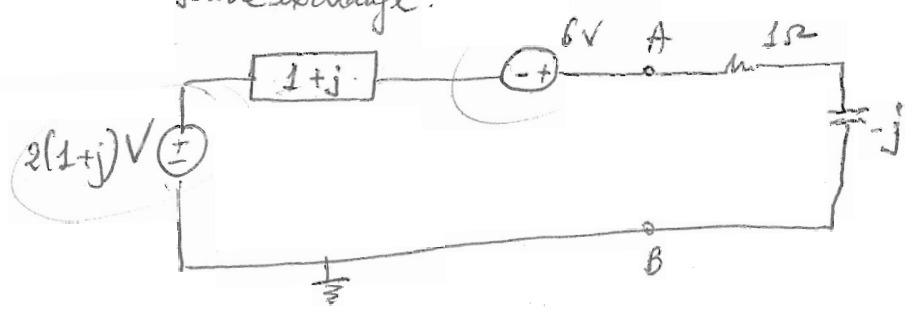


Combining the two voltage sources:

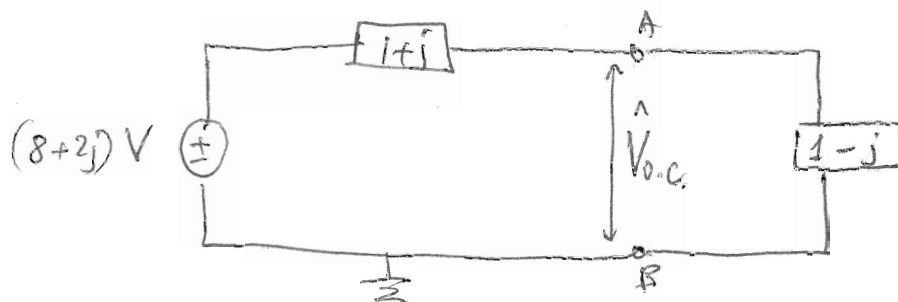


$$\hat{V}_{oc} = (8+2j) \frac{1-j}{1+j+1-j}$$


Voltage div.

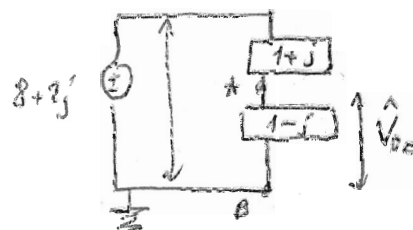
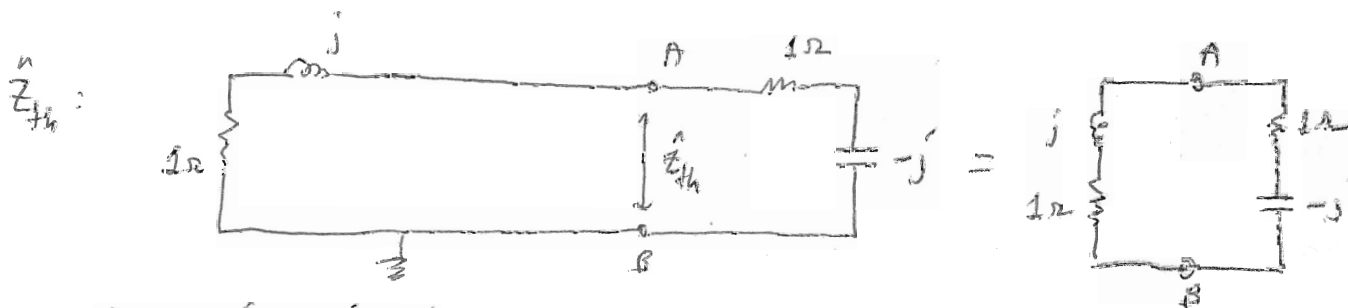
$$\hat{V}_{th} = \hat{V}_{oc} = (8+2j) \frac{(1-j)}{2} = \frac{10-6j}{2} = (5-3j) \text{ V}$$



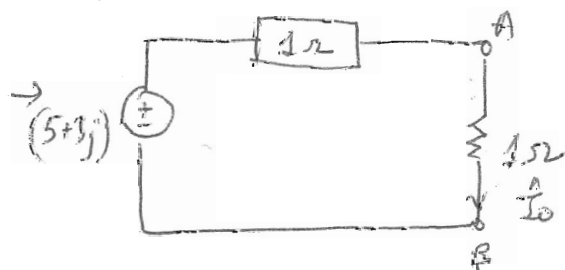
$$\hat{Z}_{th} = \frac{(1+j)(1-j)}{1+j+1-j} = \frac{2}{2} = 1 \Omega$$



$$\hat{I}_o = \frac{5+3j}{2} \text{ A} = 2.91 \angle 31^\circ \text{ A} \checkmark$$

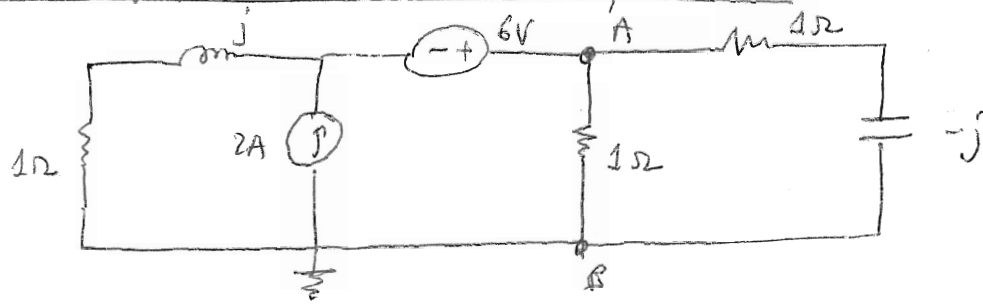
AC Analysis using phasors: Norton Equivalent:




Norton equivalent: replace a circuit b/w A & B by $\hat{I}_N$ and $\hat{Z}_{th}$

→ We will replace the circuit (without 1Ω) by a Norton equivalent
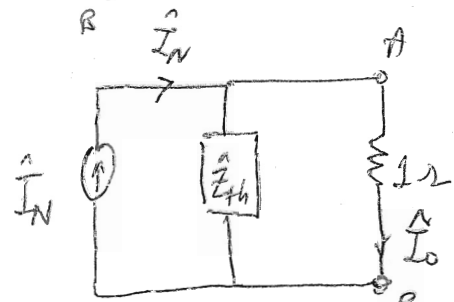
$$\left\{ \begin{array}{l} \hat{I}_N = \hat{I}_{s.c.} \text{ b/w A \& B} \\ \quad \quad \quad \hookrightarrow \text{short-circuit} \\ \hat{Z}_{th} = 1\Omega \end{array} \right.$$




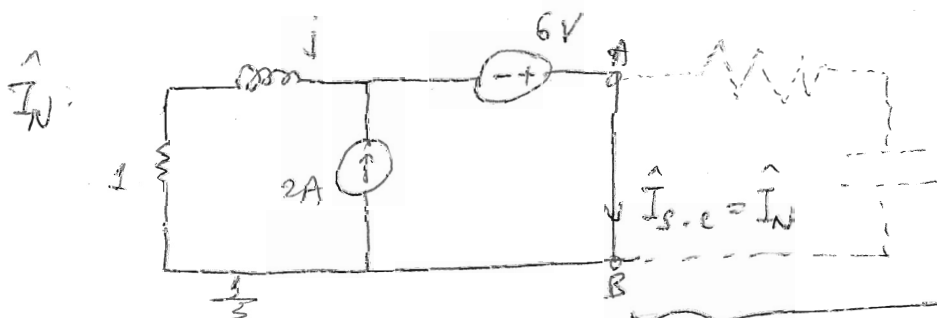Current division: $\hat{I}_0 = \hat{I}_N \frac{\hat{Z}_{th}}{1\Omega + \hat{Z}_{th}} = \hat{I}_N \frac{1}{2}$



not part of circuit as A & B are short-circuited.

Source exchange:

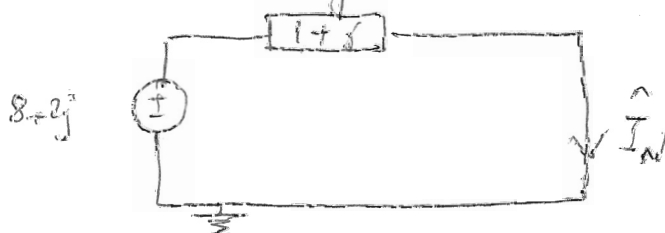

$$\hat{I}_N = \frac{8+2j}{1+j} \text{ A}$$

1


2

B

A

B

A

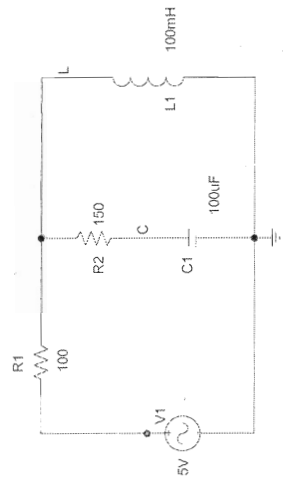

Page Size A

OrCAD, Inc.
13221 S W 68th Parkway, Suite 200
Beaverton, OR 97223
(503) 671-9500 (800) 671-9505

Page 1 of 1

January 1, 2000

Revision

1

2


27

* C:\Temp\232s07\7p76.sch

Date/Time run: 02/20/07 13:57:23

Temperature: 27.0

(A) 7p76.dat (active)

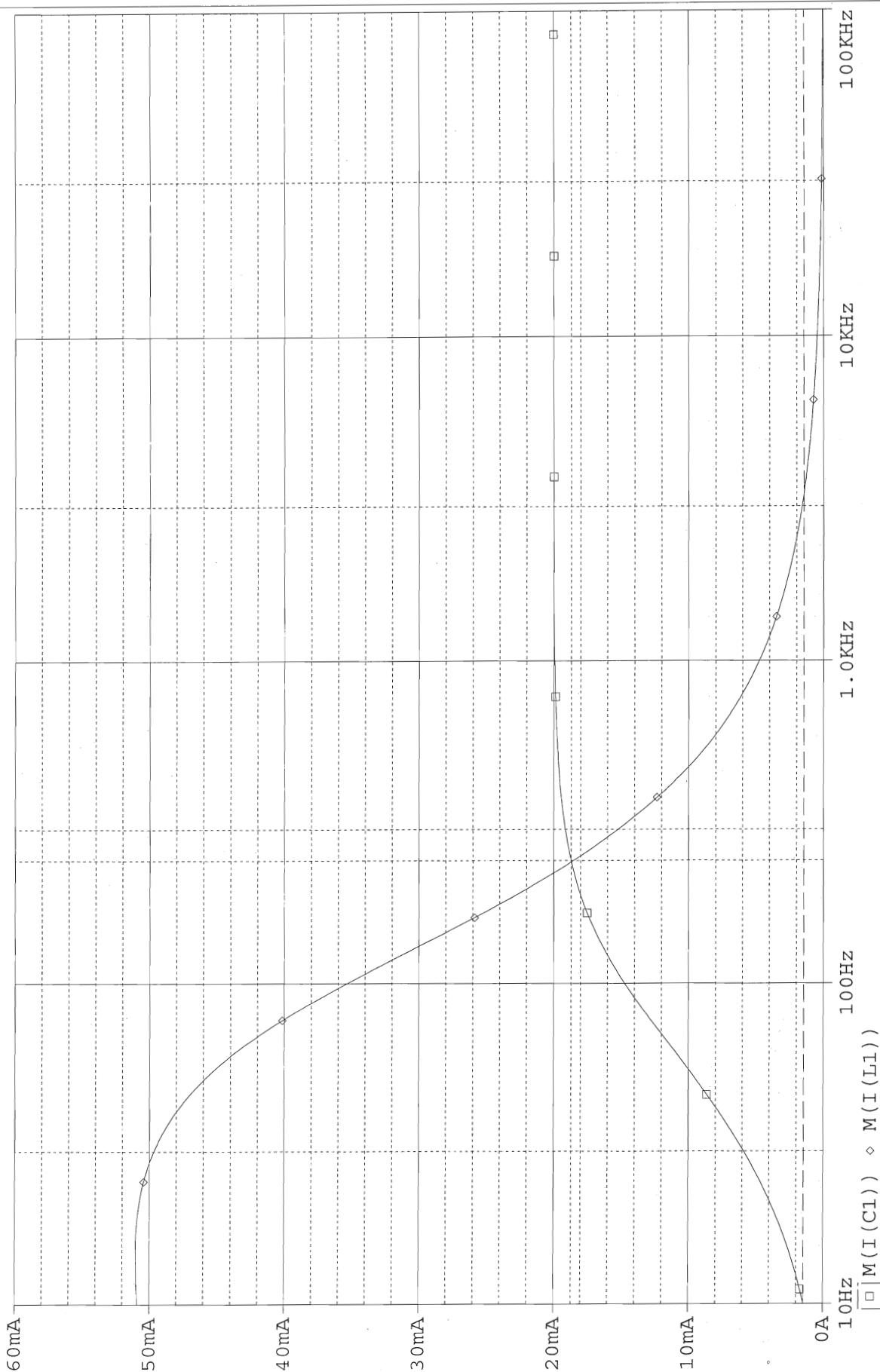

Frequency

A1: (241.481, 18.703m) A2: (10.000, 1.4620m) DIFF(A): (231.481, 17.241m)

Date: February 20, 2007

Page 1


Time: 14:03:00

* C:\Temp\232s07\7p76.sch

Date/Time run: 02/20/07 14:07:00

Temperature: 27.0

(A) 7p76.dat (active)

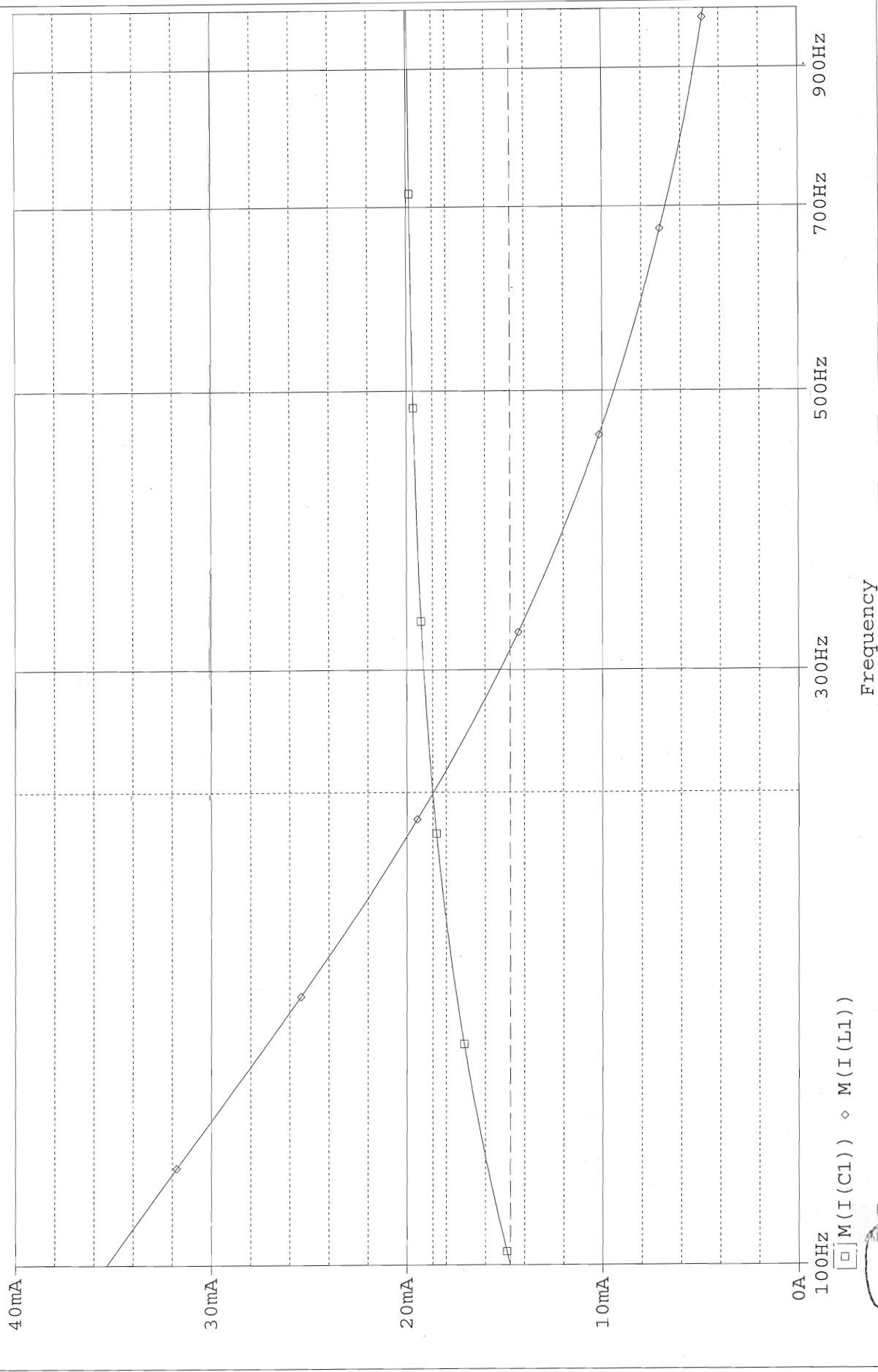

A1: (239.524, 18.684m) A2: (100.000, 14.724m) DIFF(A): (139.524, 3.9603m)


Date: February 20, 2007

Page 1


Time: 14:07:50

7.70


30

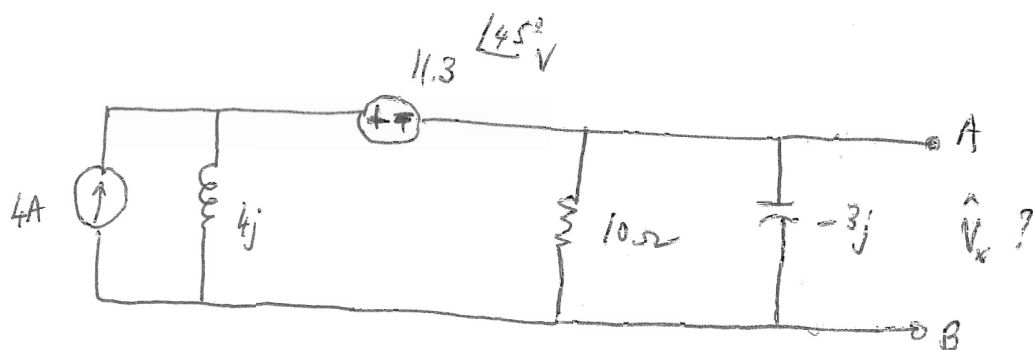

Norton's equivalent:

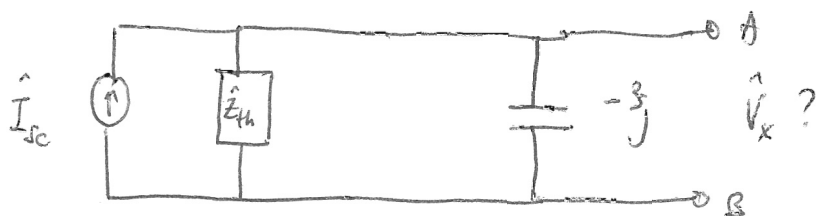


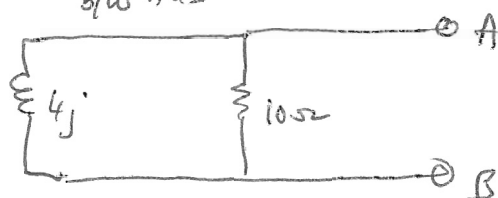$\hat{Z}_{th} = (\text{OC element, OC } I_{\text{source}}, \text{ SC } V_{\text{source}}) :$
b/w A & B




$$\rightarrow \hat{Z}_{th} = \frac{10 \times 4j}{10 + 4j}$$

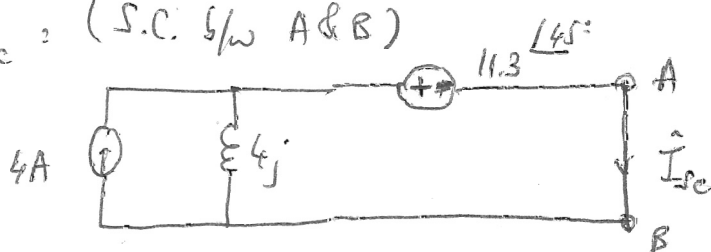$\hat{I}_{sc} : (\text{S.C. b/w A \& B})$



source exchange

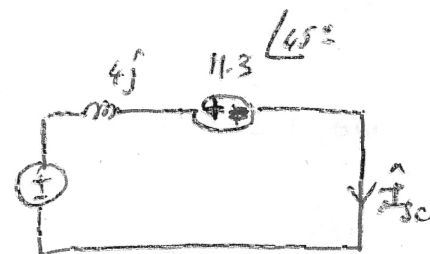

$$\hat{I}_{sc} = \frac{16j - 11.3(\cos 45 + j \sin 45)}{4j} = \frac{16j - 7.99 - j7.99}{4j}$$

$$= \frac{-7.99 + 8.01j}{4j} = \frac{11.3 \angle 135^\circ}{4 \angle 90^\circ} = 2.825 \angle 45^\circ \text{ A}$$

7.970 pspice

(32)

2

1


B

A

B

A

This is a current source pointing up

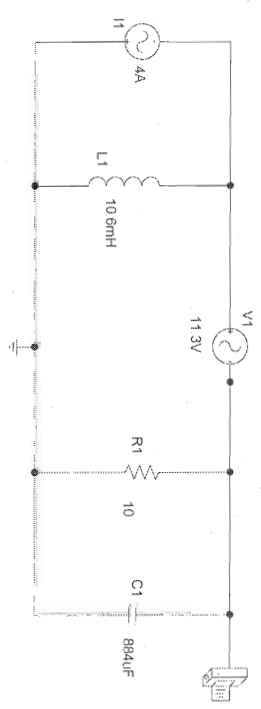

$$\rightarrow \hat{V}_x = 21.7 \angle 5.2^\circ \text{ V}$$

2

1

ORCAD, Inc.
13221 S.W. 68th Parkway, Suite 200
Beaverton, OR 97223
(503) 671-9500 (800) 671-9505

Page Size: A

Revision: January 1, 2000

Page 1 of 1