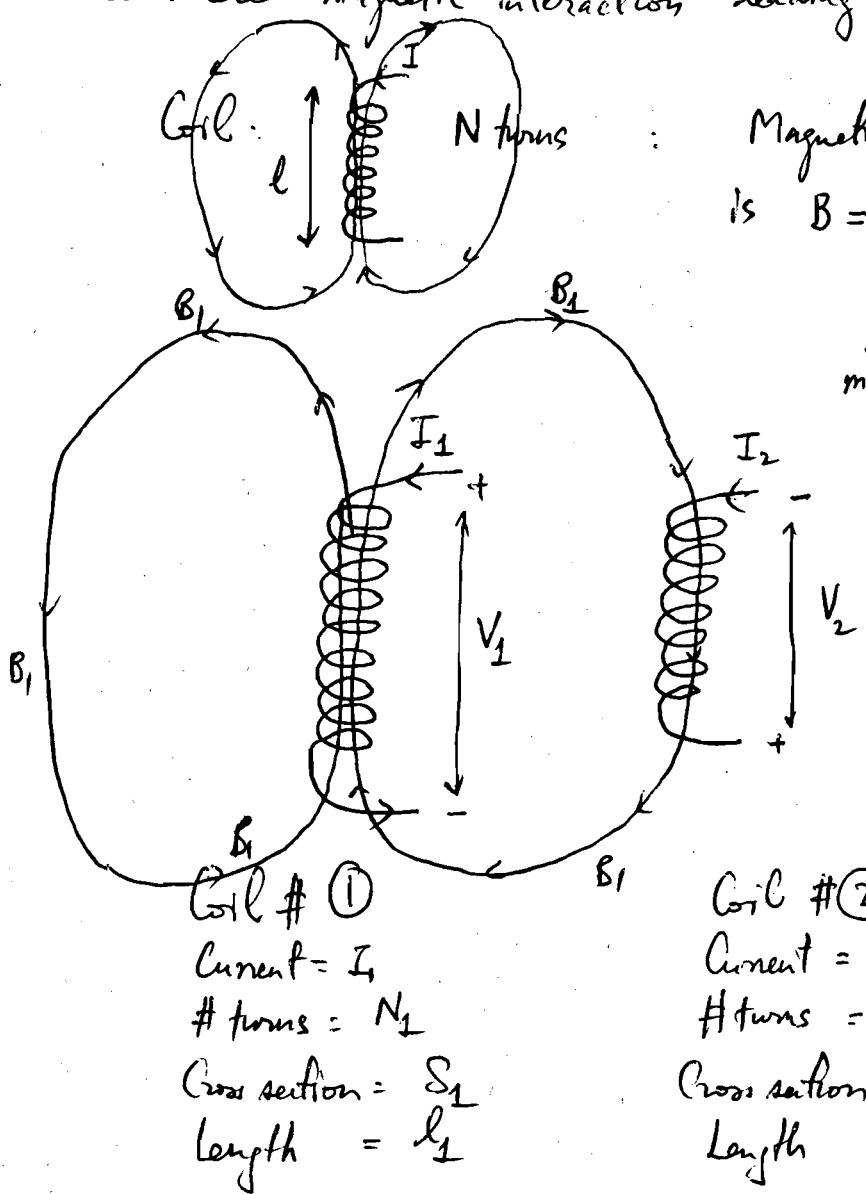


Magnetically Coupled Circuits

(7^{ed}: Ch. 8 or 8th ed: ch 10)

So far inductance L is actually self-inductance: we haven't considered magnetic interaction leading to mutual inductance.



Magnetic field created by this coil is $B = \mu \frac{N}{l} I$

μ magnetic permeability (μ_0 in vacuum)

$\frac{N}{l}$ # turns per unit length

B_1 : magnetic field due to coil #1 interacts with coil #2 and vice versa!

- | | |
|-----------------------|-----------------------|
| Coil # ① | Coil # ② |
| Current = I_1 | Current = I_2 |
| # turns = N_1 | # turns = N_2 |
| Cross section = S_1 | Cross section = S_2 |
| Length = l_1 | Length = l_2 |

Magnetic flux: $\Phi = \vec{B} \cdot \vec{S}$ (larger field and larger cross section $\rightarrow$ larger flux)

Faraday's law: induced e.m.f. = $\frac{d\Phi}{dt}$ coil not expanding

potential

$V = \frac{d\Phi}{dt} = \frac{d}{dt} (B \cdot S) \stackrel{\downarrow}{=} S \frac{dB}{dt} = S \frac{d(\mu n I)}{dt}$

$$V = \underbrace{S_{\text{un}}}_L \frac{dI}{dt} \quad \text{This is what we have been using so far.}$$

$$V_1 = L_1 \frac{dI_1}{dt} \quad \text{one coil, one current.}$$

→ Two coils, two currents I_1 & I_2 :

$$V_1 = L_1 \frac{dI_1}{dt} + \underbrace{\left(M \frac{dI_2}{dt} \right)}_{\text{mutual-inductance}}$$


self-inductance

due to magnetic interaction b/w the two coils.

$$\text{Similarly: } V_2 = L_2 \frac{dI_2}{dt} + \underbrace{\left(M \frac{dI_1}{dt} \right)}_{(M_{12} = M_{21})}$$


Conclusion: for our purposes of doing circuit analysis, the implication of including magnetic interaction is the consideration of one extra term with the correct sign: using the "dot convention"

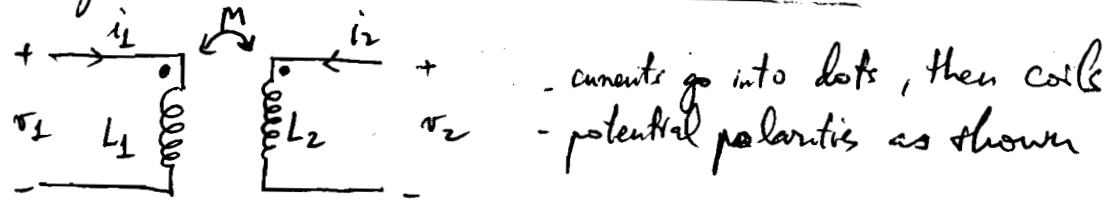Correct sign for the mutual inductance term (dot convention)




$$\left. \begin{aligned} v_1 &= L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 &= L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \end{aligned} \right\} \xrightarrow{\text{for phasors}} \begin{cases} \hat{V}_1 = j\omega L_1 \hat{I}_1 + j\omega M \hat{I}_2 \\ \hat{V}_2 = j\omega L_2 \hat{I}_2 + j\omega M \hat{I}_1 \end{cases}$$

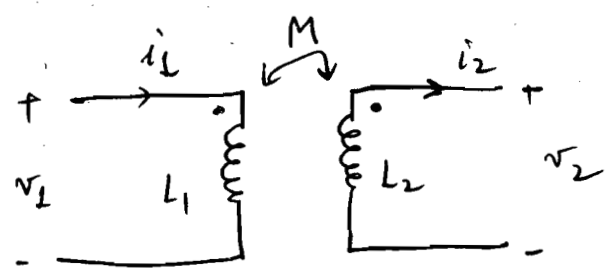$v \rightarrow \hat{V} e^{j\omega t}$
 $i \rightarrow \hat{I} e^{j\omega t}$




- one current goes into dot, then coil
- one current leaving dot
- polarities as shown
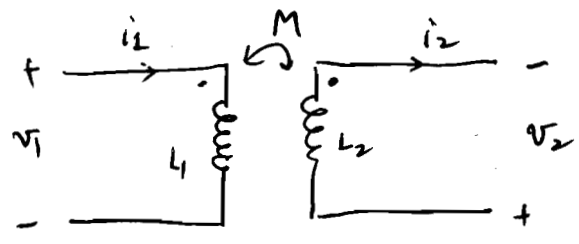
$$\left. \begin{aligned} v_1 &= L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} \\ v_2 &= -L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \end{aligned} \right\} \xrightarrow{\text{phasors}} \left\{ \begin{aligned} \hat{V}_1 &= j\omega L_1 \hat{I}_1 - j\omega M \hat{I}_2 \\ \hat{V}_2 &= -j\omega L_2 \hat{I}_2 + j\omega M \hat{I}_1 \end{aligned} \right.$$


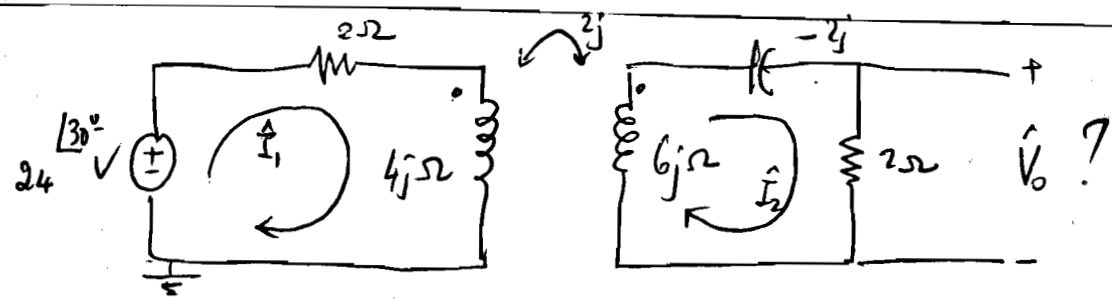
$$\left. \begin{aligned} v_1 &= L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} \\ v_2 &= L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} \end{aligned} \right\} \xrightarrow{\text{phasors}} \left\{ \begin{aligned} \hat{V}_1 &= j\omega L_1 \hat{I}_1 - M j\omega \hat{I}_2 \\ \hat{V}_2 &= j\omega L_2 \hat{I}_2 - M j\omega \hat{I}_1 \end{aligned} \right.$$




$$\left\{ \begin{aligned} \omega L_1 &= 4 \\ \omega L_2 &= 6 \\ \omega M &= 2 \\ \frac{1}{\omega C} &= 2 \end{aligned} \right.$$

Loop analysis:




$$1) \quad 24 \angle 30^\circ = 2 \hat{I}_1 + 4j \hat{I}_1 - \underbrace{2j \hat{I}_2}_{\text{New!!}}$$

$$2) \quad 0 = 6j \hat{I}_2 - \underbrace{2j \hat{I}_1}_{\text{New!!}} + (2 - 2j) \hat{I}_2$$


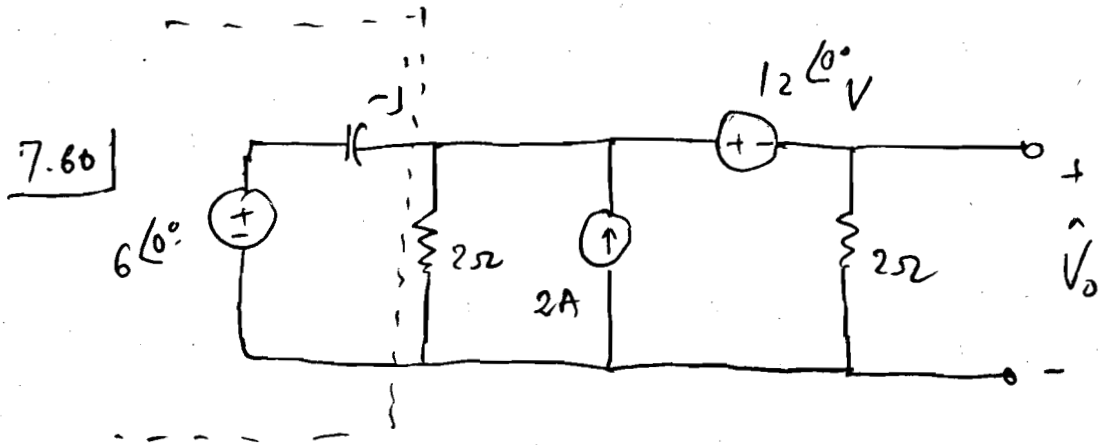
25% HW3 $\hat{V}_0 = 2 \hat{I}_2 = 5.36 \angle 3.43^\circ \text{ V}$
polar form



Source exchange

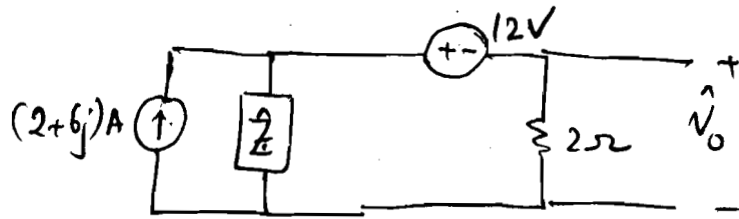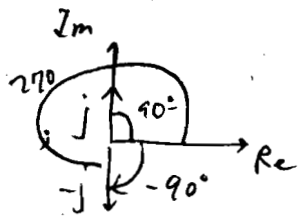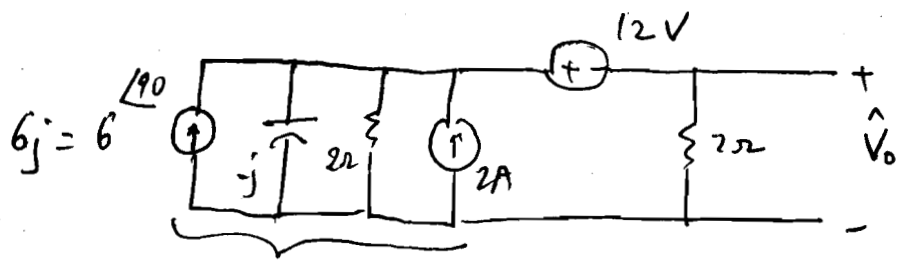
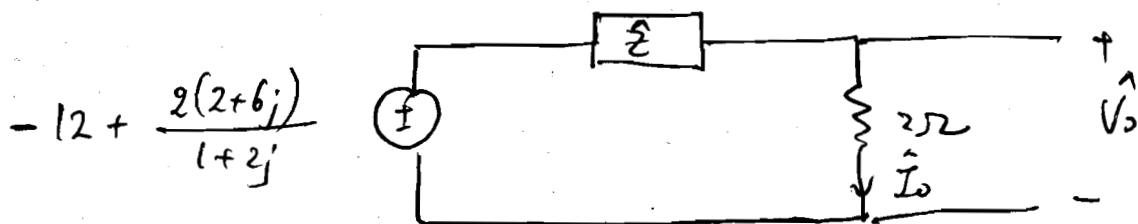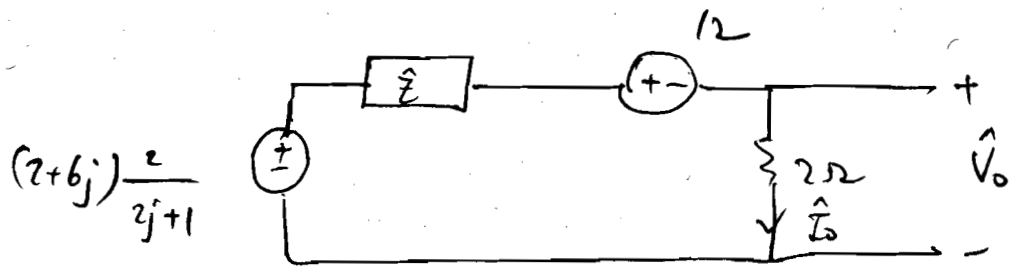
$$Z = 2 \parallel -j = \frac{-2j}{2-j} = \frac{2}{2j+1}$$




Voltage div:

$$\hat{V}_o = \left[-12 + \frac{2(2+6j)}{1+2j} \right] \frac{2}{2 + \frac{2}{2j+1}}$$


$$= \left[-12(1+2j) + 2(2+6j) \right] \frac{2}{2+4j+2}$$

$$\begin{aligned}\hat{V}_0 &= [-8 - 12j] \frac{2}{4(1+j)} \\ &= \frac{(-2 - 3j)^2}{1+j} = 2 \angle 180^\circ \frac{(2+3j)}{1+j} \\ &= 2 \angle 180^\circ \frac{\sqrt{13} \angle (\tan^{-1} \frac{3}{2})}{\sqrt{2} \angle 45^\circ} = 5.1 \angle 191.3^\circ \checkmark\end{aligned}$$

7.63

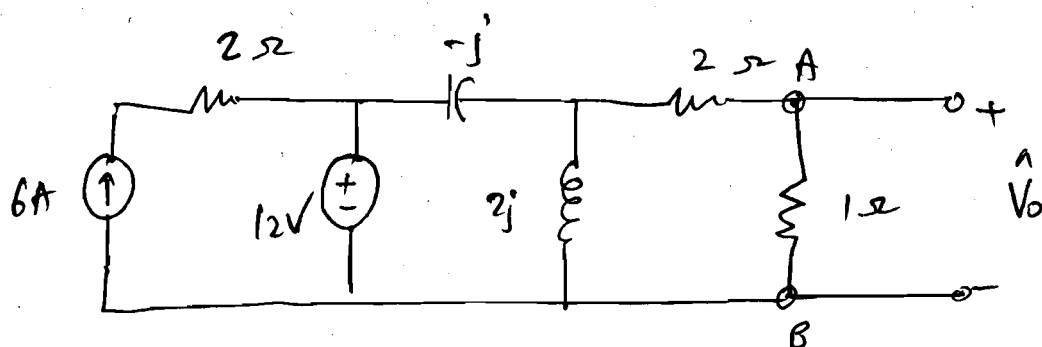


use
Thvenin's
equiv. circuit.

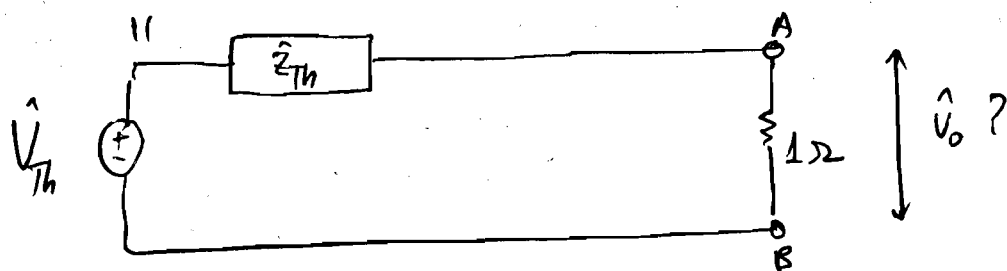



$$\hat{V}_{Th} = \hat{V}_{o.c. \text{ b/w } A \& B}$$

$$\hat{Z}_{Th} = \hat{Z}_{\text{b/w } A \& B, \text{ no sources.}}$$

$$\hat{V}_{oc} =$$

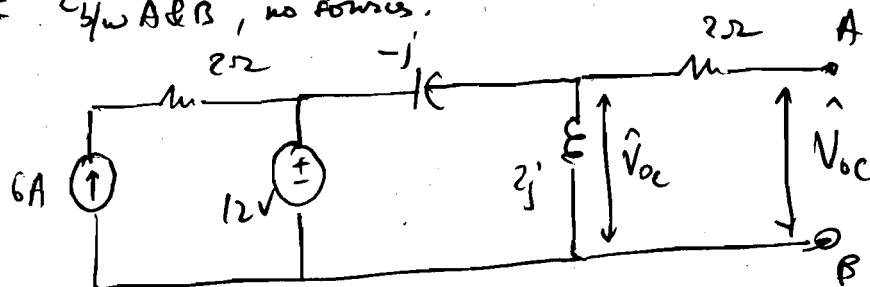


Superposition:

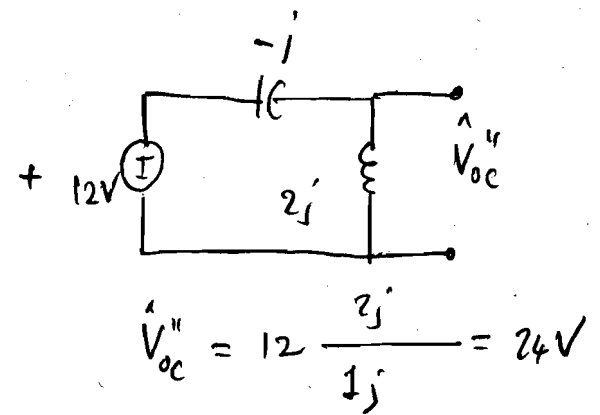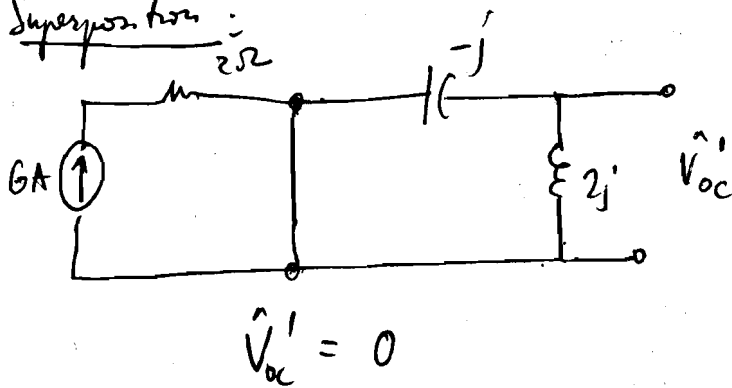


$\hat{V}_{th} = 24V$

$\hat{z}_{th} =$

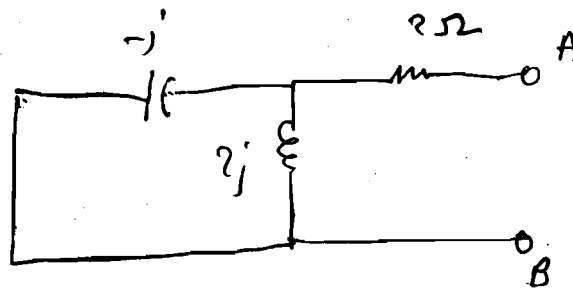
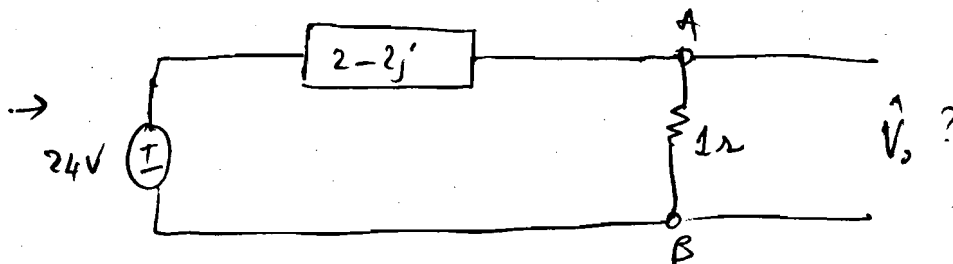
$$\begin{aligned}\hat{z}_{th} &= 2 + \frac{2j'(-j')}{2j' - j'} \\ &= 2 + \frac{2}{j'} \\ &= 2 - 2j'\end{aligned}$$




$$\hat{V}_o = 24 \frac{1}{3 - 2j'} = \frac{24}{\sqrt{13} \angle -\tan^{-1} \frac{2}{3}} = \frac{24}{\sqrt{13}} \angle \tan^{-1} \frac{2}{3}$$

$= 6.66 \angle 33.69^\circ V$

(solution is good).


Mutual inductance (Cont.)

Energy analysis:

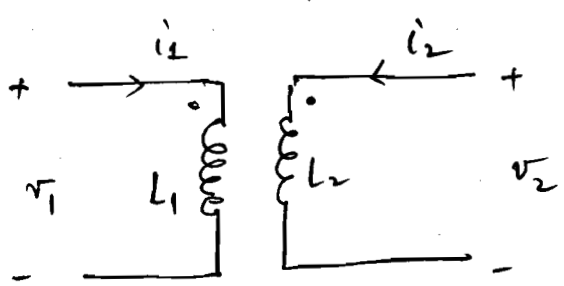

Power $P =$ energy per unit time $\rightarrow \mathcal{E} = \int P(t) dt$

We look at two time intervals:

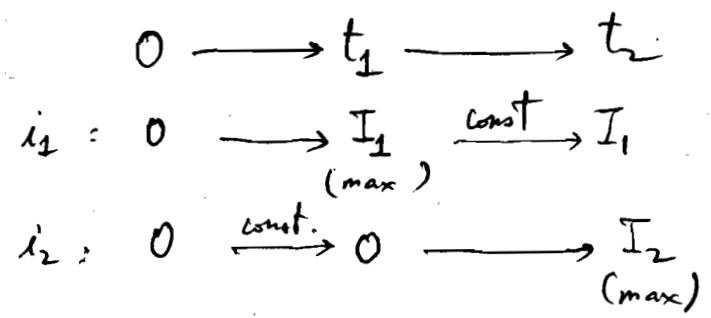

At any time: $P(t) = i_1 v_1 + i_2 v_2$

$$= i_1(t) \left[L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \right] + i_2(t) \left[L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \right]$$

$$\mathcal{E} = \underbrace{\int_0^{t_1} P(t) dt}_{i_2 \text{ const } = 0} + \underbrace{\int_{t_1}^{t_2} P(t) dt}_{i_1 = I_1 \text{ const}} = \int_0^{t_1} L_1 i_2 \frac{di_1}{dt} dt + \int_{t_1}^{t_2} \left(I_1 M \frac{di_2}{dt} + L_2 i_2 \frac{di_2}{dt} \right) dt$$

$$\mathcal{E} = L_1 \int_0^{I_1} i_2 di_1 + M I_1 \int_0^{I_2} di_2 + L_2 \int_0^{I_2} i_2 di_2$$


$$= L_1 \frac{I_1^2}{2} + M I_1 I_2 + L_2 \frac{I_2^2}{2} \rightarrow \mathcal{E} = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + (M I_1 I_2)$$

mutual magnetic interaction

Ideal Transformer:

Two coils + iron core

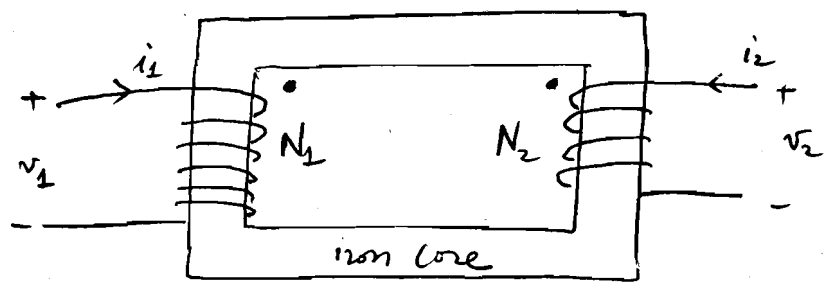To change the voltage using different number of turns



coils $\left\{ \begin{array}{l} v_1 = N_1 \frac{d\Phi_1}{dt} \\ v_2 = N_2 \frac{d\Phi_2}{dt} \end{array} \right.$

$\Phi_1 = \Phi_2$ (iron core)

$\frac{v_1}{v_2} = \frac{N_1}{N_2}$


Faraday's Law: change of magnetic flux w.r.t. time $\rightarrow$ induced voltage.

Iron core: similar to a short-circuit for electrons (electric fields), the iron core channels all magnetic field lines $\rightarrow$ can find the flux: $\Phi_1 = \Phi_2$

Ampere's Law:

$$\oint_{\text{loop}} \vec{H} \cdot d\vec{l} = i_{\text{(enclosed by loop)}} = i_1 N_1 + i_2 N_2$$

↓
amperian loop.

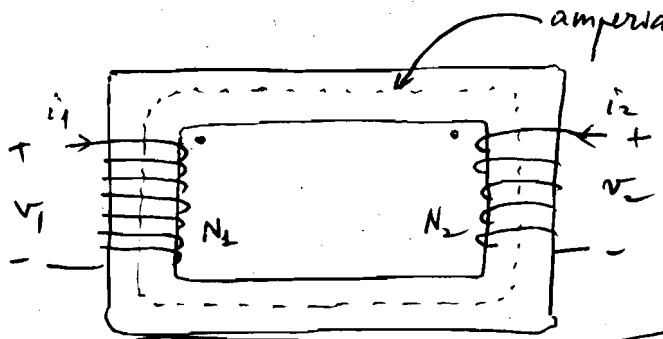


$$\vec{B} = \mu \vec{H}$$

$\downarrow$ m. induction $\downarrow$ m. permeability
 $\downarrow$ 1 for vacuum
 $\downarrow$ ∞ for iron core

$\frac{i_1}{i_2} = - \frac{N_2}{N_1}$


If $\mu = \infty \Rightarrow$ for a finite value for B H has to be 0 $\rightarrow 0 = i_1 N_1 + i_2 N_2$

Ideal transformer in a circuit

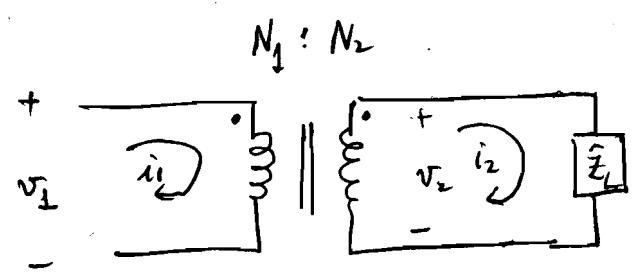

$$\begin{cases} \frac{v_1}{v_2} = \frac{N_1}{N_2} \\ \frac{i_1}{i_2} = \frac{N_2}{N_1} \end{cases}$$


HW 4: due 3/13

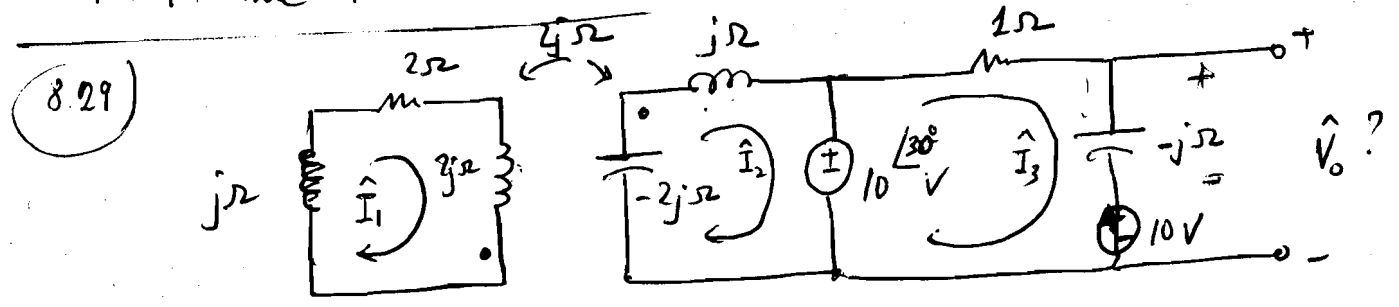

$$\begin{aligned} 1) & 3j\hat{I}_1 + 2\hat{I}_1 - \hat{I}_2 2j = 0 \\ 2) & -j\hat{I}_2 + 10\angle 30^\circ - 2j\hat{I}_1 = 0 \\ 3) & -10\angle 30^\circ + \hat{I}_3(1-j) + 10 = 0 \rightarrow \hat{I}_3 = \frac{-10 + 10\angle 30^\circ}{1-j} = 3.66\angle 150^\circ \end{aligned}$$

$\hat{V}_0 = 3.66\angle 150^\circ - 10\angle 90^\circ = 8.75\angle 158^\circ$

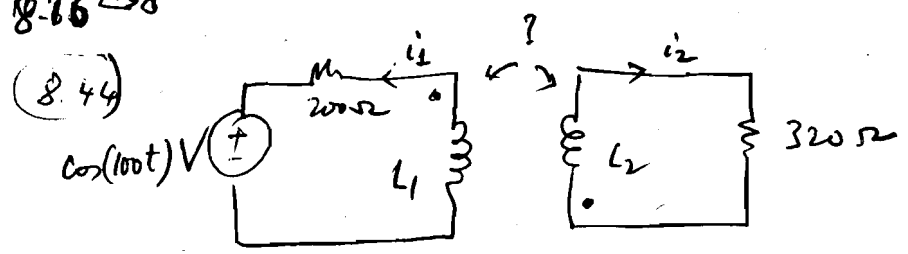$\rightarrow \hat{V}_0 = \hat{I}_3(-j) + 10 \rightarrow (\text{Eliminate } \hat{I}_1 \text{ \& } \hat{I}_2)$



$$K^2 = \frac{M^2}{L_1 L_2} \text{ : coupling coeff.}$$

$K = 0.8; L_1 = L_2 = 4H$

Then solve for $\hat{I}_2 =$