
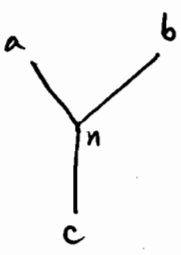
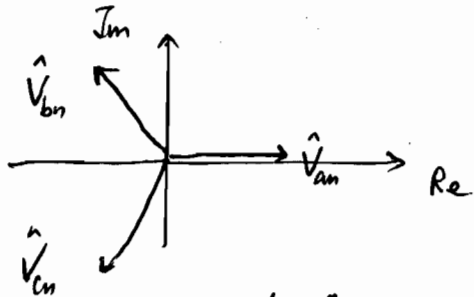


* acb balanced three-phase circuit:

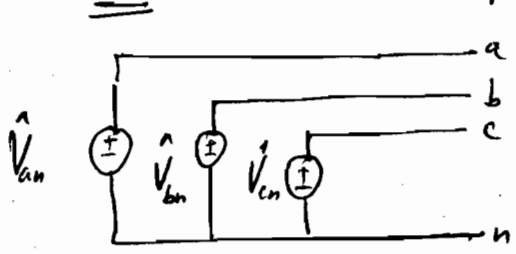


$$\begin{aligned} \hat{V}_{an} &= V_p \angle 0^\circ \\ \hat{V}_{bn} &= V_p \angle 120^\circ \\ \hat{V}_{cn} &= V_p \angle 240^\circ \end{aligned}$$

Y



$$\begin{aligned} \hat{V}_{ab} &= V_p \sqrt{3} \angle -30^\circ \\ \hat{V}_{bc} &= V_p \sqrt{3} \angle 90^\circ \\ \hat{V}_{ca} &= V_p \sqrt{3} \angle 210^\circ \end{aligned}$$

Δ

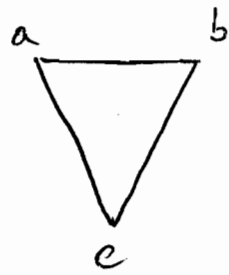


$$\begin{cases} \text{Magnitude}_\Delta = \text{magnitude}_Y \times \sqrt{3} \\ \text{Angle}_\Delta = \text{angle}_Y - 30^\circ \end{cases}$$

Now: abb balanced three-phase circuit:

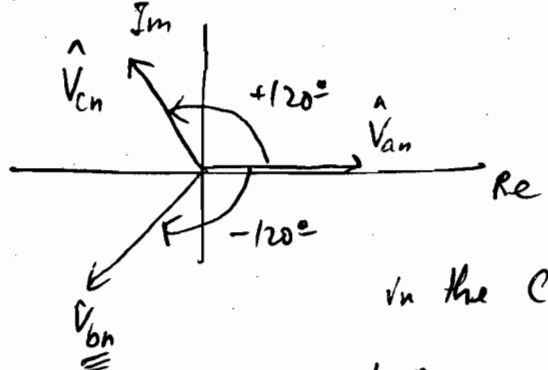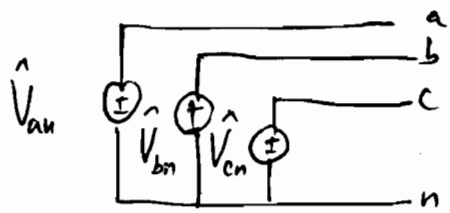

in the CW direction.

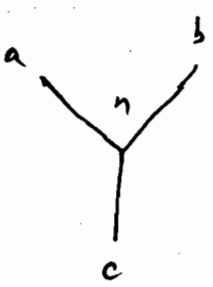


$$\begin{aligned} \hat{V}_{an} &= V_p \angle 0^\circ \\ \hat{V}_{bn} &= V_p \angle -120^\circ \\ \hat{V}_{cn} &= V_p \angle 120^\circ \end{aligned}$$

Y

$$\begin{aligned} \hat{V}_{ab} &= V_p \sqrt{3} \angle 30^\circ \\ \hat{V}_{bc} &= V_p \sqrt{3} \angle -90^\circ \\ \hat{V}_{ca} &= V_p \sqrt{3} \angle 150^\circ \end{aligned}$$


Δ

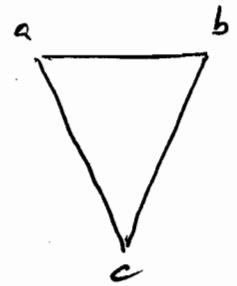

$$\begin{cases} \text{magnitude}_\Delta = \text{magnitude}_Y \sqrt{3} \\ \text{angle}_\Delta = \text{angle}_Y + 30^\circ \end{cases}$$

$$\begin{aligned}\hat{V}_{ab} &= V_p - V_p \angle -120^\circ = [\hat{V}_{ac}]_{acb} = -[\hat{V}_{ca}]_{acb} \\ &= -V_p \sqrt{3} \angle 210^\circ = V_p \sqrt{3} \angle 30^\circ \\ \hat{V}_{bc} &= V_p \angle -120^\circ - V_p \angle 120^\circ = (\hat{V}_{cn} - \hat{V}_{an})_{acb} = (-\hat{V}_{bc})_{acb} \\ &= -V_p \sqrt{3} \angle 90^\circ = V_p \sqrt{3} \angle -90^\circ \\ \hat{V}_{ca} &= V_p \angle 120^\circ - V_p \\ &= (\hat{V}_{bn} - \hat{V}_{an})_{acb} = -(\hat{V}_{ab})_{acb} = -V_p \sqrt{3} \angle -30^\circ \\ &= V_p \sqrt{3} \angle -210^\circ = V_p \sqrt{3} \angle 150^\circ\end{aligned}$$

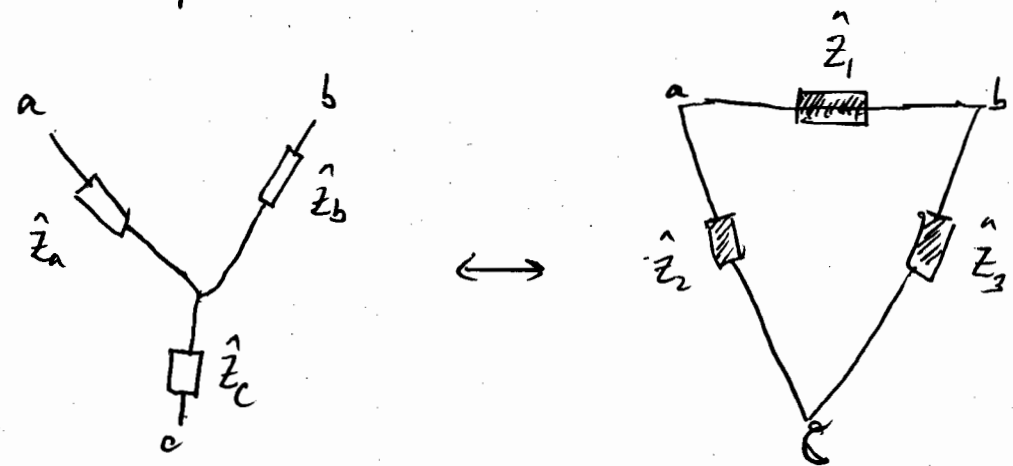We have seen the source transformation b/w γ & Δ .
The load transformation:



- ① $\underbrace{\hat{Z}_a + \hat{Z}_b}_Y = \text{total b/w a \& b} = \underbrace{\hat{Z}_1 \parallel (\hat{Z}_2 + \hat{Z}_3)}_\Delta$
- ② $\hat{Z}_a + \hat{Z}_c = \text{total b/w a \& c} = \hat{Z}_2 \parallel (\hat{Z}_1 + \hat{Z}_3)$
- ③ $\hat{Z}_b + \hat{Z}_c = \text{total b/w b \& c} = \hat{Z}_3 \parallel (\hat{Z}_1 + \hat{Z}_2)$

$$\textcircled{1} \quad \hat{z}_a + \hat{z}_b = \frac{\hat{z}_1 (\hat{z}_2 + \hat{z}_3)}{\hat{z}_1 + \hat{z}_2 + \hat{z}_3}$$

$$\textcircled{2} \quad \hat{z}_a + \hat{z}_c = \frac{\hat{z}_2 (\hat{z}_1 + \hat{z}_3)}{\hat{z}_1 + \hat{z}_2 + \hat{z}_3}$$

$$\textcircled{3} \quad \hat{z}_b + \hat{z}_c = \frac{\hat{z}_3 (\hat{z}_1 + \hat{z}_2)}{\hat{z}_1 + \hat{z}_2 + \hat{z}_3}$$

$$\textcircled{2} - \textcircled{3} \quad \hat{z}_a - \hat{z}_b = \frac{\hat{z}_1 \hat{z}_2 - \hat{z}_1 \hat{z}_3}{\hat{z}_1 + \hat{z}_2 + \hat{z}_3}$$

$$\textcircled{1} + \textcircled{2} - \textcircled{3} \quad \hat{z}_a = \frac{\hat{z}_1 \hat{z}_2}{\hat{z}_1 + \hat{z}_2 + \hat{z}_3}$$

$$\boxed{\hat{z}_a = \frac{\hat{z}_1 \hat{z}_2}{\hat{z}_1 + \hat{z}_2 + \hat{z}_3}}$$

$$\boxed{\hat{z}_b = \frac{\hat{z}_1 \hat{z}_3}{\hat{z}_1 + \hat{z}_2 + \hat{z}_3}}$$


$$\textcircled{3} - \textcircled{2} + \textcircled{1} = 2\hat{z}_b =$$

$$\frac{\hat{z}_1 \hat{z}_3 - \hat{z}_1 \hat{z}_2 + \hat{z}_1 \hat{z}_2 + \hat{z}_1 \hat{z}_3}{\hat{z}_1 + \hat{z}_2 + \hat{z}_3}$$

$$\boxed{\hat{z}_c = \frac{\hat{z}_2 \hat{z}_3}{\hat{z}_1 + \hat{z}_2 + \hat{z}_3}}$$

$$\textcircled{3} + \textcircled{2} + \textcircled{1}$$

Load transformation :

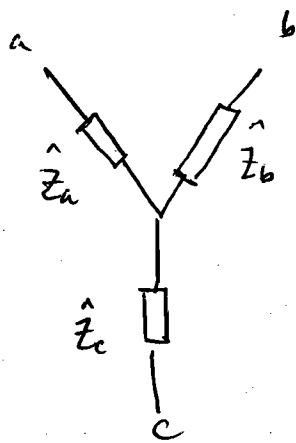

$$\hat{Z}_a = \frac{\hat{Z}_1 \hat{Z}_2}{\hat{Z}_1 + \hat{Z}_2 + \hat{Z}_3}$$


$$\hat{Z}_b = \frac{\hat{Z}_1 \hat{Z}_3}{\hat{Z}_1 + \hat{Z}_2 + \hat{Z}_3}$$

$$\hat{Z}_c = \frac{\hat{Z}_2 \hat{Z}_3}{\hat{Z}_1 + \hat{Z}_2 + \hat{Z}_3}$$

$$\hat{Z}_1 = \frac{\hat{Z}_a \hat{Z}_b + \hat{Z}_b \hat{Z}_c + \hat{Z}_a \hat{Z}_c}{\hat{Z}_c}$$

$$\hat{Z}_2 = \frac{\text{same as above}}{\hat{Z}_b}$$
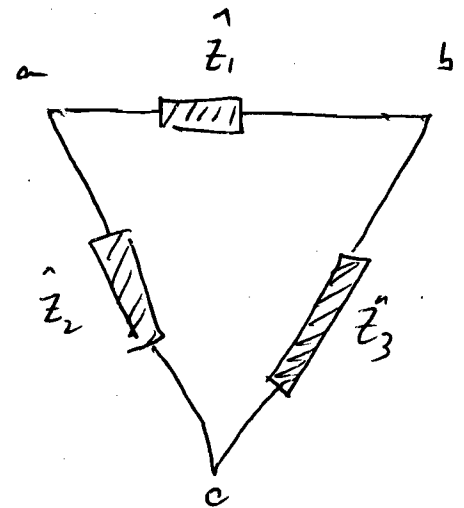
$$\hat{Z}_3 = \frac{\text{same as above}}{\hat{Z}_a}$$




For balanced loads : $\hat{Z}_a = \hat{Z}_b = \hat{Z}_c = \hat{Z}_Y \rightarrow$

$$\hat{Z}_\Delta = 3 \hat{Z}_Y$$

$$\text{or } \hat{Z}_Y = \frac{1}{3} \hat{Z}_\Delta$$

5 exam 2 points :

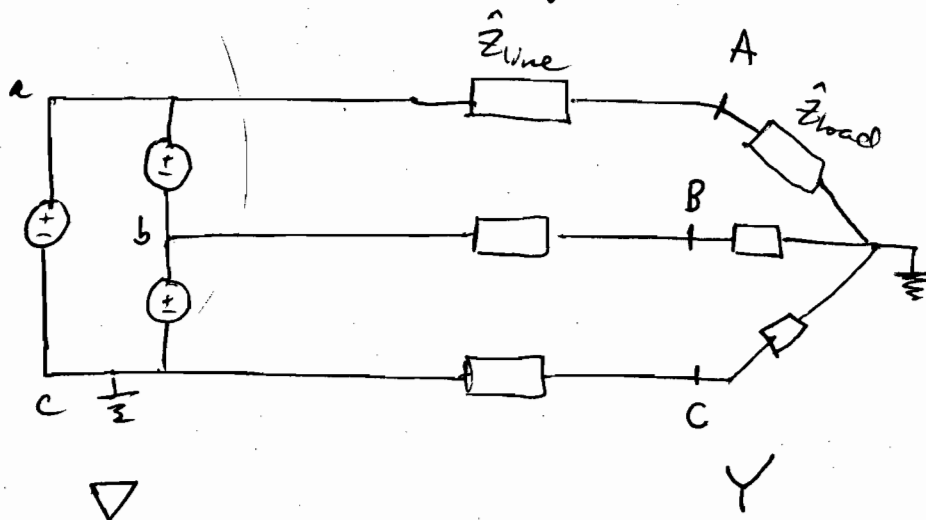Balanced three phase Δ -Y system (abc sequence)




$$\hat{Z}_{line} = 1 + 0.5j$$

$$\hat{Z}_{load} = 10 + 6j$$

$$\hat{I}_{aA} = 10 \angle -20^\circ \text{ A}_{RMS}$$

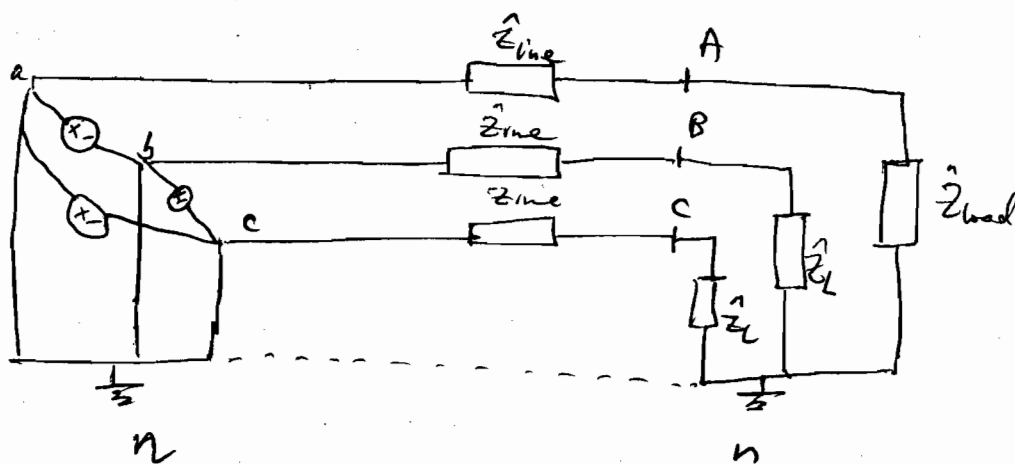$\hat{V}_{an}$? (Hint: 1st Redraw change source to Y)



9.49 (red) or 9.57 (8ed):

$$\hat{Z}_{\text{line}} = 0.08 + j0.25 \Omega$$

$$\hat{V}_L = 220 \angle 0^\circ \text{ V}_{\text{RMS}}$$

60 Hz

$$P_L = 12 \text{ kW}$$

$$P_{\text{line}} = 560 \text{ W}$$

Power factor angle at load? (inductive)

$$\text{pf}_L = \frac{P_L}{V_{\text{RMS}} I_{\text{RMS}}}$$

$$\text{Re}[\hat{S}_{\text{line}}] = \hat{I}_{\text{RMS}}^* \hat{V}_{\text{line}}$$

$$= I_{\text{RMS}}^2 \hat{Z}_{\text{line}} \rightarrow P_{\text{line}} = I_{\text{RMS}}^2 \text{Re}[\hat{Z}_{\text{line}}]$$

$$560 = I_{\text{RMS}}^2 \cdot 0.08$$

$$\text{pf}_L = \frac{12000}{220 \sqrt{\frac{560}{0.08}}} = \frac{12000}{220 \times 83.67} \approx 0.65 = \cos(\theta_v - \theta_i)$$

$$\theta_v - \theta_i = \cos^{-1} 0.65 = 49.3^\circ$$

$$\text{Inductive: } \begin{cases} \hat{Z} = j\omega L = \omega L \angle 90^\circ \\ \frac{\hat{V}}{\hat{I}} = \hat{Z} = \omega L \angle 90^\circ \end{cases}$$

$$\theta_v - \theta_i = 90^\circ$$

current lags voltage by $\frac{\pi}{2}$


$$\theta_v = 0 \rightarrow \theta_i = -49.3^\circ$$

10.19 (7ed):

Balanced 3 phase Y-Y $\hat{Z}_L = 20 + j12 \Omega$

Source abc: $\hat{V}_{an} = 120 \angle 0^\circ V_{RMS}$. If load voltage $\hat{V}_{AN} = 111.49 \angle -0.2^\circ V_{RMS}$

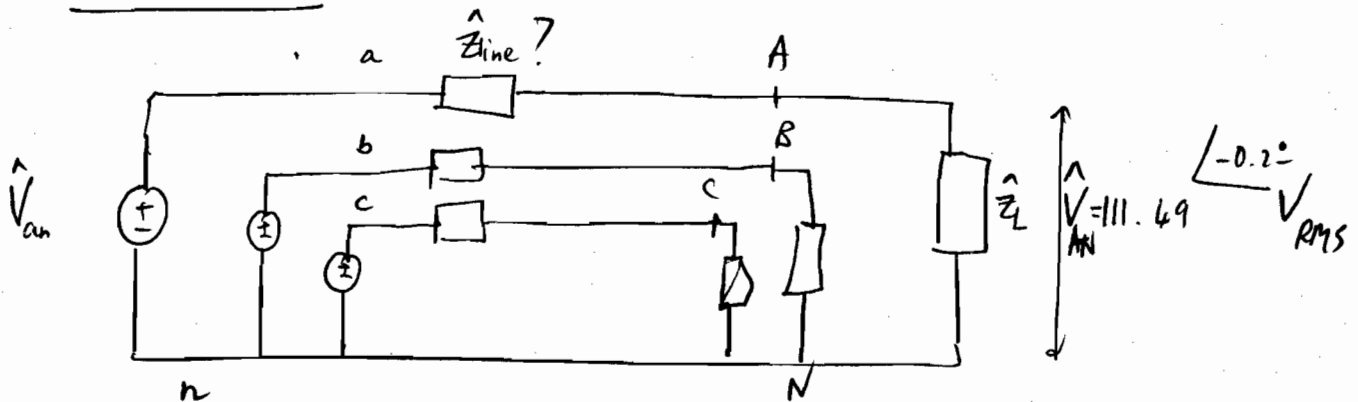Magnitude of $\hat{I}_{Line}$ if load is suddenly short-circuited.



$\hat{V}_{an} = 120 \angle 0^\circ V_{RMS}$ $\hat{V}_{bn} = 120 \angle 240^\circ V_{RMS}$; $\hat{V}_{cn} = 120 \angle 120^\circ V_{RMS}$.

Line current = $\hat{I}_{aA} = \frac{\hat{V}_{AN}}{\hat{Z}_L} = \frac{111.49 \angle -0.2^\circ}{20 + j12} = \frac{111.49 \angle -0.2^\circ}{\sqrt{544} \angle \tan^{-1} \frac{3}{5}}$

$= \frac{111.49 \angle -0.2^\circ}{23.32 \angle 30.96^\circ} = 4.78 \angle -31.16^\circ A_{RMS}$

$\hat{V}_{line} = \hat{V}_{AA} = \hat{V}_{an} - \hat{V}_{AN} = 120 \angle 0^\circ - 111.49 \angle -0.2^\circ$

$= 120 - 111.49 \cos(-0.2^\circ) + j111.49 \sin(0.2^\circ)$

$\hat{Z}_{line} = \frac{\hat{V}_{line}}{\hat{I}_{line}} = \frac{\sqrt{8.51^2 + 0.389^2} \angle \tan^{-1} \frac{0.389}{8.51}}{4.78 \angle -31.16^\circ} = \frac{8.52 \angle 2.617^\circ}{4.78 \angle -31.16^\circ} = 1.78 \angle 33.78^\circ \Omega$

→ Current in the line if the load is short-circuited is


$I_{line SC} = \frac{120}{1.78 \angle 33.78^\circ} = 67.5 \angle -33.78^\circ A_{RMS}$

Revisit the extra credit question:

Balanced, three-phase,


(abc)

Δ -Y system:

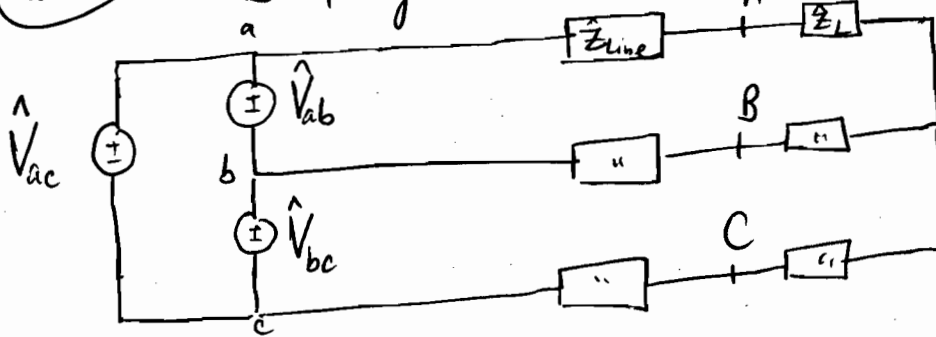

$$\hat{Z}_{line} = 1 + 0.5j ; \quad \hat{Z}_L = 10 + 6j ; \quad \hat{I}_{aA} = 10 \angle -20^\circ \text{ A}_{RMS}$$

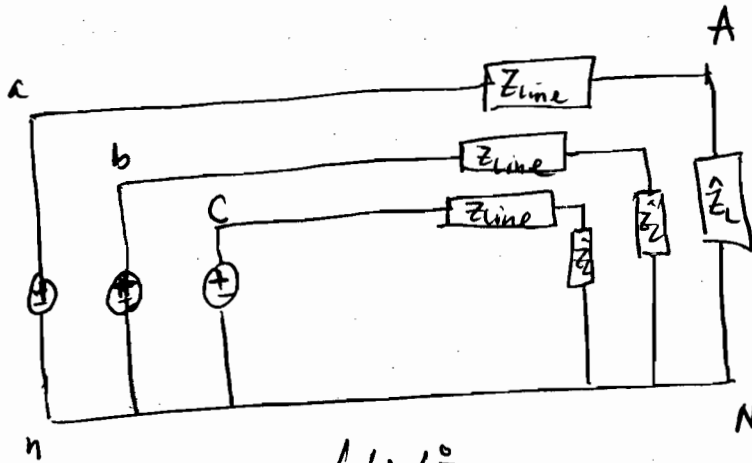$\hat{V}_{ab} = ?$ Convert source to a Y connection, find $\hat{V}_{an}$, then transform to $\hat{V}_{ab}$:




$$\begin{aligned} \hat{V}_{an} &= \hat{I}_{aA} (\hat{Z}_{line} + \hat{Z}_L) \\ &= 10 \angle -20^\circ \left(\sqrt{11^2 + 6.5^2} \angle \tan^{-1} \frac{6.5}{11} \right) \\ &= 127.7 \angle 10.6^\circ \text{ V}_{RMS} \end{aligned}$$

$$\begin{aligned} \hat{V}_{ab} &= 127.7 \sqrt{2} \angle 40.6^\circ \text{ V}_{RMS} \\ \hat{V}_{bc} &= 127.7 \sqrt{3} \angle 40.6^\circ - 120^\circ \\ \hat{V}_{ca} &= 127.7 \sqrt{3} \angle 40.6^\circ - 240^\circ \end{aligned}$$

$$\begin{aligned} \hat{V}_{bn} &= 127.7 \angle 10.6^\circ - 120^\circ \\ \hat{V}_{cn} &= 127.7 \angle 10.6^\circ - 240^\circ \end{aligned}$$

$$\hat{Z}_\Delta = 3\hat{Z}_Y = 30 + 18j \Omega$$


$\Delta - \Delta$:

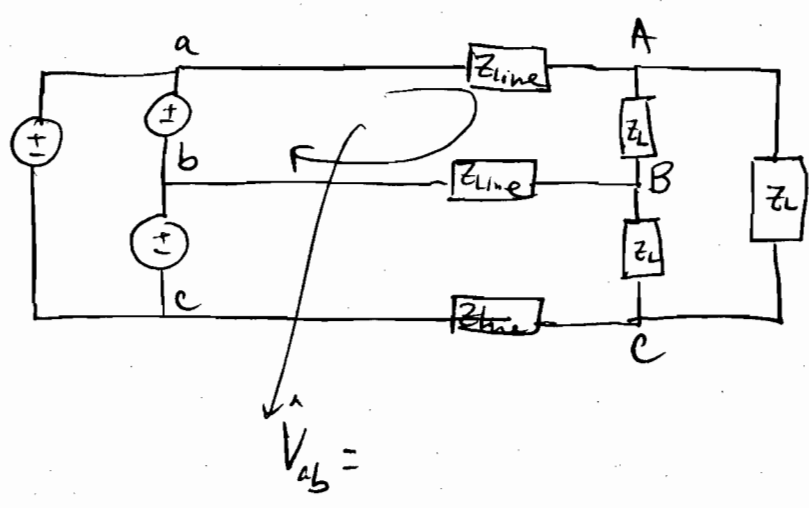

Variable Frequency Network =

$$\hat{Z}_R = R ; \quad \hat{Z}_L = j\omega L \quad \text{frequency dependence} ; \quad \hat{Z}_C = \frac{1}{j\omega C}$$

RLC circuit:

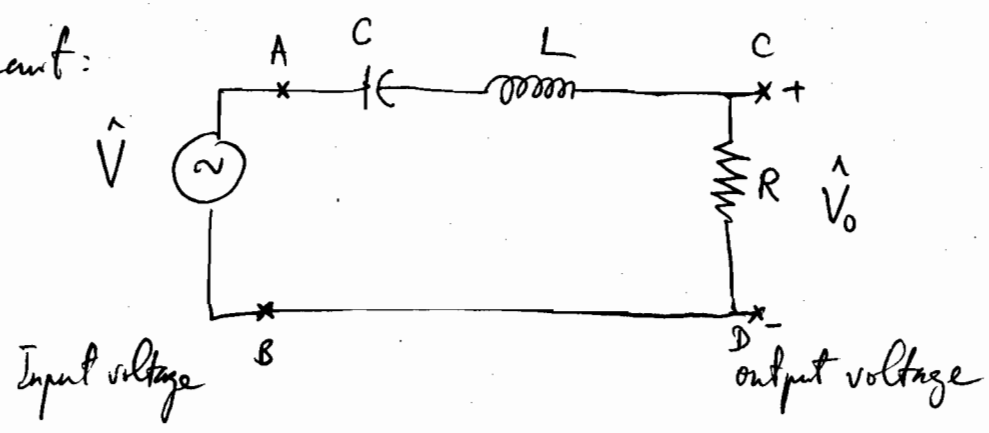

$$\text{Transfer function} \equiv \frac{\hat{V}_0}{\hat{V}} =$$

Voltage division: $\hat{V}_o = \hat{V} \frac{R}{\frac{1}{j\omega C} + j\omega L + R}$

→ Transfer function = $\frac{\hat{V}_o}{\hat{V}} = \frac{R}{\frac{1}{j\omega C} + j\omega L + R}$ a function of frequency

Conclusion: a circuit that contains some C or L in addition to R is a frequency-variable network

Characterization or classification of variable-frequency circuits:

Example (same circuit): $j\omega \rightarrow s$

$$\frac{\hat{V}_o}{\hat{V}} = \frac{R}{\frac{1}{sC} + sL + R}$$

→ Classification based on zeroes of the denominator,

$$= \frac{R \cdot \frac{s}{L}}{\left(\frac{1}{sC} + sL + R\right) \frac{s}{L}} = \frac{\frac{R}{L} s}{\frac{1}{LC} + s^2 + \frac{R}{L} s} \quad \left[\begin{array}{l} \text{Numerator} \\ \text{Denominator} \end{array} \right]$$

Zeros of the denominator: $s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$

$$x^2 + bx + c = (x - x_1)(x - x_2)$$

$$x_1 = \frac{-b + \sqrt{b^2 - 4c}}{2}$$

$$x_2 = \frac{-b - \sqrt{b^2 - 4c}}{2}$$

$$\rightarrow s = \frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}}{2}$$

$$\rightarrow s = -\frac{R}{2L} \pm \frac{1}{2L} \sqrt{R^2 - \frac{4L}{C}}$$

Case 1) $R^2 - \frac{4L}{C} = 0 \rightarrow$ Our transfer function (or circuit) has a pole of 2nd order at $(-\frac{R}{2L})$

$$\frac{\hat{V}_o}{\hat{V}} = \frac{\frac{R}{L} s}{\left(s + \frac{R}{2L}\right)^2}$$

$$2) \quad R^2 - \frac{4L}{C} > 0 \rightarrow S_{\pm} = -\frac{R}{2L} \pm \frac{1}{2L} \sqrt{R^2 - \frac{4L}{C}}$$

Our transfer function (or circuit) has two poles of 1st order at S_+ & S_-

$$\frac{\hat{V}_0}{\hat{V}} = \frac{\frac{R}{L} s}{(s - S_+)(s - S_-)} = \frac{\frac{R}{L} s}{\left(s + \frac{R}{2L} - \frac{1}{2L} \sqrt{R^2 - \frac{4L}{C}}\right) \left(s + \frac{R}{2L} + \frac{1}{2L} \sqrt{R^2 - \frac{4L}{C}}\right)}$$

$$3) \quad R^2 - \frac{4L}{C} < 0 \rightarrow S_{\pm} = -\frac{R}{2L} \pm \frac{j}{2L} \sqrt{\left|R^2 - \frac{4L}{C}\right|}$$

Our transfer function (or circuit) has two complex conjugate poles at S_+ & S_-

$$\frac{\hat{V}_0}{\hat{V}} = \frac{\frac{R}{L} s}{\left(s + \frac{R}{2L} - \frac{j}{2L} \sqrt{\left|R^2 - \frac{4L}{C}\right|}\right) \left(s + \frac{R}{2L} + \frac{j}{2L} \sqrt{\left|R^2 - \frac{4L}{C}\right|}\right)}$$

$$\text{Transfer function: } \hat{H}(s) = \frac{\hat{V}_0(s)}{\hat{V}(s)} \Rightarrow \hat{H}(j\omega) = \frac{\hat{V}_0(j\omega)}{\hat{V}(j\omega)}$$

Graphing: Bode plots $\left\{ \begin{array}{l} \text{Magnitude: } 20 \log_{10} |\hat{H}(j\omega)| \text{ w.r.t. } \log_{10} \omega \\ \text{Phase: } \angle \hat{H}(j\omega) \end{array} \right.$

frequency ω in log scale
w.r.t. freq ω in log scale

We now learn how to sketch Bode plots for a given circuit (or transfer function).

First, write the transfer function in a standard form:

$$\hat{H}(j\omega) = \frac{K_0 (j\omega)^{\pm N} (1 + j\omega\tau_1) [1 + 2\zeta_3 j\omega\tau_3 + (j\omega\tau_3)^2] \dots}{(1 + j\omega\tau_2) [1 + 2\zeta_6 j\omega\tau_6 + (j\omega\tau_6)^2] \dots}$$

τ_1 : "tau sub one"; ζ_3 : "xi sub three"

Example: previous transfer function: $\hat{H}(j\omega) = \frac{\hat{V}_o}{\hat{V}} = \frac{\frac{R}{L} j\omega}{(j\omega)^2 + j\omega \frac{R}{L} + \frac{1}{LC}}$

$$= \frac{RC j\omega}{(j\omega)^2 LC + j\omega RC + 1}$$

$$\left\{ \begin{array}{l} K_0 = RC \\ N = 1 \\ \tau_1 = 0 = \tau_2 \\ \tau_3 = 0 \\ \zeta_3 = 0 \\ \tau_6 = \sqrt{LC} \end{array} \right.$$

$$\left\{ \begin{array}{l} \tau_6 \Rightarrow 2\zeta_6 \tau_6 = RC \\ (\text{xi sub 6}) \quad \zeta_6 = \frac{RC}{2\sqrt{LC}} = \frac{R}{2} \sqrt{\frac{C}{L}} \end{array} \right.$$

Review: 1) $\left| \frac{\hat{z}_1 \cdot \hat{z}_2}{\hat{z}_3} \right| = \frac{|\hat{z}_1| \cdot |\hat{z}_2|}{|\hat{z}_3|}$



2) $\log_{10} \frac{|\hat{z}_1| \cdot |\hat{z}_2|}{|\hat{z}_3|} = \log |\hat{z}_1| + \log |\hat{z}_2| - \log |\hat{z}_3|$

Magnitude Bode plot: $20 \log_{10} |\hat{H}(j\omega)|$ versus ω in log scale

$$20 \log_{10} |\hat{H}(j\omega)| = 20 \log_{10} \frac{|k_0| |j\omega|^{\pm N} |1+j\omega\tau_1| |1+2\zeta_3 j\omega\tau_3 + (j\omega\tau_3)^2|}{|1+j\omega\tau_a| |1+2\zeta_b j\omega\tau_b + (j\omega\tau_b)^2|}$$

$$|j\omega| = \omega$$

$$= 20 \log_{10} |k_0| + 20 \log_{10} \omega^{\pm N} + 20 \log_{10} |1+j\omega\tau_1| + 20 \log_{10} |1+2\zeta_3 j\omega\tau_3 + (j\omega\tau_3)^2| \\ - 20 \log_{10} |1+j\omega\tau_a| - 20 \log_{10} |1+2\zeta_b j\omega\tau_b + (j\omega\tau_b)^2| - \dots$$

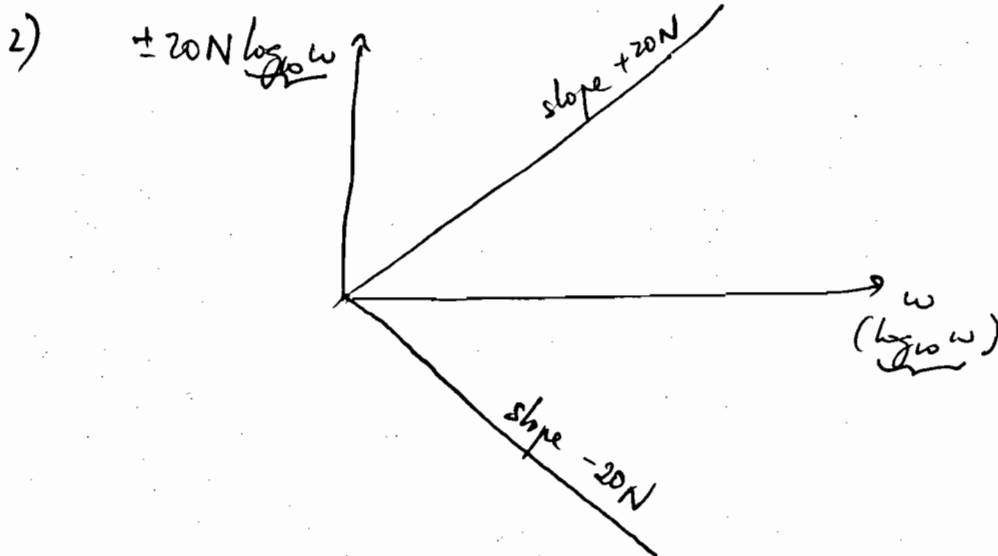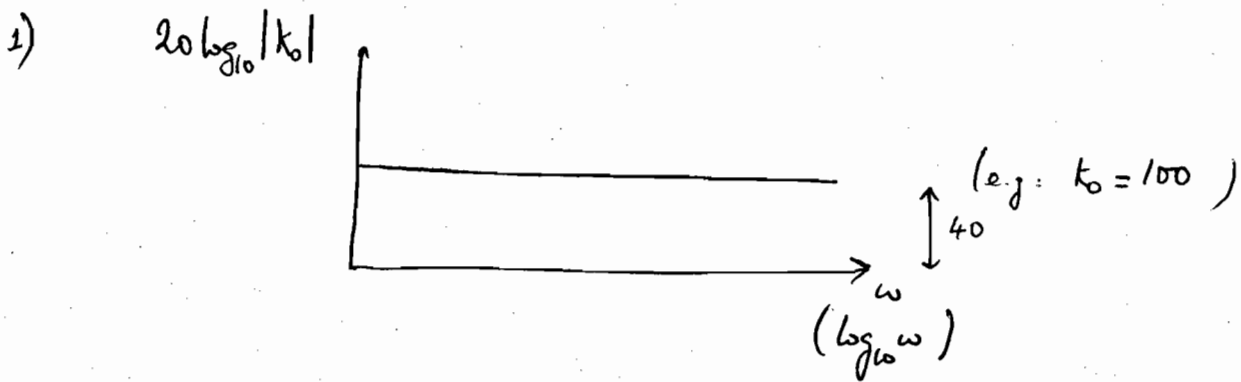

3) $20 \log_{10} |1 + j\omega\tau_1|$ use asymptotic analysis.

$$\omega \rightarrow 0 \text{ (low freq)} \rightarrow j\omega\tau_1 \ll 1 \rightarrow 20 \log_{10} |1| \approx 0$$

$$\omega \rightarrow \infty \text{ (high frequency)} \rightarrow j\omega\tau_1 \gg 1 \rightarrow 20 \log_{10} |j\omega\tau_1|$$

$$20 \log_{10} (\omega\tau_1) = 20 \log_{10} \omega + 20 \log_{10} \tau_1$$

$$\omega\tau_1 \approx 1 \text{ or } \omega_c = \frac{1}{\tau_1} \text{ (critical frequency)} \rightarrow 1 + j\omega\tau_1 \approx 1 + j$$

$$\rightarrow 20 \log_{10} \left| \frac{1+j}{\sqrt{2}} \right| = 10 \log_{10} 2 = 3 \text{ dB}$$

