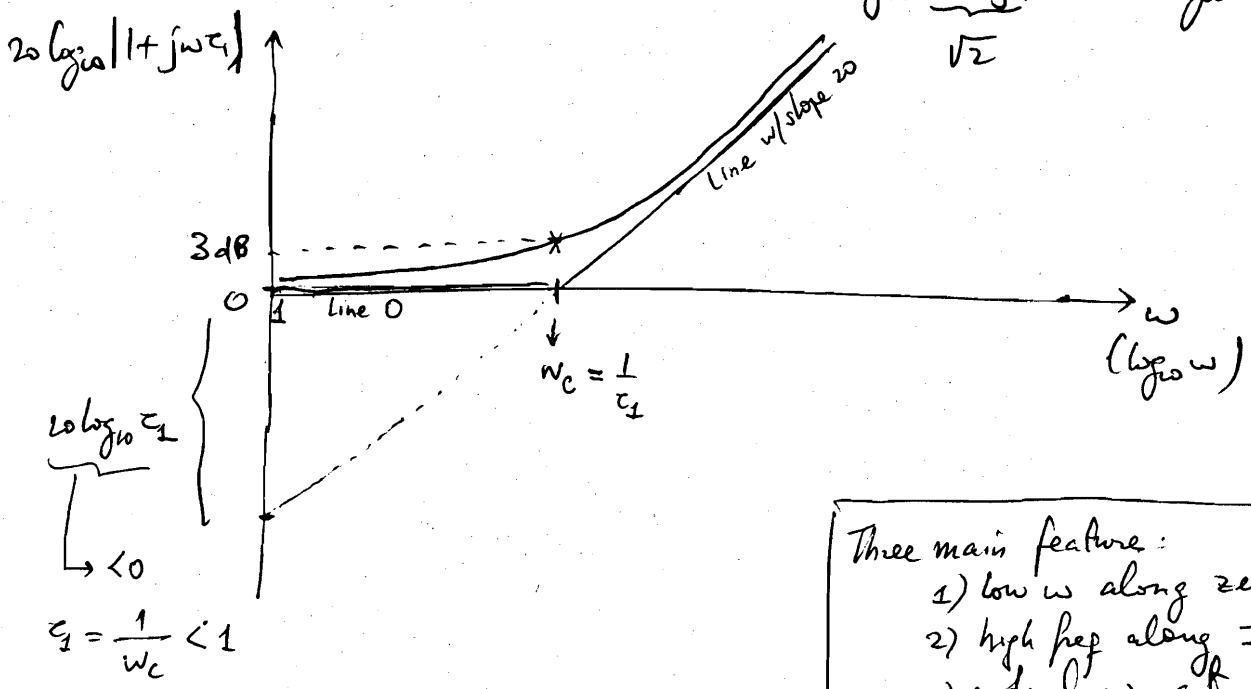


3) $20 \log_{10} |1 + j\omega\tau_1|$ use asymptotic analysis.


$\omega \rightarrow 0$ (low freq) $\rightarrow j\omega\tau_1 \ll 1 \rightarrow 20 \log_{10} |1| \approx 0$

$\omega \rightarrow \infty$ (high frequency) $\rightarrow j\omega\tau_1 \gg 1 \rightarrow 20 \log_{10} |j\omega\tau_1|$
 $20 \log_{10} (\omega\tau_1) = 20 \log_{10} \omega + 20 \log_{10} \tau_1$




$\omega\tau_1 \approx 1$ or $\omega_c = \frac{1}{\tau_1}$ (critical frequency) $\rightarrow 1 + j\omega\tau_1 \approx 1 + j$
 $\rightarrow 20 \log_{10} \frac{|1+j|}{\sqrt{2}} = 10 \log_{10} 2 = 3 \text{ dB}$





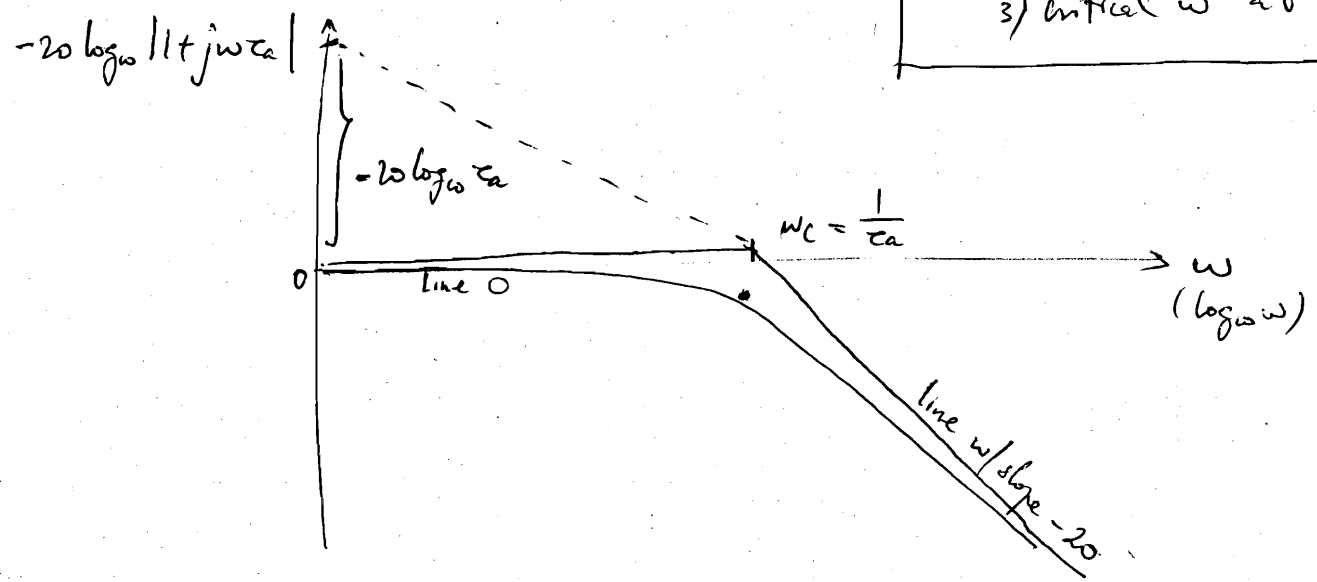Three main features:
 1) low ω along zero
 2) high freq along ± 20 slope
 3) critical ω at $\pm 3 \text{ dB}$



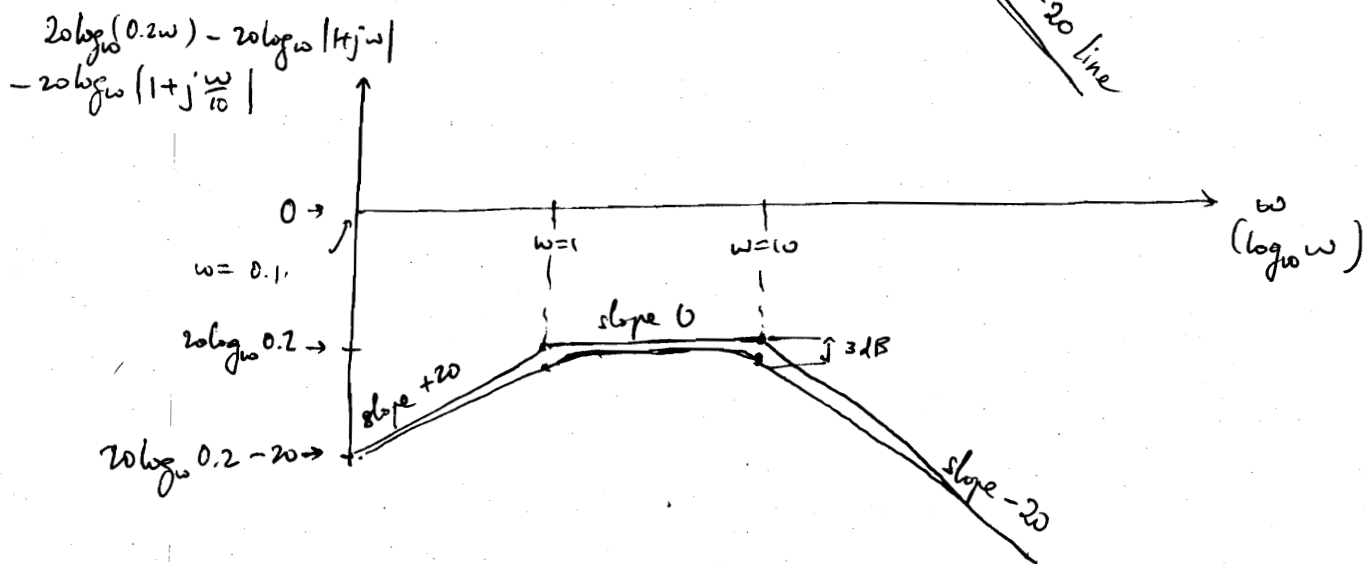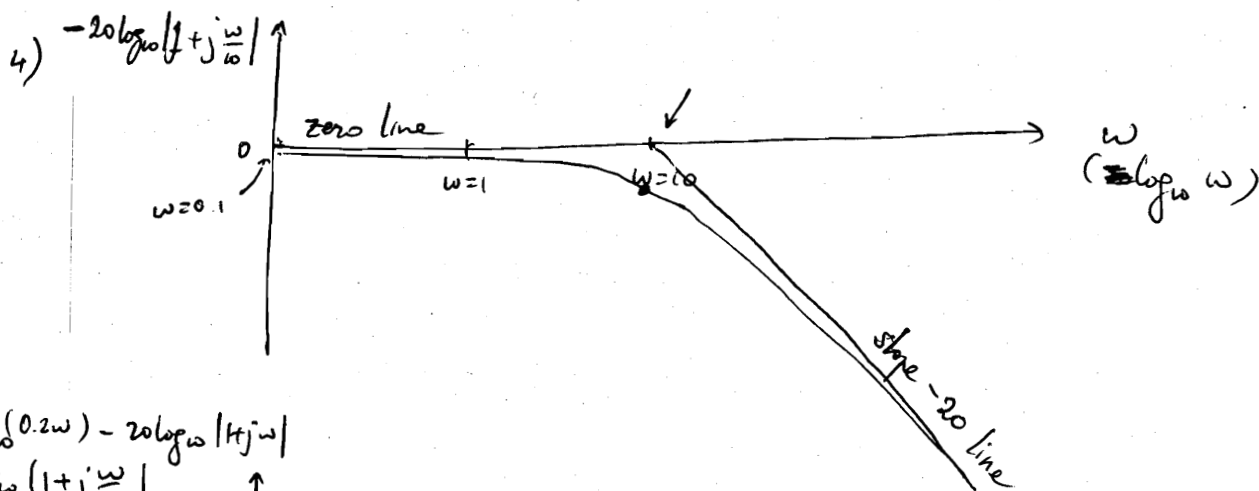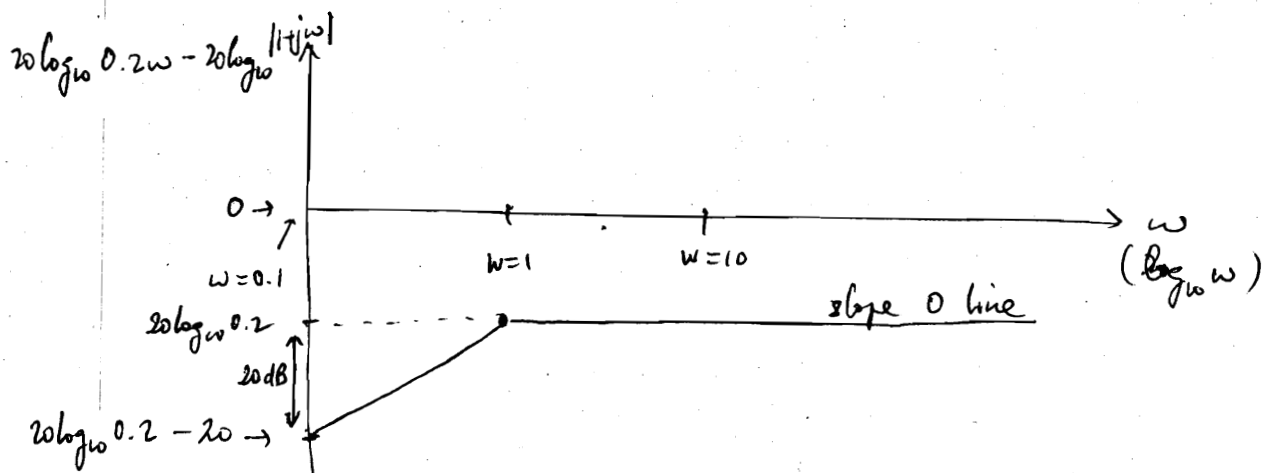Let's add these two plots together : best way to describe the result is to use pieces separated by the critical frequency ω_c
In this case : $\omega_c = 1$.



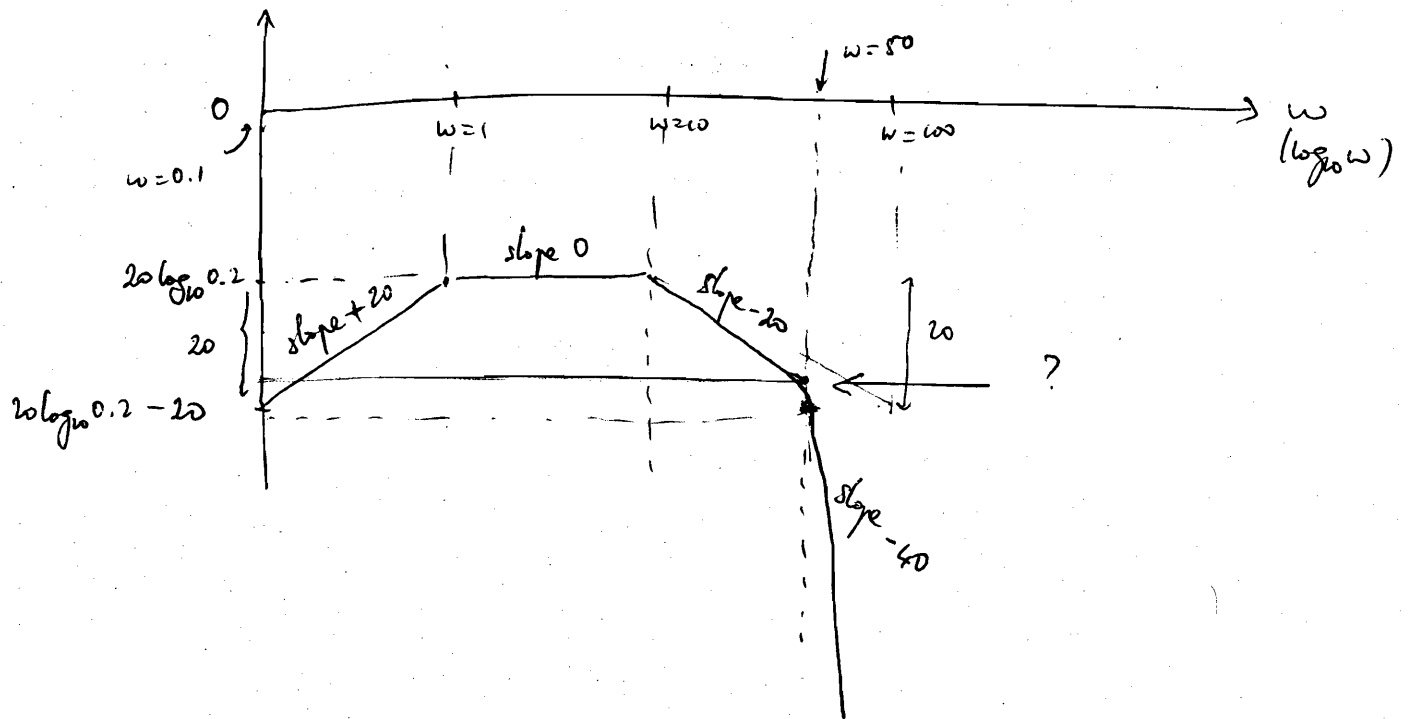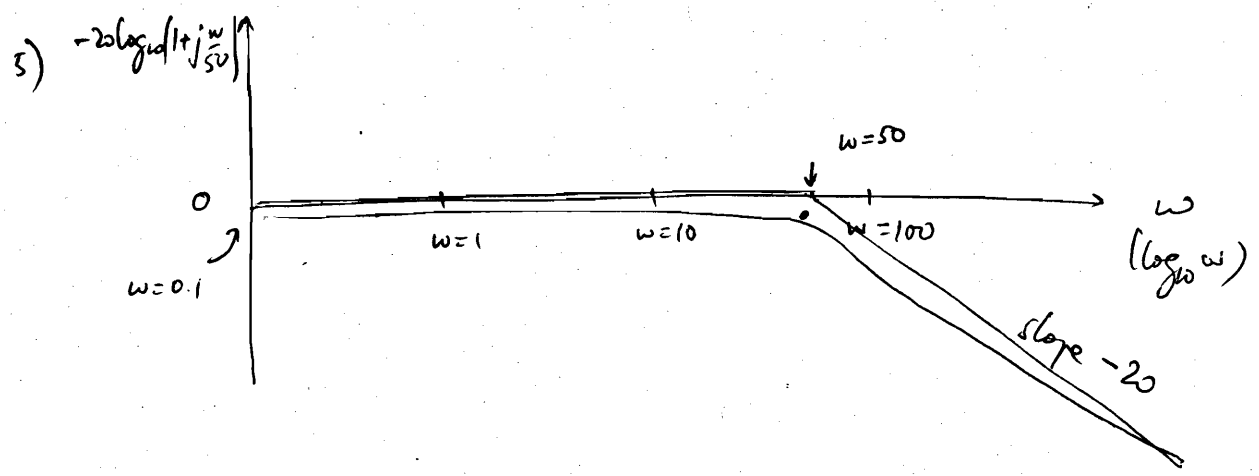

Example: plot this transfer function:


$$\hat{H}(j\omega) = \frac{100j\omega}{(1+j\omega)(10+j\omega)(50+j\omega)} \quad \text{Magnitude Bode Plot}$$

1) Write $\hat{H}$ in the standard format (always $(1 + \dots)$)

$$\hat{H}(j\omega) = \frac{\frac{100}{500} j\omega}{(1+j\omega)(1+j\frac{\omega}{10})(1+j\frac{\omega}{50})} \rightarrow |\hat{H}(j\omega)| = \frac{0.2\omega}{|1+j\omega||1+j\frac{\omega}{10}||1+j\frac{\omega}{50}|}$$

$$2) \quad 20 \log_{10} |\hat{H}| = \underbrace{20 \log_{10} 0.2}_{\text{constant}} + \underbrace{20 \log_{10} \omega}_{\text{linear}} - \underbrace{20 \log_{10} |1+j\omega|}_{1^{\text{st}} \text{ order}} - \underbrace{20 \log_{10} |1+j\frac{\omega}{10}|}_{1^{\text{st}} \text{ order}} - \underbrace{20 \log_{10} |1+j\frac{\omega}{50}|}_{1^{\text{st}} \text{ order}}$$

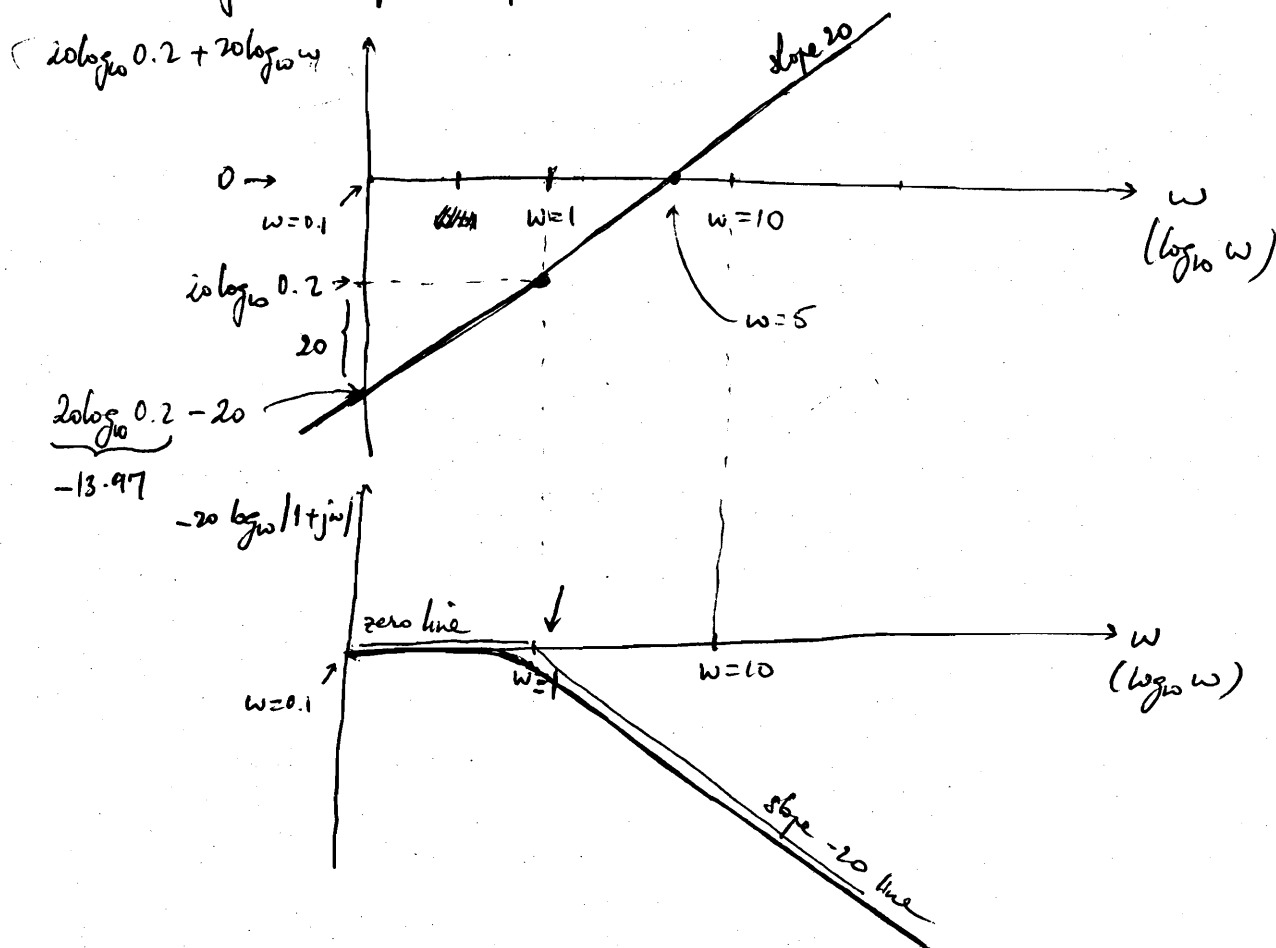3) The plot of LHS (Magnitude Bode Plot) would be the sum of the plots for each term in RHS:



Xcredit: 5 exam 3 points (20 min).

Sketch Bode plot for the following transfer function:

$$\hat{H}(j\omega) = \frac{10^5 j\omega (1 + j\frac{\omega}{10})}{(100 + j\omega)(1000 + j\omega)}$$

Bode Plot for quadratic poles and zeroes:

Standard form: $\pm 20 \log_{10} |1 + 2\zeta_b(j\omega\tau_b) + (j\omega\tau_b)^2|$

Asymptotic analysis:

1) Small ω or $\omega\tau_b \ll 1$

$$\pm 20 \log_{10} |1| \rightarrow \pm 20 \log_{10} 1 = 0$$

2) large ω or $\omega\tau_b \gg 1$

$$\pm 20 \log_{10} |1| \rightarrow \pm 20 \log_{10} |(j\omega\tau_b)^2|$$

$$= \pm 40 \log_{10}(\omega\tau_b)$$

$$= \pm 40 \log_{10} \omega \pm 40 \log_{10} \tau_b$$

line of slope ± 40


3) Critical frequency: $\omega_c = \frac{1}{\tau_b}$ ($\omega_c\tau_b = 1$)

$$\pm 20 \log_{10} |1| \rightarrow \pm 20 \log_{10} |1 + 2\zeta_b j - 1|$$

$$= \pm 20 \log_{10} (2\zeta_b)$$

ζ_b	$-20 \log_{10}(2\zeta_b)$
0.2	7.96
0.4	1.94
0.5	0
0.6	-1.58
0.8	-4.1

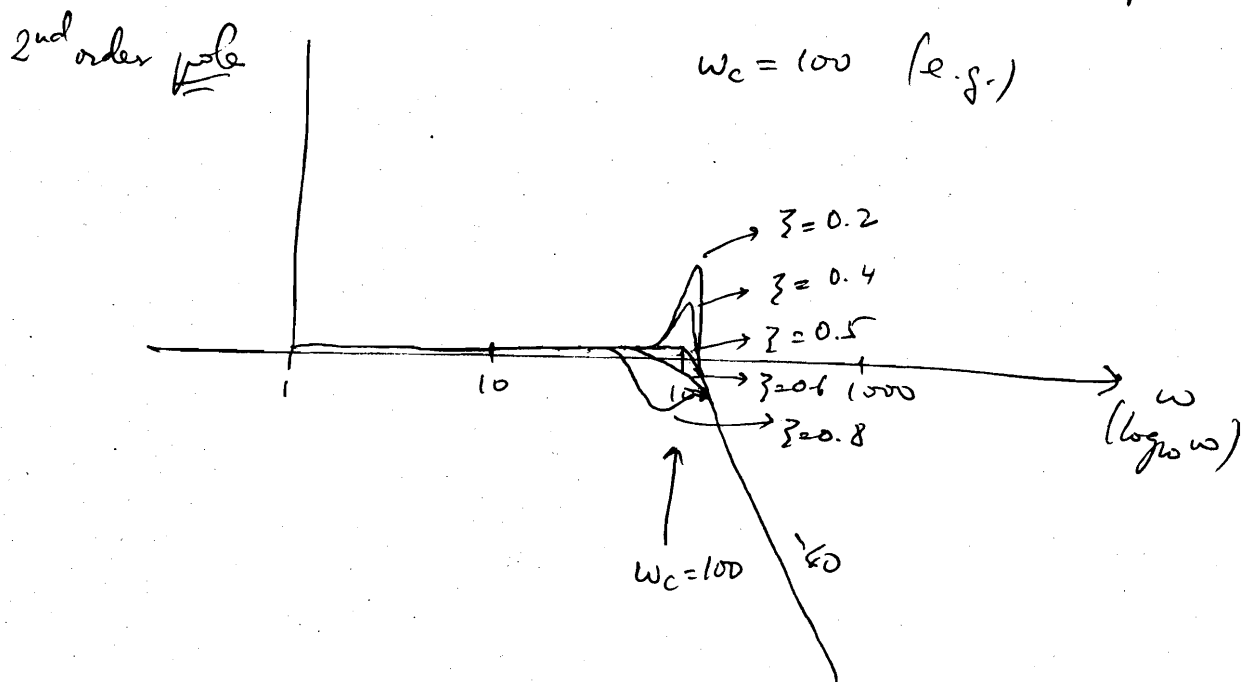This controls the change in slope
(this was -3dB for the 1st order pole)



Example:

$$\hat{H}(j\omega) = \frac{25j\omega}{(j\omega + 0.5) [(j\omega)^2 + 4j\omega + 100]}$$

standard form

$(1 + \dots)$

$$\downarrow = \frac{0.5j\omega}{(1 + j\frac{\omega}{0.5}) (1 + 4j\frac{\omega}{100} + (j\frac{\omega}{10})^2)}$$

$\omega_c = 0.5$

$\omega_c = 10$


$2\zeta = \frac{4}{10} \rightarrow \zeta = 0.2$ (big bump)

Two critical frequencies at 0.5 & 10 $\rightarrow$ 3 intervals on the freq. axis to look at:

$\rightarrow$ Before $\omega = 0.5$: $20 \log_{10} \omega + 20 \log_{10}(0.5)$
 $\downarrow$ slope 20 $\downarrow$ intercept w/ vertical axis (negative)

$\rightarrow$ Between $\omega = 0.5$ & $\omega = 10$: due to a pole at $\omega = 0.5$ with slope -20. $\rightarrow$ horizontal line.

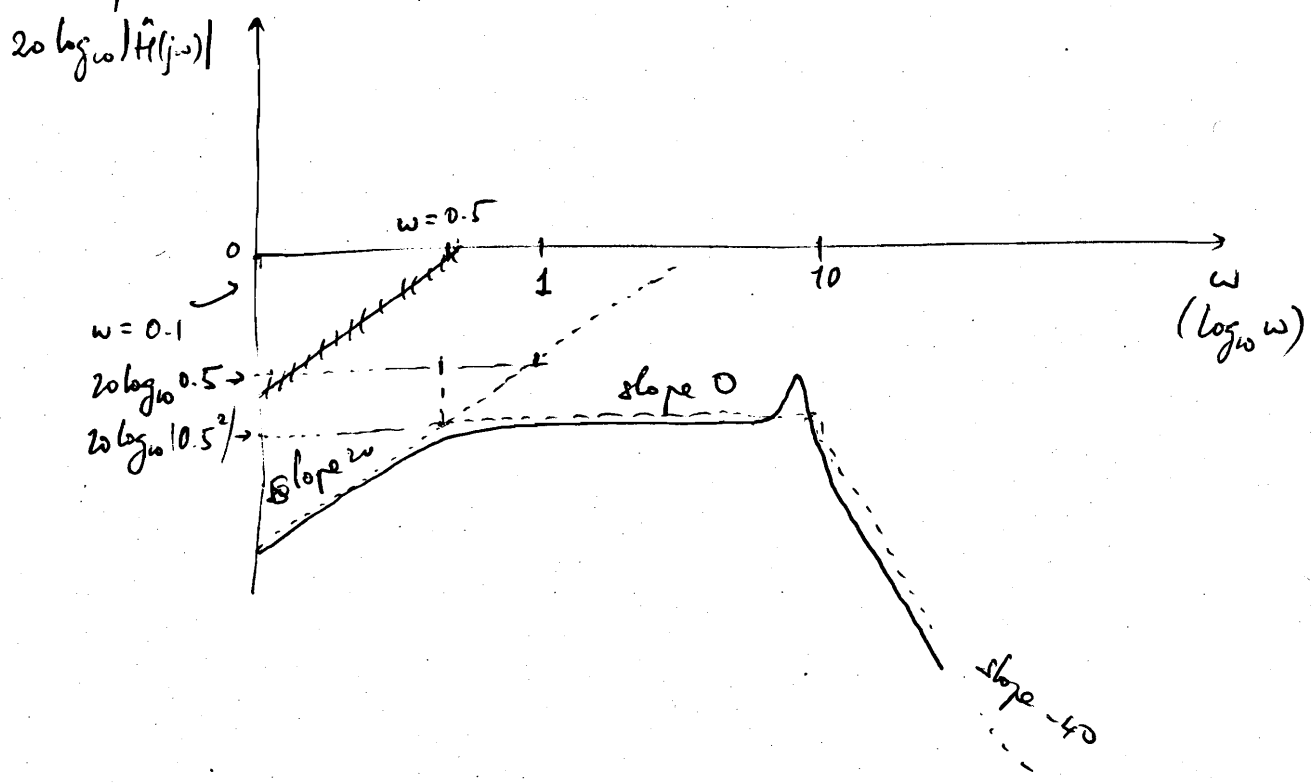$\rightarrow$ After $\omega = 10$: due to a quadratic pole at $\omega = 10$ with slope -40 $\rightarrow$ line with -40 slope.



Phase Bode Plot:

$$\hat{H}(j\omega) = \frac{0.5j\omega}{(1 + j\frac{\omega}{0.5})(1 + \frac{4}{10}j\frac{\omega}{10} + (j\frac{\omega}{10})^2)}$$

$$\angle \hat{H}(j\omega) = \angle 0.5j\omega - \angle 1 + j\frac{\omega}{0.5} - \angle 1 + \frac{4}{10}j\frac{\omega}{10} + (j\frac{\omega}{10})^2$$




$= 90^\circ$

asymptotic analysis

small $\omega \rightarrow 0^\circ$
 large $\omega \rightarrow 90^\circ$
 critical $\omega \rightarrow 45^\circ$


asymptotic analysis

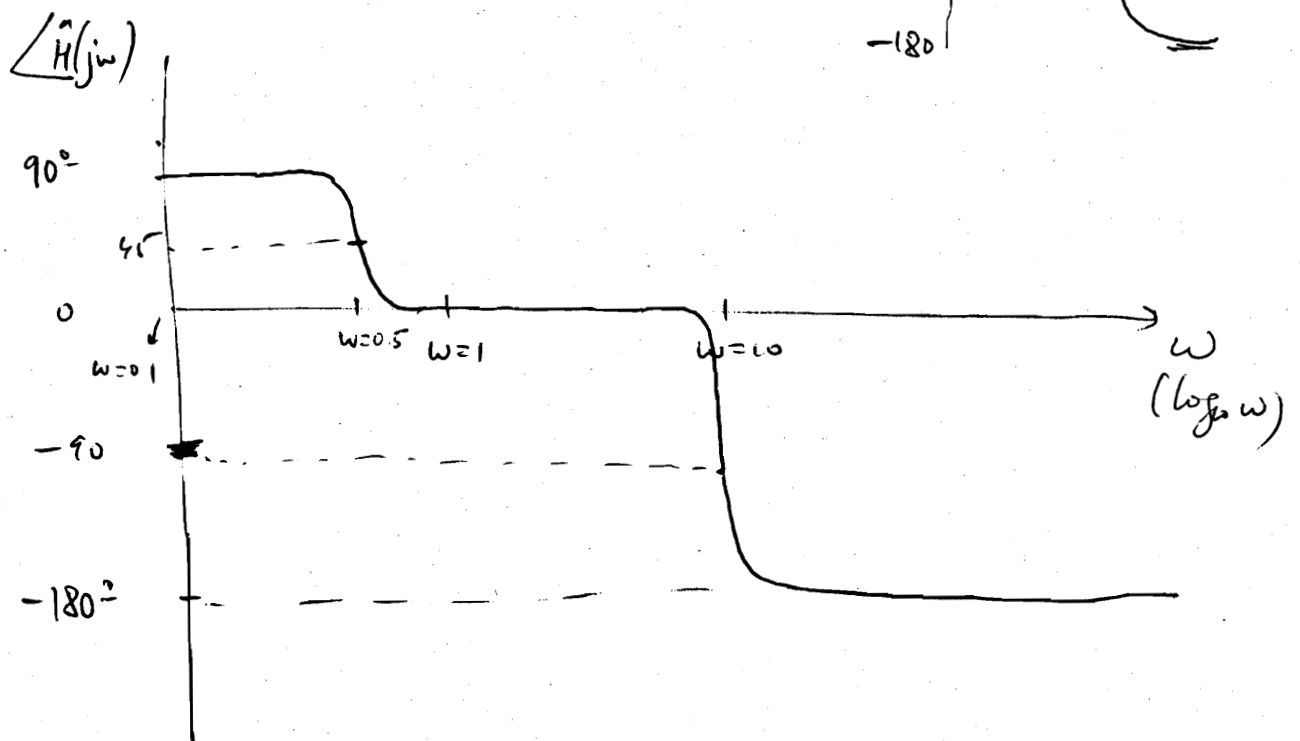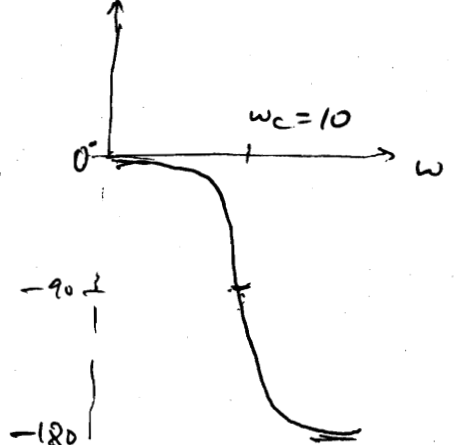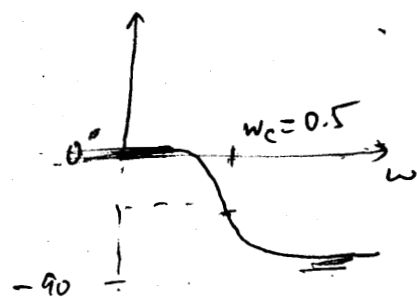small $\omega \rightarrow 0^\circ$
 large $\omega \rightarrow 180^\circ$
 critical $\omega \rightarrow \angle 0.4j = 90^\circ$



Resonant Frequency:

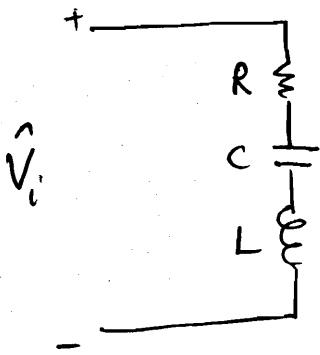Highest consumption: $\hat{Z}$ is pure resistive or $p.f. = \cos \theta$
 $p.f. = \cos 0^\circ = 1$ (or zero angle).



$$\hat{Z}(j\omega) = R + j\omega L + \frac{1}{j\omega C}$$

$$= R + j \left(\omega L - \frac{1}{\omega C} \right)$$

This is pure-resistive when
 $\omega L - \frac{1}{\omega C} = 0$ (angle 0°)

$$\rightarrow \omega^2 = \frac{1}{LC} \text{ or } \omega = \frac{1}{\sqrt{LC}}$$

resonant
freq. ω_0

$$\text{Quality factor } Q \equiv \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$


Practical applications: filter networks

What are we filtering? certain frequencies (e.g. those carried by noises)

→ Passive filters: using exclusively R, L, C (no gain)

→ Active filters: also use op-amps (gain > 1)

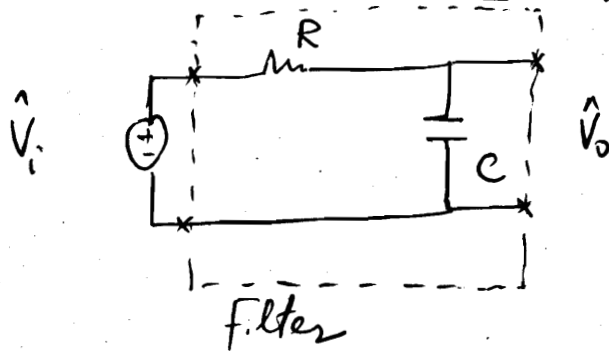
Passive - Low Pass filter: (passing low frequencies)




$$\hat{H} = \frac{\hat{V}_o}{\hat{V}_i} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R}$$

$$= \frac{1}{1 + j\omega RC}$$


$$\omega_c = \frac{1}{RC}$$

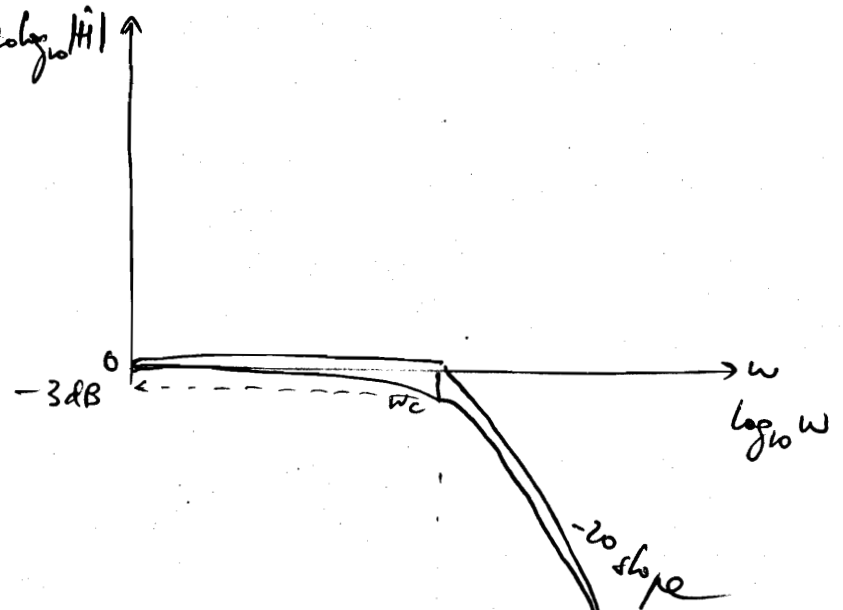

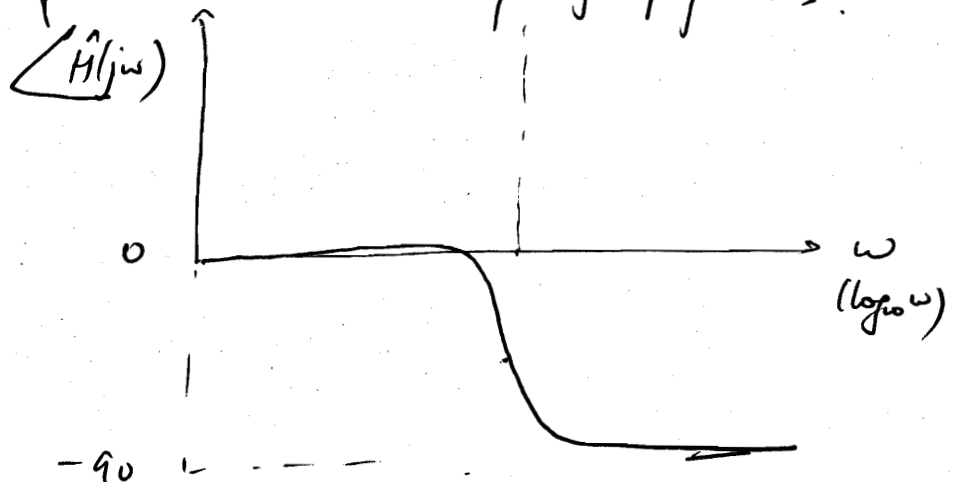This is useful when noises carry high frequencies.





Passive High-Pass Filter :

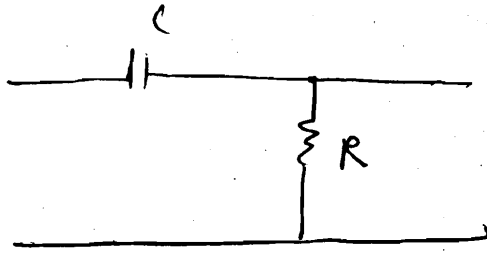


$$\hat{H}(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{j\omega RC + 1}$$

$$20 \log_{10} |\hat{H}(j\omega)| = \underbrace{20 \log_{10} RC}_{\omega_c = \frac{1}{RC}} + 20 \log_{10} \omega - 20 \log_{10} |1 + j\omega RC|$$

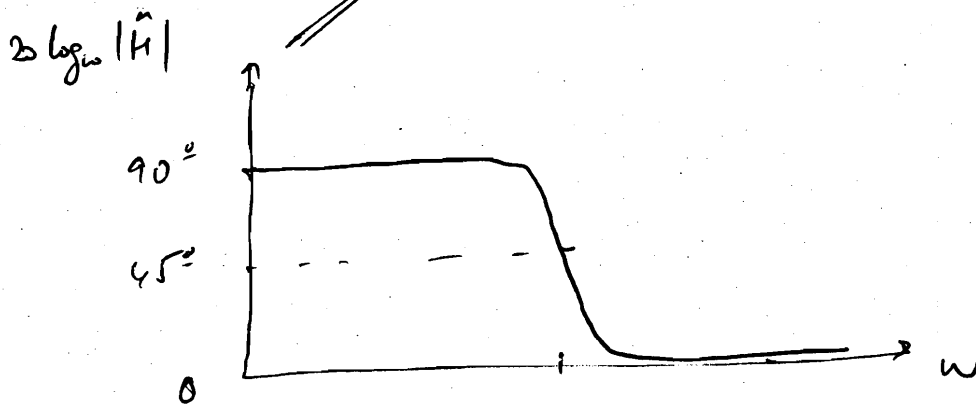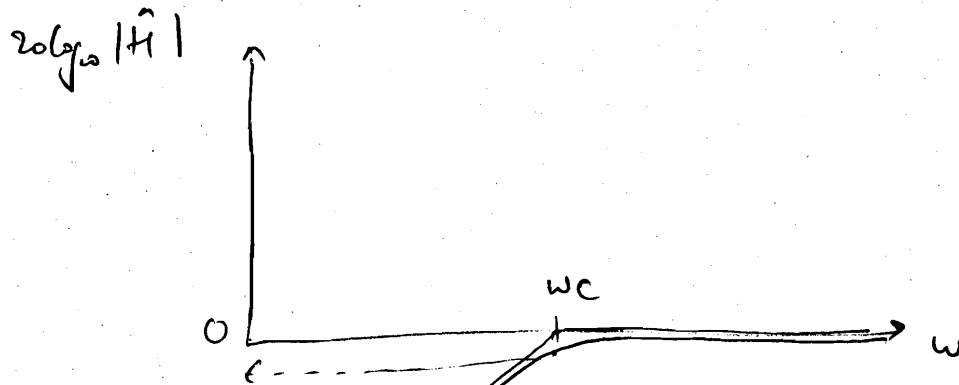

This is useful when noise carry low frequency.

11-29 (7^{ed}) or 11-30 (8^{ed}).

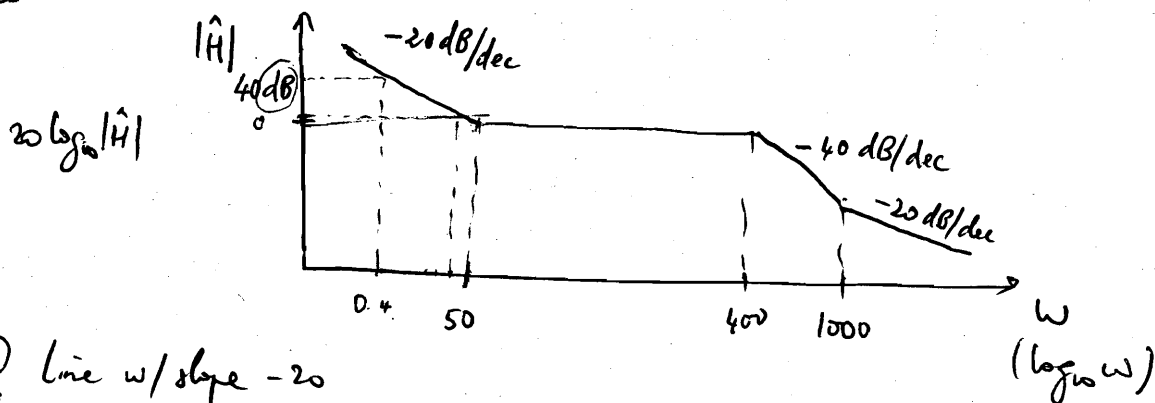

- $\omega = 0.4$
 These terms are 0
- ① line ω / slope -20
 - ② line ω / slope +20, $\omega_c = 50$
 - ③ line ω / slope -40, $\omega_c = 400$
 - Quadratic pole: $(1 + 2\zeta j\omega\tau + (j\omega\tau)^2)$
 - Double pole: $(1 + j\omega\tau)^2$
 - ④ line ω / slope +20, $\omega_c = 1000$


$$\hat{H} = \frac{(1 + j\frac{\omega}{50}) \cdot (1 + j\frac{\omega}{1000})}{j\omega (1 + j\frac{\omega}{400})^2}$$

$$20 \log_{10} |\hat{H}| = 20 \log_{10} |1 + j\frac{\omega}{50}| - 20 \log_{10} \omega - 40 \log_{10} |1 + j\frac{\omega}{400}| + 20 \log_{10} |1 + j\frac{\omega}{1000}|$$

$$40 = \underbrace{-20 \log_{10} 0.4}_{+7.96} + 20 \log_{10} K_0$$

$$K_0 = 10^{\left(\frac{40 - 7.96}{20}\right)} = 40$$
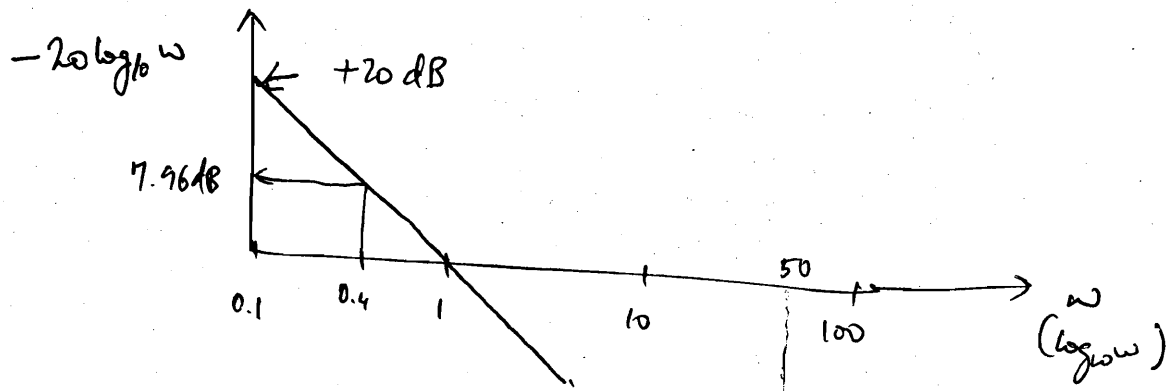
$$\hat{H} = \frac{40 (1 + j\frac{\omega}{50}) (1 + j\frac{\omega}{1000})}{j\omega (1 + j\frac{\omega}{400})^2}$$



If $K_0 = 1 \rightarrow$ the line at small freq should cut the freq axis at $\omega = 1$,


At $\omega = 0.4 \rightarrow -20 \log_{10} 0.4 = 7.96 \text{ dB}$ (but in the given Bode plot, at $\omega = 0.4$ we had $40 \text{ dB} \rightarrow$ there should a K_0 such that $20 \log_{10} K_0 = 40 - 7.96 \Rightarrow K_0 = 10^{\frac{40 - 7.96}{20}} = 40$.

11.18 (7^{ed})


$$\hat{H}(j\omega) = \frac{100 (j\omega)^2}{(1+j\omega)(10+j\omega)^2(50+j\omega)} = \frac{\textcircled{1} \frac{1}{50} \cdot \textcircled{2} (j\omega)^2}{\textcircled{3} (1+j\omega) \textcircled{4} (1+j\frac{\omega}{10})^2 \textcircled{5} (1+j\frac{\omega}{50})}$$

$\downarrow \quad \quad \quad \downarrow \quad \quad \quad \downarrow$
 $\omega_c = 1 \quad \quad \quad \omega_c = 10 \quad \quad \quad \omega_c = 50$


Standard form of $1+j\omega\tau$, etc.

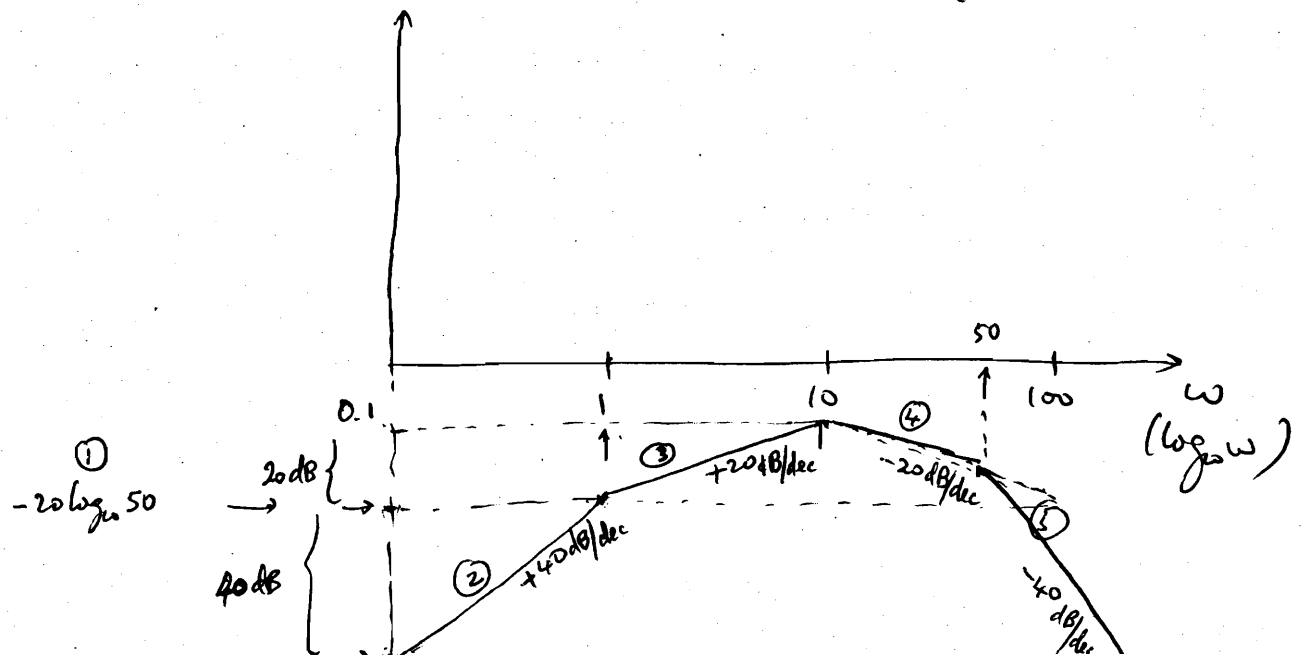


③

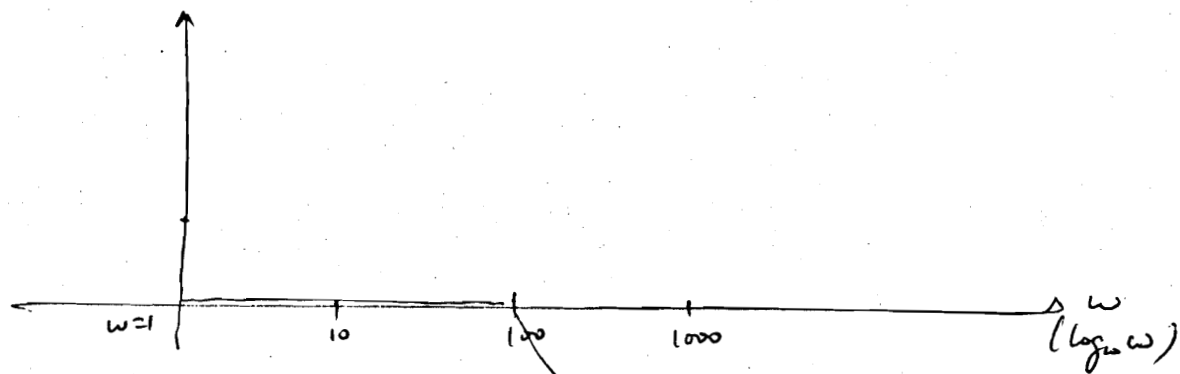




① + ② + ③

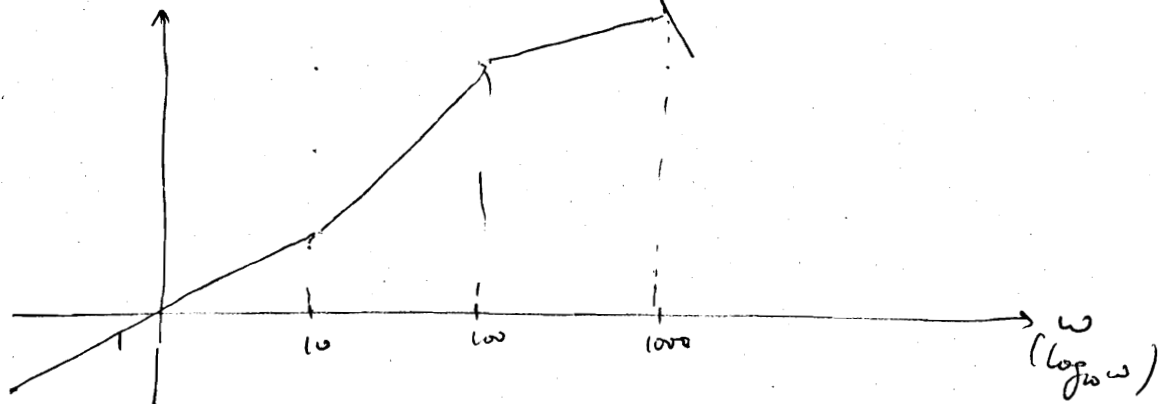


① + ② + ③ + ④

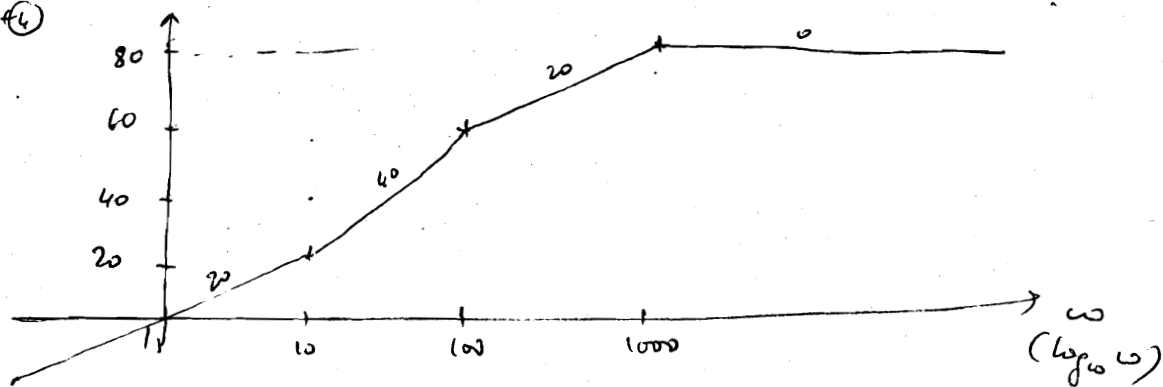

$$20 \log_{10} |H(j\omega)| = \textcircled{1} 20 \log_{10} \omega + \textcircled{2} 20 \log_{10} \left| 1 + j \frac{\omega}{10} \right| - \textcircled{3} 20 \log_{10} \left| 1 + j \frac{\omega}{1000} \right| - \textcircled{4} 20 \log_{10} \left| 1 + j \frac{\omega}{10000} \right|$$

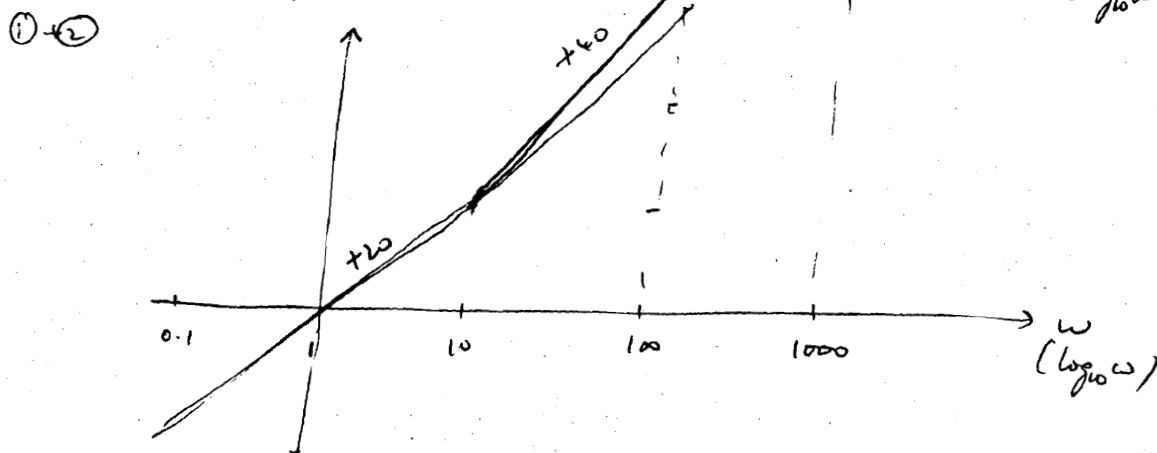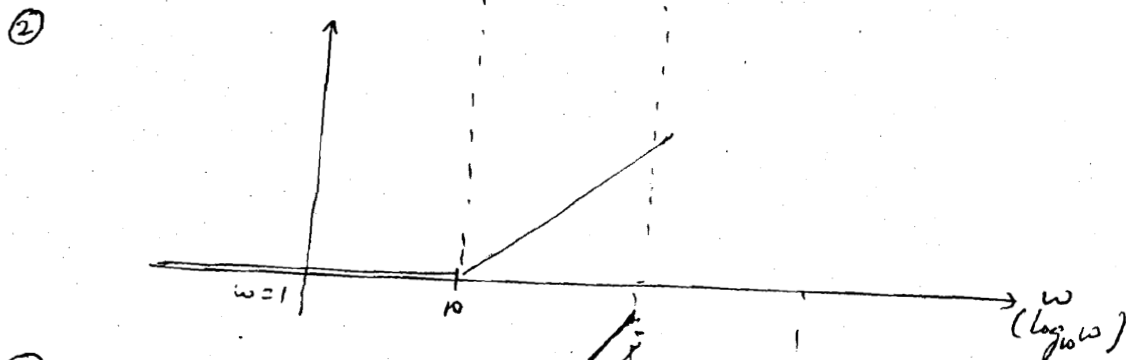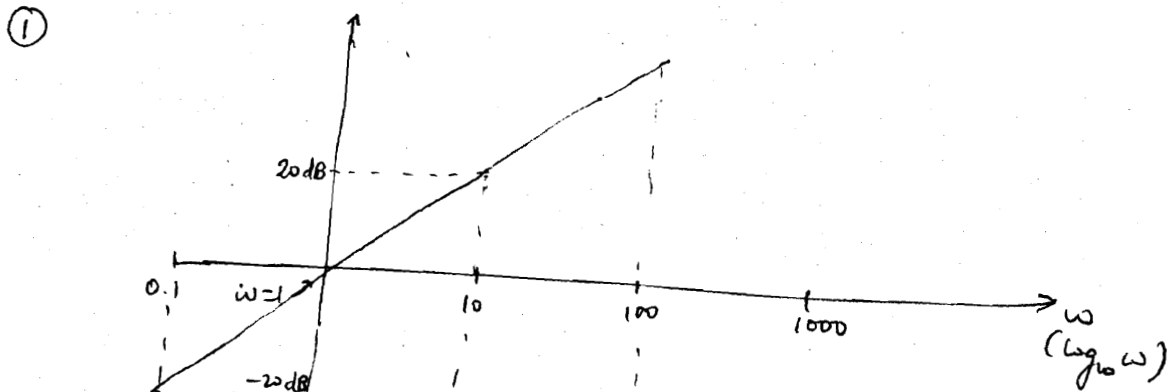

Passive Band-Pass Filter:

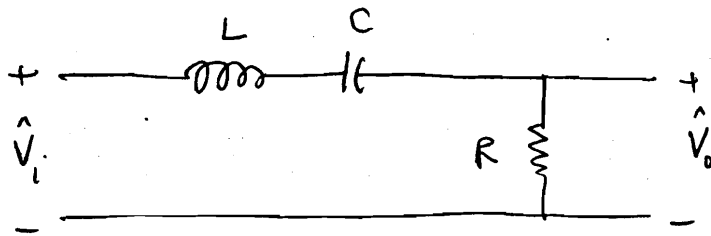

$$\hat{H} = \frac{\hat{V}_o}{\hat{V}_i} = \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$

$$\hat{H} = \frac{RC\omega}{RC\omega + j(LC\omega^2 - 1)}$$

$$\left\{ \begin{array}{l} \text{Magnitude: } |\hat{H}| = \frac{RC\omega}{\sqrt{(RC\omega)^2 + (LC\omega^2 - 1)^2}} \\ \text{Phase: } \angle \hat{H} = -\tan^{-1}\left(\frac{LC\omega^2 - 1}{RC\omega}\right) \end{array} \right.$$

Asymptotic analysis:


$$\begin{aligned} \text{Small } \omega: \omega^2 \ll \frac{1}{LC} \quad (\text{or } \omega \ll \frac{1}{\sqrt{LC}}) &\rightarrow \left\{ \begin{array}{l} |\hat{H}| = \frac{RC\omega}{\sqrt{(RC\omega)^2 + 1}} \\ \omega \ll \frac{1}{RC} \rightarrow |\hat{H}| \approx RC\omega \approx 0 \\ \angle \hat{H} = -\tan^{-1}\left(\frac{-1}{RC\omega}\right) \\ \omega \ll \frac{1}{RC} \rightarrow \angle \hat{H} = \tan^{-1}(\infty) \\ = 90^\circ \end{array} \right. \end{aligned}$$

$$\begin{aligned} \text{Large } \omega: \omega^2 \gg \frac{1}{LC} \quad (\text{or } \omega \gg \frac{1}{\sqrt{LC}}) &\rightarrow \left\{ \begin{array}{l} |\hat{H}| = \frac{RC\cancel{\omega}}{L\cancel{\omega}^2} = \frac{R}{L\omega} \\ \approx 0 \\ \angle \hat{H} = -\tan^{-1} \frac{L\cancel{\omega}^2}{R\cancel{\omega}} = -\tan^{-1} \frac{L\omega}{R} \\ = -\tan^{-1} \infty = -90^\circ \end{array} \right. \end{aligned}$$

Resonant freq: $\omega = \frac{1}{\sqrt{LC}}$

$$\begin{cases} |\hat{H}| = \frac{R(\omega)}{\sqrt{(RC\omega)^2}} = 1 \\ \angle \hat{H} = -\tan^{-1} 0 = 0^\circ \end{cases}$$

Band-pass filter:


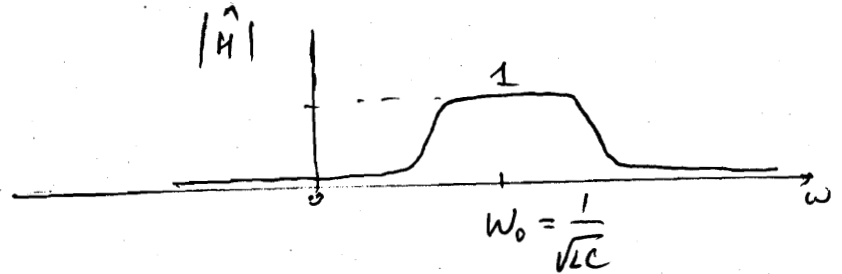


Xcredit (due 5/8) : (5 exam points)



Design a band-pass filter using only R, C elements.
Provide concrete values for R and C to make this happen.
(Simplest design please)

Active Filters using Op-Amp:


Inverting

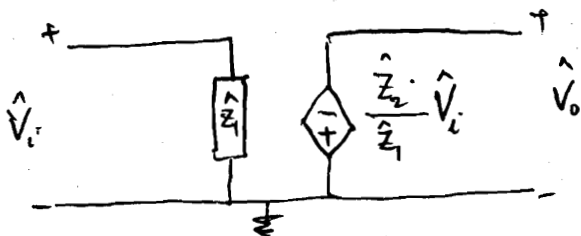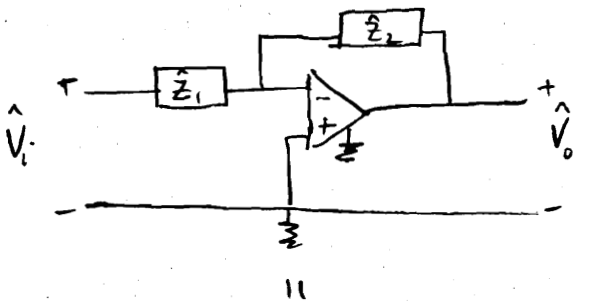

Non-inverting

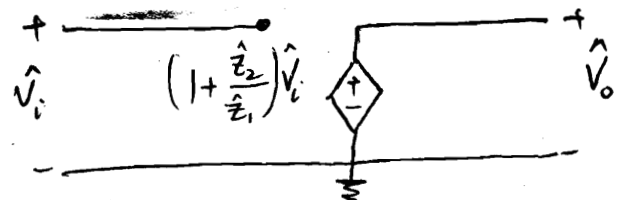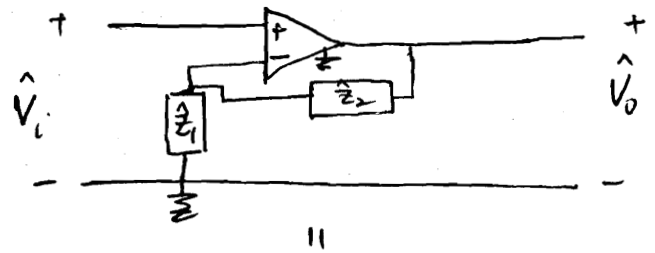

Example of an active filter:

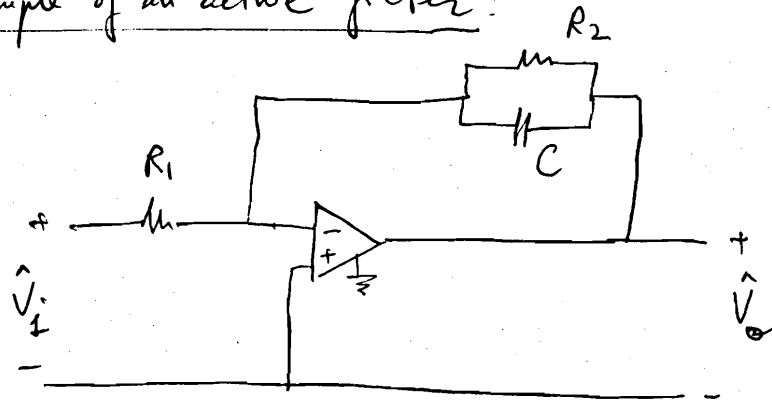


→ What type of filter?

→ What is the gain or amplification?

Make use of the equivalent circuit for the inverting configuration; find $\hat{H}$, answer questions.
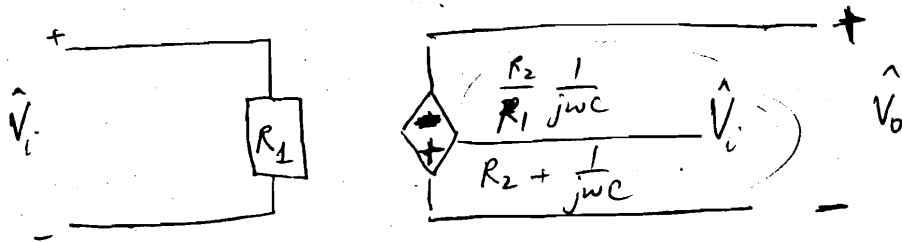
$$\hat{Z}_1 = R_1; \quad \hat{Z}_2 = R_2 \parallel C = \frac{R_2 \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}}$$



$$\hat{H} = \frac{\hat{V}_o}{\hat{V}_i} = \frac{-\frac{R_2}{R_1} \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{-\frac{R_2}{R_1}}{1 + j\omega R_2 C}$$

→ Type of filter: active low-pass filter

→ Gain is $\frac{R_2}{R_1}$ (related to the bandwidth: higher gain ~ smaller bandwidth)

Laplace Transform : (L.T.)

$$f(t) \xrightarrow{\text{direct L.T.}} \hat{F}(s) \equiv \int_0^{\infty} dt f(t) e^{-st}$$

$$s \equiv \alpha + j\omega ; \alpha > 0$$

(when $\alpha = 0 \rightarrow$ related to Fourier Transform)

in time-domain


in frequency domain (s related to ω)

$$f(t) \xleftarrow[\text{inverse}]{\text{L.T.}^{-1}} \hat{F}(s)$$

$$f(t) = \frac{1}{2\pi j} \int_{\sigma_1 - j\infty}^{\sigma_1 + j\infty} ds \hat{F}(s) e^{st} \quad (\text{integral in the complex plane})$$

We will use Partial Fraction Expansion & Properties of L.T.

- L.T. for a unit step function :

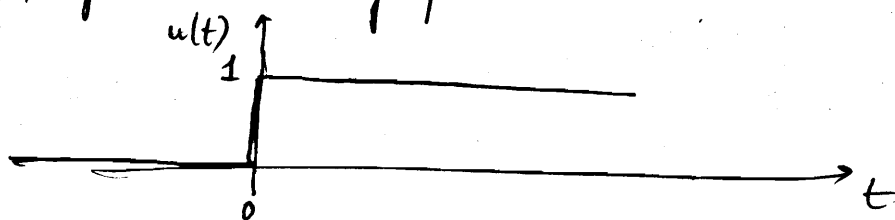


$$\text{L.T.}[u(t)] = \int_0^{\infty} dt u(t) e^{-st} = \int_0^{\infty} dt e^{-st} = \left[\frac{e^{-st}}{-s} \right]_{t=0}^{t=\infty}$$

$$= 0 - \frac{1}{-s} = \frac{1}{s}$$

$\downarrow$
($\alpha > 0$)

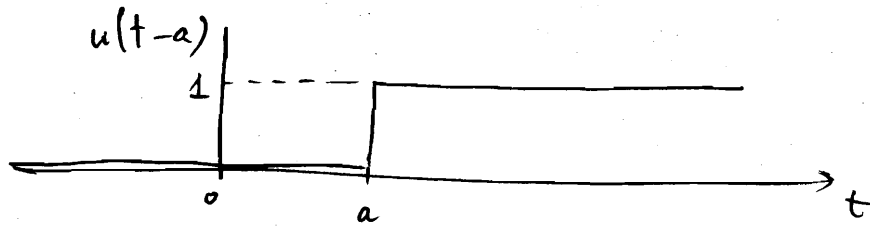- L.T. of a time-shifted unit step function:




$$\text{L.T.}[u(t-a)] = \int_0^{\infty} dt \, u(t-a) e^{-st} = \int_a^{\infty} dt \, e^{-st} = \left[\frac{e^{-st}}{-s} \right]_a^{\infty}$$

$$\stackrel{\substack{\downarrow \\ a > 0}}{=} 0 - \frac{e^{-sa}}{-s} = \underbrace{e^{-sa}}_{\substack{\uparrow \\ \text{time shift of } a \rightarrow \text{multiplication by } e^{-sa} \text{ in frequency}}} \frac{1}{s}$$

time shift of $a \rightarrow$ multiplication by e^{-sa} in frequency

- L.T. of a delta function $\delta(t)$

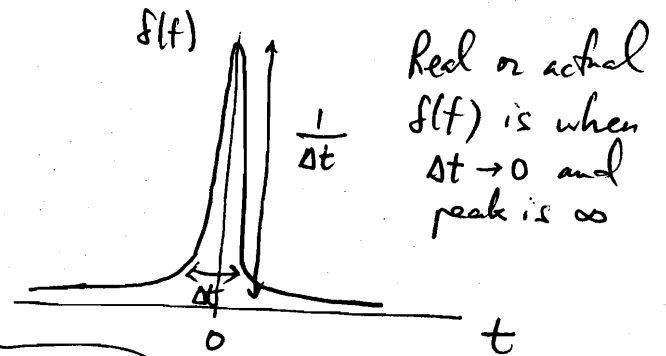

Its effect is to pick out the value of a function at its center
 $\delta(t) \rightarrow$ center at 0
 $\delta(t-a) \rightarrow$ center at a

$$\text{LT}[\delta(t)] = \int_0^{\infty} dt \, \delta(t) e^{-st} = e^{-s \cdot 0} = 1$$

$$\text{LT}[\delta(t-a)] = e^{-sa} \cdot 1 = e^{-sa}$$

• LT of $f(t) = t$?

$$LT[t] = \int_0^{\infty} dt t e^{-st} = - \frac{d}{ds} \left[\underbrace{\int_0^{\infty} dt e^{-st}}_{\frac{1}{s}} \right] = \frac{1}{s^2}$$

• LT of $f(t) = \cos \omega t$? $\rightarrow \cos \omega t = \frac{e^{j\omega t} + e^{-j\omega t}}{2}$

$$\begin{aligned} LT[\cos \omega t] &= \frac{1}{2} \int_0^{\infty} dt \left[e^{j\omega t} e^{-st} + e^{-j\omega t} e^{-st} \right] \\ &= \frac{1}{2} \int_0^{\infty} dt \left[e^{-(s-j\omega)t} + e^{-(s+j\omega)t} \right] \\ &= \frac{1}{2} \left[\frac{e^{-(s-j\omega)t}}{-(s-j\omega)} + \frac{e^{-(s+j\omega)t}}{-(s+j\omega)} \right]_0^{\infty} \\ &= \frac{1}{2} \left[\frac{1}{s-j\omega} + \frac{1}{s+j\omega} \right] \\ &= \frac{s}{s^2 + \omega^2} \end{aligned}$$

$$\begin{aligned} LT[\sin \omega t] &= \frac{1}{2j} \left[\frac{1}{s-j\omega} - \frac{1}{s+j\omega} \right] \\ &= \frac{1}{2j} \frac{2j\omega}{s^2 + \omega^2} = \frac{\omega}{s^2 + \omega^2} \end{aligned}$$