

Relevant properties of L.T. for doing inverse L.T. using P.F.E
(partial fraction expansion)

Property # 4 :


if $f(t) \xrightarrow{\text{L.T.}} \hat{F}(s)$
then $f(t-t_0) u(t-t_0) ; t_0 \geq 0 \longrightarrow e^{-st_0} \hat{F}(s)$

Proof:

$$\begin{aligned} \text{L.T.}[f(t-t_0) u(t-t_0)] &= \int_{-\infty}^{\infty} dt f(t-t_0) u(t-t_0) e^{-st} \quad \overbrace{e^{-st_0} e^{st_0}} \\ &= e^{-st_0} \int_{-\infty}^{\infty} dt f(t-t_0) u(t-t_0) e^{-s(t-t_0)} \end{aligned}$$

$$\begin{aligned} t-t_0 &\rightarrow t' \quad (t=\infty; t'=\infty) \\ dt &= dt' \end{aligned}$$
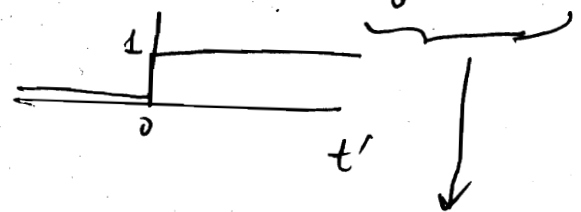
$$\int_{-t_0}^{\infty} dt' f(t') u(t') e^{-st'} = \int_0^{\infty} dt' f(t') e^{-st'}$$



$$\begin{aligned} &\text{LT}(f(t')) \\ &\quad \text{"} \\ &\hat{F}(s) \end{aligned}$$

$$= e^{-st_0} \hat{F}(s) \quad \checkmark$$

Property #8:

$$\text{if } f(t) \longrightarrow \hat{F}(s)$$

$$LT[t f(t)] \longrightarrow -\frac{d}{ds} \hat{F}(s)$$

$$LT[t f(t)] = \int_0^{\infty} dt \, t f(t) e^{-st} = -\frac{d}{ds} \underbrace{\int_0^{\infty} dt \, f(t) e^{-st}}_{\hat{F}(s)} \quad \checkmark$$

Partial Fraction Expansion (PFE)

1) Simple poles: $\frac{\hat{P}}{\hat{Q}} = \frac{\hat{k}_1}{s+p_1} + \frac{\hat{k}_2}{s+p_2} + \dots + \frac{\hat{k}_n}{s+p_n}$

($\hat{Q}$ is a polynomial of order n ; $-p_1, -p_2, \dots, -p_n$ are the roots of $\hat{Q} = 0$ or solutions)

In this case: $\hat{k}_i = \frac{(s+p_i) \hat{P}}{\hat{Q}} \bigg|_{s=-p_i}$ obvious algorithm to find $\hat{k}_i$

$$(s+p_i) \frac{\hat{P}}{\hat{Q}} = (s+p_i) \left(\frac{\hat{k}_1}{s+p_1} + \frac{\hat{k}_2}{s+p_2} + \dots + \frac{\hat{k}_i}{s+p_i} + \dots + \frac{\hat{k}_n}{s+p_n} \right)$$

All terms with $(s+p_i)$ will vanish after substitution $s=-p_i$.
One term carries no $(s+p_i)$ will remain, which give $\hat{k}_i$.

2) Complex conjugate poles:

$$\frac{\hat{P}}{\hat{Q}} = \frac{\hat{k}_1}{s + \alpha - j\beta} + \frac{\hat{k}_1^*}{s + \alpha + j\beta}$$

$-\alpha \pm j\beta$ are complex conjugate roots of $\hat{Q} = 0$

In this case: $\hat{k}_1 = \left[(s + \alpha - j\beta) \frac{\hat{P}}{\hat{Q}} \right]_{s = -\alpha + j\beta}$

$\hat{k}_1^* = \text{complex conjugate of } \hat{k}_1$

3) Multiple poles:

$$\frac{\hat{P}}{\hat{Q}} = \frac{\hat{k}_{11}}{s + p_1} + \frac{\hat{k}_{12}}{(s + p_1)^2} + \dots + \frac{\hat{k}_{1n}}{(s + p_1)^n}$$

$\hat{Q} = 0$ has one root (in this expression) p_1 with multiplicity n ($(x+1)^3$ has one root at -1 with multiplicity or order 3)

$$\hat{k}_{12} = \left[(s + p_1)^2 \frac{\hat{P}}{\hat{Q}} \right]_{s = -p_1} \quad (\text{same as before})$$

$$\hat{k}_{1, n-1} = \left[\frac{d}{ds} \left((s + p_1)^n \frac{\hat{P}}{\hat{Q}} \right) \right]_{s = -p_1}$$

$\vdots$

$$(s + p_1)^n \left(\frac{\hat{P}}{\hat{Q}} \right) = (s + p_1)^{n-1} \hat{k}_{11} + (s + p_1)^{n-2} \hat{k}_{12} + \dots + (s + p_1) \hat{k}_{1, n-1} + \hat{k}_{1n}$$

PFE for $\hat{F}(s) = \frac{10(s+3)}{(s+1)^3(s+2)}$:

$$= \frac{\hat{k}_{11}}{s+1} + \frac{\hat{k}_{12}}{(s+1)^2} + \frac{\hat{k}_{13}}{(s+1)^3} + \frac{\hat{k}_2}{s+2}$$

$$\hat{k}_{13} = \left[(s+1)^3 \hat{F}(s) \right]_{s=-1} = \left[\frac{10(s+3)}{s+2} \right]_{s=-1} = \frac{10 \cdot 2}{1} = 20$$

$$\hat{k}_{12} = \left[\frac{d}{ds} \left(\frac{10(s+3)}{s+2} \right) \right]_{s=-1} = \left[\frac{10}{s+2} - \frac{10(s+3)}{(s+2)^2} \right]_{s=-1} = 10 - 20 = -10$$

$$\hat{k}_{11} = \left[\frac{d}{ds} \left(\frac{10}{s+2} - \frac{10(s+3)}{(s+2)^2} \right) \right]_{s=-1} = \left[\frac{-10}{(s+2)^2} - \frac{10}{(s+2)^2} + \frac{20(s+3)}{(s+2)^3} \right]_{s=-1}$$

$$= 20$$

$$\hat{k}_2 = \left[(s+2) \hat{F}(s) \right]_{s=-2} = \left[\frac{10(s+3)}{(s+1)^3} \right]_{s=-2} = -10$$

$$\frac{10(s+3)}{(s+1)^3(s+2)} = \frac{20}{s+1} + \frac{-10}{(s+1)^2} + \frac{20}{(s+1)^3} + \frac{-10}{s+2}$$

What is $LT^{-1}[\hat{F}(s)]$?

$$f(t) = 20 LT^{-1}\left(\frac{1}{s+1}\right) - 10 LT^{-1}\frac{1}{(s+1)^2} + 20 LT^{-1}\frac{1}{(s+1)^3} - 10 LT^{-1}\frac{1}{s+2}$$

$$= 20e^{-t}u(t) - 10te^{-t}u(t) + 10t^2e^{-t}u(t) - 10e^{-2t}u(t)$$

Property #4: $f(t-t_0)u(t-t_0) \rightarrow e^{-st_0} \hat{F}(s)$

Dual property: (time & freq are equivalent)

$$e^{-at} f(t) \leftarrow \hat{F}(s+a)$$

$$e^{-t} u(t) \leftarrow \frac{1}{s+1} \quad (\text{since } u(t) \leftarrow \frac{1}{s})$$

Property #8 : $t f(t) \longleftrightarrow -\frac{d}{ds} \hat{F}(s)$
 $t e^{-t} u(t) \longleftrightarrow \frac{1}{(s+1)^2}$


$$\frac{1}{(s+1)^3} = -\frac{1}{2} \frac{d}{ds} \frac{1}{(s+1)^2}$$

$$\frac{1}{2} t^2 e^{-t} u(t) \longleftrightarrow \frac{1}{(s+1)^3}$$

$$f(t) = \cancel{20} u(t) [20e^{-t} - 10te^{-t} + 10t^2e^{-t} - 10e^{-2t}] \checkmark$$


$$= u(t) [10e^{-t} - 10te^{-t} + 10t^2e^{-t}]$$

13.26 :

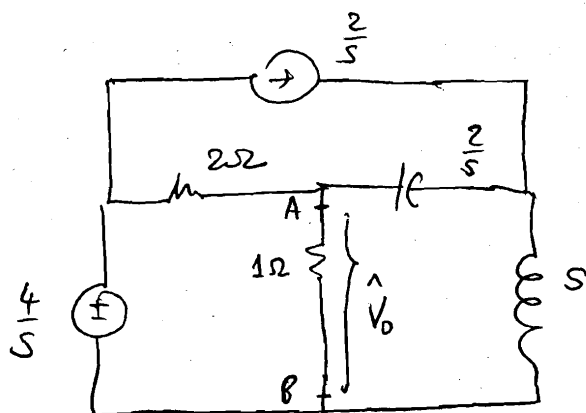

Find $\hat{V}_o$ then find $v_o(t)$

13.62 :

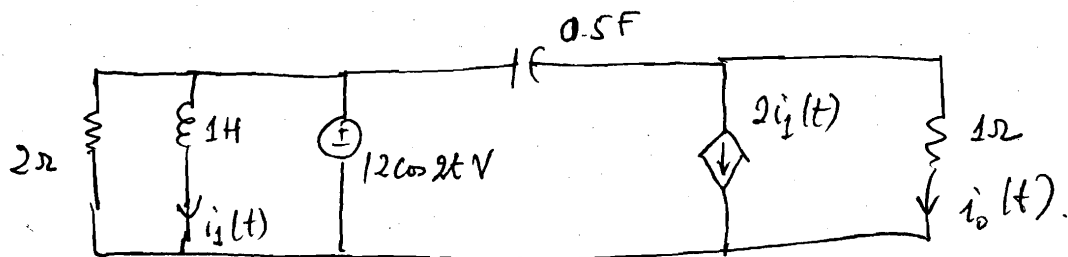

Find $\hat{I}_o$, then $i_o(t)$

If $\hat{Q}(s)=0$ has p_1 & p_2 as roots $\Rightarrow \hat{Q}(s)=(s-p_1)(s-p_2)$

(91)

12.18

a) $F(s) = \frac{10}{s^2 + 2s + 2}$; b) $F(s) = \frac{10(s+2)}{s^2 + 4s + 5}$

a) $s^2 + 2s + 2 = 0 \rightarrow s = \frac{-2 \pm \sqrt{4 - 8}}{2} = -1 \pm j$

$$\frac{10}{s^2 + 2s + 2} = \frac{\hat{k}_1}{s + 1 - j} + \frac{\hat{k}_1^*}{s + 1 + j}$$

$$\hat{k}_1 = [(s + 1 - j) \hat{F}(s)]_{s = -1 + j} = \left[\frac{10}{s + 1 + j} \right]_{s = -1 + j} = \frac{10}{2j} = -5j$$

$$\hookrightarrow \left[\cancel{(s + 1 - j)} \frac{10}{(\cancel{s + 1 - j})(s + 1 + j)} \right]_{s = -1 + j}$$

$$\rightarrow \frac{10}{s^2 + 2s + 2} = \frac{-5j}{s + 1 - j} + \frac{5j}{s + 1 + j}$$

Back to time domain:

$$\begin{aligned} & \downarrow \\ & -5j e^{-(1-j)t} u(t) + 5j e^{-(1+j)t} u(t) \\ & = -5j e^{-t} u(t) \underbrace{\left[e^{jt} - e^{-jt} \right]}_{2j \sin t} = \boxed{10 e^{-t} \sin(t) u(t)} \end{aligned}$$

$$\begin{aligned} e^{j\alpha} &= \cos \alpha + j \sin \alpha \\ e^{-j\alpha} &= \cos \alpha - j \sin \alpha \end{aligned} \quad \left\{ \begin{aligned} e^{j\alpha} - e^{-j\alpha} &= 2j \sin \alpha \\ e^{j\alpha} + e^{-j\alpha} &= 2 \cos \alpha \end{aligned} \right.$$

13.26 13.62 11.54 11.57. 11.59.

$$b) \quad F(s) = \frac{10(s+2)}{s^2+4s+5} \quad ; \quad s^2+4s+5=0 \rightarrow s = \frac{-4 \pm \sqrt{16-20}}{2} = -2 \pm j$$

$$\frac{10(s+2)}{s^2+4s+5} = \frac{\hat{k}_1}{s+2-j} + \frac{\hat{k}_1^*}{s+2+j}$$


$$\hat{k}_1 = \left[(s+2-j) \frac{10(s+2)}{(s+2-j)(s+2+j)} \right]_{s=-2+j} = \frac{10j}{2j} = 5$$

$$\hat{k}_1^* = 5$$

$$\rightarrow f(t) = 5 e^{-(2-j)t} u(t) + 5 e^{-(2+j)t} u(t)$$


$$= 5 e^{-2t} u(t) \underbrace{\left[e^{jt} + e^{-jt} \right]}_{2 \cos t} = 10 e^{-2t} \cos t u(t)$$

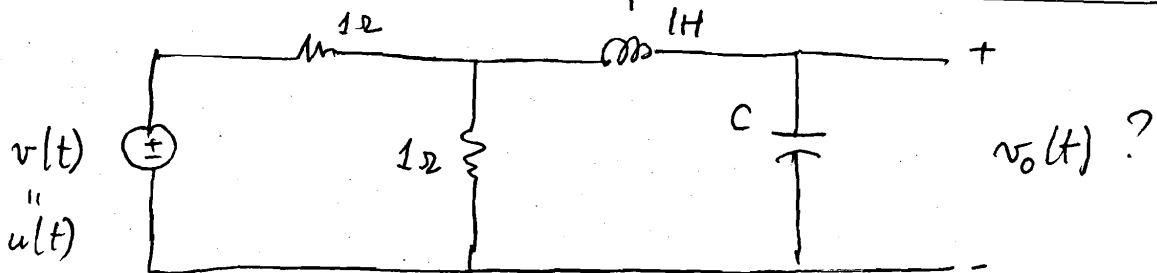Application of Laplace Transform to AC circuit analysis.



Find $\hat{V}_o(s)$, then $LT^{-1}[\hat{V}_o(s)] = v_o(t)$

↓
Redraw circuit with phasors

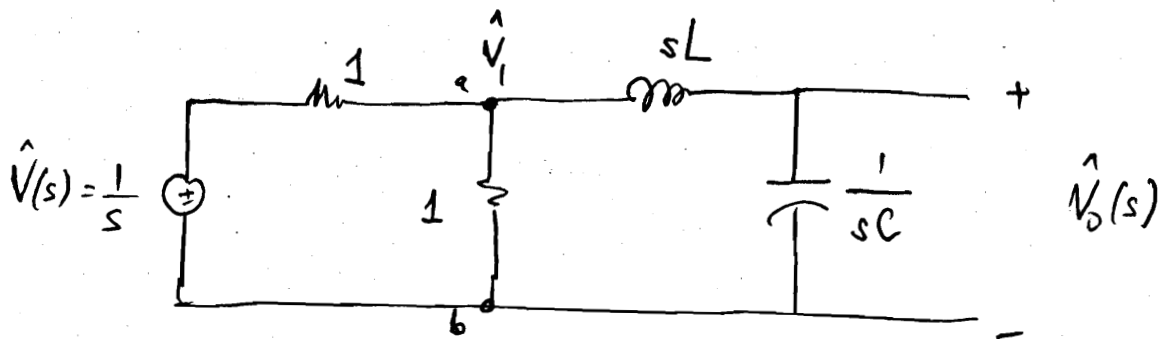

$$\hat{V}_1 = \frac{1 \left(sL + \frac{1}{sC} \right) (j\omega = s)}{1 + sL + \frac{1}{sC}} \cdot \frac{1}{s}$$

$$\hat{V}_o = \frac{\frac{1}{sC}}{sL + \frac{1}{sC}} \hat{V}_1 = \frac{\frac{1}{sC}}{sL + \frac{1}{sC}} \cdot \frac{1}{s} \cdot \frac{\cancel{sL + \frac{1}{sC}}}{1 + sL + \frac{1}{sC}}$$

$$= \frac{1}{sC} \cdot \frac{1}{s} \cdot \frac{1}{\left(1 + sL + \frac{1}{sC} + sL + \frac{1}{sC} \right)}$$

$$= \frac{1}{sC} \cdot \frac{1}{s + 2s^2L + \frac{2}{C}} \stackrel{L=1}{=} \frac{1}{sC \left(s + 2s^2 + \frac{2}{C} \right)}$$

$$= \frac{\frac{1}{2}}{sC \left(s^2 + \frac{s}{2} + \frac{1}{C} \right)} \rightarrow \text{P.F.E.}$$

$$s^2 + \frac{s}{2} + \frac{1}{C} = 0 \rightarrow s = \frac{-\frac{1}{2} \pm \sqrt{\frac{1}{4} - \frac{4}{C}}}{2}$$

$$\left\{ \begin{array}{l} C=4F \quad s = -\frac{1}{4}(1 \pm j\sqrt{3}) \\ \quad \quad \quad \text{(complex conj.)} \\ C=16F \quad s = -\frac{1}{4} \text{ (double)} \\ C=32F \quad s = -\frac{1}{4}(1 \pm \frac{1}{\sqrt{2}}) \\ \quad \quad \quad \text{(two simple poles)} \end{array} \right.$$

E.g. if $C=16F$ $(s^2 + \frac{s}{2} + \frac{1}{16}) = (s + \frac{1}{4})^2$

$$\hat{V}_0(s) = \frac{\frac{1}{2}}{s/16 (s + \frac{1}{4})^2} \stackrel{\text{P.F.E.}}{=} \cancel{\frac{1}{32}} \left(\frac{k_2}{s} + \frac{k_{11}}{(s + \frac{1}{4})} + \frac{k_{12}}{(s + \frac{1}{4})^2} \right)$$

$$k_2 = \left[s \hat{V}_0(s) \right]_{s=0} = \left[\frac{\frac{1}{32}}{(s + \frac{1}{4})^2} \right]_{s=0} = \frac{1}{2}$$


$$k_{12} = \left[(s + \frac{1}{4})^2 \hat{V}_0(s) \right]_{s=-\frac{1}{4}} = \left[\frac{\frac{1}{32}}{s} \right]_{s=-\frac{1}{4}} = -\frac{1}{8}$$

$$k_{11} = \left[\frac{1}{32} \frac{d}{ds} \left(\frac{1}{s} \right) \right]_{s=-\frac{1}{4}} = \left[-\frac{1}{32} \frac{1}{s^2} \right]_{s=-\frac{1}{4}} = -\frac{1}{2}$$

$$\rightarrow \hat{V}_0(s) = \frac{\frac{1}{2}}{s} - \frac{\frac{1}{2}}{s + \frac{1}{4}} - \frac{\frac{1}{8}}{(s + \frac{1}{4})^2}$$

$$v(t) = \frac{1}{2} u(t) - \frac{1}{2} e^{-\frac{1}{4}t} u(t) - \frac{1}{8} t e^{-\frac{1}{4}t} u(t)$$


13.26

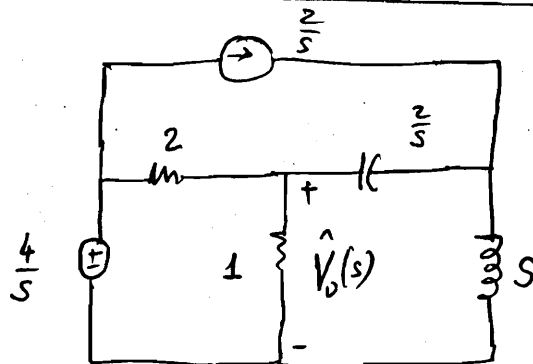

$$\hat{V}_0(s) ? \rightarrow v_0(t)$$

Thevenin Equiv.

$$\hat{V}_{oc}:$$

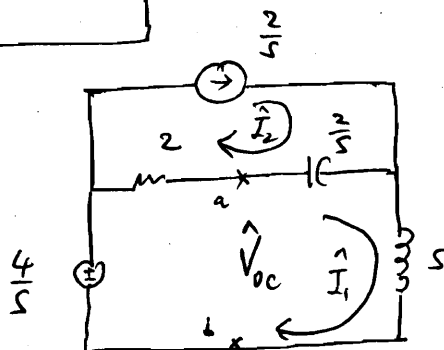

$$1) \hat{I}_2 = \frac{2}{s}$$

$$2) \frac{4}{s} = (2 + \frac{2}{s})(\hat{I}_1 - \hat{I}_2) + \hat{I}_1 s$$

$$\hat{V}_{oc} = \frac{4}{s} - 2(\hat{I}_1 - \hat{I}_2)$$


$$\rightarrow \text{Solve for } \hat{I}_1: \frac{4}{s} = (2 + s + \frac{2}{s})\hat{I}_1 - (2 + \frac{2}{s})\frac{2}{s}$$

$$\hat{I}_1 = \left(\frac{\frac{4}{s} + \frac{2}{s}(2 + \frac{2}{s})}{2 + s + \frac{2}{s}} \right) = \frac{8s + 4}{s(s^2 + 2s + 2)}$$


$$\hat{V}_{oc} = \frac{4}{s} - 2 \left(\frac{8s + 4}{s(s^2 + 2s + 2)} - \frac{2}{s} \right) = \frac{8}{s} - \frac{8(2s + 1)}{s(s^2 + 2s + 2)}$$

$$= \frac{8s^2 + 8}{s(s^2 + 2s + 2)}$$

$$\hat{Z}_{th} =$$

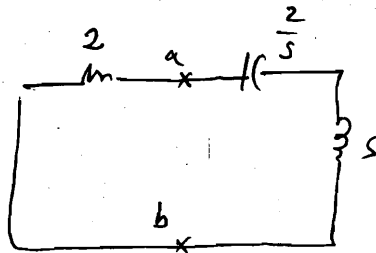
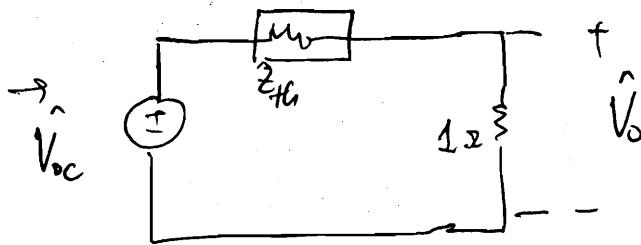
$$\hat{Z}_{th} = \frac{2(\frac{2}{s} + s)}{2 + \frac{2}{s} + s}$$



$$\hat{V}_o = \frac{4(s^2 + 1)}{s(s^2 + s + 3)}$$

$$s^2 + s + 3 = 0$$

$$s = \frac{-1 \pm \sqrt{1 - 12}}{2}$$

$$\rightarrow \text{PFE: } \hat{V}_o(s) = \frac{k_2}{s} + \frac{\hat{k}_1}{s + \frac{1}{2} - j\frac{\sqrt{11}}{2}} + \frac{\hat{k}_1^*}{s + \frac{1}{2} + j\frac{\sqrt{11}}{2}}$$

$$s = -\frac{1}{2} \pm j\frac{\sqrt{11}}{2}$$

$$V_o = \frac{V_{oc}(1)}{1+Z_{TH}} = \frac{8S+8/S}{S^2+2S+2+2S^2+4}$$

$$V_o = \frac{(8/3)(S^2+1)}{S(S^2+(2/3)S+2)}$$


$$A = 4/3$$

$$K|\underline{\theta} = 1.273|\underline{10.05^\circ}$$


$$V_o(t) = \left(\frac{4}{3} + 2.546e^{-t/3} \cos(\sqrt{17}t + 10.05^\circ)\right)V$$

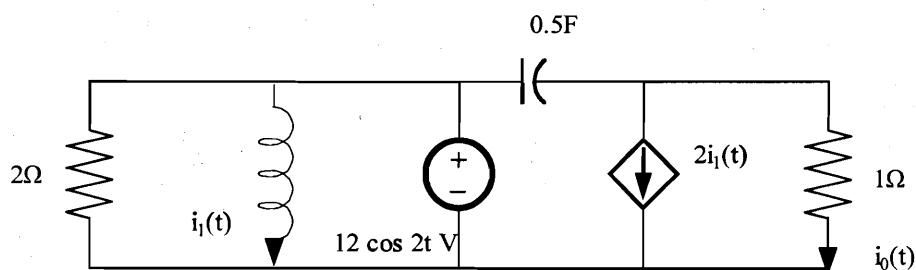Problem 13.62

Find the steady state response $i_o(t)$ for the network shown the fig.



Suggested Solution

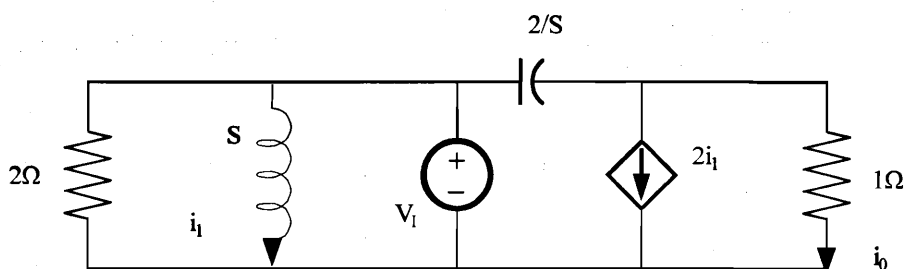

KCL

$$\frac{V_o}{1} + 2I_1 + (V_o - V_1) \frac{s}{2} = 0$$

$$I_o = V_o / 1, I_1 = V_1 / s$$

$$I_o + \frac{2V_1}{s} + I_o \left(\frac{s}{2} \right) - V_1 \left(\frac{s}{2} \right) = 0$$

or

$$I_o \left(1 + \frac{s}{2} \right) = V_1 \left(\frac{s}{2} - \frac{2}{s} \right) = V_1 \left(\frac{s^2 - 4}{2s} \right)$$

$$I_o \left(\frac{s+2}{2} \right) = V_1 \left(\frac{s^2 - 4}{2s} \right)$$

Finally

$$\frac{I_o}{V_1} = \frac{s-2}{s}$$

at steady state $s=j2$

$$V_i(t) = 12 \cos(2t)$$

$$\left. \frac{I_0}{V_i} \right|_2 = \frac{j2-2}{j2} = \sqrt{2} \angle 45^\circ$$

and

$$I_0 = |V_i| \sqrt{2} \angle 45^\circ = 12\sqrt{2} \angle 45^\circ$$

$$I_0 = 12\sqrt{2} \cos(2t + 45^\circ) A$$