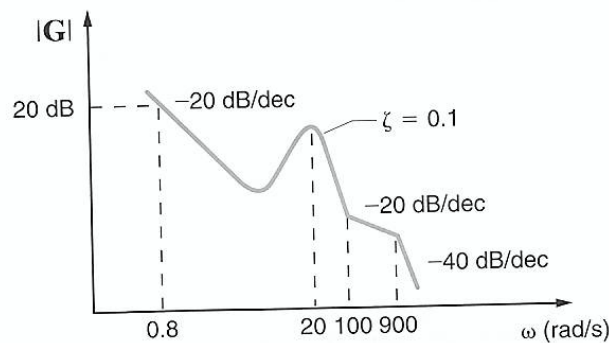


Problem 11.33

Find $G(j\omega)$ if the amplitude characteristic for this function is shown in fig 11.33.



Suggested Solution

Zeros: 2@100 r/s

Simple poles: dc & 900 r/s

Complex poles : $\tau=1/20$ s & $\zeta=0.1$

So $\omega_0=20$ r/s

& $2\zeta\omega_0=0.01$

Also,

$$H(j0.8) = 20\text{dB} = 10$$


$$H(j\omega) = \frac{k(0.1j\omega+1)^2}{(j\omega)\left(\frac{j\omega}{900}+1\right)\left(\left(\frac{j\omega}{20}\right)^2 + \frac{j\omega}{100}+1\right)}$$

$$H(j0.8) = 10 \Rightarrow K = 8$$

$$H(j\omega) = \frac{0.8(0.1j\omega+1)^2}{(j\omega)\left(\frac{j\omega}{900}+1\right)\left(\left(\frac{j\omega}{20}\right)^2 + \frac{j\omega}{100}+1\right)}$$

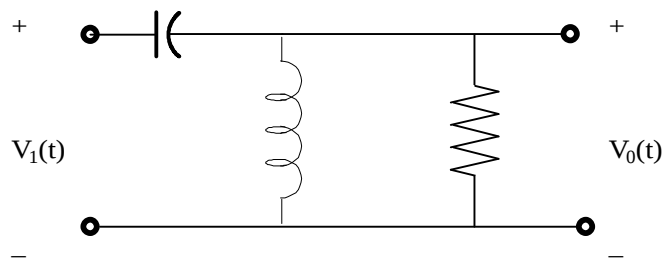Problem 11.54

Given the network in fig 11.54 sketch the magnitude characteristic of the transfer function.



Suggested Solution

$$Z_{EQ} = j\omega L \parallel (R) = \frac{j\omega L}{1 + j\omega L / R}$$

$$G_v(j\omega) = \frac{V_o}{V_1} = \frac{Z_{EQ}}{Z_{EQ} + j\omega L / C} = \frac{j\omega L}{j\omega L + \frac{1}{j\omega C} [j\omega L / R]}$$


$$G_v(j\omega) = \frac{(j\omega)^2}{(j\omega)^2 + 10j\omega + 100}$$

FIND FORM,
$$G_v(j\omega) = \frac{0.01(j\omega)^2}{(\frac{j\omega}{10})^2 + \frac{j\omega}{10} + 1}$$


NETWORK IS A HIGHPASS FILTER.

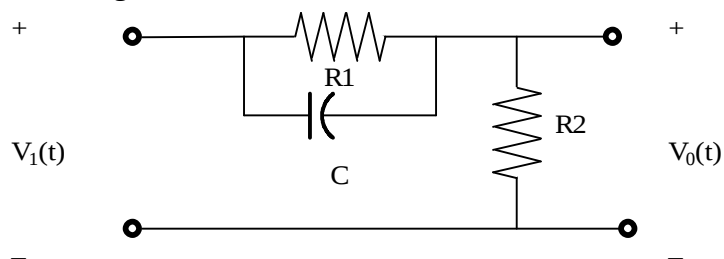Problem 11.57

Determine what type of filter the network shown in fig 11.57 represents by determining the voltage transfer function.



Suggested Solution

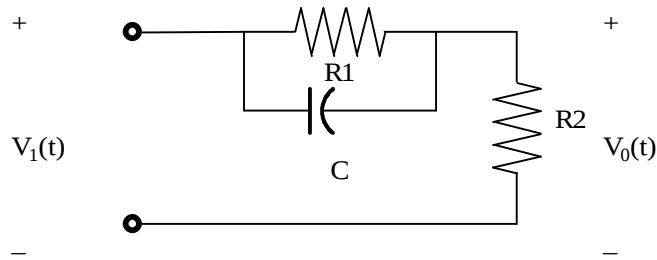

$$Z_{EQ} = R_1 \parallel \frac{1}{j\omega L} = \frac{j\omega L R_1}{R_1 + j\omega L}$$

$$G_V = \frac{V_O}{V_i} = \frac{R_2}{R_2 + Z_{EQ}} = \frac{(R_1 + j\omega L)R_2}{R_1 R_2 + j\omega L R_1 + j\omega L R_1}$$

$$G_V = \frac{1 + \frac{j\omega L}{R_1}}{1 + \frac{j\omega L}{R}}$$

$$R = R_1 \parallel R_2 < R_1$$

$$W_Z = \frac{R_1}{L}$$


$$W_P = \frac{R}{L}$$

$$W_P < W_Z$$


NETWORK IS A LOW-PASS FILTER.

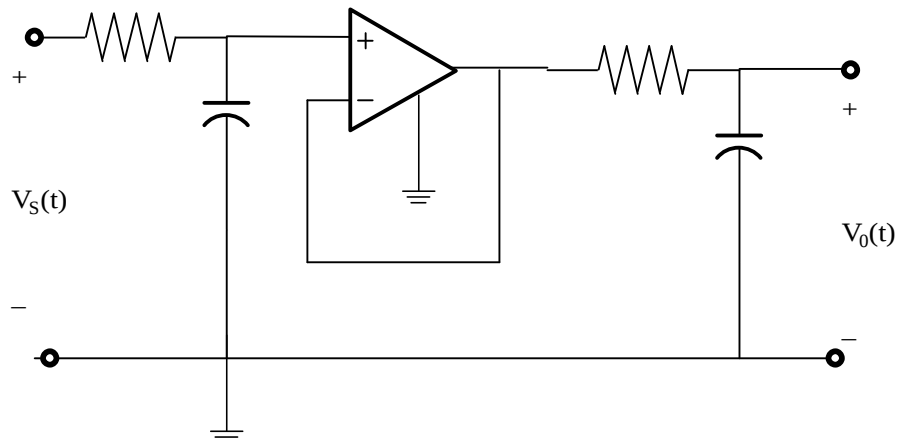Problem 11.59

Given the network shown in fig 11.59 and employing the voltage follower analyzed in chapter 3 determine the voltage transfer function and its magnitude characteristic. What type of filter does the network represent?



Suggested Solution

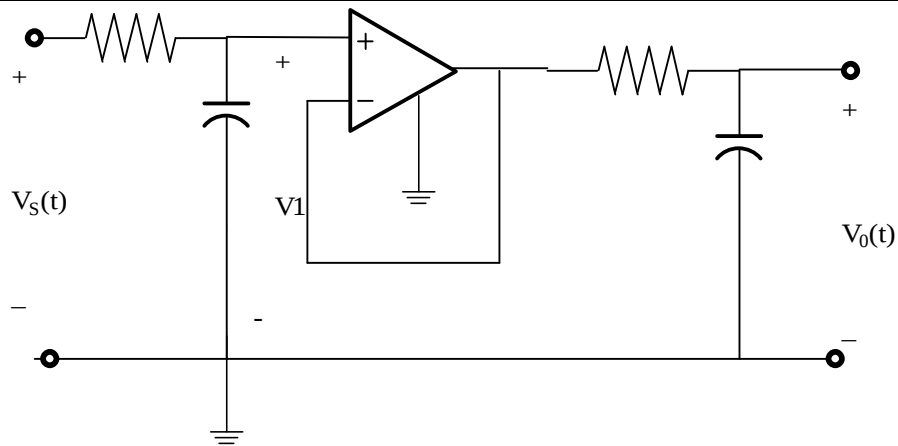

$$R = 1\Omega$$

$$C = 1F$$

$$\frac{V_1}{V_i} = \frac{1/j\omega}{(1/j\omega) + 1} = \frac{1}{1 + j\omega}$$

$$\frac{V_o}{V_1} = \left(\frac{1}{1 + j\omega} \right)^2$$

SECOND ORDER LOW-PASS