
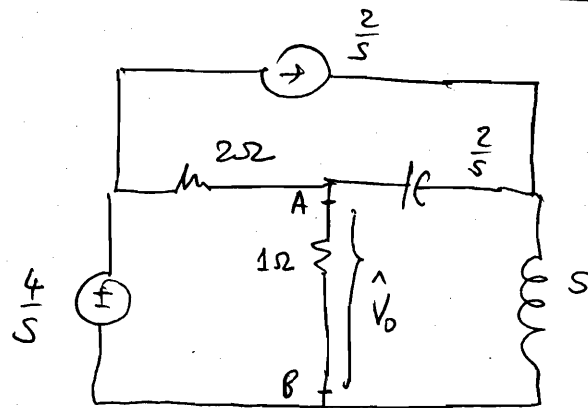


13.26 :

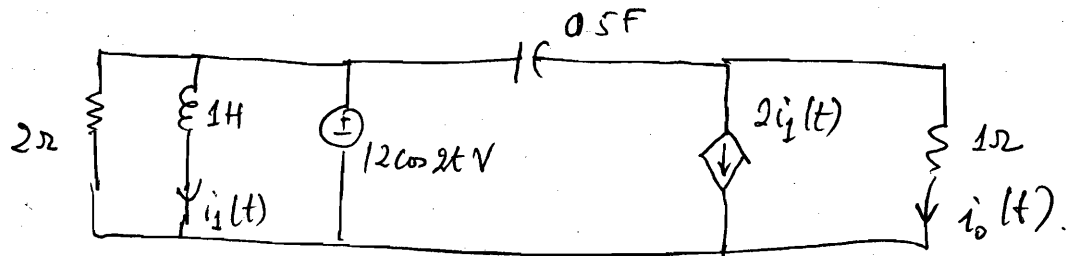

Find $\hat{V}_0$ then find $v_0(t)$

13.62 :



Find $\hat{I}_0$, then $i_0(t)$

$$V_o = \frac{V_{oc}(1)}{1+Z_{TH}} = \frac{8S+8/S}{S^2+2S+2+2S^2+4}$$

$$V_o = \frac{(8/3)(S^2+1)}{S(S^2+(2/3)S+2)}$$


$$A = 4/3$$

$$K|\theta = 1.273|10.05^\circ$$


$$V_o(t) = \left(\frac{4}{3} + 2.546e^{-t/3} \cos(\sqrt{17}t + 10.05^\circ)\right)V$$

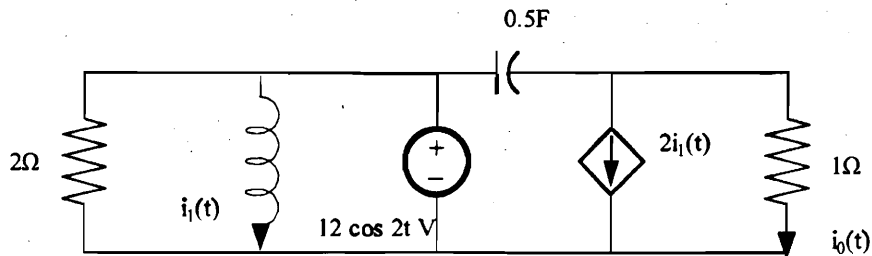Problem 13.62

Find the steady state response $i_o(t)$ for the network shown the fig.



Suggested Solution

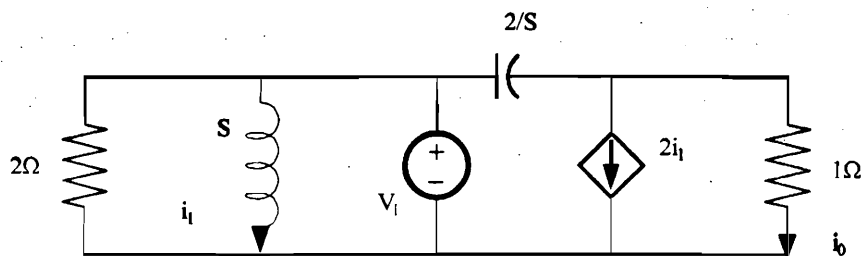

KCL

$$\frac{V_o}{1} + 2I_1 + (V_o - V_1) \frac{s}{2} = 0$$

$$I_o = V_o / 1, I_1 = V_1 / s$$

$$I_o + \frac{2V_1}{s} + I_o \left(\frac{s}{2} \right) - V_1 \left(\frac{s}{2} \right) = 0$$

or

$$I_o \left(1 + \frac{s}{2} \right) = V_1 \left(\frac{s}{2} - \frac{2}{s} \right) = V_1 \left(\frac{s^2 - 4}{2s} \right)$$

$$I_o \left(\frac{s+2}{2} \right) = V_1 \left(\frac{s^2 - 4}{2s} \right)$$

Finally

$$\frac{I_o}{V_1} = \frac{s-2}{s}$$

at steady state $s=j2$

$$V_i(t) = 12 \cos(2t)$$

$$\left. \frac{I_o}{V_i} \right|_2 = \frac{j2-2}{j2} = \sqrt{2} \angle 45^\circ$$

and

$$I_o = |V_i| \sqrt{2} \angle 45^\circ = 12\sqrt{2} \angle 45^\circ$$

$$I_o = 12\sqrt{2} \cos(2t + 45^\circ) A$$