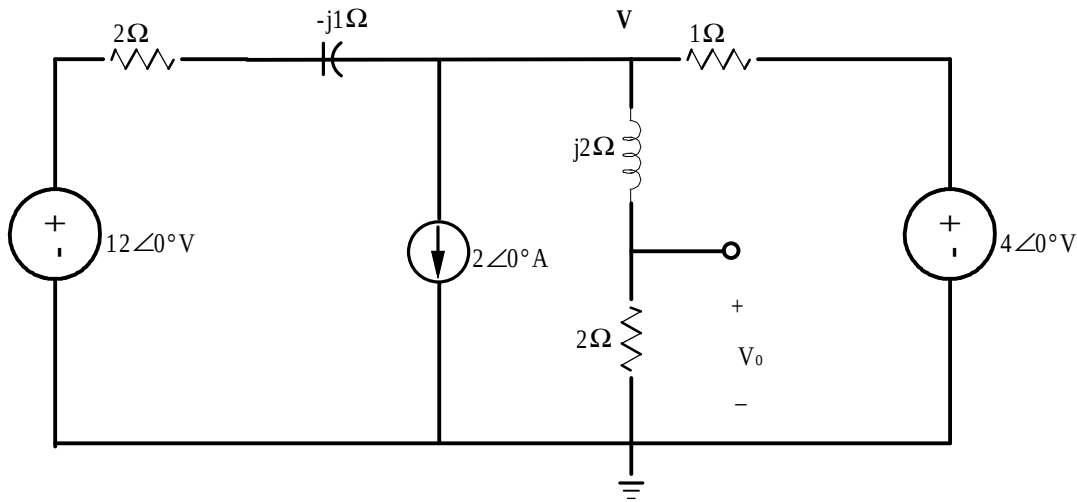


Problem 7.47

Find V_0 in the network shown using nodal analysis.



Suggested Solution

$$V_0 = V \left[\frac{2}{2 + j2} \right] = \frac{V}{\sqrt{2} \angle 45^\circ} = \frac{V}{1 + j1}$$

$$\frac{12 - V}{2 - j1} = 2 + \frac{V}{2 + j2} + \frac{V - 4}{1} = V \left[1 + \frac{1}{2 + j2} \right] - 2 = V \left[\frac{3 + j2}{2 + j2} \right] - 2$$

$$12 - V = V \left[\frac{(3 + j2)(2 - j1)}{2 + j2} \right] - 4 + j2 = V \left[\frac{8 + j1}{2 + j2} \right] - 4 + j2$$

$$16 - j2 = V \left[1 + \frac{8 + j1}{2 + j2} \right] = V \left[\frac{2 + j2 + 8 + j1}{2 + j2} \right]$$

$$16 - j2 = V \left[\frac{10 + j3}{2 + j2} \right]$$


$$V = \frac{4(8 - j1)(1 + j1)}{(10 + j3)}$$

$$V_0 = \frac{V}{1 + j1} = \frac{4(8 - j1)}{10 + j3} = \frac{32.25 \angle -7.13^\circ}{10.44 \angle 16.70^\circ}$$


$$V_0 = 3.09 \angle -23.83^\circ \text{ V}$$

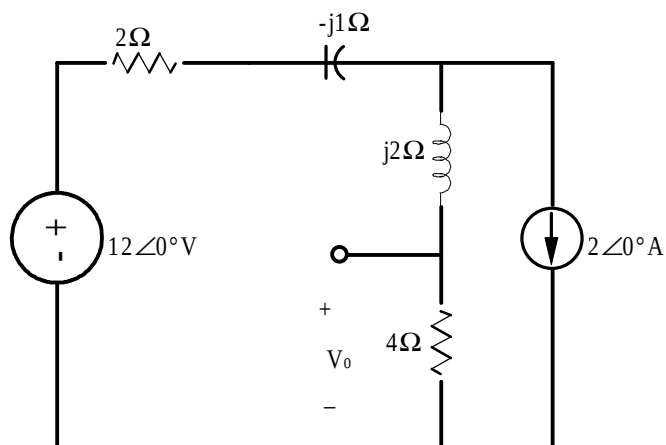Problem 7.58

Using superposition, find V_0 in the circuit shown.



Suggested Solution

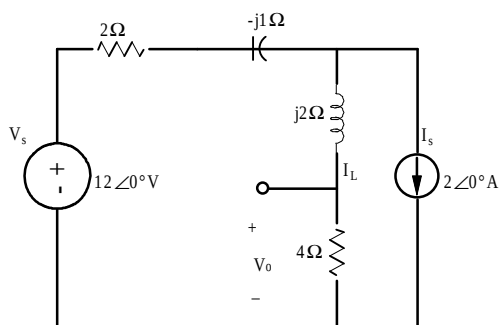

For the voltage source

$$V_1 = \frac{4}{4 + 2 + j2 - j1} (12\angle 0^\circ) = \frac{48}{6 + j1}$$

For the current source

$$I_L = I_s \left[\frac{2 - j1}{4 + 2 + j2 - j1} \right] = \frac{-4 + j2}{6 + j1}$$


$$V_2 = 4I_L = \frac{-16 + j8}{6 + j1}$$

Summing


$$V_0 = V_1 + V_2 = \frac{32 + j8}{6 + j1} = 5.41\angle 4.57^\circ \text{ V}$$

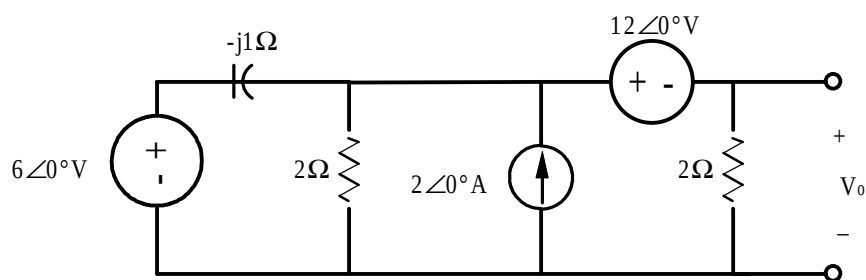Problem 7.60

Use source exchange to determine V_0 in the network shown.



Suggested Solution

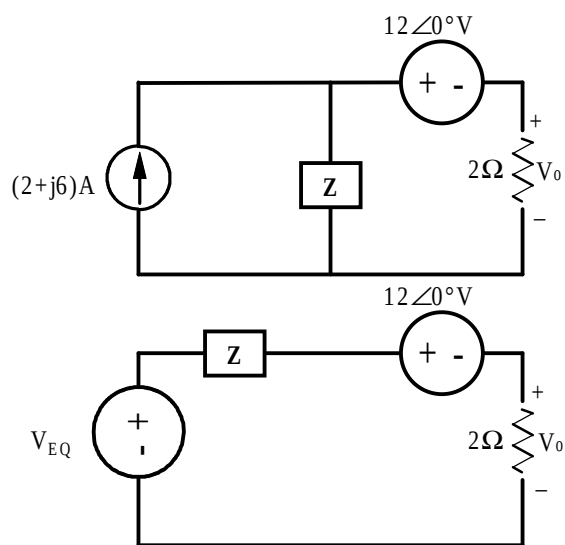


$$Z = 2 \parallel -j = \frac{-j2}{2-j1} = \frac{2}{1+j2}$$

$$V_{EQ} = (2+j6)(Z_{EQ}) = \frac{2(2+j6)}{1+j2} = 5.66\angle 8.13^\circ \text{V} = (5.60 + j0.80)\text{V}$$

$$V_0 = (V_{EQ} - 12) \left[\frac{2}{2+Z_{EQ}} \right] = (-6.4 + j0.8) \left[\frac{4}{3+j2} \right] = 7.16\angle 139.18^\circ \text{V}$$

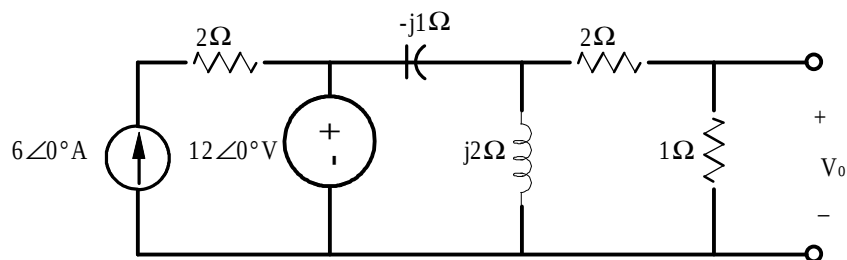Problem 7.63

Use Thevenin's theorem to find V_0 in the circuit shown.



Suggested Solution

