

Problem 8.11

Find V_o in the network in Figure P8.11


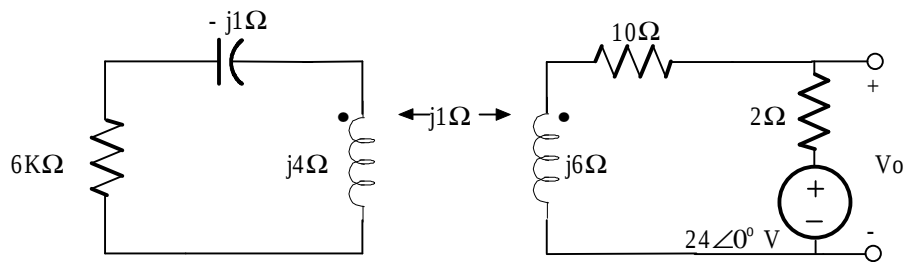


Figure 8.11

Suggested Solution

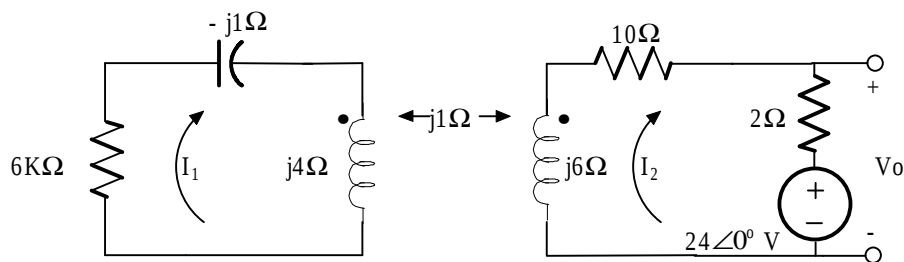

$$\begin{aligned}(6 + j3) I_1 - jI_2 &= 0 \\ -jI_1 + (12 + j6)I_2 &= -24 \\ V_o &= 2I_2 + 24\end{aligned}$$

$$\begin{aligned}I_1 &= jI_2 / (6 + j3) \Rightarrow -j (j / (6 + j3)) I_2 + (12 + j6) I_2 = -24 \\ I_2 &= -24(6 + j3) / (55 + j72) = -1.78 \angle -26.1^\circ\end{aligned}$$

$V_o = 2 I_2 + 24 = 20.86 \angle 4.32^\circ \text{ V}$

Problem 8.36

Determine the impedance seen by the source in the network shown in Figure P8.36


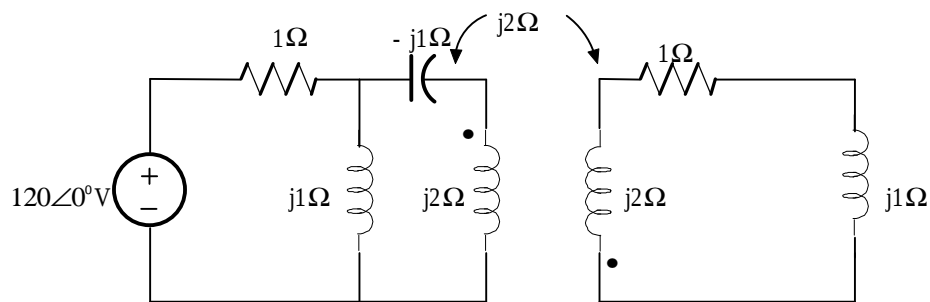


Figure P8.36

Suggested Solution

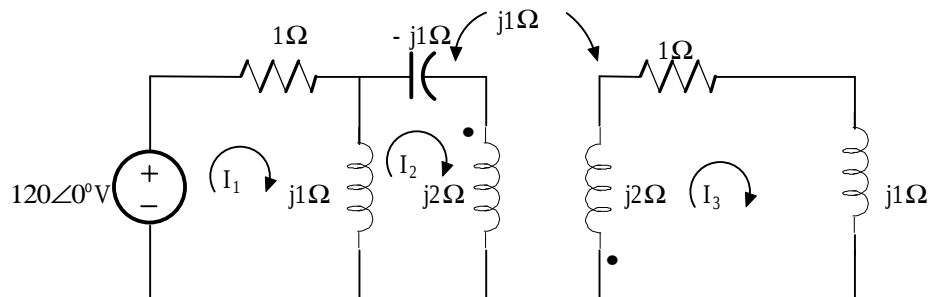

$$120 = I_1 (1 + j1) - j1 I_2 ; 0 = -j1 I_1 + j2 I_2 - j1 I_3 ; 0 = j1 I_2 + I_3 (1 + j3) \quad (1) \text{ (2) and (3)}$$

solve (3) for I_2 and substitute into (1) and (2)

$$I_2 = I_3 (-3 - j1) \Rightarrow 120 = I_1 (1 + j1) + I_3 (-1 - j3); 0 = -j1 I_1 + I_3 (2 + j5) \quad (4) \text{ and (5)}$$

Solve (5) for I_3 and substitute into (4)

$$I_3 = +j1 I_1 / (2 + j5)$$

$$120 = I_1 [1 + j1 - (1 + j3)(j1) / (2 + j5)] = I_1 [j6 / (2 + j5)]$$


$$Z_{\text{source}} = 120 / I_1 = (j6) / (2 + j5)$$

$$Z_{\text{source}} = 1.11 \angle 21.8^\circ \Omega$$

Problem 8.45

Determine the energy stored in the coupled inductors in the network in P8.44

Suggested Solution

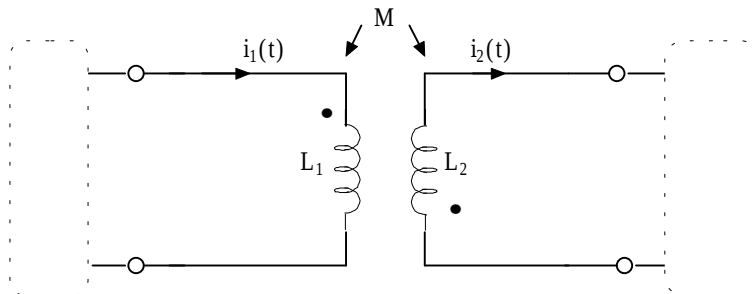

$$L_1 = L_2 = 4\text{H} \quad k = 0.8$$

$$M = 3.2\text{H}$$

From problem 11.32, $i_1(t)$ and $i_2(t)$ as defined here are

$$i_1(t) = -2.46 \cos(100t + 143.10) \text{ mA}$$

$$i_2(t) = 1.54 \cos(100t - 178.24) \text{ mA}$$

$$\omega(t) = \frac{1}{2} L_1 i_1^2(t) + \frac{1}{2} L_2 i_2^2(t) + M i_1(t) i_2(t)$$

Evaluate at $t = 2\text{ms}$

$$\omega(0.002) = 3.71 \mu\text{J}$$

Problem 8.53

Determine the input impedance seen by the source in the circuit in Figure P8.53


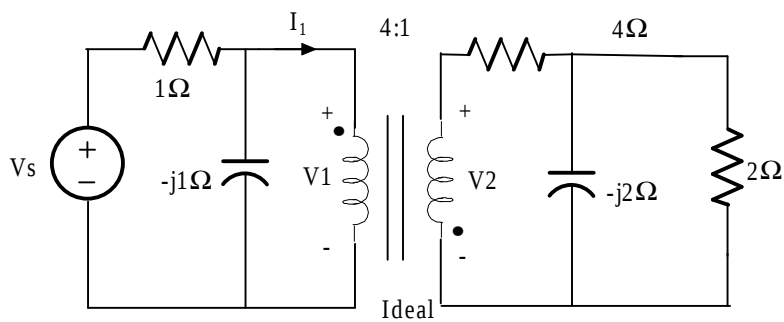


Figure P8.53

Suggested Solution

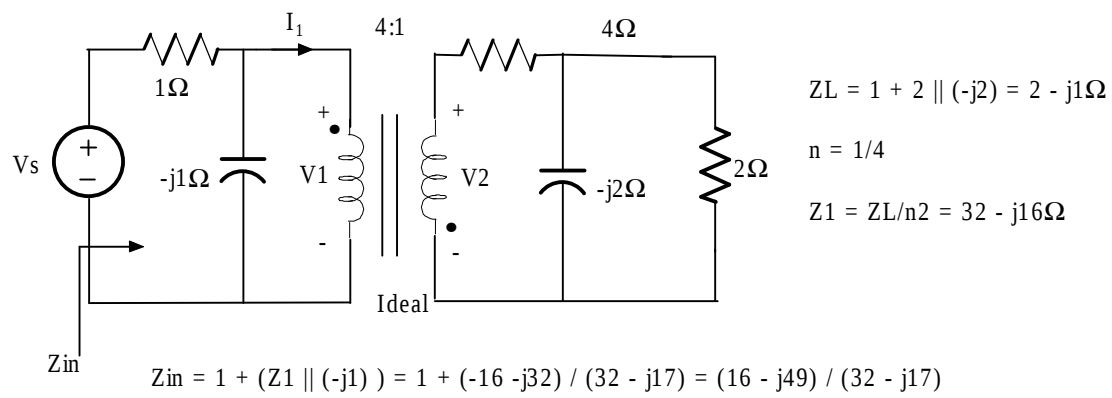

$Z_{in} = 1.42 \angle -43.94^\circ \Omega$
--