

# Circuit Analysis II

Sp '10

"Imaginary" Complex Numbers:  $\hat{z}$

$$j = \sqrt{-1} \quad \text{"imaginary factor"}$$

$$\hat{z} = \begin{cases} \bullet \text{Rectangular coordinates : } \hat{z} = x + jy & \begin{cases} \text{Re}[\hat{z}] = x \\ \text{Im}[\hat{z}] = y \end{cases} \\ \text{or Cartesian coords.} \end{cases}$$

$$\bullet \text{Polar coordinates : } \hat{z} = z e^{j\theta} \quad \begin{cases} z = \text{magnitude of } \hat{z} \\ \theta = \text{phase of } \hat{z} \text{ or angle w.r.t. Real axis.} \end{cases}$$

Having identified rectangular & polar coordinates on a same graph of  $\hat{z}$ , use trigonometry & geometry to establish connections between these two representations of a complex number  $\hat{z}$ .

$\xrightarrow{\text{Rect.}} \text{Polar : } \begin{cases} z = \sqrt{x^2 + y^2} & \text{(Pythagoras Theorem)} \\ \theta = \tan^{-1}\left(\frac{y}{x}\right) \end{cases}$	$\xrightarrow{\text{Polar}} \text{Rect. : } \begin{cases} x = z \cos \theta \\ y = z \sin \theta \end{cases}$
---	---

$\hat{z}_1 = \underbrace{-3+j4}_{\text{in 2nd quad}} \rightarrow \text{in polar form } \begin{cases} z_1 = \sqrt{9+16} = 5 \\ \theta_1 = \tan^{-1}\left(\frac{4}{-3}\right) = -53.13^\circ \end{cases} \quad \downarrow \quad \theta_1 = -53.13^\circ + 180^\circ = 126.87^\circ$

$$\hat{z}_2 = 3 - j4$$

↳ in 4<sup>th</sup> quadrant

$\theta_1 = -53.13^\circ \checkmark$   
(No need to fix!)

De Moivre formula:

$$e^{j\theta} = \cos \theta + j \sin \theta$$

↳  $e^{j\frac{\pi}{2}} = \underbrace{\cos \frac{\pi}{2}}_{0} + j \underbrace{\sin \frac{\pi}{2}}_{1} = j$

so the imaginary factor  $j$  has a phase of  $\frac{\pi}{2}$  or  $90^\circ \rightarrow$  This is consistent with the rectangular representation of a complex number where the imaginary part is along the Y-axis

What is the use of imaginary complex numbers in AC Circuit analysis?

• AC circuits : work with sinusoidal signals :

$$x(t) = A \cos(\omega t + \theta)$$

↓                    ↓                    ↓  
Amplitude      angular frequency      phase

• AC linear circuits : frequency is unchanged throughout circuit  $\rightarrow$  a sinusoid in AC circuit can be identified with only two out of three quantities :  $A, \theta$

Since imaginary complex numbers involve 2 quantities  $\rightarrow$   
a perfect match for a description of sinusoids in linear AC  
circuits.

"Phasors" = vectors with an amplitude and a phase.  
 $\rightarrow$  Our imaginary complex numbers will be ~~the~~ called "phasors"

$$x(t) = A \cdot \cos(\omega t + \theta)$$

$$= \operatorname{Re} [ A \cdot e^{j(\omega t + \theta)} ] = A \cdot \underbrace{\operatorname{Re} [ e^{j(\omega t + \theta)} ]}_{\cos(\omega t + \theta)}$$

↓  
no imaginary factor, it's a real number  
(de Moivre formula)

$$\downarrow$$

Properties of exponentials:  $e^{j(\omega t + \theta)} = e^{j\omega t} \cdot e^{j\theta}$

$$= \operatorname{Re} [ \underbrace{A \cdot e^{j\theta}}_{\text{phasor}} \underbrace{\dots e^{j\omega t}}_{\text{same everywhere in a linear AC circuit.}} ]$$


A sinusoid is associated with a phasor (or its real part)

## Comparing sinusoids using phasors:

- Phasors are vectors in the complex plane with a magnitude & a phase :

$\underline{Ae}^{j\theta}$  is a phasor with amplitude A & phase  $\theta$   
polar form of a complex number.

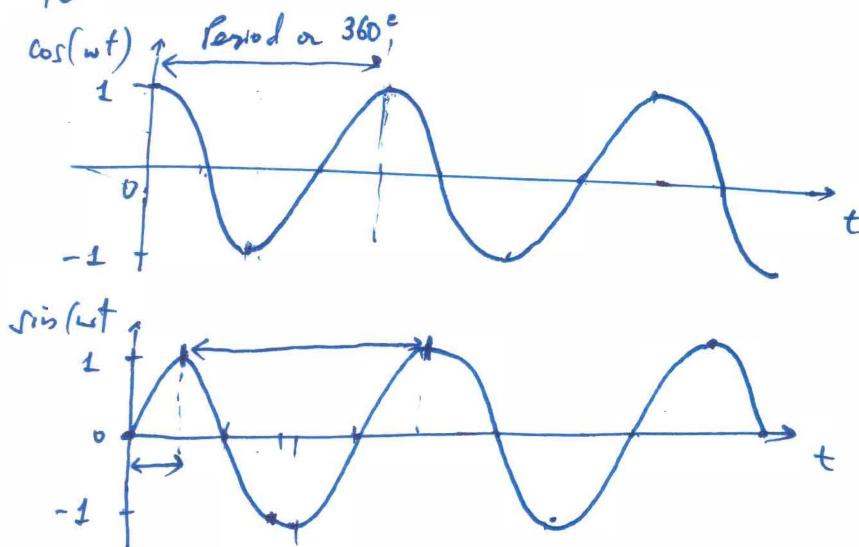- From trigonometry : cos is a sin with a phase shift of  $90^\circ$ :



If we shift  $\sin(wt)$  a quarter of a period to the left that is  $\cos(wt)$ . A quarter of a period is  $\frac{360^\circ}{4} = 90^\circ$  :

$$\cos(wt) = \sin(wt + 90^\circ)$$

Let's compare two sinusoids:  $\begin{cases} v_1(t) = 12 \sin(100t + 60^\circ) \\ v_2(t) = -6 \cos(100t + 30^\circ) \end{cases}$

(5)

$$= 12 \sin(100t - 30^\circ + 90^\circ)$$

$$\rightarrow v_1(t) = 12 \cos(100t - 30^\circ)$$

$$\rightarrow v_2(t) = 6 \cos(100t + 30^\circ - 180^\circ) = 6 \cos(100t - 150^\circ)$$

~~Clock~~ Counterclockwise (standard convention):

$v_1$  is ahead of  $v_2$  by  $120^\circ$


Using phasors: sinusoids are represented by vectors in the complex plane:

$$v_1(t) \rightarrow 12 e^{j(-30^\circ)} = \hat{v}_1$$

$$v_2(t) \rightarrow 6 e^{j(-150^\circ)} = \hat{v}_2$$

Im

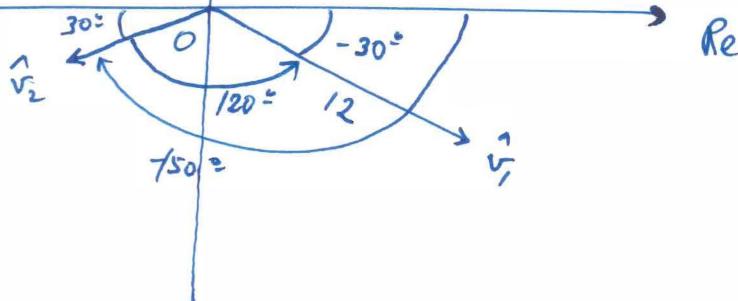$\hat{v}_1$  is ahead of  $\hat{v}_2$  by  $120^\circ$



Impedance are phasors in linear AC circuits.

Impedance = extension of the resistances


$$\hat{Z} = \frac{\hat{V}}{\hat{I}}$$

(ratios of complex values  
or phasors)

$$R = \frac{v}{i}$$

(ratios of real values)

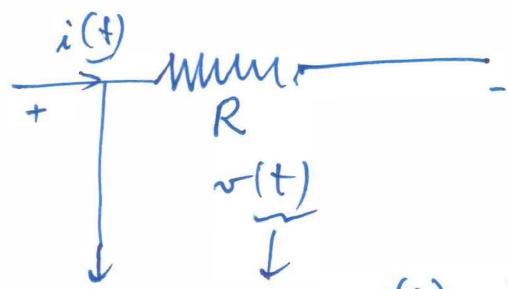What is the connection b/w  $\hat{Z}$  &  $R$  ?



By Ohm's law:

$$R = \frac{v(t)}{i(t)}$$

Linear AC circuits :  $i(t) = I \cos(\omega t + \theta_I) = \operatorname{Re}[I e^{j\theta_I} \cdot e^{j\omega t}]$   
 $v(t) = V \cos(\omega t + \theta_v) = \operatorname{Re}[V e^{j\theta_v} \cdot e^{j\omega t}]$

$$\operatorname{Re}[I e^{j\theta_I} \cdot e^{j\omega t}] = \operatorname{Re}[I e^{j(\omega t + \theta_I)}] = I \operatorname{Re}[e^{j(\omega t + \theta_I)}]$$

$$= I \operatorname{Re}[\underbrace{\cos(\omega t + \theta_I)}_{\hat{V} \text{ voltage phasor}} + j \sin(\omega t + \theta_I)]$$

$$= I \cos(\omega t + \theta_I)$$

$$R = \frac{v(t)}{i(t)} = \frac{\operatorname{Re}[V e^{j\theta_v} \cdot e^{j\omega t}]}{\operatorname{Re}[I e^{j\theta_I} \cdot e^{j\omega t}]} = \operatorname{Re}\left[\frac{V e^{j\theta_v}}{I e^{j\theta_I}}\right]$$

$$\operatorname{Re}\left[\frac{V e^{j\theta_v} \cdot e^{j\omega t}}{I e^{j\theta_I} \cdot e^{j\omega t}}\right] = \operatorname{Re}\left[\hat{Z}\right]$$

$\hat{I}$  current phasor

Discussion:

$$R = \operatorname{Re}[\hat{Z}]$$

$$\hat{Z} = \frac{\hat{V}}{\hat{I}} = \frac{V e^{j\theta_v}}{I e^{j\theta_I}} = \frac{V}{I} e^{j(\theta_v - \theta_I)}$$

$\theta_v$ : phase of voltage


$\theta_I$ : phase of current

At a resistor:  
voltage & current are  
in phase  $\theta_v - \theta_I = 0$

$$\boxed{\hat{Z}_R = \frac{V}{I} = R}$$

Impedance @ a resistor is  $R$

Impedance @ a capacitor:

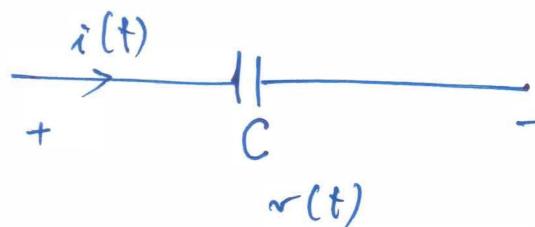

$$i(t) = C \frac{dv}{dt}$$

Linear AC circuits  $\rightarrow$   $i(t)$  &  $v(t)$  are sinusoids  
 $\downarrow$   
 $R, L, C$

$\rightarrow i(t) = I \omega_s (\omega t + \theta_I) = \operatorname{Re}[I e^{j\theta_I} \cdot e^{j\omega t}]$

$$\begin{aligned} \operatorname{Re}[I e^{j\theta_I} \cdot e^{j\omega t}] &= C \frac{d}{dt} \operatorname{Re}[V e^{j\theta_v} \cdot e^{j\omega t}] \\ &= C \operatorname{Re} \left[ \underbrace{V e^{j\theta_v}}_{\hat{V}} \cdot \underbrace{\frac{d}{dt} e^{j\omega t}}_{j\omega e^{j\omega t}} \right] \end{aligned}$$

(Voltage  
phase)

$$\operatorname{Re}[\hat{I} \cdot e^{j\omega t}] = C \operatorname{Re}[j\omega \hat{V} \cdot e^{j\omega t}] = \operatorname{Re}[j\omega C \hat{V} e^{j\omega t}]$$


$$\hat{I} \cdot e^{j\omega t} = j\omega C \cdot \hat{V} \cdot e^{j\omega t}$$

$$\frac{\hat{V}}{\hat{I}} = \frac{1}{j\omega C} \quad \text{or}$$

$$\hat{Z}_C = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

$$j \cdot j = \sqrt{-1} \cdot \sqrt{-1} = (-1)^{1/2} \cdot (-1)^{1/2} = (-1)^{1/2+1/2} = -1$$

Impedance @ an inductor :

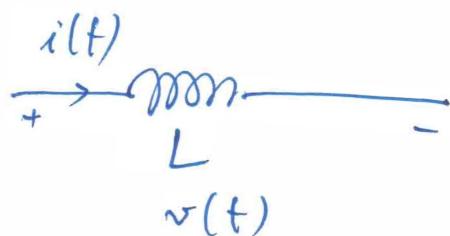

$$v(t) = L \frac{di}{dt}$$

linear AC circuits.


$$\operatorname{Re} [\underbrace{V e^{j\theta_v}}_{\hat{V}} \cdot e^{j\omega t}] = L \frac{d}{dt} \operatorname{Re} [\underbrace{I e^{j\theta_i}}_{\hat{I}} \cdot e^{j\omega t}]$$

$$= \operatorname{Re} [j\omega L \underbrace{I e^{j\theta_i}}_{\hat{I}} e^{j\omega t}]$$

$$\hat{V} e^{j\omega t} = j\omega L \hat{I} e^{j\omega t}$$

$$\frac{\hat{V}}{\hat{I}} = j\omega L \quad \text{or} \quad \boxed{\hat{Z}_L = j\omega L}$$
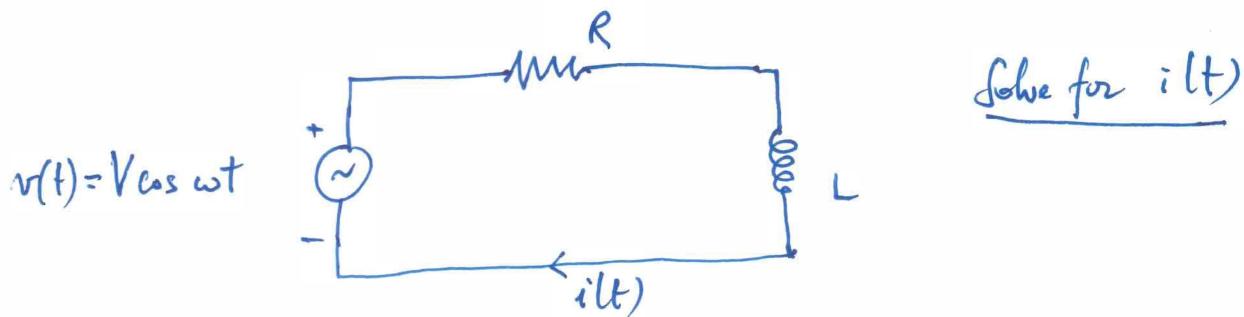
## Advantage in Using Phasors for Linear AC Analysis:



Method #1: using time-domain information

Loop Analysis:

$$V_{\text{cos} \omega t} = \underbrace{R \cdot i(t)}_{\substack{\text{potential} \\ \text{gain} \\ \text{across}}} + \underbrace{L \cdot \frac{di}{dt}}_{\substack{\text{potential} \\ \text{drop} \\ \text{across } L}}$$

AC source

Solve for  $i(t)$ :

- a) linear AC circuit  $\rightarrow$  sinusoid w/ same frequency  $\omega$  & different phase

$$i(t) = I \cos(\omega t + \theta)$$

↑ magnitude, ↑ phase  
2 unknowns!

b) Observation (freq.)

$$i(t) = I [\cos \omega t \cos \theta - \sin \omega t \sin \theta]$$

$$= \underbrace{I \cos \theta}_{\equiv I_1} \cos \omega t + \underbrace{\frac{I(-\sin \theta)}{\equiv I_2} \sin \omega t}$$

$$= I_1 \cos \omega t + I_2 \sin \omega t$$

(2 unknowns:  $I_1$  &  $I_2$ )

c) Plug  $i(t)$  into Loop Analysis's equation:

$$\left\{ \begin{array}{l} V_{loop} = R [I_1 \cos \omega t + I_2 \sin \omega t] + L \omega [-I_1 \sin \omega t + I_2 \cos \omega t] \\ V_{loop} = (RI_1 + \omega LI_2) \cdot \cos \omega t + (RI_2 - \omega LI_1) \cdot \sin \omega t \end{array} \right.$$

- Note:  $\cos \omega t$  &  $\sin \omega t$  are out of phase by  $90^\circ$  or perpendicular in a (phasors) complex plane.

$$\rightarrow \left\{ \begin{array}{l} RI_2 - \omega LI_1 = 0 \\ RI_1 + \omega LI_2 = V \end{array} \right. \quad \left. \begin{array}{l} \text{2 equations for 2} \\ \text{unknowns } I_1 \text{ & } I_2 \end{array} \right.$$

$\downarrow$

$$I_2 = \frac{\omega L}{R} I_1 \rightarrow RI_1 + \frac{(\omega L)^2}{R} I_1 = V$$

$$I_1 = \frac{R}{R^2 + (\omega L)^2} V$$

$$I_2 = \frac{\omega L}{R^2 + (\omega L)^2} V$$

- Write  $i(t) = I_1 \cos \omega t + I_2 \sin \omega t = I \cos(\omega t + \theta)$
- or write  $I$  &  $\theta$  in terms of  $I_1$  &  $I_2$

$$\left\{ \begin{array}{l} I = \sqrt{I_1^2 + I_2^2} \\ \theta = -\tan^{-1} \frac{I_2}{I_1} \end{array} \right. \quad \begin{array}{l} \text{b/c } I_1 = I \cos \theta \\ I_2 = -I \sin \theta \end{array}$$

$$\frac{I_2}{I_1} = -\tan \theta \rightarrow \theta = -\tan^{-1} \frac{I_2}{I_1}$$

(11)

$$I = \sqrt{\frac{R^2}{[R^2 + (\omega L)^2]} V^2 + \frac{(\omega L)^2}{[R^2 + (\omega L)^2]} V^2} = \frac{V}{\sqrt{R^2 + (\omega L)^2}}$$


$$I = \frac{V}{\sqrt{R^2 + (\omega L)^2}}$$

$$\theta = -\tan^{-1} \frac{I_2}{I_1} = -\tan^{-1} \left( \frac{\omega L}{R} \right)$$

$$i(t) = \frac{V}{\sqrt{R^2 + (\omega L)^2}} \cos \left( \omega t - \tan^{-1} \frac{\omega L}{R} \right)$$


Current in an AC RL circuit using Loop Analysis

Method #2 : using Phasors

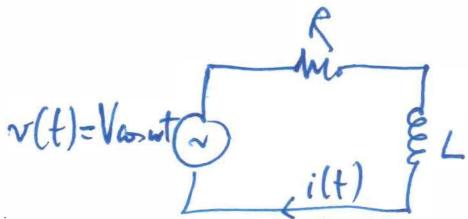

Time-domain

$$i(t) = I \cos(\omega t + \theta)$$

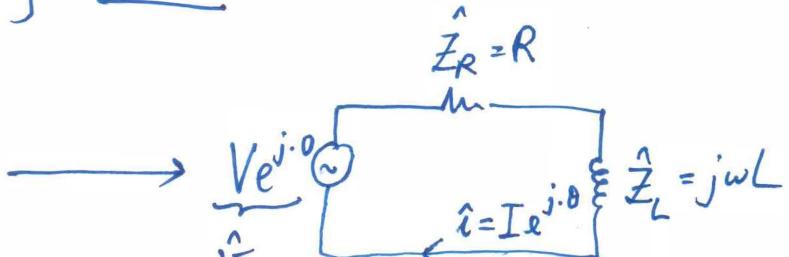

Frequency-domain

or Phasor version of  
same circuit.

Note: Ohm's Law is valid in both time & frequency domain! Find current phasor, then convert back into time-domain.

$$\hat{i} = \frac{\hat{v}}{\hat{Z}_R + \hat{Z}_L} = \frac{V e^{j·θ}}{R + j\omega L} = \frac{V}{R + j\omega L} =$$

$$i = \frac{V}{R+j\omega L} \quad \text{To get or write } i(t) = I \cos(\omega t + \theta) \quad (12)$$

→ just need the magnitude & phase of  $\frac{V}{R+j\omega L}$ :

$$I = \frac{|V|}{|R+j\omega L|} = \frac{V}{\sqrt{R^2 + (\omega L)^2}}$$

$$\begin{aligned} \theta &= \text{Angle}(V) - \text{Angle}(R+j\omega L) \\ &= \theta - \tan^{-1} \frac{\omega L}{R} \end{aligned}$$

$$i(t) = \frac{V}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t - \tan^{-1} \frac{\omega L}{R})$$


(1 page vs 2 pages)

$$\hat{z} = \frac{\hat{a}}{b} \quad \text{in polar coords.} \quad Ze^{j\theta_z} = \frac{ae^{j\theta_a}}{be^{j\theta_b}}$$

$$= \frac{a}{b} e^{j(\theta_a - \theta_b)}$$

$$\rightarrow \theta_z = \theta_a - \theta_b$$
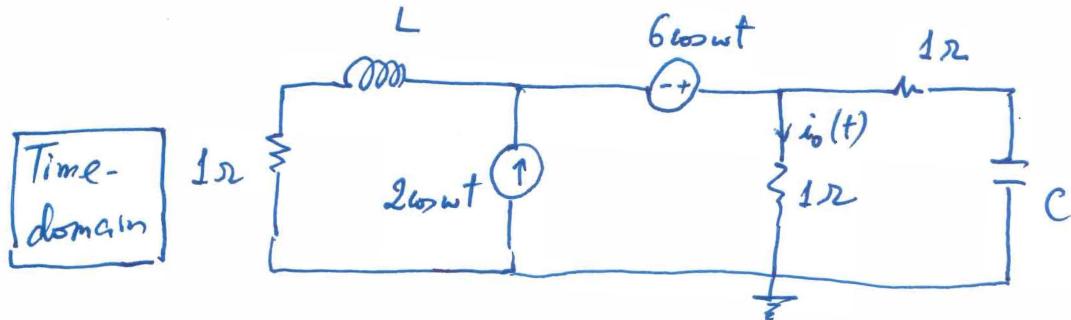
## Analysis Techniques AC Circuits using Phasors




$$L = 2.65 \text{ mH}$$

$$C = 2.65 \text{ mF}$$

$$\omega = 2\pi f; f = 60 \text{ Hz}$$

Solve for  $i_o(t)$

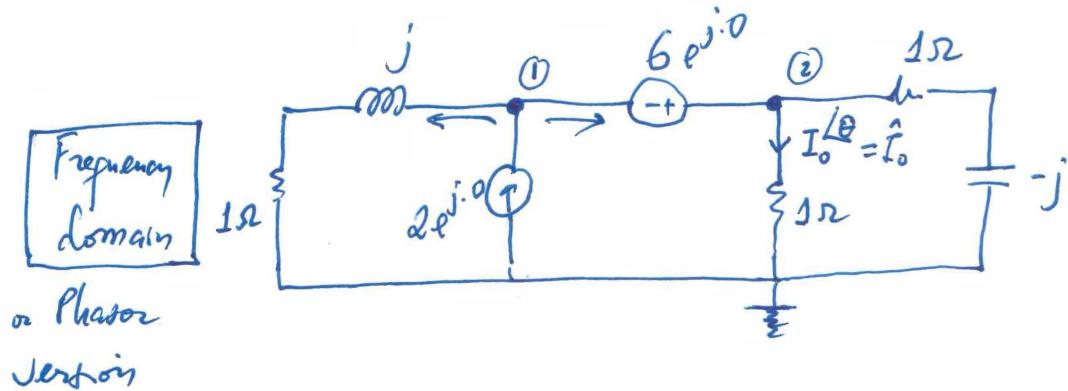

Different Methods

Solve for  $I_o$  &  $\theta$

$$i_o(t) = I_o \cos(\omega t + \theta)$$

$$\hat{Z}_L = j\omega L = j2\pi \cdot 60 \cdot 2.65 \cdot 10^{-3} = j1 = j$$

$$\hat{Z}_C = \frac{1}{j\omega C} = \frac{1}{j2\pi \cdot 60 \cdot 2.65 \cdot 10^{-3}} = \frac{1}{j} = -j$$

Note:

$$\begin{cases} 6e^{j0} = 6^{\angle 0} \\ Ze^{j\theta} = Z^{\angle \theta} \end{cases}$$


Node Analysis :

Step 1: Identify the nodes: 2 →  $\hat{V}_1$  &  $\hat{V}_2$  ( $\hat{V}_2 = \hat{V}_1 + 6$ )  
 → only one independent node, for example pick node #1

Step 2: Write Kirchoff's Law for currents @ node #1  
 $\sum_i I_i = 0$  { current into node : +  
 current leaving node : - }

(14)

Assuming

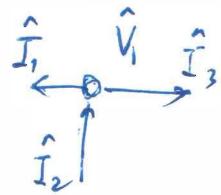

$$\text{Ohm's Law: } -\hat{I}_1 + \hat{I}_2 - \hat{I}_3 = 0$$

$$-\frac{\hat{V}_1}{1+j} + 2 - \left( \hat{V}_2 + \frac{\hat{V}_2}{1-j} \right) = 0$$

Plug-in  $\hat{V}_2 = \hat{V}_1 + 6$   
 $\hat{V}_1 = \hat{V}_2 - 6 \rightarrow -\frac{\hat{V}_2 - 6}{1+j} + 2 - \hat{V}_2 - \frac{\hat{V}_2}{1-j} = 0$

$$-\hat{V}_2 \left( \frac{1}{1+j} + 1 + \frac{1}{1-j} \right) + \frac{6}{1+j} + 2 = 0$$

$$\Rightarrow \hat{V}_2 = \frac{\frac{6}{1+j} + 2}{\frac{1}{1+j} + \frac{1}{1-j} + 1} = \frac{\frac{6+2j}{1+j}}{\frac{1-j+1+j}{2} + 1}$$

$$= \frac{\frac{8+2j}{1+j}}{2}$$

Multiplying complex conjugates:

$$(a+jb)(a-jb) = a^2 + b^2 = |a+jb|^2$$

↓  
Magnitude of.

$$= \frac{4+j}{1+j}$$

$$(1+j)(1-j) = 1+1 = 2$$


$$\frac{\hat{V}_2}{1+j} = \hat{V}_2 = \frac{4+j}{1+j} A = \frac{\sqrt{17} e^{j \tan^{-1}(1/4)}}{\sqrt{2} e^{j 45^\circ}} \stackrel{\sim 14^\circ}{=} 2.91 e^{j (-31^\circ)}$$

Need convert  
into polar form  
→ Magnitude & phase  
To go back to time-domain.

$$i_o(t) = 2.91 \cdot \cos(377t - 31^\circ) A$$

Loop Analysis (using the same circuit):

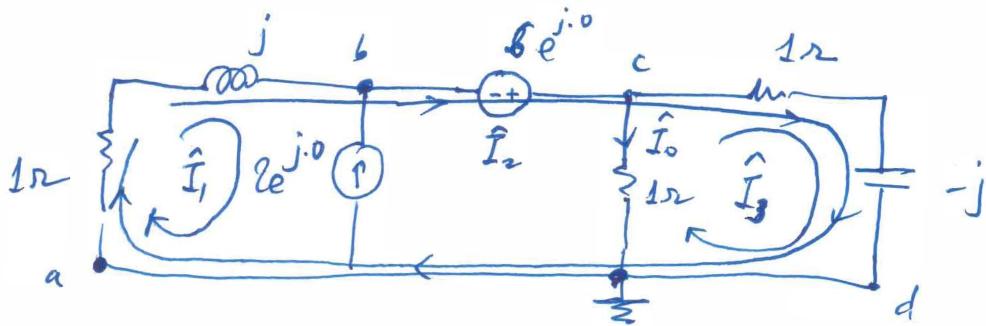Step 1: Identify the loops: 3 (3 small or 2 small + 1 big)



I<sub>1</sub>, I<sub>2</sub>  
CW CW

Step 2: Write Kirchhoff's law for voltage (KVL) for each of three loops

$$\begin{cases} 1) \quad \hat{I}_1 = -2A \quad (\hat{I}_1 \text{ was assumed to be CW}) \\ 2) \quad -( \hat{I}_1 + \hat{I}_2 )(1+j) + 6 - ( \hat{I}_2 + \hat{I}_3 )(1-j) = 0 \\ 3) \quad - \hat{I}_3 \cdot 1 - ( \hat{I}_2 + \hat{I}_3 ) \cdot (1-j) = 0 \end{cases}$$

Current x Impedance  $\rightarrow$  Potential drop.

Sign convention  $\left\{ \begin{array}{l} \text{Potential drop: -} \\ \text{Potential gain: +} \end{array} \right.$

3 eqs & 3 unknowns:  $\hat{I}_1, \hat{I}_2, \hat{I}_3$  solve for  $\hat{I}_3$  since  $\hat{I}_0 = -\hat{I}_3$

$$3) \quad -\underline{\hat{I}_3} - \underline{\hat{I}_3(1-j)} - \hat{I}_2(1-j) = 0$$

$$-\underline{\hat{I}_3} \frac{(1+1-j)}{(2-j)} - \hat{I}_2(1-j) = 0$$

$$\hat{I}_2 = -\underline{\hat{I}_3} \frac{(2-j)}{(1-j)}$$

Plugging this result back into 2):

$$-(-2 - \underline{\hat{I}_3} \frac{2-j}{1-j})(1+j) + 6 - \underbrace{\left( \hat{I}_3 - \underline{\hat{I}_3} \frac{2-j}{1-j} \right)}_{\hat{I}_3 \left( 1 - \frac{2-j}{1-j} \right)} (1-j) = 0$$

$$\hat{I}_3 \left( 1 - \frac{2-j}{1-j} \right) = \hat{I}_3 \left( \frac{-1}{1-j} \right)$$

(16)

$$\hat{I}_3 \left( \frac{2-j}{1-j} (1+j) + \frac{1-j}{1-j} \right) + 2(1+j) + 6 = 0$$

$$\hat{I}_3 \left( \frac{3+j + 1-j}{1-j} \right) + 8+2j = 0$$

$$\hat{I}_3 - \frac{4}{1-j} + 8+2j = 0$$

$$\hat{I}_3 = - \frac{8+2j}{\frac{4}{1-j}} = \frac{(8+2j)(1-j)}{-4}$$

$$= - \frac{10-6j}{4}$$

*4th quadrant*

$$\hat{I}_o = -\hat{I}_3 = \frac{10-6j}{4} = \frac{5-3j}{2} = \frac{\sqrt{34} e^{j \tan^{-1}(-\frac{3}{5})}}{2}$$



Need to convert  
to polar form.

$$\boxed{\hat{I}_o = 2.91 \angle j(-31^\circ)}$$


$$\boxed{i_o(t) = 2.91 \cos(377t - 31^\circ) \text{ A}}$$
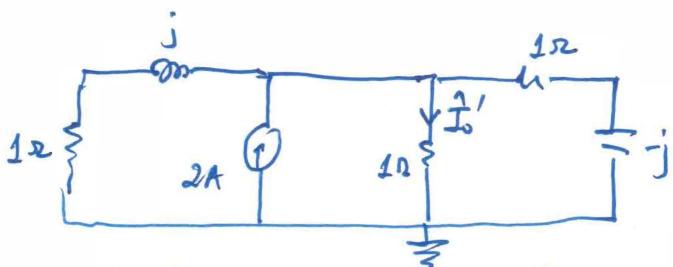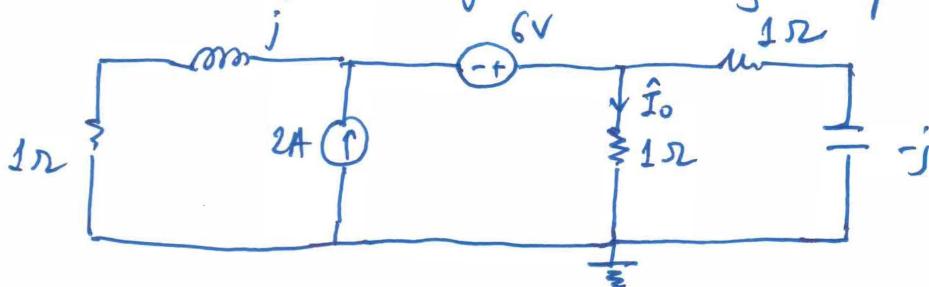
## Superposition Analysis:

If we have 2 or more sources in a same circuit, can combine results from single source using series/parallel combinations of impedances.




(Voltage source is short-circuited)

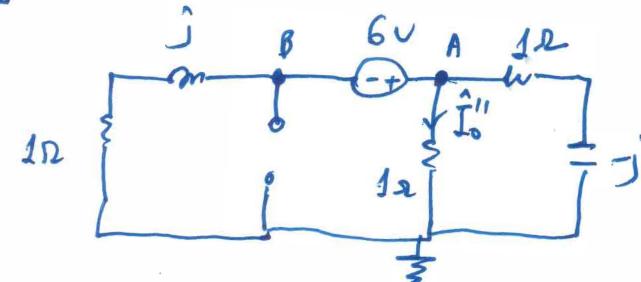

(Current source is open-circuited)

$$\hat{I}_o = \hat{I}_o' + \hat{I}_o''$$


Superposition Method.

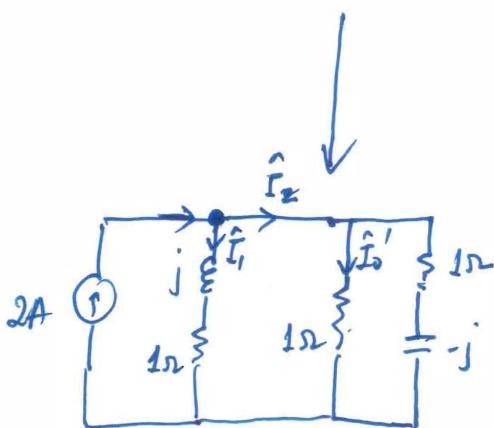

Current division:

$$\hat{I}_2 = 2A \frac{1+j}{1+j + \frac{1(1-j)}{2-j}}$$
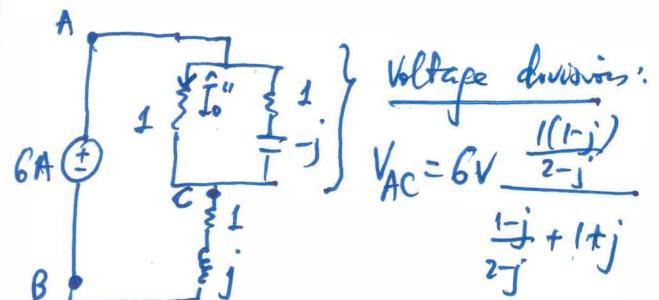
$$\begin{aligned} \hat{I}' &= \hat{I}_2 \cdot \frac{1-j}{2-j} \\ &= 2A \cdot \frac{1+j}{1+j + \frac{1-j}{2-j}} \cdot \frac{1-j}{2-j} \\ &= \frac{4A}{(1+j)(2-j) + 1-j} = \frac{4}{3+j+1-j} = 1A \end{aligned}$$



$$V_{AC} = 6V \frac{1-j}{1-j + (1+j)(2-j)} = 6V \frac{1-j}{1-j + 3+j}$$


$$V_{AC} = \frac{6}{4}(1-j)$$

$$\hat{I}_o'' = \frac{\frac{6}{4}(1-j)}{1} = \frac{3}{2}(1-j) A$$

$$\begin{cases} \hat{I}_o = \hat{I}_o' + \hat{I}_o'' = 1 + \frac{3}{2}(1-j) = \frac{5-3j}{2} \\ \text{Convert into polar form: } \sqrt{\frac{5^2 + 3^2}{2}} \angle \tan^{-1}(-\frac{3}{5}) = 2.91 \angle -31^\circ A \end{cases}$$
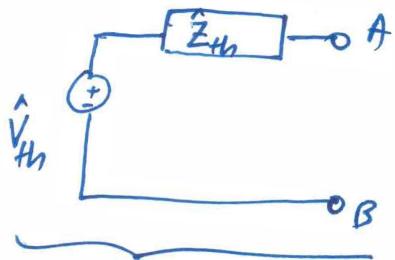
## AC Thvenin's Equivalent Analysis

To replace circuit b/w A & B by :  
 (without the element or  
 load between A & B)





Thvenin's equivalent  
 circuit b/w A & B

$$\hat{V}_{th} = \hat{V}_{o.c.} \text{ b/w A & B}$$


open circuit voltage between A & B

$$\hat{Z}_{th} = \hat{Z}_{Y_w A \& B} / w \text{ no source.}$$

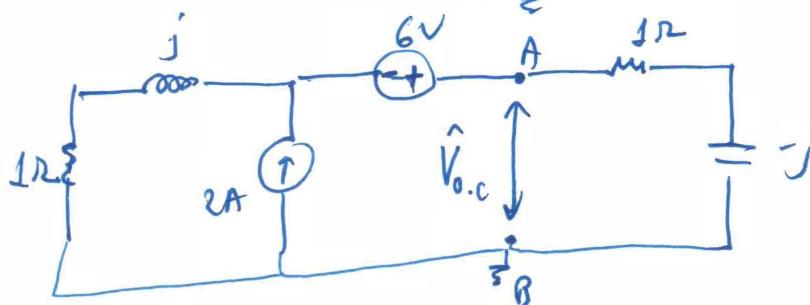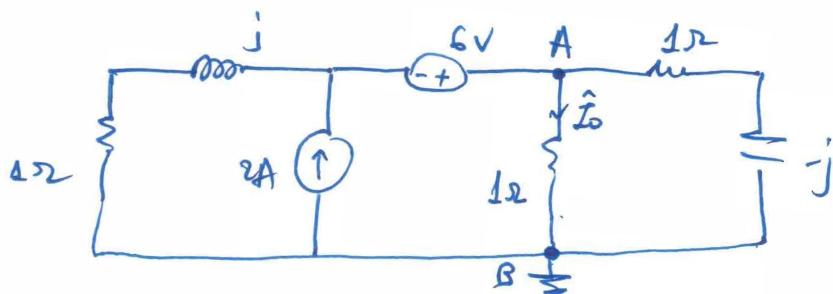Current source: open circuit  
 Voltage source: short-circuit.





Also use Source Exchange:

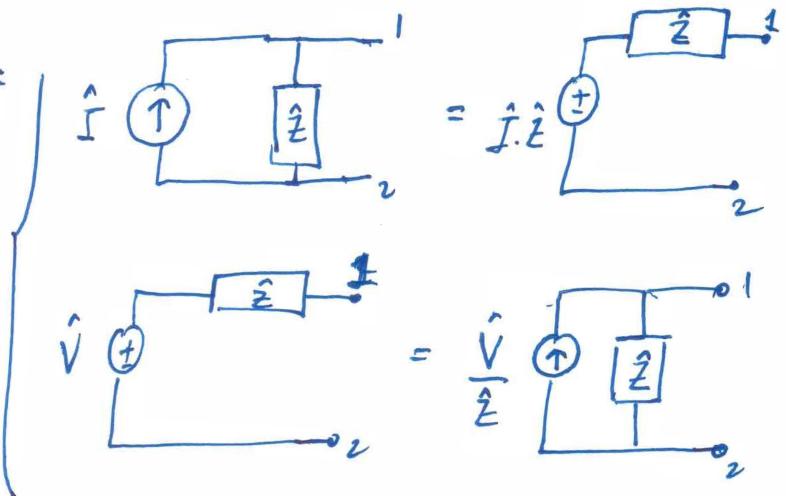

In our circuit:

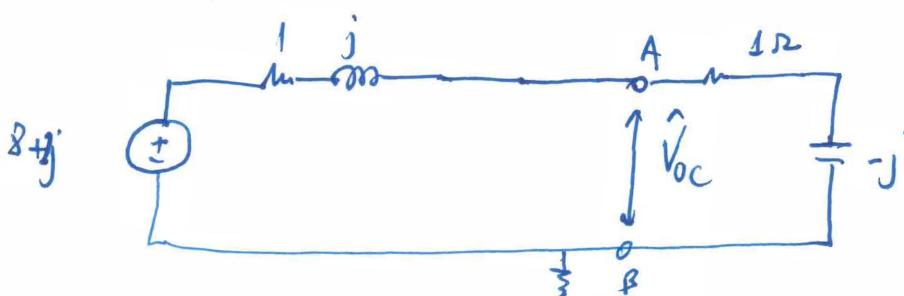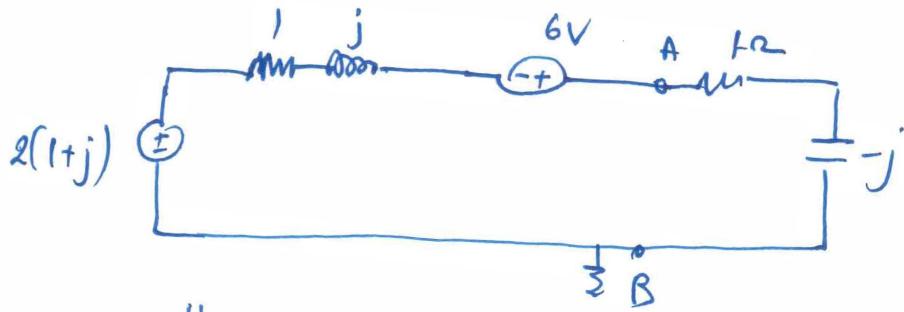
$$\begin{array}{c} j \\ \downarrow \\ \text{Circuit diagram: } \end{array} = \boxed{\text{Circuit diagram: } 2(1+j) V}$$




$$\begin{aligned} \text{Voltage division:} \\ \hat{V}_{oc} &= (8+j) \frac{1-j}{1+j + 1-j} \end{aligned}$$

$$\begin{aligned} &= (4+j)(1-j) \\ &= (5-3j) \text{ V} \end{aligned}$$


$\hat{Z}_{th}$ :

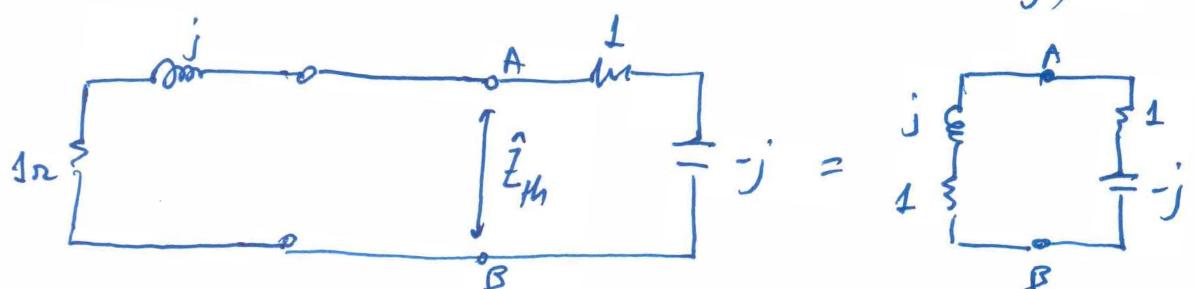
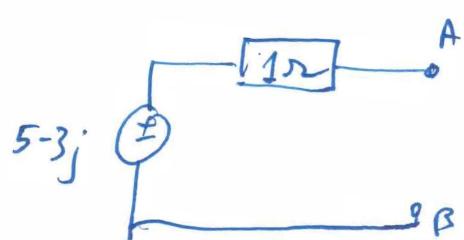
$$\hat{Z}_{th} = (1+j) // (1-j) = \frac{(1+j)(1-j)}{1+j + 1-j} = \frac{2}{2} = 1 \Omega$$




Now put back the load b/w A & B :

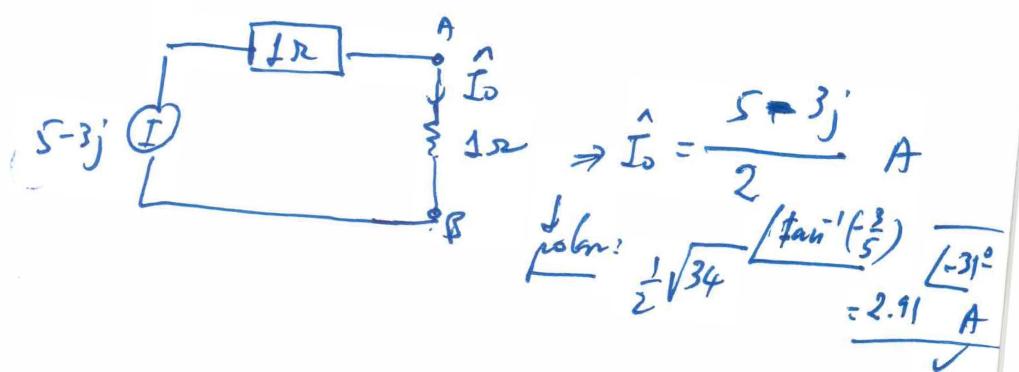

$$\begin{aligned} I_o &= \frac{5-3j}{2} \text{ A} \\ \text{Power: } &\frac{1}{2} \sqrt{34} \frac{\tan^{-1}(3/5)}{(-3)^2} = 2.91 \text{ A} \end{aligned}$$
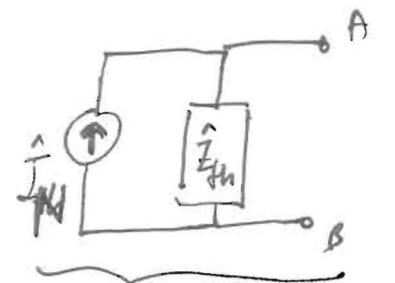
## AC Norton's Equivalent Analysis


↓  
To replace the circuit b/w A & B  
(without the load between A & B)



Norton's equivalent  
circuit b/w A & B


$$\hat{I}_N = \hat{I}_{(S.C.)} \text{ b/w A & B}$$
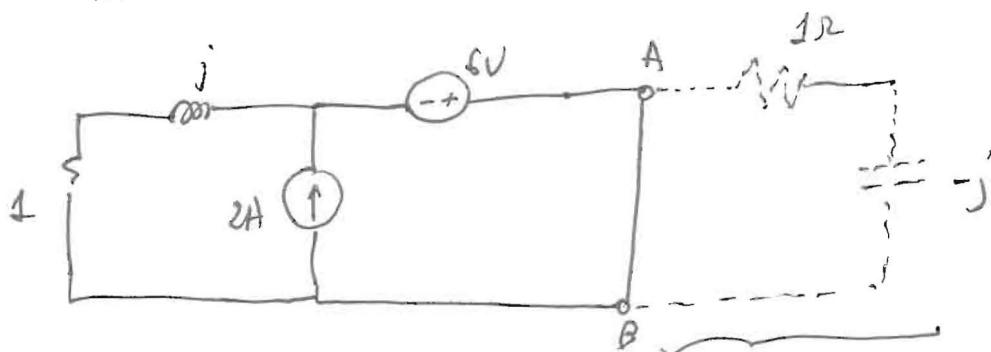
$$\hat{Z}_{th} = 1\Omega \rightarrow \underline{\text{short circuit}}$$




No current here if A & B  
are short-circuited!

Source Exchange on


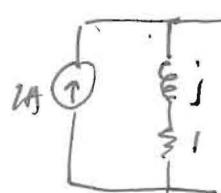

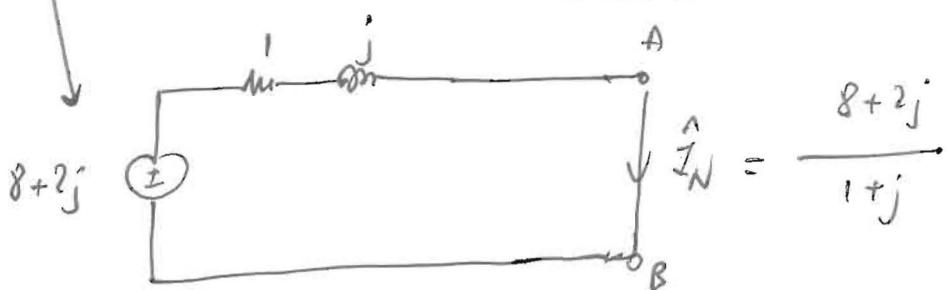
$$= 2+2j \text{ } \textcircled{1} \text{ } j$$



(21)

Norton's Equivalent :

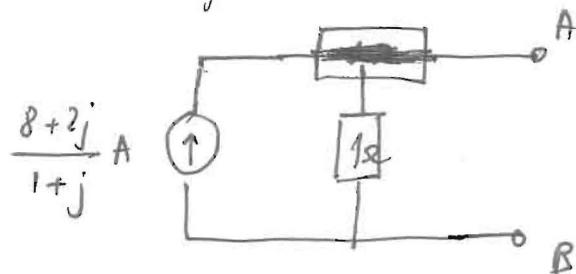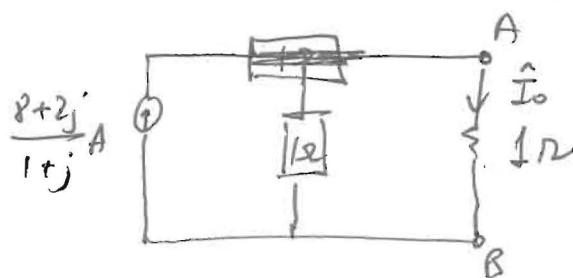Put back the load of  $1\Omega$  b/w A & B :

→ Current division :

$$\hat{I}_o = \frac{1}{2} \frac{8+2j}{1+j} = \frac{4+j}{1+j}$$

$$= \frac{(4+j)(1-j)}{2}$$

$$= \frac{5-3j}{2}$$

$$\rightarrow \text{Polar form: } \hat{I}_o = \frac{1}{2} \sqrt{34} \angle -\tan^{-1} \frac{3}{5} = 2.91 \angle -31^\circ \text{ A}$$

$$\rightarrow \text{Back to time domain: } i_o(t) = 2.91 \cos(377t - 31^\circ)$$

(22)


(7.38)

$$\hat{V}_s = 5.9 \angle -23.5^\circ V$$



$$\boxed{\hat{I}_0 = 2A} \rightarrow \hat{V}_s ?$$

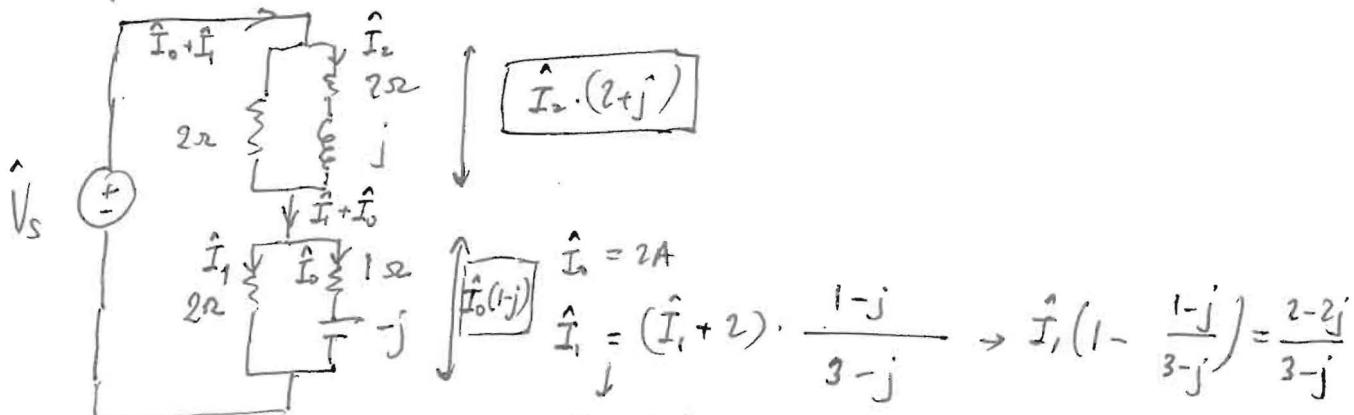Methods of Analysis: multiple, but first let's try parallel & series combination since there is only one source.



$$\hat{I}_0 = 2A$$

$$\hat{I}_1 = (\hat{I}_0 + 2) \cdot \frac{1-j}{3-j} \rightarrow \hat{I}_1 (1 - \frac{1-j}{3-j}) = \frac{2-2j}{3-j}$$

Current div.

$$\hat{I}_2 = \frac{\frac{2-2j}{3-j}}{1 - \frac{1-j}{3-j}} = \frac{2-2j}{3-j - 1+j} = 1-j$$

$$\rightarrow \text{Total current is } \hat{I}_0 + \hat{I}_1 + \hat{I}_2 = 2 + 1-j = 3-j$$

Getting  $\hat{I}_2$ :

$$(\text{Current div.}): \quad \hat{I}_2 = (3-j) \cdot \frac{2}{4+j}$$


$$\rightarrow \hat{V}_s = \hat{I}_2 (2+j) + \hat{I}_0 (1-j) = \frac{2(3-j)}{4+j} (2+j) + 2(1-j)$$

$$= 2 \cdot \frac{7+j + 5 - 3j}{4+j} = 2 \cdot \frac{12 - 2j}{4+j} = 4 \cdot \frac{6-j}{4+j}$$

$$\text{Polar form: } \hat{V}_s = 4 \frac{\sqrt{37}}{\sqrt{17}} \angle -\tan^{-1}\frac{1}{6} - \tan^{-1}\frac{1}{4} = 5.9 \angle -9.46^\circ - 14^\circ = 5.9 \angle -23.5^\circ \checkmark$$

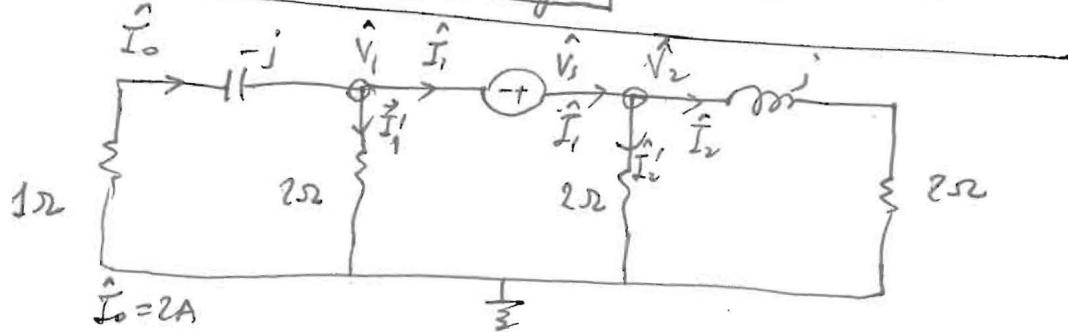(23)

Let's also use a Node Analysis on this same circuit.



→ Two nodes →  $\hat{V}_1$  &  $\hat{V}_2$

→ KCL @ each node:

$$\text{Node 1: } \hat{I}_o - \hat{I}_1 - \hat{I}_1' = 0$$

Write currents in terms of  $\hat{V}_1$  &  $\hat{V}_2$  using Ohm's Law:

$$\left[ \frac{0 - \hat{V}_1}{1-j} - \frac{\hat{V}_2 - 0}{2 \parallel (2+j)} - \frac{\hat{V}_1 - 0}{2} = 0 \right]$$

$$\text{Node 2: } \hat{I}_1 - \hat{I}_2 - \hat{I}_2' = 0$$

$$\hat{I}_1 = \hat{I}_2 + \hat{I}_2'$$

$$= \frac{\hat{V}_2}{2+j} + \frac{\hat{V}_2}{2} = \hat{V}_2 \left( \frac{1}{2+j} + \frac{1}{2} \right)$$

$$= \hat{V}_2 \cdot \frac{2+2j}{2(2+j)} = \frac{\hat{V}_2}{\cancel{\frac{2(2+j)}{2+2j}}}$$

$$= \frac{\hat{V}_2}{2 \parallel (2+j)} \quad (\text{we already used this info in Node #1})$$

→ Only need to solve for Node 1 equation!

$$2A = \hat{I}_o = \frac{-\hat{V}_1}{1-j} \rightarrow \hat{V}_1 = -2(1-j)$$

$$\rightarrow -\hat{V}_1 \left( \frac{1}{1-j} + \frac{1}{2} \right) - \hat{V}_2 \cdot \left( \frac{2+2j}{2(2+j)} \right) = 0$$

$$\chi(1-j) \frac{2+1-j}{z(v_j)} = \hat{V}_2 - \frac{4+j}{z(2+j)}$$

$$\hat{V}_2 = \frac{(3-j)}{4+j} z(2+j)$$

$$\hat{V}_x = \hat{V}_2 - \hat{V}_1 = 2 \frac{(3-j)(2+j)}{4+j} + 2(1-j)$$

$$= 2 \frac{7+j + (1-2j)(4+j)}{4+j} = 2 \frac{11+9j}{4+j}$$

$$= 2 \frac{7+j + 5-3j}{4+j} = 2 \frac{12-2j}{4+j}$$

$$= 4 \frac{6-j}{4+j} \rightarrow 4 \frac{\sqrt{37}}{\sqrt{17}} \angle -\tan^{-1}\frac{1}{6} - \tan^{-1}\frac{1}{4}$$

Polar form

$$= 5.9 \angle -23.5^\circ V \quad \checkmark$$

A

B


1

1

2

2

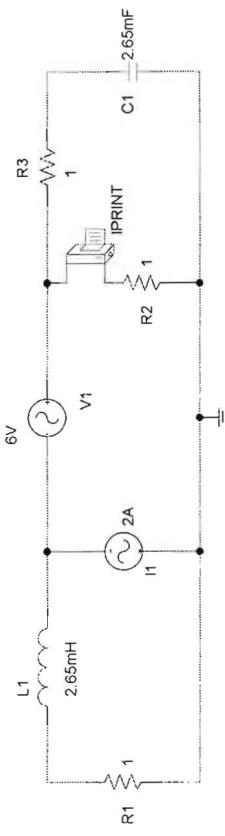- 1.- Implement circuit using Get New Parts  
In current sources IAC, current flows from + to -! For IPRINT, set AC=yes,  
MAG=yes, PHASE=yes
- 2.- Analysis/Setup then select AC Sweep  
with 1 points f=60Hz to 60Hz
- 3.- Analysis/Simulate
- 4.- Analysis/Examine Output, make sure current agrees with pencil and paper methods



Page Size: A

OrCAD, Inc.  
1321 S.W. 68th Parkway, Suite 200  
Beaverton, OR 97223  
(503) 671-9500 (800) 671-9505

B

A

V\_PRINT1 PRINT1(1=\$N\_0005 2=\$N\_0001 )

.ENDALIASES

\*\*\*\* RESUMING analysis\_example.cir \*\*\*\*

.probe

.END

02/11/10 13:57:46 \*\*\*\*\* Evaluation PSpice (Nov 1999) \*\*\*\*\*

\* G:\CMSDec1908\e232\Sp10\analysis\_example.sch

\*\*\*\* SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

\*\*\*\*\*

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(\$N_0001)	0.0000			(\$N_0002)	0.0000		
(\$N_0003)	0.0000			(\$N_0004)	0.0000		
(\$N_0005)	0.0000						

\*\*\*\*\*

VOLTAGE SOURCE CURRENTS

NAME	CURRENT
V_V1	0.000E+00
V_PRINT1	0.000E+00

TOTAL POWER DISSIPATION 0.00E+00 WATTS

02/11/10 13:57:46 \*\*\*\*\* Evaluation PSpice (Nov 1999) \*\*\*\*\*

\* G:\CMSDec1908\e232\Sp10\analysis\_example.sch

\*\*\*\* OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG C

\*\*\*\*\*

02/11/10 13:57:46 \*\*\*\*\* Evaluation PSpice (Nov 1999) \*\*\*\*\*

\* G:\CMSDec1908\e232\Sp10\analysis\_example.sch

\*\*\*\* AC ANALYSIS TEMPERATURE = 27.000 DEG C

Page 2

## analysis\_example.out

\*\*\*\*\*

FREQ IM(V\_PRINT1)IP(V\_PRINT1)

6.000E+01 2.917E+00 -3.095E+01


JOB CONCLUDED

*Agree with pencil + paper methods!*

TOTAL JOB TIME .20


□

(7.70)

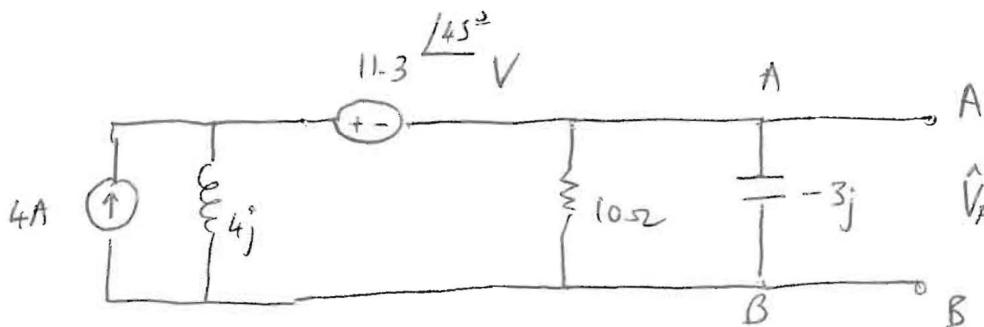


$\hat{V}_{AB}$  ? Use Norton's Theorem.


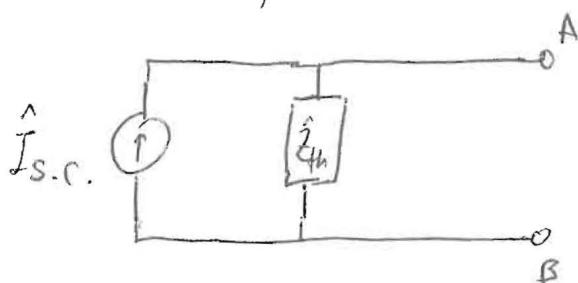
Norton's Equivalent b/w A & B without load -3j



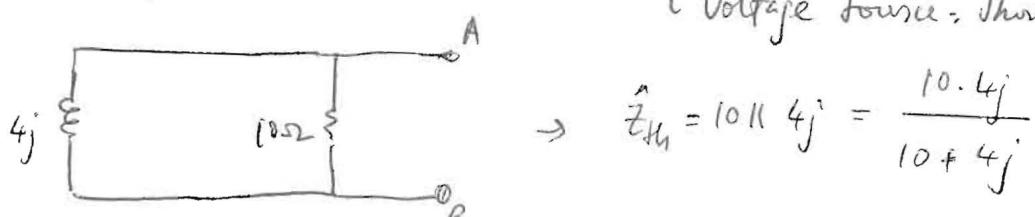$\hat{z}_{th}$  : equiv. impedance b/w A & B when  $\left\{ \begin{array}{l} \text{Current source: Open circuit} \\ \text{Voltage source: Short-circuit} \end{array} \right.$



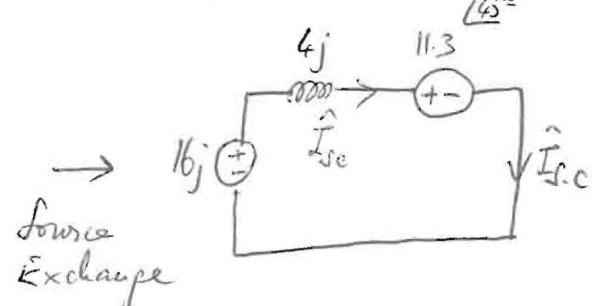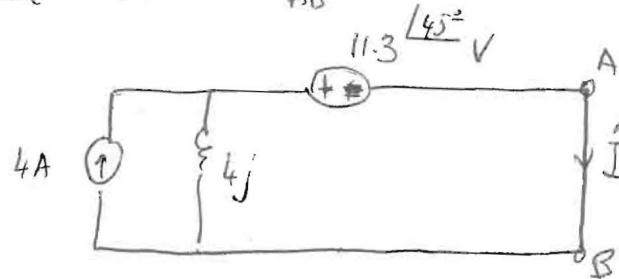$\hat{I}_{sc} = \hat{I}_N = \hat{I}_{AB}$  when load is short-circuited.




$$\hat{I}_{sc} = \frac{16j - 11.3(\cos 45^\circ + j \sin 45^\circ)}{4j} = \frac{16j - 7.99 - j7.99}{4j}$$

Ohm's Law

$$= \frac{-7.99 + 8.01j}{4j}$$
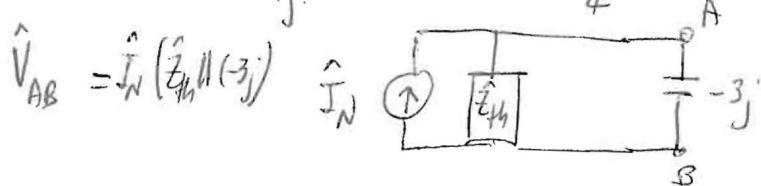
$$= \frac{11.3 \angle 135^\circ}{4 \angle 90^\circ} = 2.825 \angle 45^\circ \text{ A}$$



$$\hat{V}_{AB} = 2.825 \angle 45^\circ$$

$$\frac{\frac{40j(-3j)}{10+4j}}{\frac{40j}{10+4j} - 3j}$$

$$= 21.7 \angle 5.19^\circ$$

$$\frac{120}{40j - 30j + 12} = \frac{120}{12 + 10j} = 60 \frac{1}{\sqrt{36+25}} \angle \tan^{-1} \frac{5}{6}$$

$$= 7.68 \angle -39.8^\circ$$

1


2

B

A

(30)

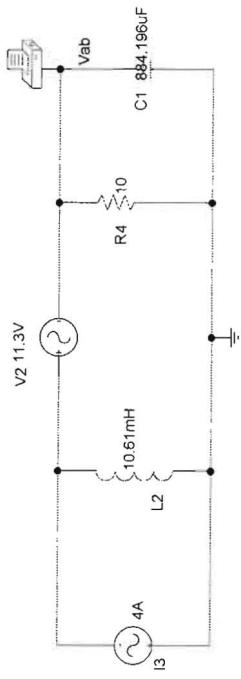- 1.- Implement circuit using Get New Parts in current sources IAC, current flows from + to -I. For VAC, set AC<sub>PHASE</sub>=45, L=4/377, C=1/(3\*377)=884uF  
For VPRINT1, set AC=yes, MAG=yes; PHASE=yes



- 2.- Analysis/Setup then select AC Sweep with 1 points f=60Hz to 60Hz

- 3.- Analysis/Simulate

- 4.- Analysis/Examine Output, make sure current agrees with pencil and paper methods

Page Size:

A

OrCAD, Inc.  
13221 S.W. 68th Parkway, Suite 200  
Beaverton, OR 97223  
(503) 671-9500 (800) 671-9505

2

A

B

1

(31)

7p70.out

\*\*\*\*\* 02/16/10 13:52:11 \*\*\*\*\* Evaluation PSpice (Nov 1999) \*\*\*\*\*  
\* G:\CMSDec1908\c232\Sp10\7p70.sch

\*\*\*\* CIRCUIT DESCRIPTION

\*\*\*\*\*

\* Schematics Version 9.1 - web update 1  
\* Tue Feb 16 13:52:04 2010

\*\* Analysis setup \*\*

.ac LIN 1 60 60  
.OP

\* From [PSPICE NETLIST] section of pspiceev.ini:  
.lib "nom.lib"

.INC "7p70.net"

\*\*\*\* INCLUDING 7p70.net \*\*\*\*  
\* Schematics Netlist \*

I\_I3 0 \$N\_0001 DC 0A AC 4A  
V\_V2 \$N\_0001 Vab DC 0V AC 11.3V 45  
R\_R4 0 Vab 10

.PRINT AC  
+ VM([Vab])  
+ VP([Vab])  
L\_L2 0 \$N\_0001 10.61mH  
C\_C1 0 Vab 884.196uF

\*\*\*\* RESUMING 7p70.cir \*\*\*\*  
.INC "7p70.als"

\*\*\*\* INCLUDING 7p70.als \*\*\*\*  
\* Schematics Aliases \*

.ALIASES  
I\_I3 I3(+=0 -=\$N\_0001 )  
V\_V2 V2(+=\\$N\_0001 -=Vab )  
R\_R4 R4(1=0 2=Vab )  
L\_L2 L2(1=0 2=\$N\_0001 )  
C\_C1 C1(1=0 2=Vab )  
-(Vab=Vab)  
.ENDALIASES

\*\*\*\* RESUMING 7p70.cir \*\*\*\*

(32)

7p70.out

.probe

.END

0 \*\*\*\* 02/16/10 13:52:11 \*\*\*\*\* Evaluation PSpice (Nov 1999) \*\*\*\*\*

\* G:\CMSDec1908\e232\Sp10\7p70.sch

\*\*\*\* SMALL SIGNAL BIAS SOLUTION TEMPERATURE = 27.000 DEG C

\*\*\*\*\*

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
------	---------	------	---------	------	---------	------	---------

( Vab)	0.0000	(\$N_0001)	0.0000				
--------	--------	------------	--------	--	--	--	--

VOLTAGE SOURCE CURRENTS  
NAME CURRENT

V\_V2 0.000E+00

TOTAL POWER DISSIPATION 0.00E+00 WATTS

0 \*\*\*\* 02/16/10 13:52:11 \*\*\*\*\* Evaluation PSpice (Nov 1999) \*\*\*\*\*

\* G:\CMSDec1908\e232\Sp10\7p70.sch

\*\*\*\* OPERATING POINT INFORMATION TEMPERATURE = 27.000 DEG C

\*\*\*\*\*

0 \*\*\*\* 02/16/10 13:52:11 \*\*\*\*\* Evaluation PSpice (Nov 1999) \*\*\*\*\*

\* G:\CMSDec1908\e232\Sp10\7p70.sch

\*\*\*\* AC ANALYSIS TEMPERATURE = 27.000 DEG C

\*\*\*\*\*

FREQ	VM(Vab)	VP(Vab)
------	---------	---------

6.000E+01	2.173E+01	5.129E+00
-----------	-----------	-----------

Agree with pencil & paper method.

▼

A

↑

A

1



2

1

2

- 1.- Implement circuit using Get New Parts  
Label the middle and right branches by  
double clicking them type in C and L,  
respectively

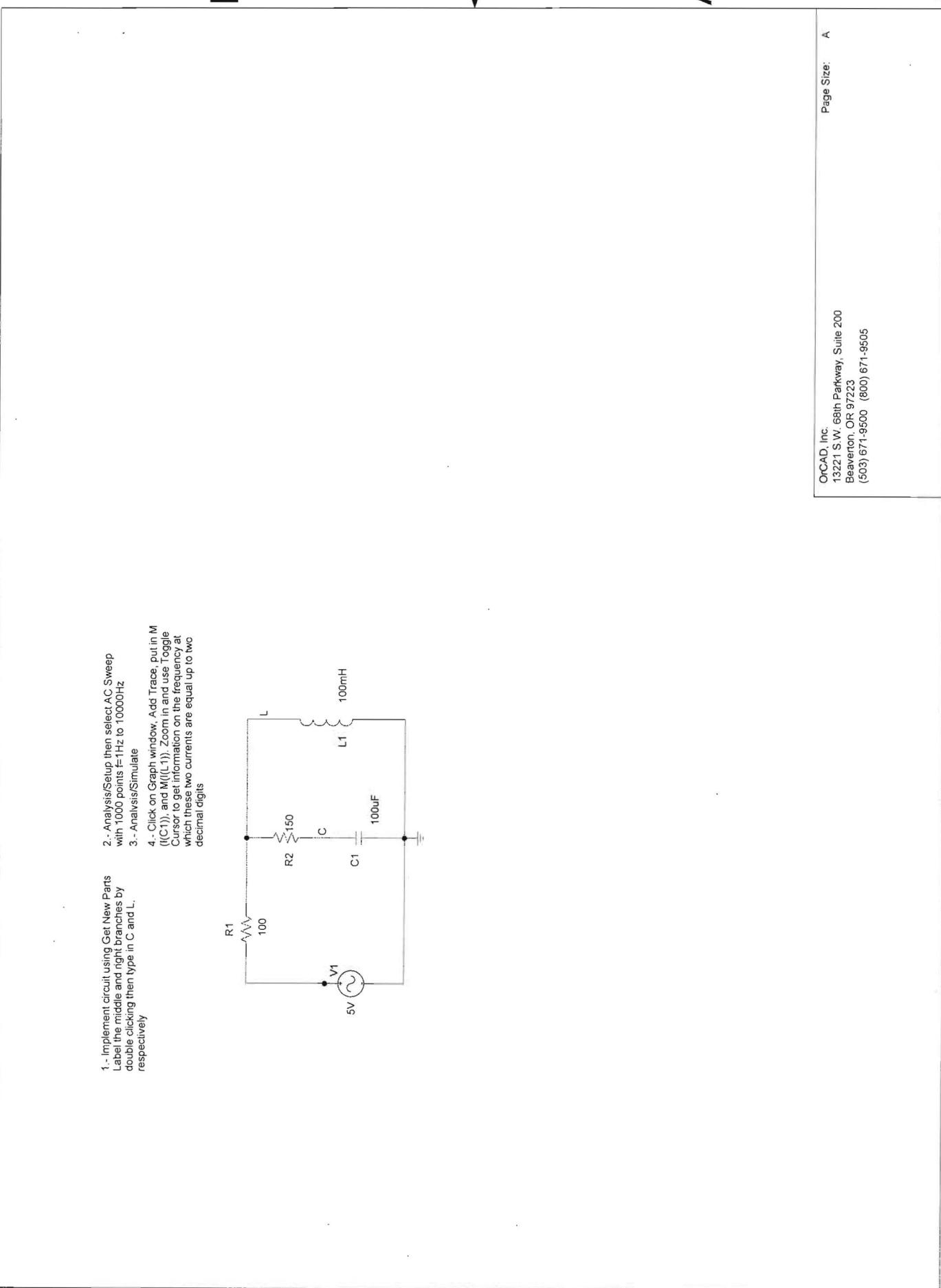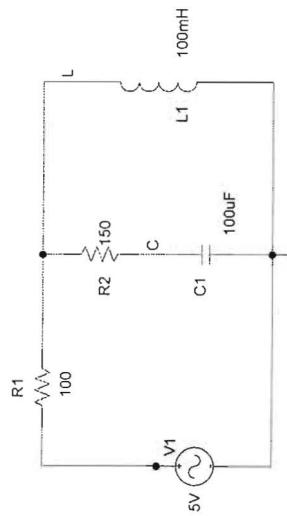
- 2.- Analysis/Setup then select AC Sweep  
with 1000 points f=1Hz to 10000Hz  
3.- Analysis/Simulate  
4.- Click on Graph window. Add Trace, put in M  
(I(C1), and M(I(L1)). Zoom in and use Toggle  
Cursor to get information on the frequency at  
which these two currents are equal up to two  
decimal digits



Date/Time run: 02/18/08 14:27:30

\* C:\Temp\232s07\7p76.sch

Temperature: 27.0

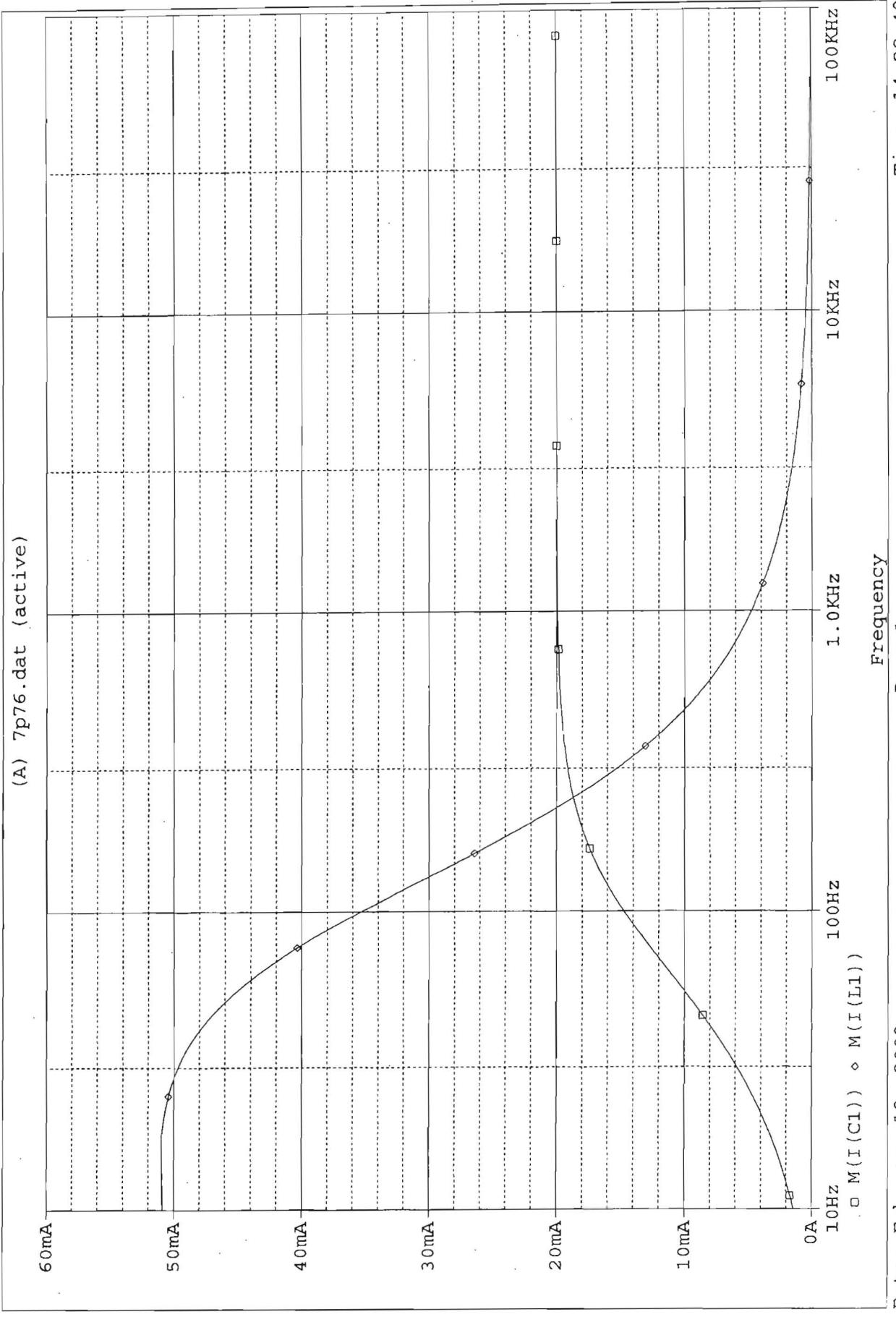

Date: February 18, 2008

Page 1

Time: 14:28:40

34

Date/Time run: 02/18/08 14:33:26

\* C:\Temp\232s07\7p76.sch

Temperature: 27.0

