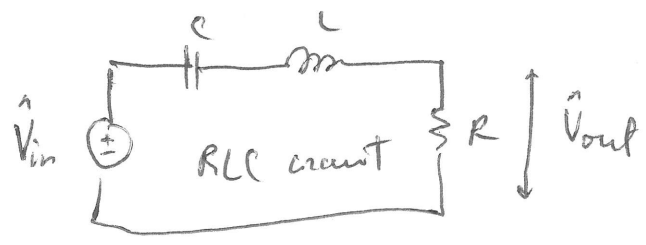


Variable Frequency Network (cont.)

Classifying variable-frequency circuits based on their transfer function (denominator).

Transfer function is a rational function in general: denominator dictates the behavior of a rational function. (if a numerator is 0 it is still o.k., but if a denominator is 0 $\rightarrow$ the function blows up!)



$$\frac{\hat{V}_{out}}{\hat{V}_{in}} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}}$$

It's not a linear response in frequency

Standard notation (Laplace Transforms are frequently used in AC circuit analysis): $j\omega \rightarrow s$

$$\frac{\hat{V}_{out}}{\hat{V}_{in}} = \frac{R}{\left(R + sL + \frac{1}{sC}\right) \times \frac{s}{L}} = \frac{\frac{R}{L}s}{\frac{R}{L}s + s^2 + \frac{1}{LC}}$$

polynomial form

Coefficient of highest order term in the polynomial has to be 1 if possible.

Denominator: a quadratic polynomial in s :

$$s^2 + \frac{R}{L}s + \frac{1}{LC}$$

Classifying circuit or the transfer function $\rightarrow$ look at different solutions for this quadratic polynomial:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$x^2 + bx + c = 0 \rightarrow \begin{cases} x_1 = \frac{-b + \sqrt{b^2 - 4c}}{2} \\ x_2 = \frac{-b - \sqrt{b^2 - 4c}}{2} \end{cases}$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \rightarrow \begin{cases} s_1 = \frac{-\frac{R}{L} + \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}}{2} = -\frac{R}{2L} + \frac{1}{2L} \sqrt{\frac{R^2 - 4L}{C}} \\ s_2 = -\frac{R}{2L} - \frac{1}{2L} \sqrt{\frac{R^2 - 4L}{C}} \end{cases}$$

Discriminant

Argument of the square root is the "discriminant" → it distinguishes

3 cases:

Case 1) $R^2 - \frac{4L}{C} = 0 \rightarrow$ one double root $s_1 = s_2 = -\frac{R}{2L}$

$$\frac{\hat{V}_{out}}{\hat{V}_{in}} = \frac{\frac{R}{L}s}{(s-s_1)(s-s_2)} = \frac{\frac{R}{L}s}{(s + \frac{R}{2L})^2}$$

This transfer function has a pole of order 2 @ $s_1 = -\frac{R}{2L}$

Case 2) $R^2 - \frac{4L}{C} > 0 \rightarrow$ two different roots:

$$s_{1,2} = -\frac{R}{2L} \pm \frac{1}{2L} \sqrt{|R^2 - \frac{4L}{C}|}$$

$$\frac{\hat{V}_{out}}{\hat{V}_{in}} = \frac{\frac{R}{L}s}{(s + \frac{R}{2L} - \frac{1}{2L} \sqrt{|R^2 - \frac{4L}{C}|})(s + \frac{R}{2L} + \frac{1}{2L} \sqrt{|R^2 - \frac{4L}{C}|})}$$

↳ This transfer function has two poles of order 1 or two simple poles.

Case 3) $R^2 - \frac{4L}{C} < 0 \rightarrow$ two complex conjugate roots:

$$s_{1,2} = -\frac{R}{2L} \pm \frac{j}{2L} \sqrt{\left| \frac{4L}{C} - R^2 \right|} \quad (\text{Recall } j \equiv \sqrt{-1})$$

$$\frac{\hat{V}_{out}}{\hat{V}_{in}} = \frac{\frac{R}{L}s}{\left(s + \frac{R}{2L} - \frac{j}{2L} \sqrt{\left| \frac{4L}{C} - R^2 \right|}\right) \left(s - \frac{R}{2L} + \frac{j}{2L} \sqrt{\left| \frac{4L}{C} - R^2 \right|}\right)}$$

$\rightarrow$ This transfer function has two complex conjugate poles.

In general: $\hat{H}(s) = \frac{\hat{V}_{out}(s)}{\hat{V}_{in}(s)} \quad \text{or} \quad \hat{H}(j\omega) = \frac{\hat{V}_{out}(j\omega)}{\hat{V}_{in}(j\omega)}$

$$(1) \quad \hat{H}(j\omega) = \frac{K_0 (j\omega)^{\pm N} (1 + j\omega\tau_1) [1 + 2\zeta_3 j\omega\tau_3 + (j\omega\tau_3)^2] \dots}{(1 + j\omega\tau_a) [1 + 2\zeta_b j\omega\tau_b + (j\omega\tau_b)^2] \dots}$$

τ_1 or "tau sub one"; ζ_3 or "xi sub three"; etc...

In our example:

$$(2) \quad \hat{H}(j\omega) = \frac{\frac{R}{L} j\omega}{(j\omega)^2 + \frac{R}{L} j\omega + \frac{1}{LC}} \quad \frac{\times LC}{\times LC} = \frac{RC j\omega}{LC(j\omega)^2 + RC j\omega + 1}$$

Bode plots: standard format: independent term should be 1.

Comparing (2) to (1): $K_0 = RC$; $N = +1$; $\tau_1 = 0$; $\tau_3 = 0$
 $\tau_a = 0$; $\tau_b = \sqrt{LC}$; $\zeta_b = \frac{RC}{2\sqrt{LC}} = \frac{R}{2} \sqrt{\frac{C}{L}}$
 $2\zeta_b \tau_b = RC \rightarrow \zeta_b = \frac{RC}{2\tau_b}$

τ_b will define critical points in the Bode plot; ζ_b will define the

Bode Plots

→ visualizing the frequency response of the transfer function or the circuit itself.



2 types $\left\{ \begin{array}{l} \text{Magnitude: plot of } 20 \log_{10} |\hat{H}(j\omega)| \text{ vs. } \omega \\ \text{Phase: plot of angle of } \hat{H} \text{ vs. } \omega \end{array} \right.$

Magnitude of a complex rational function:

Review:

$$\left\{ \begin{array}{l} 1) \left| \frac{\hat{z}_1 \cdot \hat{z}_2}{\hat{z}_3} \right| = \frac{|\hat{z}_1| \cdot |\hat{z}_2|}{|\hat{z}_3|} \\ 2) \log_{10} \frac{|\hat{z}_1| \cdot |\hat{z}_2|}{|\hat{z}_3|} = \log_{10} |\hat{z}_1| + \log_{10} |\hat{z}_2| - \log_{10} |\hat{z}_3| \end{array} \right.$$


3) $|j\omega| = \omega \cdot |j| = \omega$
 4) $\log_{10} \hat{z}_1^2 = 2 \log_{10} \hat{z}_1$

$$\begin{aligned} 20 \log_{10} |\hat{H}(j\omega)| &= 20 \log_{10} \frac{|k_o| \cdot |j\omega|^{\pm N} \cdot |1 + j\omega\tau_1| \cdot |1 + 2\zeta_3 j\omega\tau_3 + (j\omega\tau_3)^2| \dots}{|1 + j\omega\tau_a| \cdot |1 + 2\zeta_b j\omega\tau_b + (j\omega\tau_b)^2| \dots} \\ &= 20 \log_{10} |k_o| + 20 \log_{10} \omega^{\pm N} + 20 \log_{10} |1 + j\omega\tau_1| \\ &\quad + 20 \log_{10} |1 + 2\zeta_3 j\omega\tau_3 + (j\omega\tau_3)^2| + \dots \\ &\quad - 20 \log_{10} |1 + j\omega\tau_a| - 20 \log_{10} |1 + 2\zeta_b j\omega\tau_b + (j\omega\tau_b)^2| - \dots \end{aligned}$$

To sketch Bode Plot of any transfer function: learn how to sketch each of these typical terms:

- 1) $20 \log_{10} |k_o|$
- 2) $\pm 20 \log_{10} \omega$
- 3) $\pm 20 \log_{10} |1 + j\omega\tau|$
- 4) $\pm 20 \log_{10} |1 + 2\zeta_b j\omega\tau_b + (j\omega\tau_b)^2|$

1) $20 \log_{10} |K_o|$ vs. ω $\rightarrow$ normally in log scale = to include a large range of frequency to include very small, intermediate & very large frequencies.

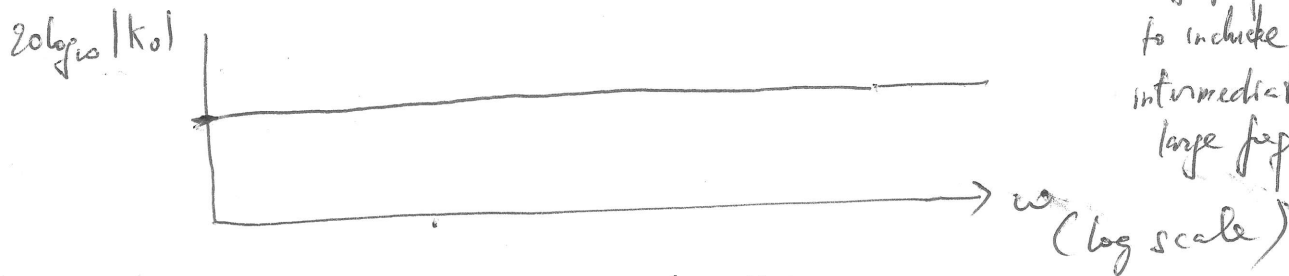

Whatever initial value it has, it will keep the same value throughout the entire ω -axis.

ω	$\log_{10} \omega$
0.001	-3
0.1	-1
1	0
10	1
1000	3

2) $\pm 20N \log_{10} \omega$ vs. ω $\rightarrow$ log scale.

