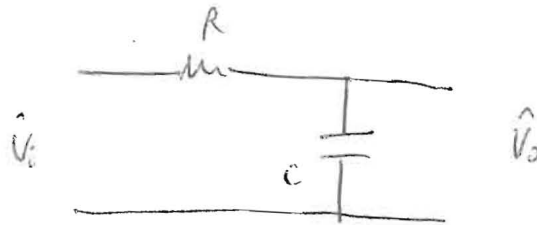


Passive Low-Pass


(92)




$$\hat{H}(j\omega) = \frac{\hat{V}_o}{\hat{V}_i} : \text{passing } \hat{V}_i \text{ to } \hat{V}_o \text{ @ low frequencies.}$$

$$= \frac{1}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} \rightarrow \boxed{\omega_c = \frac{1}{RC}}$$

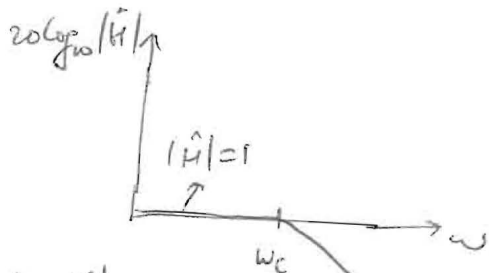(see PSPACE example for numerical confirmation)





Passive High-Pass

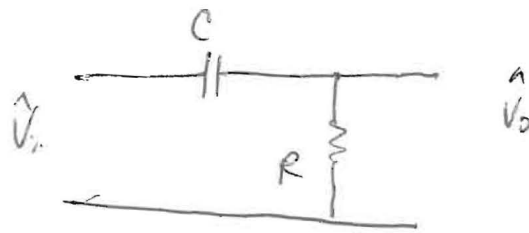

$$\hat{H}(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$



is passing $\hat{V}_i$ to $\hat{V}_o$ @ high frequencies.

$$\boxed{\omega_c = \frac{1}{RC}}$$

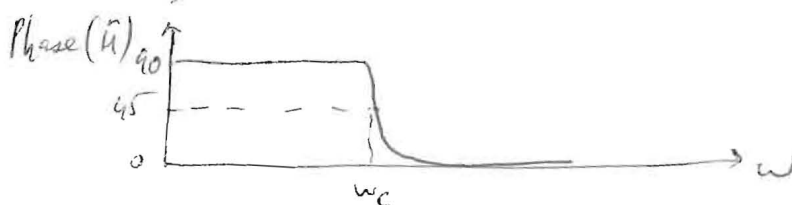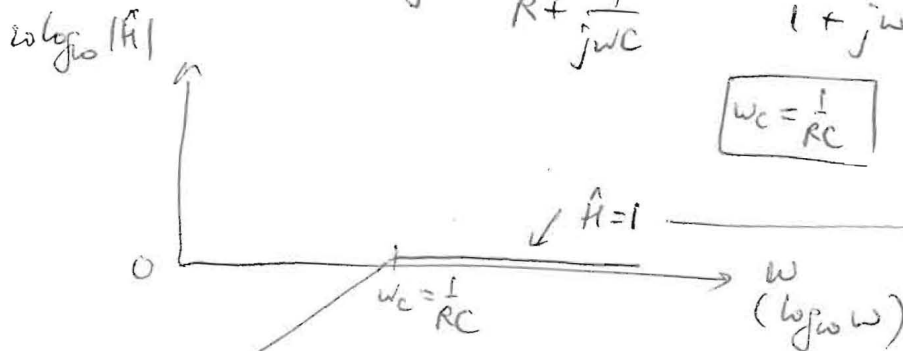


Passive Band-Pass

1)

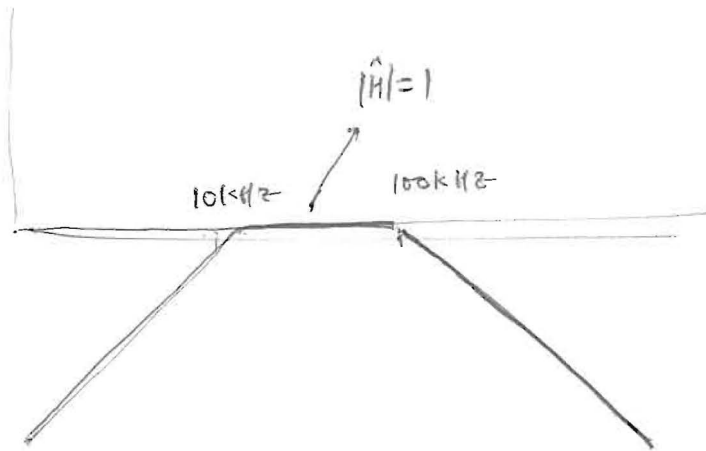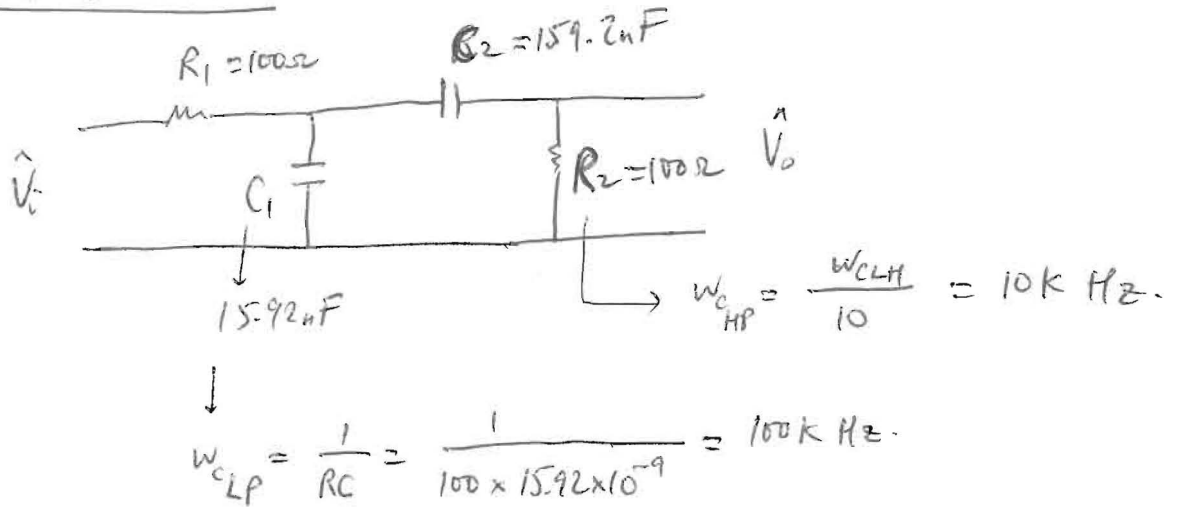

This circuit is passing $V_i \rightarrow V_o$ when $10 \text{ K} < \omega < 100 \text{ K}$

2) Using R, L, C circuit.

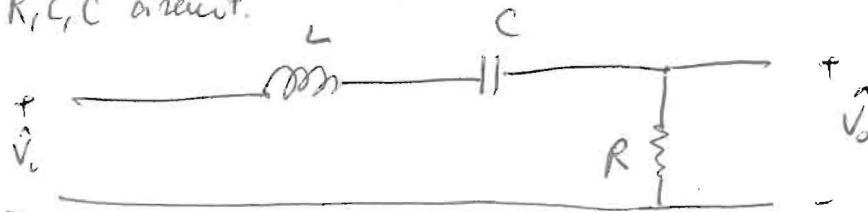

$$\hat{H} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{R}{R + j(\omega L - \frac{1}{\omega C})}$$

Resonant frequency is a frequency @ which reactive impedance cancels to zero: $\omega L = \frac{1}{\omega C} \rightarrow \omega_0 \equiv \frac{1}{\sqrt{LC}}$. Also in this example @ resonant freq $\rightarrow V_o = V_i$.
Quality factor: $Q \equiv \omega_0 \frac{L}{R} = \frac{1}{\sqrt{LC}} \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$

$$\hat{H} = \frac{R}{R[1 + j(\omega \frac{L}{R} - \frac{1}{\omega RC})]}$$





$$\omega \frac{L}{R} = \frac{1}{\omega RC} \rightarrow \omega = \omega_0$$

$$\omega_0 \frac{L}{R} = \frac{1}{\omega_0 RC} = \boxed{\frac{\omega_c}{\omega_0} \equiv Q}$$

$$\left\{ \begin{array}{l} Q > 1 \rightarrow \omega_c > \omega_0 \\ Q < 1 \rightarrow \omega_c < \omega_0 \end{array} \right.$$


$$\boxed{RC = \frac{1}{\omega_c}} \rightarrow \text{when there would be no } L$$

$$\omega_c = 0.01 \quad \omega_0 = 0.1$$

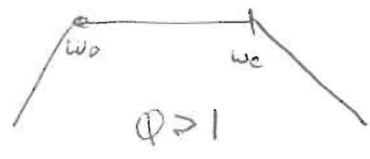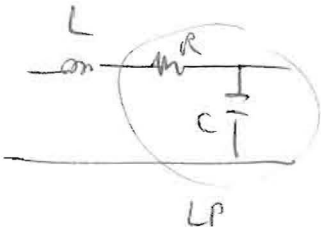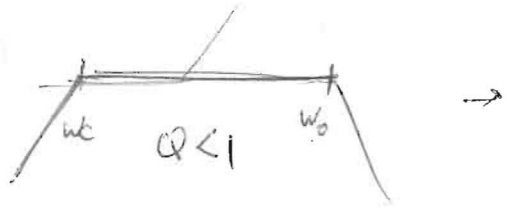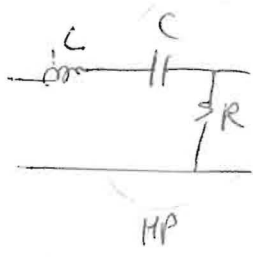

Meaning of Q :-

Bandpass:

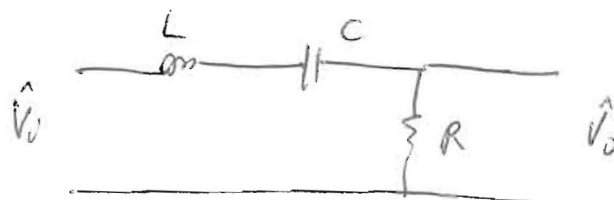

$$\hat{H}(j\omega) = \frac{R}{R + j(\omega L - \frac{1}{\omega C})} = \frac{RC\omega}{RC\omega + j(\omega^2 LC - 1)}$$

→ Magnitude: $|\hat{H}| = \frac{RC\omega}{\sqrt{(RC\omega)^2 + (\omega^2 LC - 1)^2}}$

→ Phase: $\angle \hat{H} = -\tan^{-1}\left(\frac{\omega^2 LC - 1}{RC\omega}\right)$



$\omega^2 LC = \frac{\omega^2}{\frac{1}{LC}}$

Asymptotic analysis:

Small ω :
 $\omega^2 \ll \frac{1}{LC} \approx \omega^2 LC \ll 1 \rightarrow \begin{cases} |\hat{H}| = \frac{RC\omega}{\sqrt{(RC\omega)^2 + 1}} \xrightarrow{\omega \rightarrow 0} RC\omega \approx 0 \\ \angle \hat{H} = +\tan^{-1} \frac{+1}{RC\omega} \xrightarrow{\omega \rightarrow 0} \tan^{-1} \infty = 90^\circ \end{cases}$


Large ω :
 $\omega^2 \gg \frac{1}{LC} \approx \omega^2 LC \gg 1 \rightarrow \begin{cases} |\hat{H}| = \frac{RC\omega}{\sqrt{(RC\omega)^2 + \omega^4 LC^2}} \approx \frac{RC\omega}{\omega^2 LC^2} \rightarrow 0 \\ \angle \hat{H} = -\tan^{-1} \frac{\omega^2 LC^2}{RC\omega} = -\tan^{-1} \frac{\omega L}{R} \xrightarrow{\omega \rightarrow \infty} -90^\circ \end{cases}$

Resonant frequency:
 $\omega^2 = \frac{1}{LC} \quad (\omega = \omega_0) \rightarrow \begin{cases} |\hat{H}| = \frac{RC\omega}{RC\omega} = 1 \\ \angle \hat{H} = 0 \end{cases}$

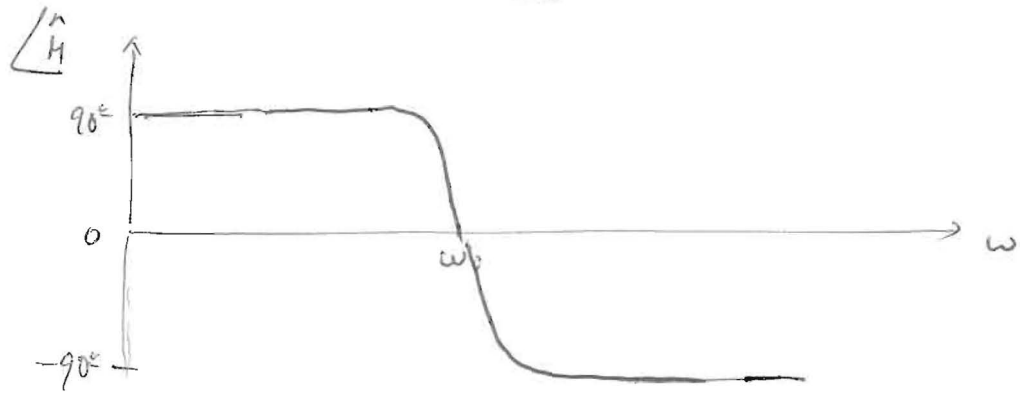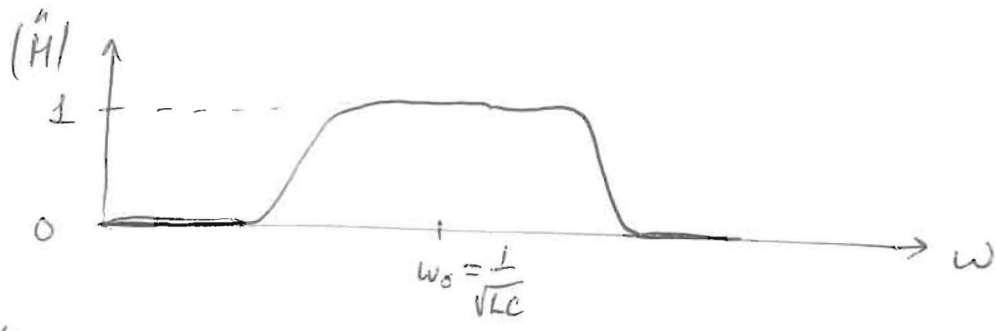


Op-Amp reviews :


Inverting

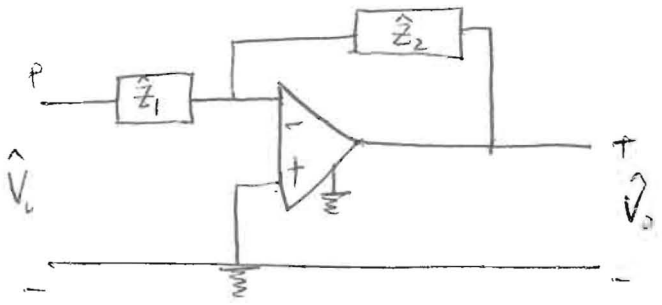


Non-inverting

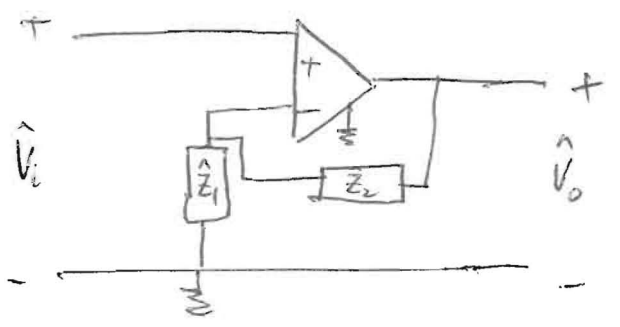


Equivalent circuit

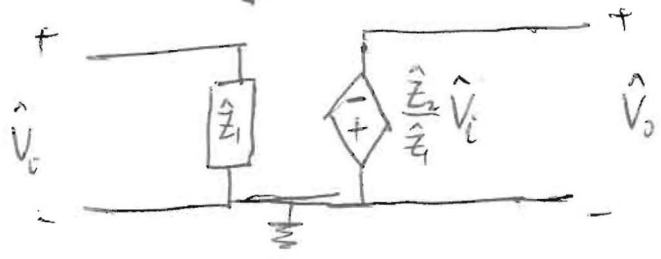

Equivalent circuit

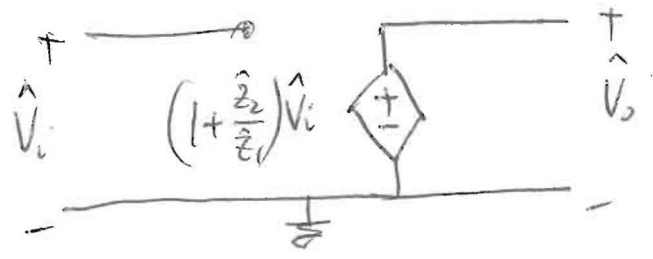


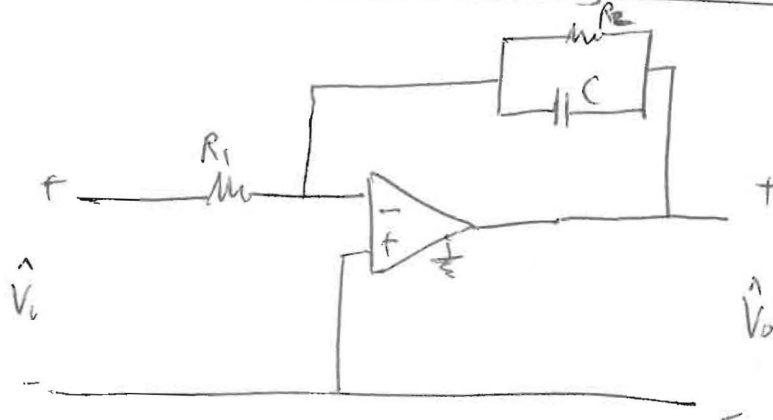Active - Low - Pass Filter using Op-Amp :



$$\left. \begin{aligned} \hat{Z}_1 &\equiv R_1 \\ \hat{Z}_2 &= R_2 \parallel C = \frac{R_2 \frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{1 + j\omega R_2 C} \end{aligned} \right\} \frac{\hat{Z}_2}{\hat{Z}_1} = \frac{\frac{R_2}{R_1}}{1 + j\omega R_2 C}$$

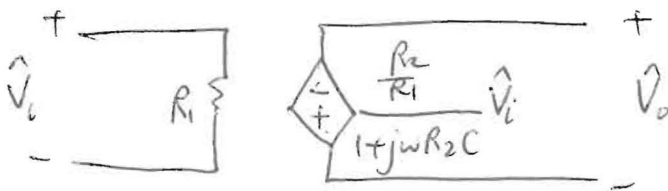Using the equivalent circuit for a ~~non~~ inverting Op-Amp:



$$\hat{H} = \frac{\hat{V}_o}{\hat{V}_i} = \frac{-\frac{\frac{R_2}{R_1}}{1 + j\omega R_2 C}}{1} \quad \checkmark$$

$$\hat{H} = \left(- \right) \frac{\frac{R_2}{R_1}}{1 + j\omega R_2 C}$$

↓ Inverting op-Amp
↓ Low-Pass Filter.

Now compared to a simple RC low-pass is $\frac{R_2}{R_1}$ which could give a gain in addition to passing V_i to V_o (when $R_2 > R_1$)

Connection b/w gain & bandwidth : since R_2 is in the

$$w_c = \frac{1}{R_2 C} \quad ; \quad \uparrow R_2 \rightarrow \text{high gain but also lower } w_c \text{ or shorter bandwidth!}$$

Laplace Transform :

$f(t)$
Time-domain
(function of time)

integral in time.

$$\hat{F}(s) \equiv \int_0^{\infty} dt f(t) e^{-st}$$

Frequency-domain
(function of frequency)

$s \equiv \alpha + j\omega$; $\alpha > 0$
↓
ang. frequency
(when $\alpha \rightarrow 0 \rightarrow$ Laplace T.
is related to Fourier T.)


$$f(t) = \frac{1}{2\pi j} \int_{\sigma_1 - j\infty}^{\sigma_1 + j\infty} ds \hat{F}(s) e^{+st}$$

$\hat{F}(s)$

integral in the complex plane. | instead $\rightarrow$ Partial Fraction Expansion & Properties of Laplace Transform.

Simple functions :

1) Unit Step Function $u(t)$

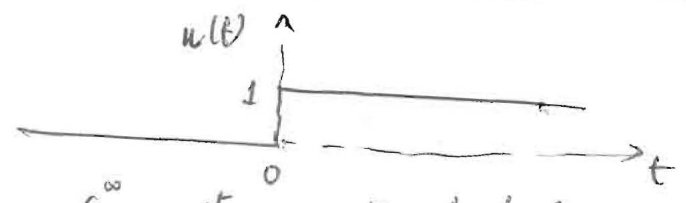


$$\begin{aligned} \hookrightarrow L[u(t)] &= \int_0^{\infty} dt u(t) e^{-st} = \int_0^{\infty} dt e^{-st} = \left[\frac{e^{-st}}{-s} \right]_{t=0}^{t=\infty} \\ &= \left[\frac{e^{-\alpha\infty} e^{-j\omega\infty}}{-(\alpha + j\omega)} - \frac{e^{-(\alpha + j\omega) \cdot 0}}{-(\alpha + j\omega)} \right] \end{aligned}$$

$$\boxed{s = \alpha + j\omega}$$

$$\boxed{\alpha > 0}$$

$$\boxed{L[u(t)] = \frac{1}{s}}$$

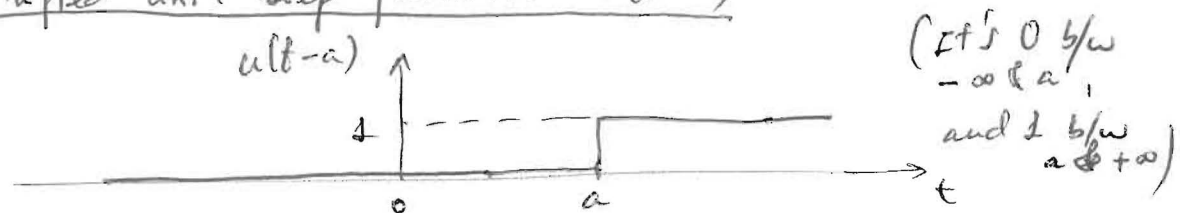2) Time-shifted unit step function: $u(t-a)$




$$\begin{aligned} L[u(t-a)] &= \int_0^{\infty} dt \, u(t-a) e^{-st} = \underbrace{\int_0^a dt \, 0 \cdot e^{-st}}_0 + \int_a^{\infty} dt \, e^{-st} \\ &= \left[\frac{e^{-st}}{-s} \right]_{t=a}^{t=\infty} = \frac{0 - e^{-sa}}{-s} = \frac{e^{-sa}}{s} \end{aligned}$$

$$\boxed{L[u(t-a)] = \frac{e^{-sa}}{s} = \underbrace{\frac{1}{s}}_{L[u(t)]} \cdot e^{-sa}}$$

Generalization: when f is shifted by a in time, $L[f(t)]$ gets multiplied by e^{-sa} .

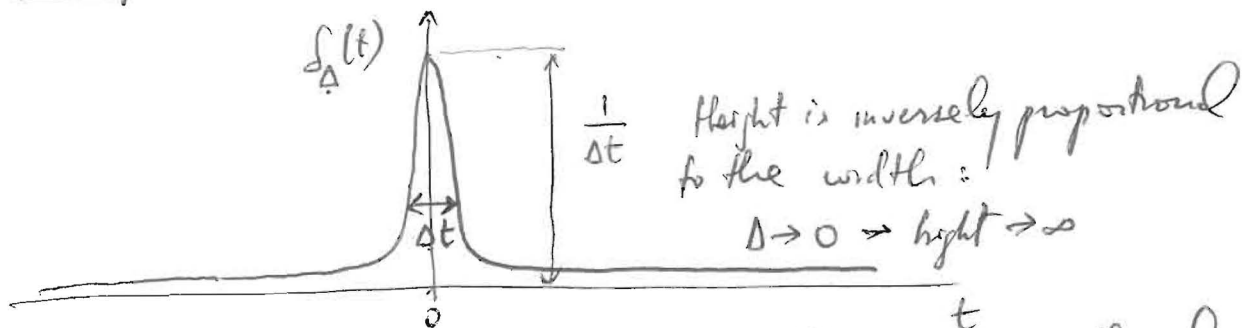3) Delta function $\delta(t) = \lim_{\Delta \rightarrow 0} \delta_{\Delta}(t)$



- The real $\delta(t)$ is very thin & very tall!
- Center of real $\delta(t)$ is same as center of $\delta_{\Delta}(t)$ → in this case center is 0
- If the center is @ a :
 $\delta(t-a)$ (@ $-a \rightarrow \delta(t+a)$)

Important to remember about the delta function: when it is showing in an integral it will pick one value of the integrand to be the integral (since it is so thin & so tall!) will pick only one value. dominate over anything.

The value it picks is the value of the integrand @ $x=a$

$$\int_0^\infty dt \underbrace{\delta(t-a)}_{\text{center @ } a} \underbrace{f(t)}_{\text{integrand}} = f(a)$$

$$L[\delta(t)] = \int_0^\infty dt \underbrace{\delta(t)}_{\text{center @ } 0} \underbrace{e^{-st}}_{\text{integrand}} = e^{-s \cdot 0} = 1$$

$$L[\delta(t-a)] = \int_0^\infty dt \underbrace{\delta(t-a)}_{\text{center @ } a} \underbrace{e^{-st}}_{\text{integrand}} = e^{-sa}$$

(since we are shifting the signal $f(t) = \delta(t)$ by a its Laplace Transform which is 1 gets multiplied by e^{-sa} .)

4) $f(t) = t$

$$L[t] = \int_0^\infty dt \ t e^{-st} = -\frac{d}{ds} \left[\underbrace{\int_0^\infty dt \ e^{-st}}_{\frac{1}{s}} \right] = \frac{1}{s^2}$$

alternative trick to the integration by parts

5) $f(t) = \cos \omega t$

$$\cos(\omega t) = \frac{e^{-j\omega t} + e^{j\omega t}}{2}$$

Recall: $e^{j\theta} = \cos \theta + j \sin \theta$
 $e^{-j\theta} = \cos \theta - j \sin \theta$
$$\frac{e^{j\theta} + e^{-j\theta}}{2} = \cos \theta$$

$$\begin{aligned} \mathcal{L}[\cos(\omega t)] &= \frac{1}{2} \int_0^{\infty} dt (e^{-j\omega t} + e^{j\omega t}) e^{-st} = \frac{1}{2} \int_0^{\infty} dt \left[e^{-(s+j\omega)t} + e^{-(s-j\omega)t} \right] \\ &= \frac{1}{2} \left[\frac{e^{-(s+j\omega)t}}{-(s+j\omega)} \right]_{t=0}^{t=\infty} + \frac{1}{2} \left[\frac{e^{-(s-j\omega)t}}{-(s-j\omega)} \right]_{t=0}^{t=\infty} \end{aligned}$$

$\swarrow$

$s = \sigma + j\omega$
 $\sigma > 0$

$$\begin{aligned} &= \frac{1}{2} \left[\frac{1}{s+j\omega} + \frac{1}{s-j\omega} \right] \\ &= \frac{1}{2} \frac{s-j\omega + s+j\omega}{(s+j\omega)(s-j\omega)} = \boxed{\frac{s}{s^2 + \omega^2}} \end{aligned}$$

6) $f(t) = \sin \omega t$

$$\sin(\omega t) = \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$$

$\downarrow$

$$\begin{aligned} \mathcal{L}[\sin(\omega t)] &= \frac{1}{2j} \left[\frac{1}{s-j\omega} - \frac{1}{s+j\omega} \right] = \frac{1}{2j} \frac{s+j\omega - s+j\omega}{s^2 + \omega^2} \\ &= \boxed{\frac{\omega}{s^2 + \omega^2}} \end{aligned}$$