

→ For other codes: add a parity bit:

<u>8 4 2 1</u>	<u>Parity bit</u> (so total number of ones is always odd)
0000	1
0001	0
0010	0
0011	1
0100	0
0101	1
0111	0

→ Can detect a simple error: 00001 → 01001

There's an error
(# of ones is even!)

→ Can't detect a double error 00001 → 11001

→ Can detect a triple error ...

Ch 3 Boolean Algebra & Combinational Networks

Boolean Algebra :

a) Commutative

$$A + B = B + A$$

Associative

$$b) (A + B) + C = A + (B + C)$$

c) Neutral Element

$$A + 0 = A$$

d) Distributive

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$\boxed{+ = \text{OR}}$$

$$A \cdot B = B \cdot A$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

$$A \cdot 1 = A$$


$$\boxed{A + B \cdot C = (A + B) \cdot (A + C)}^*$$

$$\boxed{\cdot = \text{AND}}$$

$$* \underbrace{A + 1 \cdot 1}_{(A + 1)} = (A + 1) \cdot (A + 1) \Rightarrow A + 1 = 1$$

Truth Tables : X OR Y

X	Y	X + Y
0	0	0
0	1	1
1	0	1
1	1	1

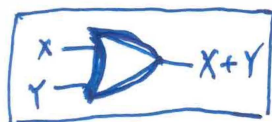

X AND Y

X	Y	X \cdot Y
0	0	0
0	1	0
1	0	0
1	1	1




NOT or

Complement of A is $\bar{A}$

$$A + \bar{A} = 1$$


$$A \cdot \bar{A} = 0$$

X	$\bar{X}$
0	1
1	0

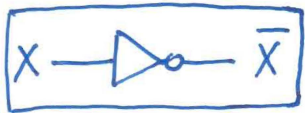


(NOR)

X	Y	$\overline{X+Y}$
0	0	1
1	0	0
0	1	0
1	1	0

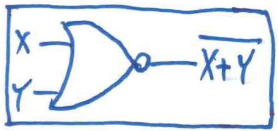


(NAND)

X	Y	$\overline{X \cdot Y}$
0	0	1
1	0	1
0	1	1
1	1	0

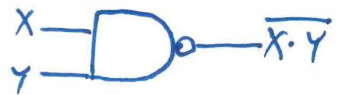


(XOR)

X	Y	$X \oplus Y$
0	0	0
1	0	1
0	1	1
1	1	0

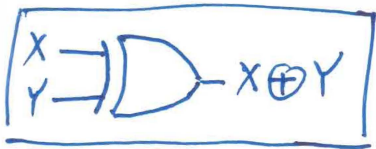

(XNOR)

X	Y	$\overline{X \oplus Y}$
0	0	1
1	0	0
0	1	0
1	1	1

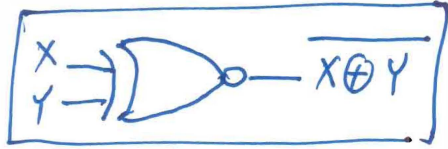

Corollaries from Boolean Algebra:

a) $\overline{\overline{A}} = A$

Proof: $A + \overline{A} = 1 \rightarrow \overline{A} = 1 - A$
 $\rightarrow \overline{\overline{A}} = 1 - \overline{A} = 1 - (1 - A)$
 $= A$

b) $\overline{A+B} = \overline{A} \cdot \overline{B}$

DeMorgan's Law #1

Proof: use truth tables:

A	B	$\overline{A+B}$
0	0	1
1	0	0
0	1	0
1	1	0

A	B	$\overline{A}$	$\overline{B}$	$\overline{A} \cdot \overline{B}$
0	0	1	1	1
1	0	0	1	0
0	1	1	0	0
1	1	0	0	0

A more general proof:

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

$\iff$

$A+B + \overline{A} \cdot \overline{B} = 1 \in \text{Need To prove This}$

Since: $A+B + \overline{A+B} = 1$

$\downarrow$ Distributive Property of Boolean Algebra

$$(\underbrace{A+B+\overline{A}}_1) \cdot (\underbrace{A+B+\overline{B}}_1)$$

$$= (\underbrace{B+1}_1) \cdot (\underbrace{A+1}_1)$$

$$= 1 \quad \checkmark$$

De Morgan's Law #2:

$$\overline{AB} = \bar{A} + \bar{B}$$

Since $A \cdot B + \overline{A \cdot B} = 1$

Different strategy: using a different property for complements:

$$\begin{cases} A + \bar{A} = 1 \\ A \cdot \bar{A} = 0 \end{cases}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B} \longrightarrow A \cdot B \cdot \overline{A \cdot B} = 0$$

$$A \cdot B \cdot (\bar{A} + \bar{B}) = 0 \quad \text{Need to prove this.}$$

$$\begin{aligned} & \overbrace{A \cdot B \cdot \bar{A}}^0 + \overbrace{A \cdot B \cdot \bar{B}}^0 \\ & \underbrace{B \cdot (A \cdot \bar{A})}_0 + \underbrace{A \cdot (B \cdot \bar{B})}_0 = 0 \quad \checkmark \end{aligned}$$

Absorption Law:

$$a) \quad A + A \cdot B = A$$

Proof: $A = A \cdot 1$

$$A \cdot 1 + A \cdot B = A \cdot \underbrace{(1+B)}_1 = A \quad \checkmark$$

$$b) \quad A \cdot (A+B) = A$$

Proof: $A \cdot (A+B) = A \cdot A + A \cdot B = A + A \cdot B = A \quad \checkmark$

Since: $A \cdot A = A \cdot (1 - \bar{A}) = A - \underbrace{A \cdot \bar{A}}_0 \Rightarrow \boxed{A \cdot A = A}$

$$\boxed{A + A = A} \quad \checkmark$$

Since $A + A \cdot 1 = A$ ($B=1$ in absorption Law).

Boolean Formulas & Functions:

Formulas: boolean combinations of literals (a literal is a variable or its complement: x or $\bar{x}$)
 $xyz + x\bar{y}z + \bar{x}yz$, etc.

Functions: map a set of variables (eg. x, y, z) to a unique formula.

$$f(x, y, z) = (\bar{x} + y)z$$

$$f(w, x, y, z) = z(x + \bar{y}) \cdot (w + \bar{x} + \bar{y})$$

Canonical Formulas from a truth table: $\left\{ \begin{array}{l} \text{Minterm} \\ \text{Max term} \end{array} \right.$

Truth table $\leftrightarrow$ Function

	x	y	z	f(x,y,z)	
m=0 $\leftarrow$	0	0	0	0	
m=1 $\leftarrow$	0	0	1	1	$\leftrightarrow \bar{x} \cdot \bar{y} \cdot z$: this term only gives one for entry #2 (m=1)
m=2 $\leftarrow$ $\left. \begin{array}{l} 2 \\ 3 \end{array} \right\}$ entries	0	1	0	0	
m=3	0	1	1	1	$\leftrightarrow \bar{x} \cdot y \cdot z$: this term only gives one for entry #4 (m=3)
m=4	1	0	0	1	$\leftrightarrow x \cdot \bar{y} \cdot \bar{z}$: this term only gives one for entry #5 (m=4)
m=5	1	0	1	0	
m=6	1	1	0	0	
m=7	1	1	1	0	

Minterm Canonical Formula for this function or truth table:

Look at the ones: there are three ones $\rightarrow$ 3 terms:

$$\left\{ \begin{array}{l} f(x,y,z) = \underbrace{\bar{x} \cdot \bar{y} \cdot z}_{\text{entry \#2 only}} + \underbrace{\bar{x} \cdot y \cdot z}_{\text{entry \#4 only}} + \underbrace{x \cdot \bar{y} \cdot \bar{z}}_{\text{entry \#5 only}} \quad (\text{Standard}) \\ f(x,y,z) = \sum m(1, 3, 4) \quad (m\text{-notation}) \end{array} \right.$$

Maxterm Canonical Formula:

Look at the zeroes: five zeroes in the truth table
→ five factors.

	x	y	z	f(x,y,z)	
M=0	0	0	0	0	→ $x+y+z$: only gives zero for entry #1 (gives 1 for rest of entries)
1	0	0	1	1	
2	0	1	0	0	→ $x+\bar{y}+z$: gives zero for entry #3, (gives 1 for the rest)
3	0	1	1	1	
4	1	0	0	1	
5	1	0	1	0	→ $\bar{x}+y+\bar{z}$ (only for entry #6, gives 0)
6	1	1	0	0	→ $\bar{x}+\bar{y}+z$
7	1	1	1	0	→ $\bar{x}+\bar{y}+\bar{z}$

$$\left\{ \begin{array}{l} f(x,y,z) = (x+y+z)(x+\bar{y}+z)(\bar{x}+y+\bar{z})(\bar{x}+\bar{y}+z)(\bar{x}+\bar{y}+\bar{z}) \\ \text{(Standard)} \\ f(x,y,z) = \prod M(0, 2, 5, 6, 7) \quad \text{(M-notation)} \end{array} \right.$$

Formula manipulation: Converting to a standard Minterm, Canonical

$$f(x,y,z) = \overline{(x+y)} + (y+xz) \cdot (x+\bar{y})$$

Use Boolean Algebra properties in Table 3.1 (p. 70):

De Morgan: $\overline{(x+y)} = \bar{x} \cdot \bar{y}$

Distributive: $(y+xz) \cdot (x+\bar{y}) = y \cdot x + \underbrace{y \cdot \bar{y}}_0 + \underbrace{x \cdot z \cdot x}_{\boxed{x \cdot x = x}} + x \cdot z \cdot \bar{y}$

$$f(x,y,z) = \bar{x} \cdot \bar{y} + \underbrace{x \cdot y}_{(z+\bar{z})} + \underbrace{x \cdot z}_{(z+\bar{z})} + \underbrace{x \cdot \bar{y} \cdot z}_{(y+\bar{y})}$$

$$= \bar{x} \cdot \bar{y} \cdot z + \bar{x} \cdot \bar{y} \cdot \bar{z} + \underbrace{x \cdot y \cdot z + x \cdot y \cdot \bar{z}}_{\text{(dup)}} + \underbrace{x \cdot \bar{y} \cdot z + x \cdot \bar{y} \cdot \bar{z}}_{\text{(dup)}}$$

Dropping duplicates:

23


$$f(x, y, z) = \bar{x}\bar{y}z + \bar{x}\bar{y}\bar{z} + x.y.z + x.y\bar{z} + x\bar{y}\bar{z}.$$

3.19


Draw logic diagram using gates: AND (.) & OR (+)



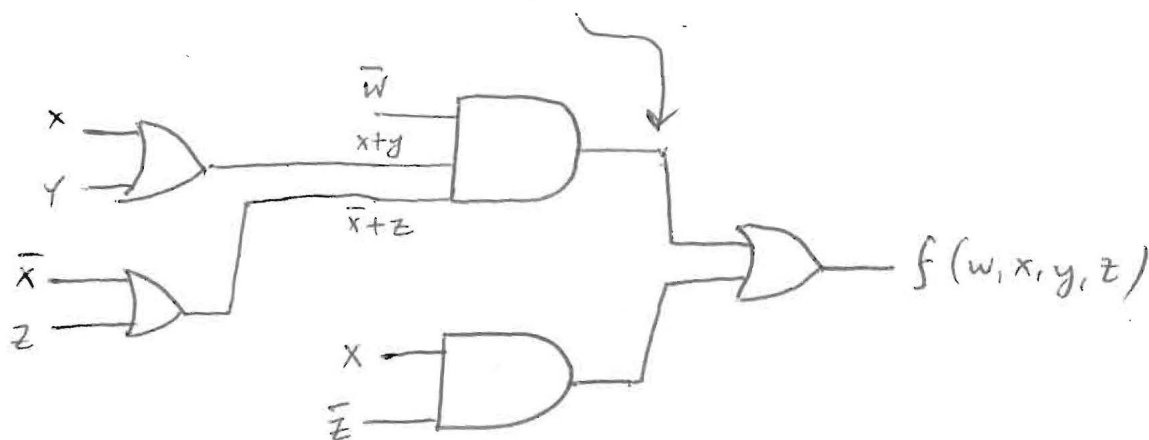
a) $f(w, x, y, z) = \bar{w} \cdot (x+y) \cdot (\bar{x}+z) + x \cdot \bar{z}$



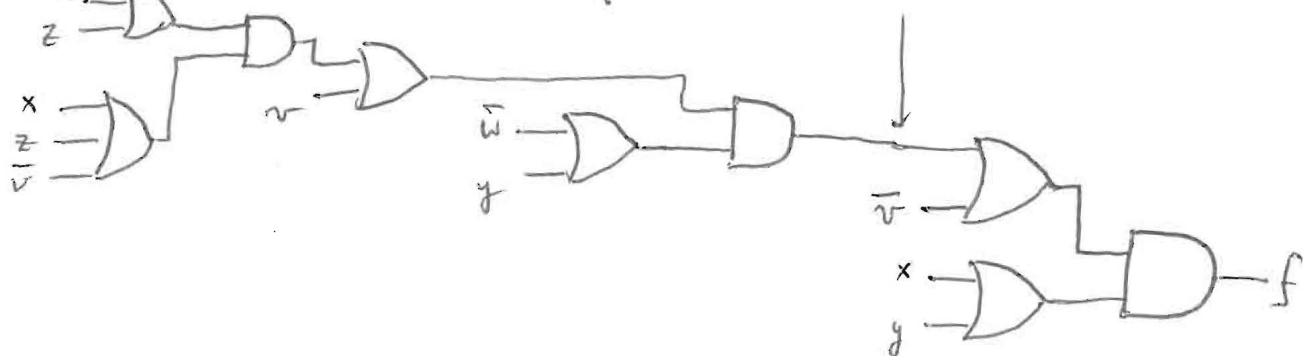b) $f(v, w, x, y, z) = (x+y) \cdot \left\{ \bar{v} + (\bar{w}+y) \cdot [v + (\bar{w}+z) \cdot (\bar{v}+x+z)] \right\}$


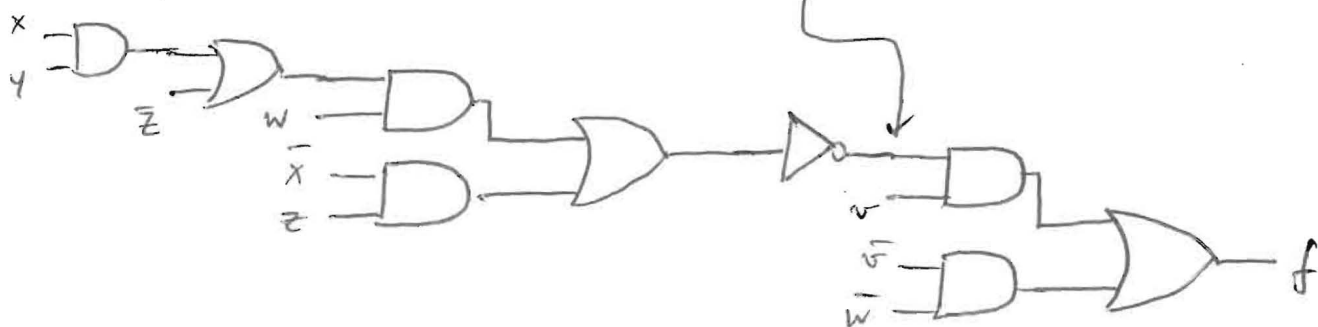
$$c) f(v, x, y, z) = v \cdot [w \cdot (x \cdot y + \bar{z}) + \bar{x} \cdot z] + \bar{v} \cdot \bar{w}$$



Formula Manipulation (cont.) Converting to a Standard Maxterm Canonical.

$$f(x, y, z) = \overline{(x+y)} + (y+x \cdot z) \cdot (x+\bar{y})$$

Use Boolean Algebra properties in Table 3.1 (p. 70):

• Distributive on $(y+x \cdot z) = (y+x) \cdot (y+z)$

• De Morgan on $\overline{(x+y)} = \bar{x} \cdot \bar{y}$

$$f(x, y, z) = \bar{x} \cdot \bar{y} + (y+x) \cdot (y+z) \cdot (x+\bar{y})$$

$$= (\bar{x} \cdot \bar{y} + y+x) \cdot (\bar{x} \cdot \bar{y} + y+z) \cdot (\bar{x} \cdot \bar{y} + x+\bar{y})$$

↑
Distributive

$$= (\underbrace{\bar{x} + y+x}_1) \cdot (\underbrace{\bar{y} + y+x}_1) \cdot (\underbrace{\bar{x} + y+z}_1) \cdot (\underbrace{\bar{y} + y+z}_1) \cdot (\underbrace{\bar{x} + x+\bar{y}}_1) \cdot (\underbrace{\bar{y} + x+\bar{y}}_1)$$

Distributive

$$\left\{ \begin{array}{l} 1+y=1 \checkmark, \quad 1+\bar{y}=1 \quad ? \quad \text{Absorption law: } A+A \cdot B = A \\ \bar{y}+\bar{y}=\bar{y} \quad \text{Absorption Law: } A+A \cdot 1 = A \end{array} \right.$$

$$f(x, y, z) = (\bar{x} + y + z) (x + \bar{y}) \quad = (\bar{x} + y + z) (x + \bar{y} + z \cdot \bar{z})$$

$$+ z \cdot \bar{z} \quad = (\bar{x} + y + z) (x + \bar{y} + z) (x + \bar{y} + \bar{z}) \checkmark$$

Formula Manipulation:

Expansion about a variable:

$$a) f(x_1, x_2, \dots, x_n) = x_i \cdot f(x_1, x_2, \dots, x_n) \Big|_{x_i=1} + \bar{x}_i \cdot f(x_1, x_2, \dots, x_n) \Big|_{x_i=0}$$

$$b) f(x_1, x_2, \dots, x_n) = [x_i + f(x_1, x_2, \dots, x_n) \Big|_{x_i=0}] \cdot [\bar{x}_i + f(x_1, x_2, \dots, x_n) \Big|_{x_i=1}]$$

Example: $f(w, x, y, z) = \bar{w} \cdot \bar{z} + (wx + y) \cdot z$

Expand f about x : use a):

$$\begin{aligned} f(w, x, y, z) &= x \cdot [\bar{w} \cdot \bar{z} + (w \cdot 1 + y) \cdot z] + \bar{x} \cdot [\bar{w} \cdot \bar{z} + (w \cdot 0 + y) \cdot z] \\ &= x \cdot [\bar{w} \cdot \bar{z} + (w + y) \cdot z] + \bar{x} \cdot [\bar{w} \cdot \bar{z} + y \cdot z] \end{aligned}$$

Reduction Theorems : or Shannon's Reduction Theorems

$$a) x_i \cdot f(x_1, x_2, \dots, x_i, \dots, x_n) = x_i \cdot f(x_1, x_2, \dots, \underset{\substack{\uparrow \\ \text{replaced } x_i \text{ by } 1}}{1}, \dots, x_n)$$

$$b) x_i + f(x_1, x_2, \dots, x_i, \dots, x_n) = x_i + f(x_1, x_2, \dots, \underset{\substack{\uparrow \\ \text{replaced } x_i \text{ by } 0}}{0}, \dots, x_n)$$

$$c) \bar{x}_i \cdot f(x_1, x_2, \dots, x_i, \dots, x_n) = \bar{x}_i \cdot f(x_1, x_2, \dots, \underset{\substack{\uparrow \\ \text{replaced } x_i \text{ by } 0}}{0}, \dots, x_n)$$

$$d) \bar{x}_i + f(x_1, x_2, \dots, x_i, \dots, x_n) = \bar{x}_i + f(x_1, x_2, \dots, \underset{\substack{\uparrow \\ \text{replaced } x_i \text{ by } 1}}{1}, \dots, x_n)$$

Boolean Algebra
 Formula manipulation: standard minterms/maxterms canonical reduction theorems.
 And/Or gates.
 Logic Design: logic circuit to accomplish certain goal.

↳ 1st Example: Odd-Parity Bit Generator.

(Total number of 1's should be odd → error detection)
including parity bit

Step 1:

Truth Table.

8 w	4 x	2 y	1 z	P
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$\bar{w} \cdot \bar{x} \cdot \bar{y} \cdot \bar{z}$$

$$\bar{w} \cdot \bar{x} \cdot y \cdot z$$

$$\bar{w} \cdot x \cdot \bar{y} \cdot z$$

$$\bar{w} \cdot x \cdot y \cdot \bar{z}$$

$$w \cdot \bar{x} \cdot \bar{y} \cdot z$$

$$w \cdot \bar{x} \cdot y \cdot \bar{z}$$


$$w \cdot x \cdot \bar{y} \cdot \bar{z}$$

$$w \cdot x \cdot y \cdot z$$

Step 2: minterm canonical for this truth table: (focusing on the ones) → 8 terms.


$$P(w, x, y, z) = \bar{w} \cdot \bar{x} \cdot \bar{y} \cdot \bar{z} + \bar{w} \bar{x} y z + \bar{w} x \bar{y} z + \bar{w} x y \bar{z} + w \bar{x} \bar{y} z + w \bar{x} y \bar{z} + w x \bar{y} \bar{z} + w x y z$$

Step 3: Logic Gate Implementation

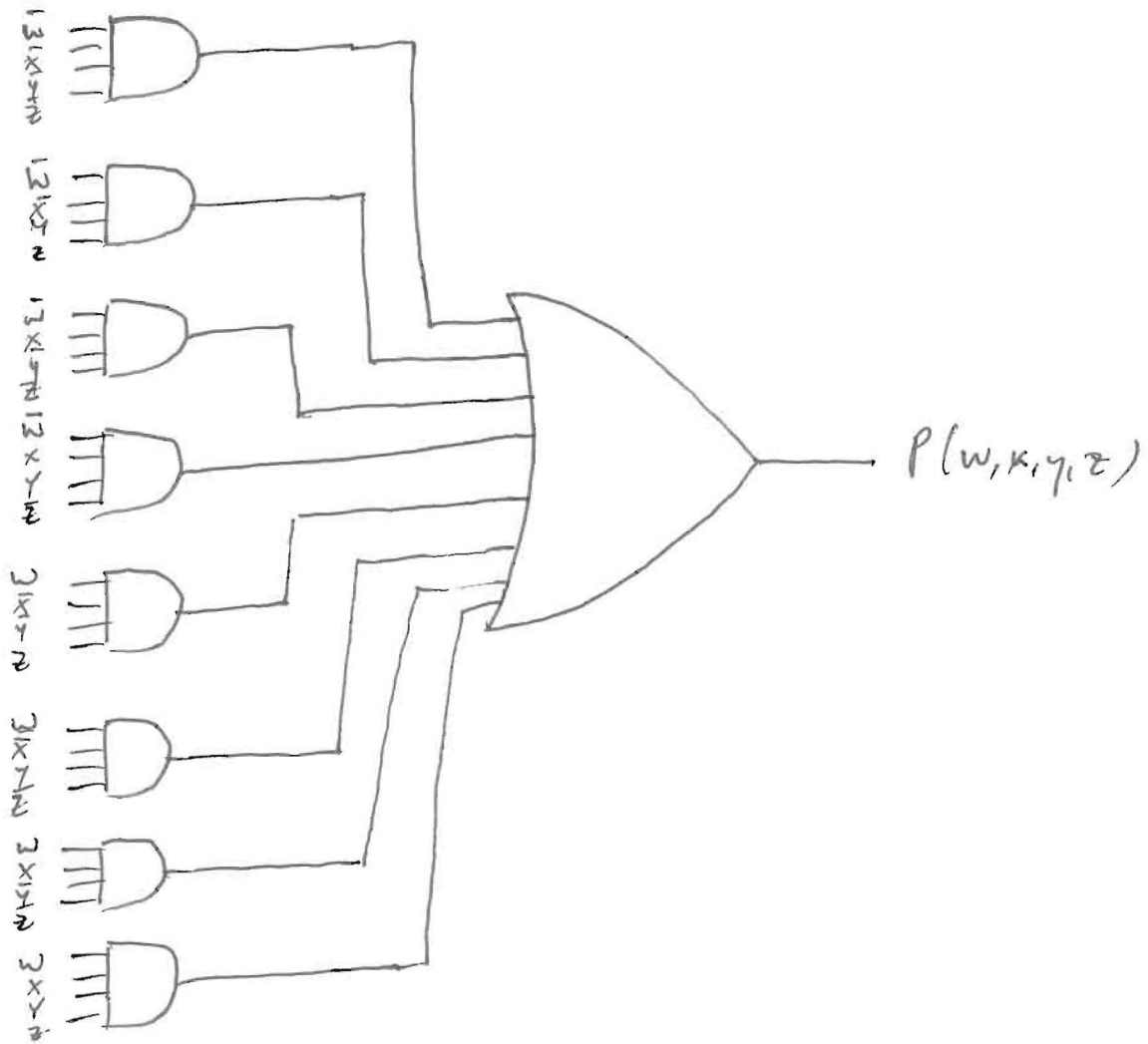

Additional Boolean & Gates Operations


X	Y	AND	NAND	OR	NOR
		$X \cdot Y$	$\overline{X \cdot Y}$	$X + Y$	$\overline{X + Y}$
0	0	0	1	0	1
0	1	0	1	1	0
1	0	0	1	1	0
1	1	1	0	1	0

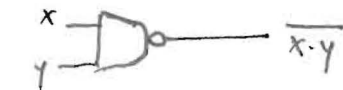NAND : $\text{nand}(x, y) = \overline{x \cdot y} \rightarrow$ 

De Morgan $\nearrow = \bar{x} + \bar{y} \rightarrow$ 

2 Alternate symbols for a nand gate.

NOR : $\text{nor}(x, y) = \overline{x + y} \rightarrow$ 

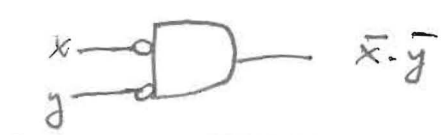
De Morgan $= \bar{x} \cdot \bar{y} \rightarrow$ 


2 Alternate symbols for a nor gate

NAND & NOR gates are universal : it is possible to write ANY combinational network in terms of only NAND's or NOR's

NAND gates :

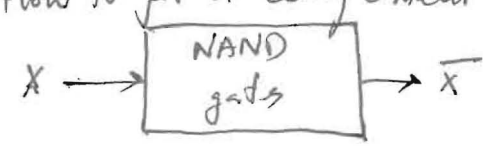a) How to get a complement with only NAND gates ?



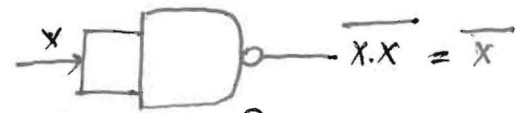Boolean Algebra : $x \cdot x = \bar{x} \rightarrow$  $\bar{x} \cdot \bar{x} = \bar{x}$

b) How to make an OR out of NAND's ?



Boolean Algebra: De Morgan's:


$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$\overline{\bar{x} \cdot \bar{y}} = \bar{\bar{x}} + \bar{\bar{y}}$$

$$= x + y$$


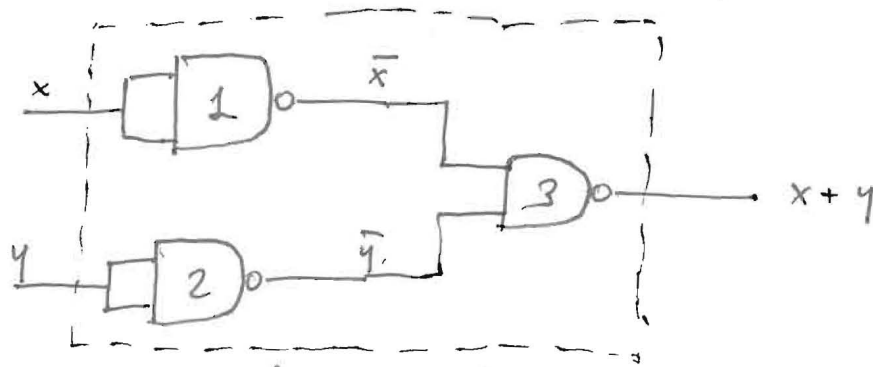
(29)

Find $\bar{x}$ & $\bar{y}$ then use a NAND



Equivalent OR using
3 NAND'S


6) How to make an AND out of NAND'S ?

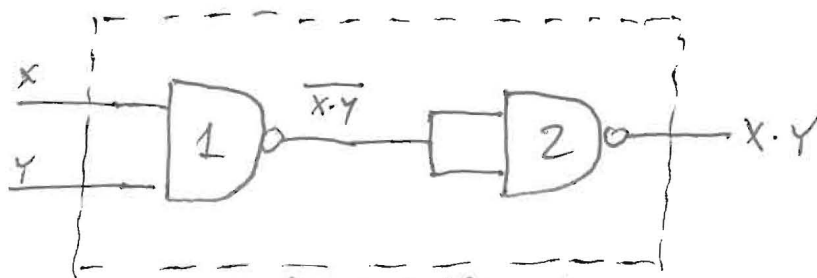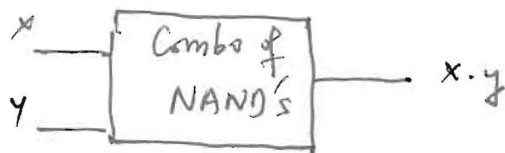


Equivalent AND using
2 NAND'S

NOR Gates:

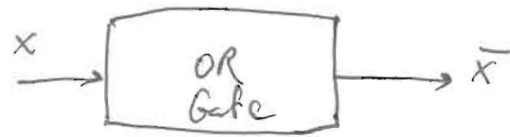
a) How to get a complement using NOR gates?



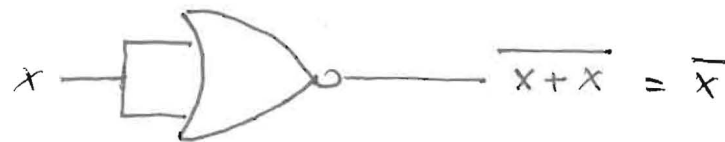Boolean Algebra: $x + x = x$ (Absorption Law)



b) OR using NOR's:

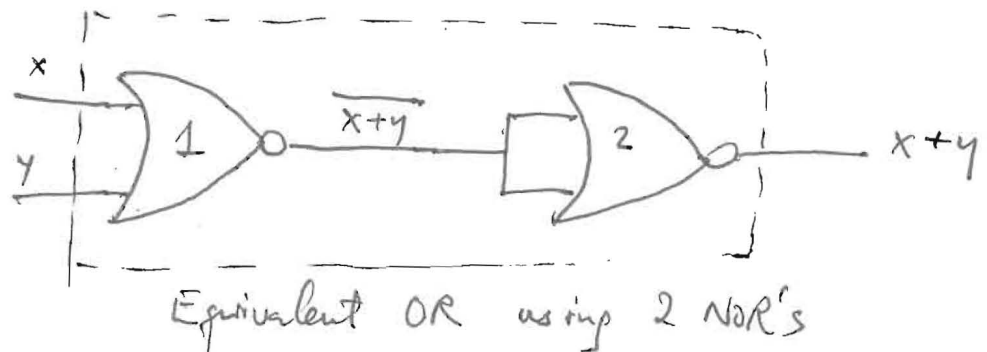


c) AND using NOR's:

$$\hookrightarrow \overline{x+y} = \bar{x} \cdot \bar{y}$$

$$\overline{\bar{x} + \bar{y}} = x \cdot y$$

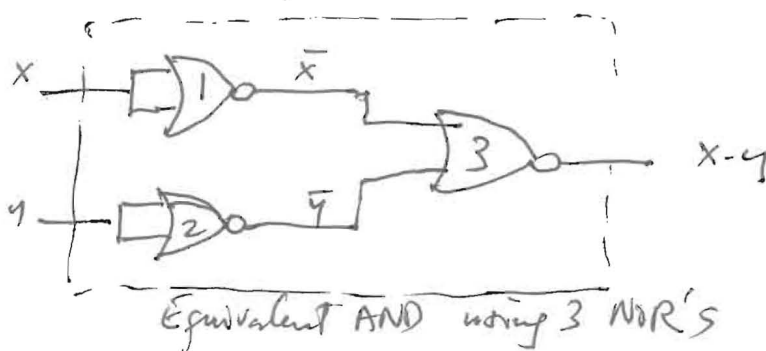Find $\bar{x}$ & $\bar{y}$ then use a NOR:




Create a Combinational Network using only NAND's.

Example: $f(x, y, z) = x \cdot (\bar{y} + z)$

1st:

AND
↓
2 NAND's

OR
↓
3 NAND's

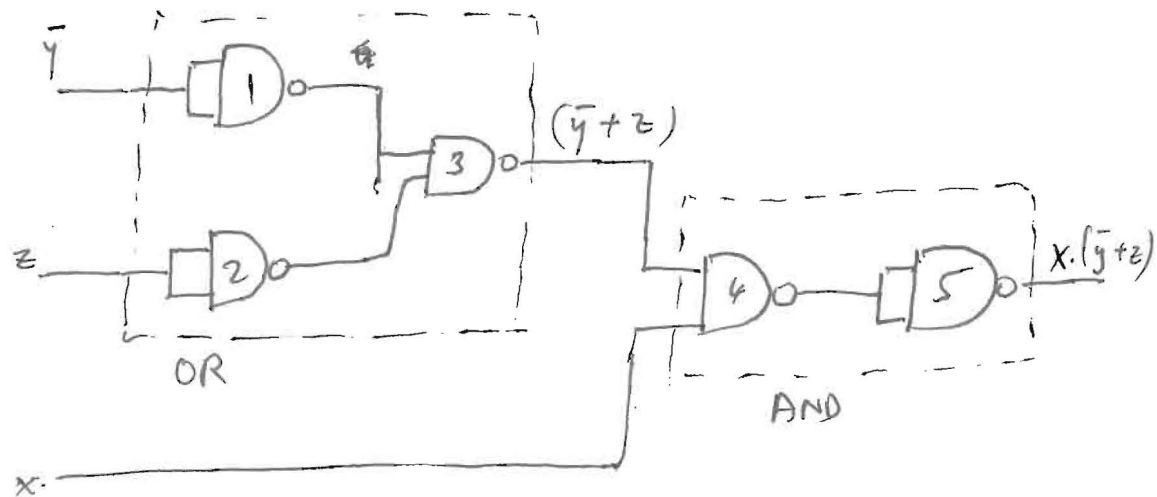


2nd:

Since NAND includes a complement, let's start by complementing our expression:

$$\bar{f} = \overline{x \cdot (\bar{y} + z)} = \text{NAND}(x, \bar{y} + z)$$

$$\begin{aligned} \text{Note: } \bar{y} + z &= \overline{y \cdot \bar{z}} \quad (\text{De Morgan's law}) \\ &= \text{NAND}(y, \bar{z}) \end{aligned}$$

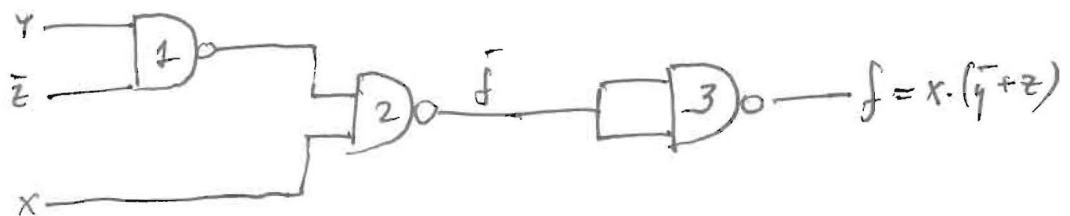
One more NAND will be used to complement $\bar{f}$




* Complement your expression & use De Morgan's law when possible.

Exclusive - OR

		XOR
X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

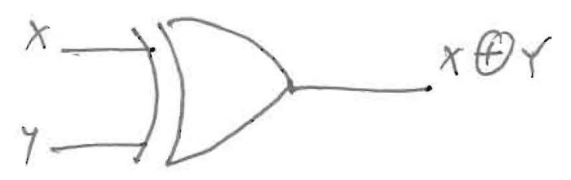

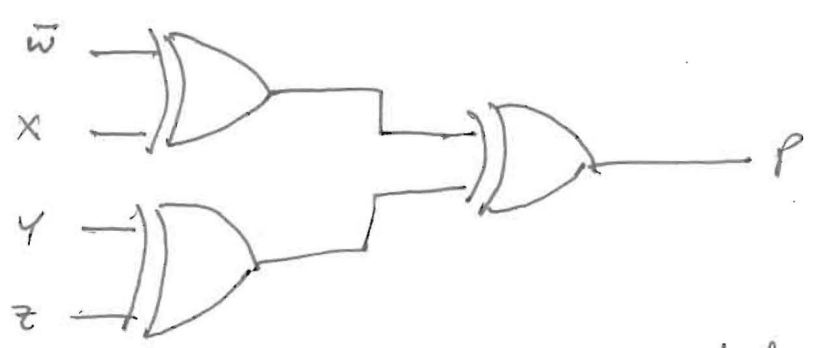↳ Odd-Parity can be generated with only 3 XOR's !



(instead of 8 AND's + 1 OR before)

Properties of X-OR see Table 3.16 (p. 112)

Exclusive - OR (Cont.) (XOR)



X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

$$X \oplus Y = \bar{X}Y + X\bar{Y}$$

X	Y	$\bar{X}Y + X\bar{Y}$
0	0	0
0	1	1
1	0	1
1	1	0

Properties (Table 3.16, pg. 112)

$$(i) a) \boxed{X \oplus Y = \bar{X}Y + X\bar{Y} = (X+Y)(\bar{X}+\bar{Y})}$$

Boolean algebraic properties

Distributive property:

$$(X+Y)(\bar{X}+\bar{Y}) = (X+Y)\bar{X} + (X+Y)\bar{Y} = Y\bar{X} + X\bar{Y} = X\bar{Y} + Y\bar{X} \checkmark$$

$$(X\bar{X} = Y\bar{Y} = 0 \Rightarrow \text{Table 3.1 pg. 70})$$

$$b) \overline{X \oplus Y} = \overline{\bar{X}Y + X\bar{Y}} = \overline{\bar{X} \cdot Y} \cdot \overline{X \cdot \bar{Y}} = (X+\bar{Y})(\bar{X}+Y)$$

De Morgan's Law:

$$\begin{cases} \overline{A+B} = \bar{A} \cdot \bar{B} \\ \overline{A \cdot B} = \bar{A} + \bar{B} \end{cases}$$

Distributive Property:

$$(X+\bar{Y})(\bar{X}+Y) = (X+\bar{Y})\bar{X} + (X+\bar{Y})Y = \bar{Y}\bar{X} + X\bar{Y} = \bar{X}\bar{Y} + X\bar{Y}$$

$$\boxed{\overline{X \oplus Y} = \bar{X}\bar{Y} + X\bar{Y} = (X+\bar{Y})(\bar{X}+Y)}$$

$X \oplus Y$: commutative, associative, distributive;
neutral element is 0 ($X \oplus 0 = X$)

$$iv) a) \quad \bar{X} \oplus \bar{Y} \stackrel{?}{=} X \oplus Y$$

use i)

$$\bar{X} \oplus \bar{Y} = \bar{X} \cdot \bar{Y} + \bar{\bar{X}} \cdot \bar{\bar{Y}} = \bar{X} \cdot \bar{Y} + X \cdot Y = X \oplus Y \quad \checkmark$$

$$b) \quad \bar{X} \oplus Y \stackrel{?}{=} X \oplus \bar{Y} \stackrel{?}{=} \overline{X \oplus Y}$$

use i)

$$\begin{aligned} \bar{X} \oplus Y &= \bar{X} \cdot Y + \bar{\bar{X}} \cdot \bar{Y} = \bar{X} \cdot Y + X \cdot \bar{Y} \\ X \oplus \bar{Y} &= X \cdot \bar{Y} + \bar{X} \cdot Y = \bar{X} \cdot Y + X \cdot \bar{Y} \end{aligned} \quad \left. \vphantom{\begin{aligned} \bar{X} \oplus Y \\ X \oplus \bar{Y} \end{aligned}} \right\} \text{equal.}$$

Use Exclusive-OR (XOR) to simplify the odd-parity bit formula:

$$\begin{aligned} p(w, x, y, z) &= \overline{\bar{w} \bar{x} \bar{y} \bar{z}} + \overline{\bar{w} \bar{x} y \bar{z}} + \overline{\bar{w} x \bar{y} \bar{z}} + \overline{\bar{w} x y \bar{z}} + \overline{w \bar{x} \bar{y} \bar{z}} + \overline{w \bar{x} y \bar{z}} + \overline{w x \bar{y} \bar{z}} \\ &\quad + \overline{w x y \bar{z}} \\ &= \underbrace{\bar{w} \bar{x} (\bar{y} \bar{z} + y \bar{z})}_{y \oplus z} + \underbrace{\bar{w} x (\bar{y} \bar{z} + y \bar{z})}_{y \oplus z} + \underbrace{w \bar{x} (\bar{y} \bar{z} + y \bar{z})}_{y \oplus z} + \underbrace{w x (\bar{y} \bar{z} + y \bar{z})}_{y \oplus z} \end{aligned}$$

$$= \underbrace{(\bar{w} \bar{x} + w x)}_{w \oplus x} (y \oplus z) + \underbrace{(\bar{w} x + w \bar{x})}_{(w \oplus x)} (y \oplus z)$$

$$= \overline{(w \oplus x) \cdot (y \oplus z)} + (w \oplus x) \cdot (y \oplus z)$$

$$= \overline{(w \oplus x) \oplus (y \oplus z)} \quad iv) \quad \overline{(w \oplus x) \oplus (y \oplus z)}$$

$$= (w \oplus x) \oplus (y \oplus z) \quad iv) \quad (w \oplus x) \oplus (y \oplus z)$$

(3 XOR's $\rightarrow$ odd-parity bit)

$$f_i(x, y, z) = y \cdot z + x \cdot y$$

$$\begin{aligned}
 \text{Min-term Canonical for } f_2(x, y, z) &= \bar{x}\bar{y}z + \bar{x}yz + \underbrace{xy\bar{z}}_{\substack{\downarrow \text{drop } \bar{z} \\ \downarrow \text{drop } \bar{y}}} + xyz \\
 &= \bar{x} \cdot z + xy + (\bar{x} + x) \cdot yz \\
 &= \bar{x} \cdot z + x \cdot y + y \cdot z.
 \end{aligned}$$

$$\text{Since } f_1 \text{ implies } f_2 \Rightarrow \underbrace{x \cdot y + y \cdot z}_{f_1} \text{ implies } \underbrace{x \cdot y + y \cdot z + \bar{x} \cdot z}_{f_2}$$

Ch 4: Simplification of Boolean Expressions (Cont.)

Implicants & Implicates:

Product term (in a minterm canonical expression of a function) is an implicant of the function (since it implies the function)

x	y	z	f(x,y,z)
0	0	0	0
0	0	1	1 ←
0	1	0	0
0	1	1	1 ←
1	0	0	1 ←
1	0	1	0
1	1	0	0
1	1	1	0

$f(x,y,z) = \bar{x}\bar{y}z + \bar{x}yz + x\bar{y}\bar{z}$

product term → gives a 1 as value for function
Since when a product term is 1 the function can't be 0 → product term implies function or is an implicant of the function.

Sum term (is a maxterm canonical for this example)

x	y	z	f(x,y,z)
0	0	0	0 ←
0	0	1	0 ←
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0 ←
1	1	0	0 ←
1	1	1	0 ←

$f(x,y,z) = (x+y+z)(x+\bar{y}+z)(\bar{x}+y+\bar{z})(\bar{x}+\bar{y}+z)(\bar{x}+\bar{y}+\bar{z})$

Here the function implies the sum term → sum term is an implicate of the function.

Irredundant Disjunctive & Conjunctive Normal Formulas

Can be achieved by using prime implicants or implicates.

A prime implicant is a product term that if any further literal is removed, it ~~is~~ no longer implies the function.

Example:

x	y	z	f(x,y,z)
0	0	0	1 ←
0	0	1	1 ←
0	1	0	1 ←
0	1	1	1 ←
1	0	0	0
1	0	1	1 ←
1	1	0	0
1	1	1	0

5 product terms:

$f(x,y,z) = \bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}z$

all five are implicants of f.

Look at $\bar{y}z$: is it an implicant of this function?
or whenever $\bar{y}z = 1$, can the function be 0? No → $\bar{y}z$ is
y=0 z=1

an implicant of the function. → $\bar{y}z$ is not a prime implicant
of f. Since if we drop literal x, $\bar{y}z$ is still an implicant of f.

An irredundant disjunctive normal formula (IDNF) is achieved when consists of product terms that are prime implicants and if a term is dropped the function is not the same.

A prime implicate: is a sum term that if any further literal is removed it is no longer implied by the function (or no longer an implicate of the function).

Karnaugh Maps:

Different representation of the Truth Table & the Boolean function.

x	y	$f(x,y)$
0	0	0
0	1	1
1	0	1
1	1	0

↔

x \ y	0	1
0	$f(0,0)$	$f(0,1)$
1	$f(1,0)$	$f(1,1)$

↔

x \ y	0	1
0	0	1
1	1	0

Example of a Karnaugh map for a 2-variable Boolean function.

x	y	z	$f(x,y,z)$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

↔

x \ yz	00	01	11	10
0	1	0	0	1
1	1	1	0	0

Karnaugh Map for a 3-variable Boolean function

[Note: 11 appears before 10]

so there is always a flip of one value between adjacent cells, including the last & the first cells horizontally (also vertically)

w	x	y	z	f(w,x,y,z)
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

↓
odd-parity bit

same z

same y

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	0	1
11	1	0	1	0
10	0	1	0	1

Karnaugh map for a 4-variable Boolean function.

Karnaugh Maps & Canonical Formulas:

$f(w, x, y, z) = \bar{w}\bar{x}\bar{y}\bar{z} + \bar{w}\bar{x}\bar{y}z + \bar{w}\bar{x}y\bar{z} + \bar{w}\bar{x}yz + \bar{w}x\bar{y}\bar{z} + \bar{w}x\bar{y}z + w\bar{x}\bar{y}\bar{z} + w\bar{x}\bar{y}z$
 (Minterm canonical or SOP formula) → each product gives a one or an implicant of the function.

↪

wx \ yz	00	01	11	10
00	1 0	1 1	0 3	1 2
01	1 4	1 5	0 7	0 6
11	0 12	0 13	0 15	0 14
10	1 8	0 9	0 11	1 10

Canonical Formula → Karnaugh Map.
 ↓
 $\sum m(0, 1, 2, 4, 5, 8, 10)$

Karnaugh Map → Canonical Formula → Maxterm Canonical or POS: focus on the zeroes: product of nine sums:

$$f(w, x, y, z) = (w+x+y+z)(w+x+y+\bar{z})(w+x+\bar{y}+z)(w+x+\bar{y}+\bar{z})(w+\bar{x}+y+z)(w+\bar{x}+y+\bar{z})(w+\bar{x}+\bar{y}+z)(w+\bar{x}+\bar{y}+\bar{z})(\bar{w}+x+y+z)(\bar{w}+x+y+\bar{z})(\bar{w}+x+\bar{y}+z)$$

↓

$$\prod M(3, 7, 6, 9, 11, 12, 13, 14, 15)$$

3.33

Use Truth table or use properties of Boolean operations.

$$f_d(x_1, x_2, \dots, x_n) = \bar{f}(\bar{x}_1, \bar{x}_2, \dots, \bar{x}_n) \quad \left\{ \begin{array}{l} \text{complement of function} \\ \text{is assigned to the complement} \\ \text{of the variables} \end{array} \right.$$

X-OR			dual function	dual of (x ⊕ y)		
x	y	$x \oplus y$		x	y	
0	0	0	→	1	1	1
0	1	1		1	0	0
1	0	1		0	1	0
1	1	0		0	0	1

OR			NOR		X-NOR
x	y	$x + y$	$\overline{x + y}$		
0	0	0	1		1
0	1	1	0		0
1	0	1	0		0
1	1	1	0	→	1

Same.