

Six-variable Karnaugh Map: $f(\underbrace{uvw}_8 \underbrace{xyz}_8)$

8x8 Table : cell # for decimal notation

		xyz							
		000	001	011	010	110	111	101	100
uvw	000	0	1	3	2	6	7	5	4
	001	8	9	11	10	14	15	13	12
	011	24	25	27	26	30	31	29	28
	010	16	17	19	18	22	23	21	20
uvw	110	48	49	51	50	54	55	53	52
	111	56	57	59	58	62	63	61	60
	101	40	41	43	42	46	47	45	44
	100	72	73	75	74	78	79	77	76

Find prime implicants : $\left\{ \begin{array}{l} \text{- Karnaugh map (visual)} \\ \text{- Quine - McCluskey (algorithmic)} \end{array} \right.$
 $\downarrow$
 computational purpose

Quine - McCluskey Method:

Given a logic function: $f(w, x, y, z) = \sum m(1, 3, 4, 5, 7, 8, 15)$

(sum of 7 products)

Recall: decimal notation: 4 variables
→ 16 entries: 0 (0000), 1 (0001), ... 15 (1111)

$$f(w, x, y, z) = \bar{w}\bar{x}\bar{y}z + \bar{w}\bar{x}yz + \bar{w}x\bar{y}\bar{z} + \bar{w}x\bar{y}z + \bar{w}xyz + w\bar{x}\bar{y}\bar{z} + \cancel{w\bar{x}\bar{y}z} + wxyz$$

	w	x	y	z	f
0	0	0	0	0	
1	0	0	0	1	1
2	0	0	1	0	
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	
10	1	0	1	0	
11	1	0	1	1	
12	1	1	0	0	
13	1	1	0	1	
14	1	1	1	0	
15	1	1	1	1	1

	Column #1	Column #2	Column #3
1	$\bar{w}\bar{x}\bar{y}z \checkmark$	13 $\bar{w}\bar{x}z \checkmark$	13, 57 $\bar{w}z$
3	$\bar{w}\bar{x}yz \checkmark$	15 $\bar{w}\bar{y}z \checkmark$	15, 37
4	$\bar{w}x\bar{y}\bar{z} \checkmark$	37 $\bar{w}yz \checkmark$	
5	$\bar{w}x\bar{y}z \checkmark$	45 $\bar{w}x\bar{y}$	
7	$\bar{w}xy\bar{z} \checkmark$	57 $\bar{w}xz \checkmark$	
8	$w\bar{x}\bar{y}\bar{z}$	7, 15 $x\bar{y}\bar{z}$	
15	$wxyz \checkmark$		

1) Use property: comparing two products:

$$\boxed{AB + \bar{A}B = B}$$

(eliminate the only different variable in the two adding products)

2) Put a check mark on non-prime implicants (since they imply a simpler implicant)

3) Repeat comparison: (13), 14, (15), ... (57), 58, 515.
34, 35, (37), 38, ... 78, (715)
(45), 47, 48, 415.

Note 8 is still a prime implicant of the function!

4) Repeat comparing process in column #2

13 & 57 implies $\bar{w}z$, they are not prime implicants $\rightarrow$ add a check mark to both.

15 & 37 implies $\bar{w}z$ also, add check marks.

$\Rightarrow$ Prime implicants for $f(w, x, y, z)$:

$$w\bar{x}\bar{y}\bar{z}, \bar{w}x\bar{y}, x\bar{y}z, \bar{w}z$$

Can make this process more systematic? use 01-

Column #1	01-	index (# of ones)	Column #1	index (# of ones)
1	$\bar{w}\bar{x}\bar{y}z$	0001	1	0001
3	$\bar{w}\bar{x}y\bar{z}$	0011	4	0100
4	$\bar{w}x\bar{y}\bar{z}$	0100	8	1000
5	$\bar{w}x\bar{y}z$	0101	3	0011
7	$\bar{w}xy\bar{z}$	0111	5	0101
8	$w\bar{x}\bar{y}\bar{z}$	1000	7	0111
15	$wxy\bar{z}$	1111	15	1111

By using "01-" notation and grouping entries based on their index, we can reduce the number of needed comparisons: we only need to compare entries belonging to groups whose index differs by one. No need to compare group of index 1 with group of index 3 or 4, etc. Only compare groups 1 & 2; 2 & 3; 3 & 4

Column #1 (index)

1	0001	(1)	✓
4	0100	(1)	✓
8	1000	(1)	
3	0011	(2)	✓
5	0101	(2)	✓
7	0111	(3)	✓
15	1111	(4)	✓

Column #2 (index)

13	00-1	(1)
15	0-01	(1)
37	0-11	(2)
57	01-1	(2)
715	-111	(3)
45	010-	(1)

Column #2 (index)

13	00-1	(1)	✓
15	0-01	(1)	✓
45	010-	(1)	
37	0-11	(2)	✓
57	01-1	(2)	✓
715	-111	(3)	

Column #3 (index)

13 & 57	0--1	(1)
15 & 37	0--1	(1)

Prime implicants

8	1000	($w\bar{x}\bar{y}\bar{z}$)
4,5	010-	($\bar{w}x\bar{y}$)
7,15	-111	($x\bar{y}z$)
13 & 57	0--1	($\bar{w}z$)

Another Example of Quine - McCluskey : an incomplete function

$$f(x, w, x, y, z) = \underbrace{\sum m(4, 5, 9, 11, 12, 14, 15, 27, 30)}_{\text{nine ones}} + \underbrace{dc(1, 17, 25, 26, 31)}_{\text{five unknowns}}$$

Recall Karnaugh map: unknowns or - were considered as ones. $\rightarrow$ same here!

Nine ones + five dashes $\rightarrow$ 14 entries or product terms to simplify: First we need to group them by index:

	m	entry	index (# of ones)	Column #1	Column #2
nine ones	4	00100	1	4	00100
	5	00101	2	5	00101
	9	01001	2	9	01001
	11	01011	3	12	01100
	12	01100	2	11	01011
	14	01110	3	14	01110
	15	01111	4	15	01111
	27	11011	4	27	11011
	30	11110	4	30	11110
five unknowns	1	00001	1		
	17	10001	2		
	25	10001	3		
	26	11010	3		
	31	11111	5		

- * compare b/w consecutive groups to use $A\bar{B} + AB = A$
- * Column #1 needs to include unknown entries as well (see next page)

m	Column #1 (Index)
1	00001 ✓ (1)
4	00100 ✓
5	00101 ✓
9	01001 ✓ (2)
12	01100 ✓
17	10001 ✓
11	01011 ✓
14	01110 ✓ (3)
25	11001 ✓
26	11010
15	01111 ✓
27	11011 ✓ (4)
30	11110 ✓
31	11111 ✓ (5)

Column #2
1,5 00-01 → Prime
1,9 0-001 ✓
1,17 -0001 (1)
4,5 0010- → Prime
4,12 0-100 → Prime
9,11 010-1 ✓
9,25 -1001 ✓ (2)
12,14 011-0 → Prime
17,25 1-001 ✓
11,15 01-11 ✓
11,27 -1011 ✓
14,15 0111- ✓ (3)
14,30 -1110 ✓
25,27 110-1 ✓
26,27 1101- ✓
25,30 11-10 ✓

Column 1 → Column 2: all same except for one digit change, if yes mark those entries as not prime implicants.

15,31 -1111 ✓
27,31 11-11 ✓ (4)
30,31 1111 - ✓

Column #3
1,9,17,25 --001 (1) → Prime
9,11,25,27 -10-1 (2) → Prime
9,25,11,27 -10-1
11,15,27,31 -1-11 → Prime
11,27,15,31 -1-11 (3)
14,15,30,31 -111- → Prime
14,30,15,31 -111-
26,27,30,31 11-1- → Prime
26,30,27,31 11-1-

Column #4
No match

Our function has 9 prime implicants:
 $00-01$, $0010-$, $0-100$, $011-0$, $--001$, $-10-1$, $-1-11$,
 $\bar{v}\bar{w}\bar{y}z$, $\bar{v}\bar{w}x\bar{y}$, $\bar{v}x\bar{y}\bar{z}$, $\bar{v}w\bar{x}\bar{z}$, $\bar{x}\bar{y}z$, $w\bar{x}z$, wyz
 $-111-$, $11-1-$
 wxy , vwy

Quine-Mccluskey Method:

Two functions:

$$a) f(w, x, y, z) = \sum m(1, 3, 4, 5, 7, 8, 15)$$

4 prime implicants: $w\bar{x}\bar{y}\bar{z}, \bar{w}x\bar{y}, x\bar{y}z, \bar{w}z$

$$b) f(v, w, x, y, z) = \sum m(4, 5, 9, 11, 12, 14, 15, 27, 30)$$

$$+ dc(1, 19, 25, 26, 31)$$

Nine prime implicants: $\bar{v}\bar{w}\bar{y}z, \bar{v}\bar{w}x\bar{y}, \bar{v}x\bar{y}\bar{z}, \bar{v}wx\bar{z}, \bar{x}\bar{y}z, w\bar{x}z, wyz, wx\bar{y}, vwy$

We found all prime implicants for each of these functions, not all are essential. Next task:

- 1) Find minimum expressions $\rightarrow$ build prime implicant Table.
- 2) Find least cost expression

a)

		m_1	m_3	m_4	m_5	m_7	m_8	m_{15}
8	A: $w\bar{x}\bar{y}\bar{z}$						x	
4, 5	B: $\bar{w}x\bar{y}$			x	x			
7, 15	C: $x\bar{y}z$					x		x
1, 3, 5, 7	D: $\bar{w}z$	x	x		x	x		

Min terms in columns
 Prime implicants in rows

A prime implicant is essential if it is the only implicant for some min term

Essential prime implicants: A(m_8), B(m_4), C(m_{15}), D(m_1 or m_3)

Min-expression: a combination of all ^{essential} prime implicants that covers all min terms (seven min terms in this example).

$$f_{\min} = A + B + C + D \quad \text{only one possibility to cover all min terms} \rightarrow \text{we are done!}$$

$$f_{\min}(w, x, y, z) = w\bar{x}\bar{y}\bar{z} + \bar{w}x\bar{y} + xyz + \bar{w}z$$

(b)

Prime implicant table

		m_4	m_5	m_9	m_{11}	m_{12}	m_{14}	m_{15}	m_{27}	m_{30}
1, 9, 17, 25 A	$\bar{x}\bar{y}z$			X						
9, 11, 25, 27 B	$w\bar{x}z$			X	X				X	
11, 15, 27, 31 C	wyz				X		X	X		
14, 15, 30, 31 D	wxy						X	X		X
26, 27, 30, 31 E	$\bar{v}wy$								X	X
1, 5 F	$\bar{v}\bar{w}\bar{y}z$		X							
4, 5 G	$\bar{v}\bar{w}x\bar{y}$	X	X							
4, 12 H	$\bar{v}x\bar{y}\bar{z}$	X				X				
12, 14 I	$\bar{v}wx\bar{z}$					X	X			

Do not include unknown min terms in columns.

Essential prime implicants: the only prime implicant for some min term: ~~A~~ (m_4) none. We need to find different min. combinations that cover all min terms ($m_4, m_5, m_9, m_{11}, m_{12}, m_{14}, m_{15}, m_{27}, m_{30}$)

$$f_I = B + D + G + H$$

↓
For lower cost, look for prime implicant that covers most number of min terms: B covers 3 min terms, D covers 3 other min terms, (covered: $m_9, m_{11}, m_{14}, m_{15}, m_{27}, m_{30}$)

Need to cover now: m_4, m_5, m_{12}

G covers (m_4, m_5)

H or I covers (m_{12})

$$f_{II} = B + D + G + I$$

Observation: in example (a) all prime implicants were used to cover the min terms. In example (b) ^{only} some prime implicants were needed to cover all min terms.

$$f_{III} = B + D + F + H$$

$$f_{IV} = B + C + E + G + I$$

Observation: f_I, f_{II}, f_{IV} have lowest costs since we found them maximizing min term coverage for each prime implicant:

$$f_I(v, w, x, y, z) = w\bar{x}z + wx\bar{y} + \bar{v}\bar{w}x\bar{y} + \bar{v}x\bar{y}\bar{z}$$

$$f_{II}(v, w, x, y, z) = w\bar{x}z + wx\bar{y} + \bar{v}\bar{w}x\bar{y} + \bar{v}wx\bar{z}$$


$$f_{III}(v, w, x, y, z) = w\bar{x}z + wx\bar{y} + \bar{v}\bar{w}\bar{y}z + \bar{v}x\bar{y}\bar{z}$$

ch5 Logic Design with MSI Components & PLDs.

MSI : Medium-scale integrated circuits (10-100 gates)

PLD : Programmable Logic Devices.

Binary Adders & Subtractors :

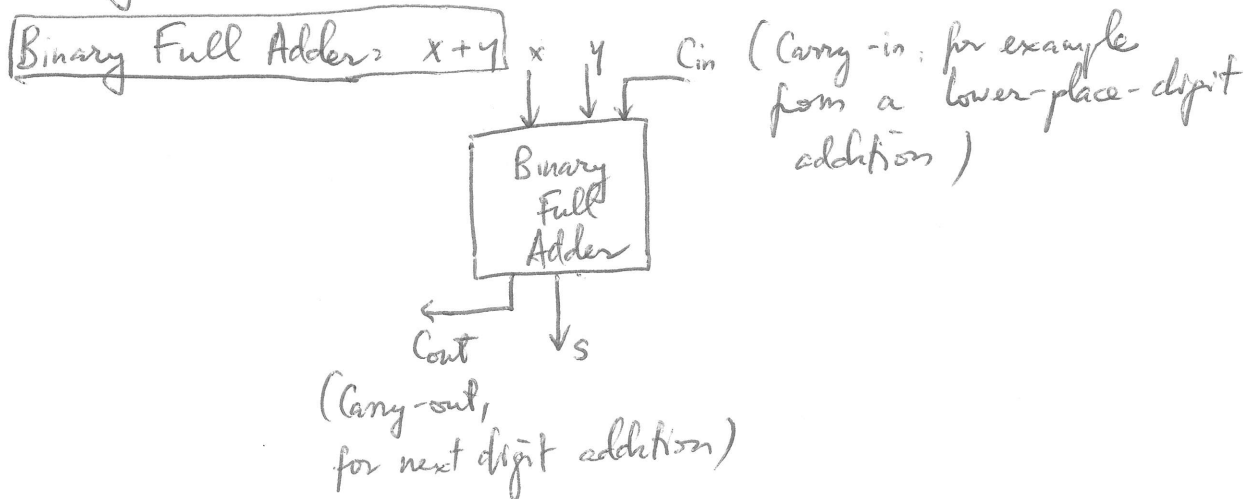

Truth Table:

x	y	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

($0+0+0=0$ with nothing to carry out)

Now: Karnaugh Map $\rightarrow$ simplified function for logic gates.

S	y C _{in}			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

Cont	y C _{in}			
	00	01	11	10
0	0	0	1	0
1	0	1	1	1

3 groups of 2 ones
→ 3 terms of 2 literals

Karnaugh map: largest blocks or groups of ones (8, 4, 2, 1)

$$S = \bar{x}\bar{y}C_{in} + \bar{x}y\bar{C}_{in} + x\bar{y}\bar{C}_{in} + xyC_{in}$$

(standard min term canonical, no simplification was possible)


Some saving using xor gates?

$$\begin{cases} ab' + a'b = a \oplus b \\ a\bar{b} + \bar{a}b = a \oplus b \end{cases}$$


$$\begin{aligned} S &= \bar{x}(\bar{y}C_{in} + y\bar{C}_{in}) + x(\bar{y}\bar{C}_{in} + yC_{in}) \\ &= \bar{x} \cdot (y \oplus C_{in}) + x \cdot (y \oplus C_{in}) \\ &= x \oplus (y \oplus C_{in}) \end{aligned}$$

$$\text{Cont} = \begin{matrix} (A) & (B) & (C) \\ yC_{in} & xC_{in} & xy \end{matrix}$$

Binary Full Adder: Logic diagram:

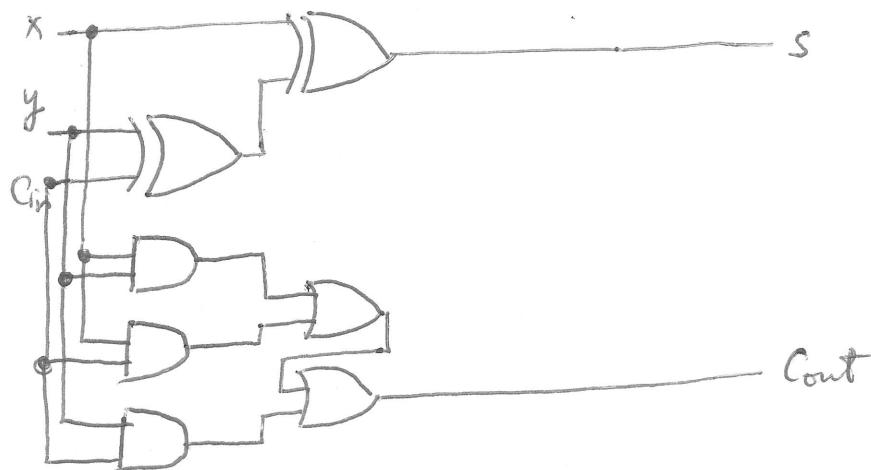

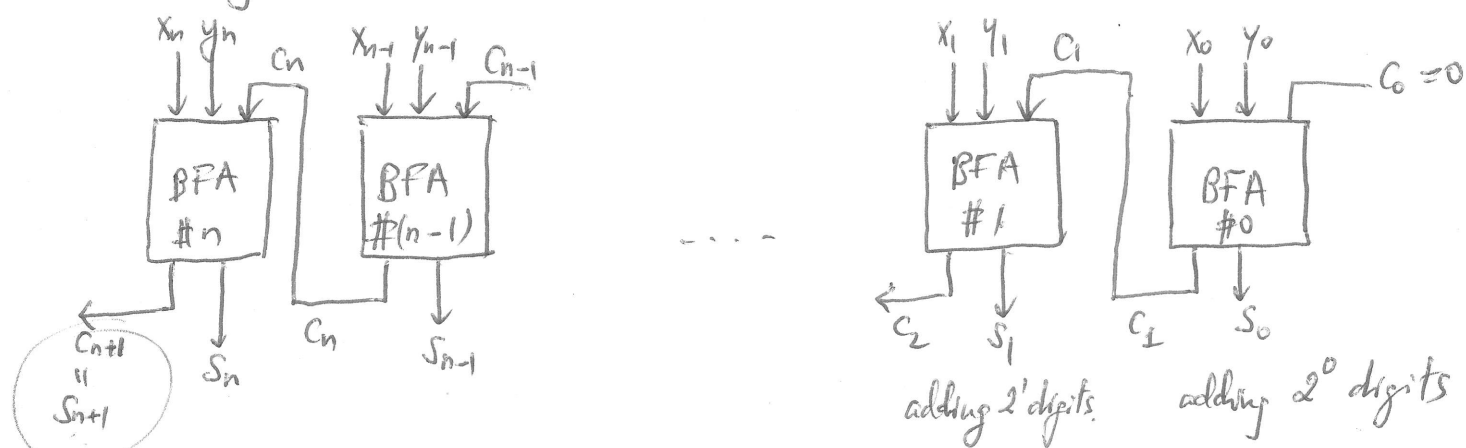To add two n -digits binary numbers : combine n single-digit binary adders in series: first add the lowest digits ($C_{in} = 0$)



Note: when adding two n -digits binary numbers we will get in general: a $(n+1)$ digit binary number:

$$\begin{array}{r}
 10 \\
 + 11 \\
 \hline
 101
 \end{array}$$

↓
the $(n+1)$ digit is also the last carry-out!

so we have $S_{n+1} = C_{n+1}$

To subtract two n -digit binary numbers : can make BFS (Binary Full Subtractor) or add the 2's complement of the second number to the first number : $N_1 - N_2 = N_1 + \overline{\overline{N_2}}$.


Note: a 2's complement of a binary is also a 1's complement plus 1

$\left\{ \begin{array}{l} 1's \text{ complement of } 0 \text{ is } 1 \\ 1's \text{ complement of } 1 \text{ is } 0 \end{array} \right.$


Note: $\overline{N_2}$ is 1's complement of N_2

$\overline{\overline{N_2}}$ is 2's complement of N_2 (in base 2) or the 10's complement of N_2 in base 10, etc.

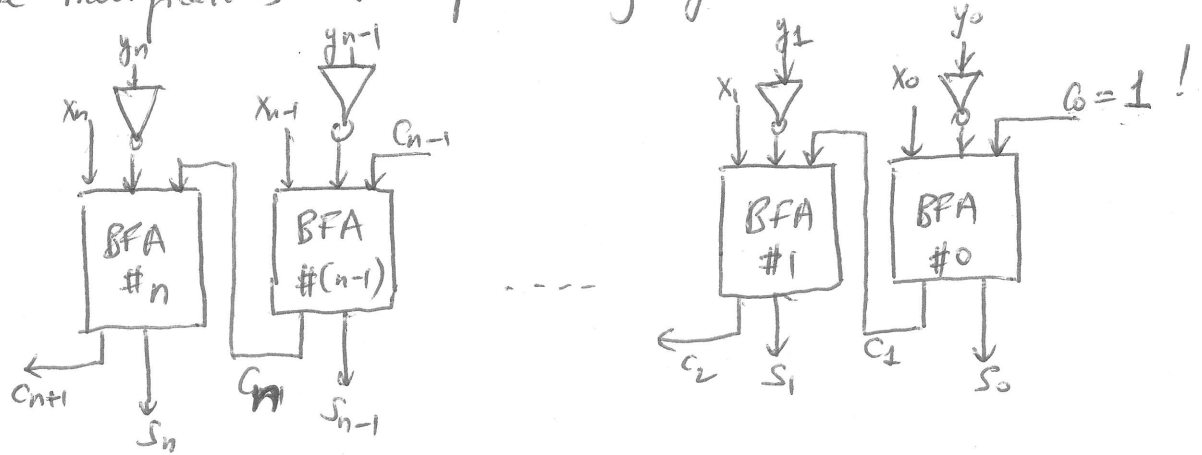Using these properties we can perform a subtraction for two n -digit binary numbers using a similar combination of BFA's with some modifications: 1-complementing y_0 & add one by setting $C_0 = 1$



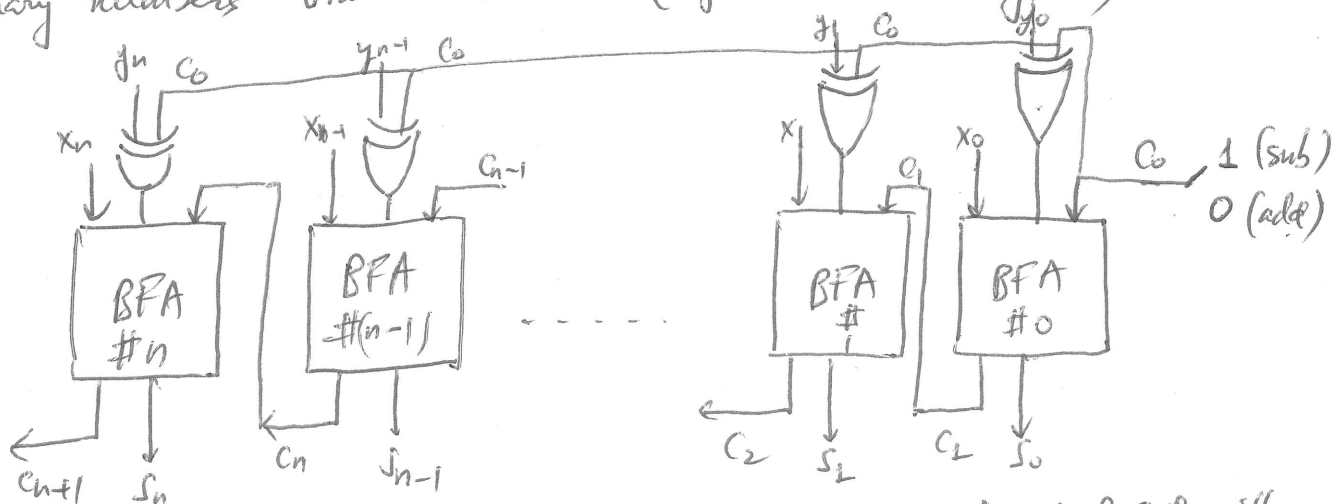We can combine these into one combination that allows performing addition or subtraction of the same two n -digit binary numbers via a switch (of the 1st carry in)



Note: XOR Gate will produce y_0 if $C_0 = 0$ or $\bar{y}_0$ if $C_0 = 1$

example: $y_0 = 1$ if

$C_0 = 0$ (add) $\rightarrow$ XOR gives 1

b) if $C_0 = 1$ (sub) $\rightarrow$ XOR gives 0 or the complement of 1

Note: this works in sequence: need to wait until the carry-out is produce before the next add/sub $\rightarrow$ "ripple effect".