
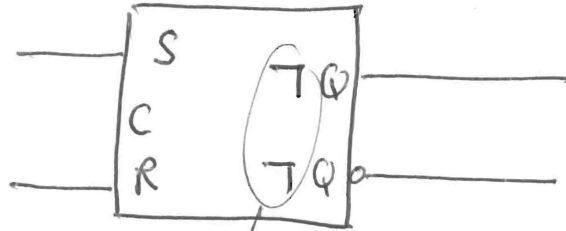


MS SR Flip Flop

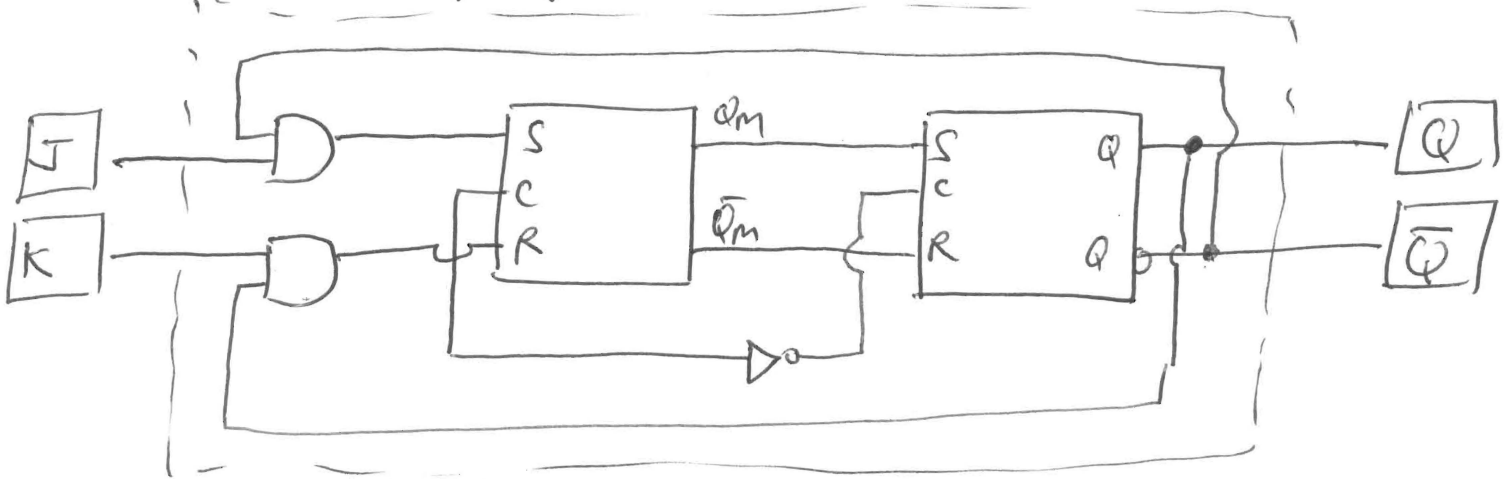

output is activated on the right edge of clock pulse (when input $\rightarrow$ output)


MS - JK Flip flops



MS-JK


S	R	C	Q	$\bar{Q}$
1	1	0	Q	$\bar{Q}$
0	0	1	Q	$\bar{Q}$
0	1	1	0	1
1	0	1	1	0
1	1	1	$\bar{Q}$	Q



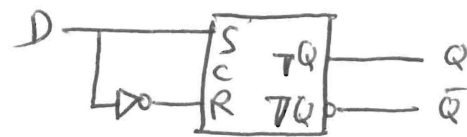

MS D Flip-flops : add an inverter b/w S & R in the MS-SR

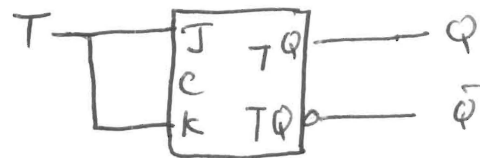
MS T Flip-flops : same as MS-JK with J & K connected.



Edge-Triggered D-Flip Flops :

Setting & resetting of flip flop occurs during an edge of the clock pulse (normally the rising edge or positive edge).

logic diagram with 6 NAND's:

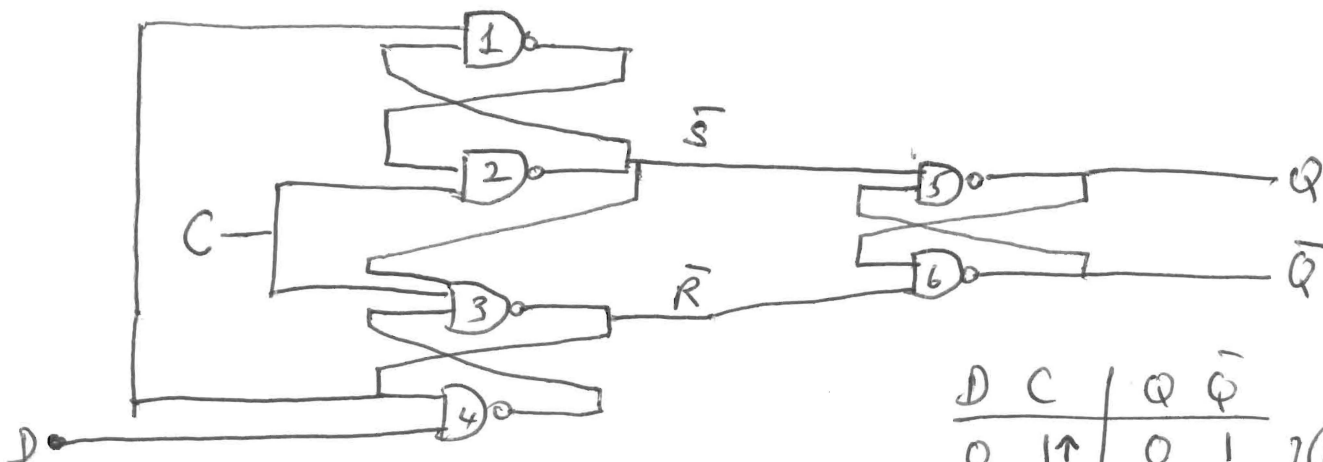

D	C	Q	Q̄
0	1↑	0	1
1	1↑	1	0
—	0	Q	Q̄
—	1	Q	Q̄

(C rising to 1)
(C at 1 → D is not transferred)

D input goes to output only during the positive edge of C (↑ increasing). When C at high (or 1) : D is not transferred to the output, which will keep the same state it was in.

MBS Flip flops

Pulse-Triggered

$$\begin{cases} \text{MS-SR} & Q^+ = S + \bar{R}Q \\ \text{MS-JK} & Q^+ = \bar{Q}J + Q\bar{K} \\ \text{MS-D} & Q^+ = D \\ \text{MS-T} & Q^+ = Q \oplus T \end{cases}$$

Edge-Triggered = D

Current state: $Q (\bar{Q})$

Next state: $Q^+ (\bar{Q}^+)$

MS-SR

S	R	Q	Q^+
0	0	0	0
0	0	1	1

Bistable

MS-D

0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

Unpredictable


SR

00 Bistable

10 10

01 01

11 unpredictable.

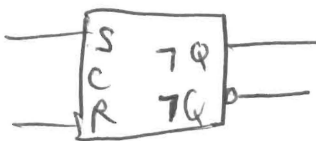

MS-SR

Q^+ k-map: MS-SR

Q^+	SR			
	00	01	11	10
0	0	0	-	1
1	1	0	-	1

Groups of ones & unknowns.
4, 2

$$Q^+ = S + Q\bar{R}$$

Characteristic equation for MS-SR (next state from current state & inputs SR)

MS-JK : MS-SR with 2 AND's

J	$\bar{Q}$	$S = J \cdot \bar{Q}$
0	0	0
0	1	0
1	0	0
1	1	1

K	Q	$R = K \cdot Q$
0	0	0
0	1	0
1	0	0
1	1	1

J	K	$\bar{Q}$	Q	S	R
0	0	1	0	0	0
0	1	1	0	0	0
1	0	1	0	0	0
1	1	1	0	0	0

MS-JK

To compare with MS-SR:

SR	$Q\bar{Q}$	(C=1)
00	Bistable	
01	01	
10	10	
11	$\bar{Q}Q$	

Q^+ K-map for **MS-JK**


Q^+	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$$Q^+ = \bar{Q}J + Q\bar{K}$$

Groups of ones & unknowns:
2 groups of two ones each

MS-Dinverter b/w S & R in MS-SR $\rightarrow$

True table for MS-D is a subtable of MS-SR!

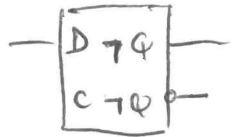k-map: MS-D

		SR	
		Q^+	
Q	0	0	1
	1	0	1

Note: $S = \bar{R} \equiv D$

$$Q^+ = D$$

MS-TSame as MS-JK with $J = K$.

See subtable for MS-T.

$$Q^+ = \bar{Q}T + Q\bar{T} = T \oplus Q$$


		JK	
		Q^+	
Q	0	0	1
	1	1	0

Next class:

Network


Combinational: outputs only depend on current inputs
Sequential: outputs depend on current & previous inputs: or the network has memory (Ch 7)

Ch 7: Synchronous Sequential Network:

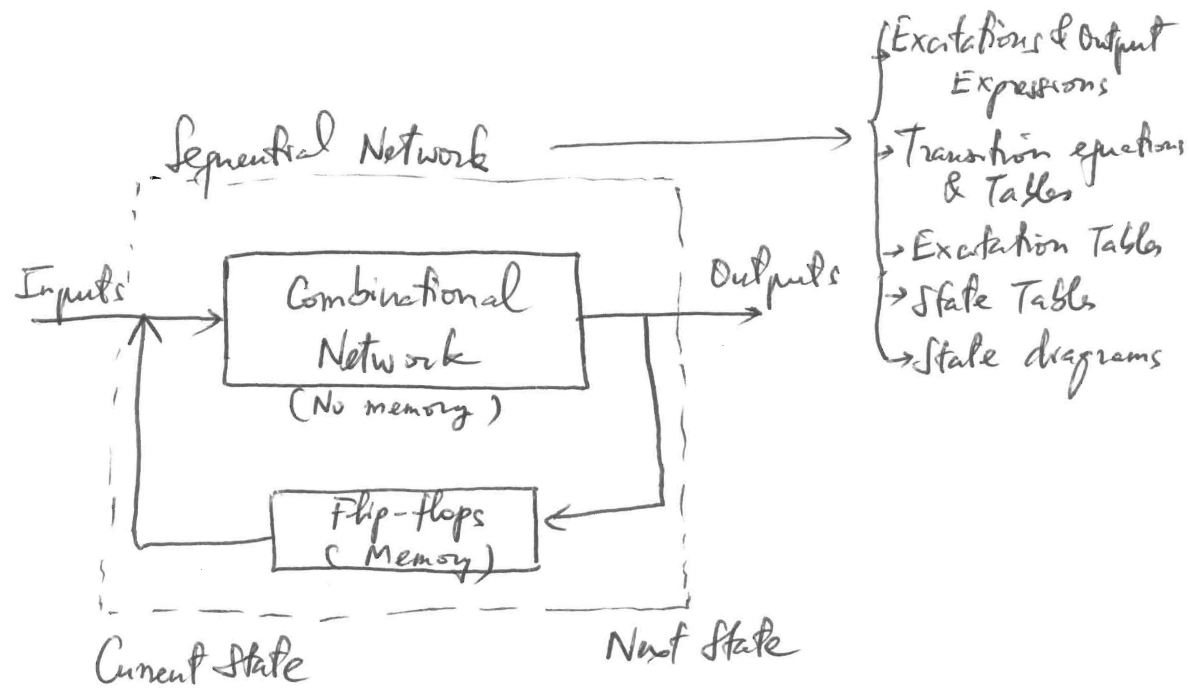

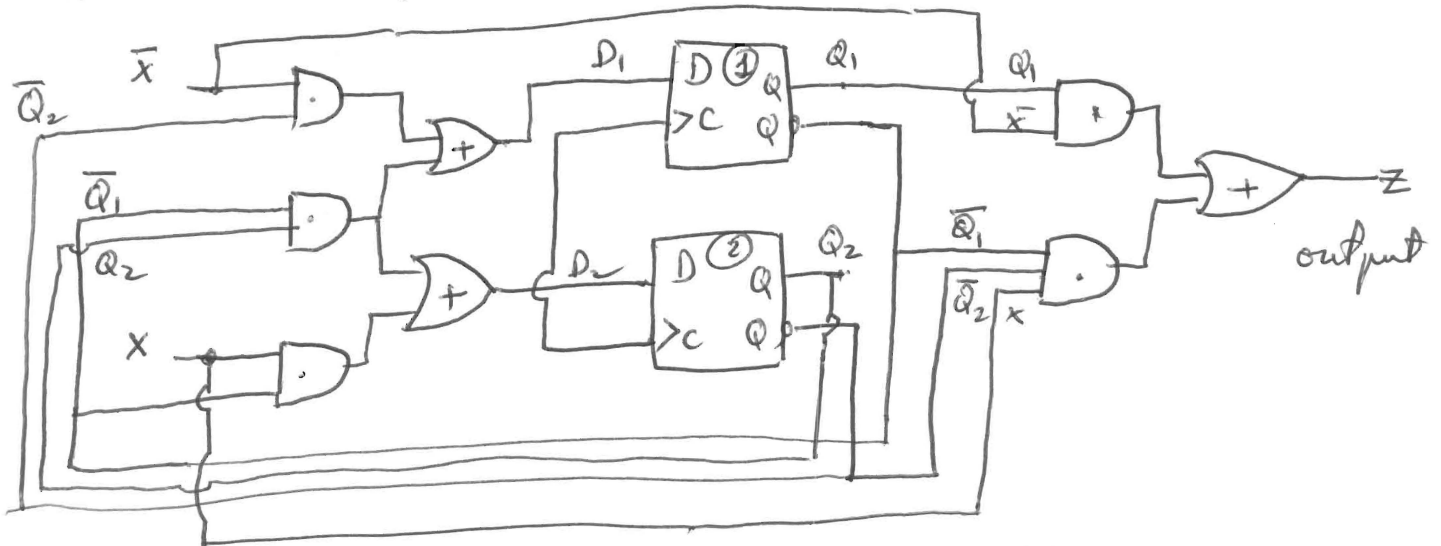Example: seq. network using D Flip-flops (characteristic eq. $Q^+ = D$)

Same Clocks $\rightarrow$ synchronous network.



Excitations : D_1 & D_2

From the network diagram

$$\begin{cases} D_1 = \bar{x} \cdot \bar{Q}_2 + \bar{Q}_1 \cdot Q_2 \\ D_2 = x \cdot \bar{Q}_1 + \bar{Q}_1 \cdot Q_2 \end{cases}$$

Output : $z = Q_1 \cdot \bar{x} + \bar{Q}_1 \cdot \bar{Q}_2 \cdot x$ (3)

Transition equations:

relate inputs to outputs @ flip-flops
Characteristic eq for D flip-flops.

$$Q_1^+ = D_1 = \bar{x} \cdot \bar{Q}_2 + \bar{Q}_1 \cdot Q_2 \quad (1)$$

$$Q_2^+ = D_2 = x \cdot \bar{Q}_1 + \bar{Q}_1 \cdot Q_2 \quad (2)$$

Next states

Transition table: shows current state, next state, output.

Present state (Q_1, Q_2)	Next state (Q_1^+, Q_2^+)		Output (z)	
	input (x)		input (x)	
	0	1	0	1
00	⁽¹⁾ ₁ ⁽²⁾ ₀	⁽¹⁾ ₀ ⁽²⁾ ₁	0	1
01	1 1	1 1	0	0
10	1 0	0 0	1	0
11	0 0	0 0	1	0

$(1) \downarrow Q_1^+ = \bar{Q}_2 + \bar{Q}_1 \cdot Q_2$ $(1) Q_1^+ = \bar{Q}_1 \cdot Q_2$
 $(2) Q_2^+ = \bar{Q}_1 \cdot Q_2$ $(2) Q_2^+ = \bar{Q}_1 + \bar{Q}_1 \cdot Q_2$
 $(3) z = Q_1$ $(3) z = \bar{Q}_1 \cdot \bar{Q}_2$

Excitation Table: shows current state, excitation, output.

Present state (Q_1, Q_2)	Excitation (D_1, D_2)		Output (z)	
	input (x)		input (x)	
	0	1	0	1
00	1 0	0 1	0	1
01	1 1	1 1	0	0
10	1 0	0 0	1	0
11	0 0	0 0	1	0

$D_1 = Q_1^+ = \bar{Q}_2 + \bar{Q}_1 \cdot Q_2$ $D_1 = Q_1^+ = \bar{Q}_1 \cdot Q_2$
 $D_2 = Q_2^+ = \bar{Q}_1 \cdot Q_2$ $D_2 = Q_2^+ = \bar{Q}_1 + \bar{Q}_1 \cdot Q_2$

In this example, since $\begin{cases} D_1 = Q_1^+ \\ D_2 = Q_2^+ \end{cases}$ The transition table is identical to the Excitation Table!


State Table: Transition Table with a letter notation for states

Present state (Q_1, Q_2)	Next state (Q_1^+, Q_2^+)		Output (Z)	
	input (x)		input (x)	
	0	1	0	1
00 $\rightarrow$ A	C	B	0	1
01 $\rightarrow$ B	D	D	0	0
10 $\rightarrow$ C	C	A	1	0
11 $\rightarrow$ D	A	A	1	0

Abbreviated version:

Present state (Q_1, Q_2)	Next state (Q_1^+, Q_2^+) / output (Z)	
	0	1
A	C, 0	B, 1
B	D, 0	D, 0
C	C, 1	A, 0
D	A, 1	A, 0

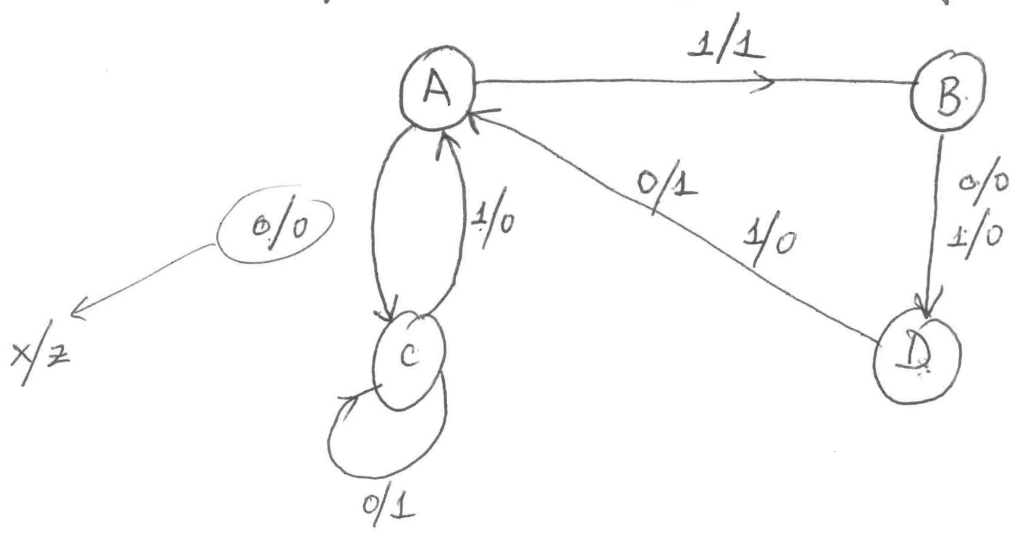State Diagram (for our synchronous sequential network)



Using the State Table.

Network Terminal Behavior

time output ($z(t)$)
for a given input sequence.


(94)

$x = 0011011101$ (input sequence)
 $\uparrow$
 state = ACCABDABDA B (state sequence) $\rightarrow$ using state diagram & input sequence.
 (Starts @ A)
 $\downarrow$
 $z = 0101001011$ (output sequence)

Use state diagram
 To write the state sequence given the input sequence

- Initial state is A & input $x=0$, next state is C.
- Current state is C & input is 0, next state is C
- Current state C & input is 1, next state is A

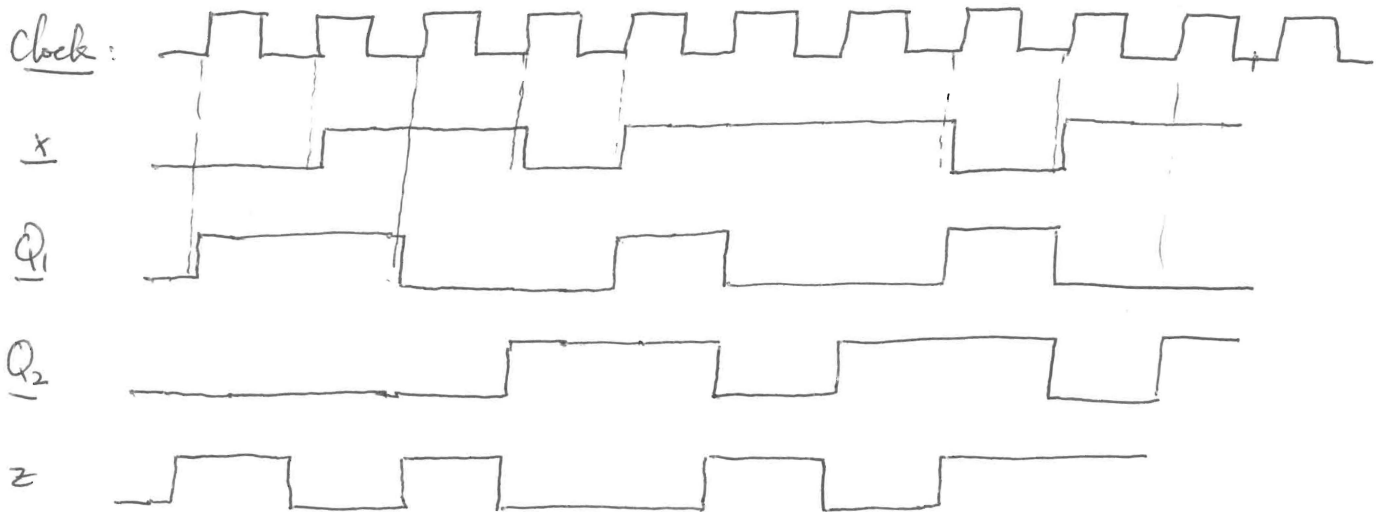* D-Flip Flops are positive edge-triggered



Another example of SSN (Synchronous Seq. Network)

Sequence Recognizer for two 4-bit numbers: $\boxed{0110}/\boxed{1001}$:

Output a 1 if ^{input}current is 0 given the previous three inputs were $\boxed{011}$ or if current input is 1 and previous three inputs were $\boxed{100}$

Given an input sequence: $\rightarrow$ They can overlap!

$x =$ $\boxed{0011}\boxed{0111}\boxed{1001}\boxed{0110}\boxed{0011}\boxed{0011}1100101$
 $z =$ 0000100000100000101

State Diagram:

$\boxed{011}0$ $\uparrow$ current(B) or $\boxed{100}1$ $\uparrow$ current(C)


Define state based on sequences of interest

A :	no input is received
B :	last input was a 0
C :	last input was a 1
D :	last two inputs were 01
E :	last two inputs were 10
F :	last three inputs were 011
G :	last three inputs were 100

Related

Related

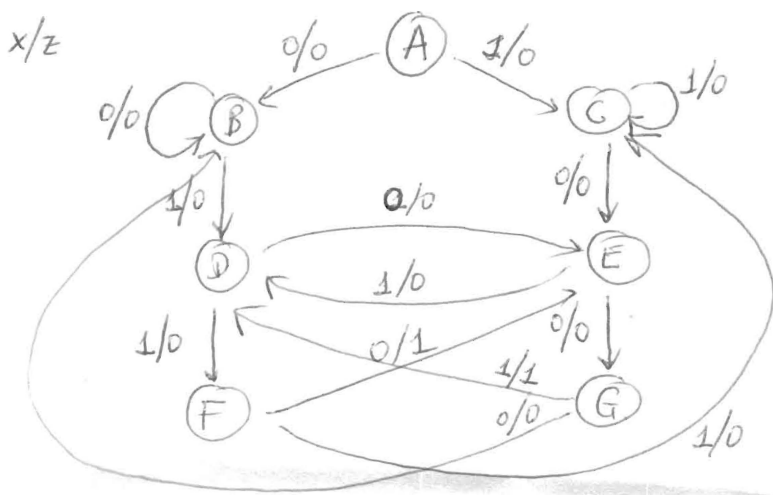Connections: $\textcircled{A} \begin{cases} x=0 \rightarrow \textcircled{B} \\ x=1 \rightarrow \textcircled{C} \end{cases}$



Output z : will be 0 unless $\begin{cases} \textcircled{F} \& x=0 \\ \textcircled{G} \& x=1 \end{cases}$

$\textcircled{F} \begin{cases} x=0 \rightarrow 0110 \rightarrow z=1 \\ x=1 \rightarrow 0111 \rightarrow z=0 \rightarrow \textcircled{C} \end{cases}$

State Table (For our 0110 or 1001 sequence recognizer)

Using the state diagram:

Present state	Next state Input x =		Output Input x =	
	0	1	0	1
A	B	C	0	0
B	B	D	0	0
C	E	C	0	0
D	E	F	0	0
E	G	D	0	0
F	E	C	1	0
G	B	D	0	1

Handling of unused states:

Example: 3 binary inputs $\rightarrow$ 8 different states.

If only five states are defined (e.g. A, B, C, D, E) $\rightarrow$ 3 are unused.

We'd like design a network based on the following state table

Present state	Next state Input x =		Output Input x =	
	0	1	0	1
A	A	B	0	0
B	C	D	1	0
C	A	D	0	1
D	E	A	1	1
E	C	B	0	0

K-map: we need our states into binary inputs:

	Q_1	Q_2	Q_3
A $\rightarrow$	0	0	0
B $\rightarrow$	0	0	1
C $\rightarrow$	0	1	0
D $\rightarrow$	0	1	1
E $\rightarrow$	1	0	0

Rewrite State Table using binary bits:

Present State $Q_1 Q_2 Q_3$	Next State $Q_1^+ Q_2^+ Q_3^+$ $x =$		Output z $x =$	
	$x =$		$x =$	
	0	1	0	1
000 ✓	000	001	0	0
001 ✓	010	011	1	0
010 ✓	000	011	0	1
011	100	000	1	1
100	010	001	0	0
101	—	—	—	—
110	—	—	—	—
111	—	—	—	—

} unknowns

4 Kmaps: Q_1^+ , Q_2^+ , Q_3^+ , z with 4 inputs each: Q_1, Q_2, Q_3, x

Q_1^+

		$Q_3 x$			
		00	01	11	10
$Q_1 Q_2$	00	0	0	0	0
	01	0	0	0	1
	11	—	—	—	—
	10	0	0	—	—

Q_2^+

		$Q_3 x$			
		00	01	11	10
$Q_1 Q_2$	00	0	0	1	1
	01	0	1	0	0
	11	1	—	—	—
	10	1	0	—	—

Q_3^+

		$Q_3 x$			
		00	01	11	10
$Q_1 Q_2$	00	0	1	1	0
	01	0	1	0	0
	11	—	—	—	—
	10	0	1	—	—

z

		$Q_3 x$			
		00	01	11	10
$Q_1 Q_2$	00	0	0	0	1
	01	0	1	1	1
	11	—	—	—	—
	10	0	0	—	—

Characteristic equations for Q_1^+ , Q_2^+ , Q_3^+ , z :

$$Q_1^+ = Q_2 Q_3 \bar{x};$$

$$Q_2^+ = \overline{Q_1 Q_3 \bar{x}} + \overline{Q_2 Q_3 x} + \overline{Q_1 Q_2 Q_3}$$

$$Q_1 \bar{x} + \bar{Q}_2 Q_3 + Q_2 \bar{Q}_3 x$$

$$Q_3^+ = \bar{Q}_3 x + \bar{Q}_2 x;$$

$$z = Q_2 x + Q_3 \bar{x}$$

Use D- flip flops :
(Three of them
for the 3 bits)

$$Q_1^+ = D_1 = Q_2 Q_3 \bar{x}$$

$$Q_2^+ = D_2 = Q_1 \bar{x} + \bar{Q}_2 Q_3 + Q_2 \bar{Q}_3 x$$

$$Q_3^+ = D_3 = \bar{Q}_3 x + \bar{Q}_2 x$$

$$Z = Q_2 x + Q_3 \bar{x}$$

